

Nodal Analysis offers us a method to easily identify and solve for a set of circuit voltages, with a proper set of independent equations immediately apparent.


- Once we have the node voltages, we can easily solve for any other variable.

The basic procedure:

- (1) Select a reference node from which all other node voltages are to be measured. Define its potential to be zero.
- (2) Label voltages at the remaining nodes with respect to the reference. These are the unknowns which will be solved for.
- (3) Write KCL at each non-reference node. Express the KCL equations in terms of the node voltages and device constitutive relations (v-i relations).
[see below for exceptions/modifications]
- (4) Solve the KCL equations for the node voltages.
- (5) Back solve for any other variables of interest.

Example 1:

4 nodes

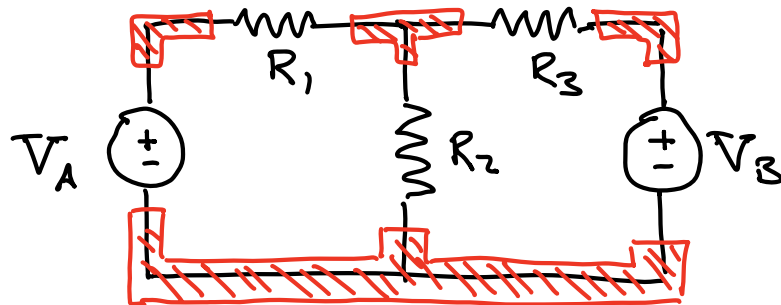


- (1) Select reference node. Could use any node, but some make analysis easier or are more natural.
 - Good to select a node connecting to as many independent voltage sources as possible, as this reduces the number of variables to solve for.
 - Beyond that it is good to select a node with many branches connected to it, as this slightly simplifies the equations.
 - Sometimes, an application makes the selection natural (e.g. choosing ground as the reference node).

The bottom node is a good fit in this example

Circuits Nodal Analysis 2: Supernodes + Simplification (2)

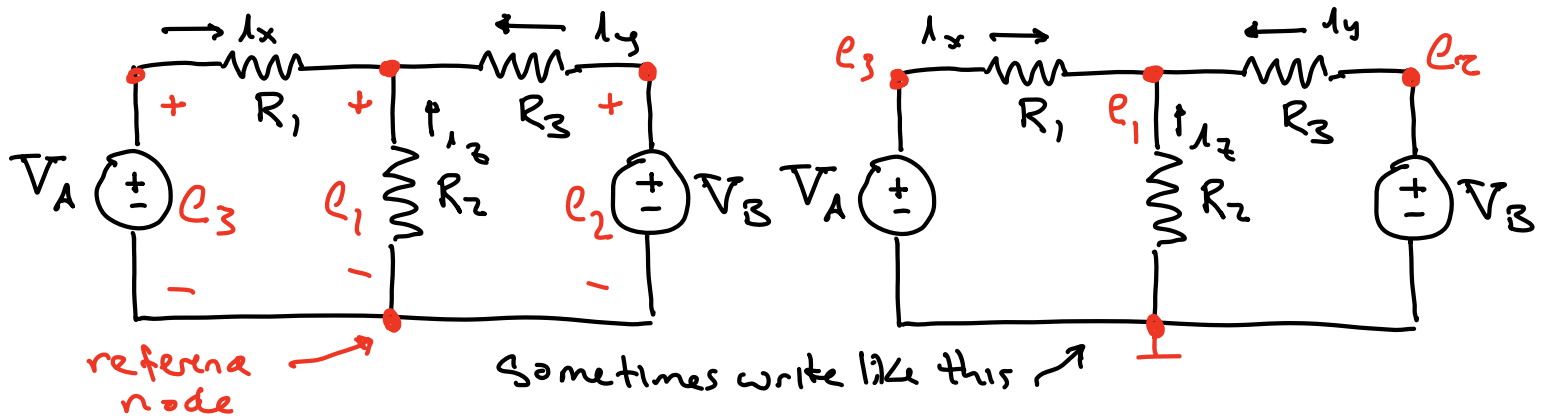(2) Label all nodes w/ voltages wrt. reference node.



- This is a good selection of a reference node, because while we have 3 non-reference nodes, we already know 2 of the node voltages from the independent voltage sources:

$e_3 = V_A$, $e_2 = V_B$
 So don't need to solve for them. This leaves only e_1 as an unknown to solve for.

(3) Write KCL in terms of node voltages

$$\text{KCL @ } e_1: \quad i_x + i_y + i_z = 0$$

$$\left(\frac{V_A - e_1}{R_1} \right) + \left(\frac{V_B - e_1}{R_3} \right) - \frac{e_1}{R_2} = 0$$

(4) Solve for the unknown node voltage(s):

$$R_2 R_3 V_A + R_1 R_2 V_B = R_2 R_3 e_1 + R_1 R_2 e_1 + R_1 R_3 e_1$$

$$e_1 = \frac{R_2 R_3 V_A + R_1 R_2 V_B}{R_2 R_3 + R_1 R_2 + R_1 R_3}$$


(5) Back solve for any other variables of interest

$$\begin{aligned} \text{e.g. } i_x &= \frac{V_A - e_1}{R_1} = \frac{V_A}{R_1} - \frac{R_2 R_3 V_A + R_1 R_2 V_B}{R_1 R_2 R_3 + R_1^2 R_2 + R_1^2 R_3} \\ &= \frac{R_1 R_2 V_A + R_1 R_3 V_A - R_1 R_2 V_B}{R_1 R_2 R_3 + R_1^2 R_2 + R_1^2 R_3} \end{aligned}$$

Special Cases: Nodal analysis always works, but there are some special cases. One involves "floating" independent voltage sources (i.e. independent voltage sources connected between 2 non-reference nodes).

- Such sources are a problem, because we cannot express the current through an independent voltage source in terms of its voltage! This causes a problem for calculating KCL
- We have a method for fixing this: SUPERNODES!

Example 2 (Circuit requiring supernode)

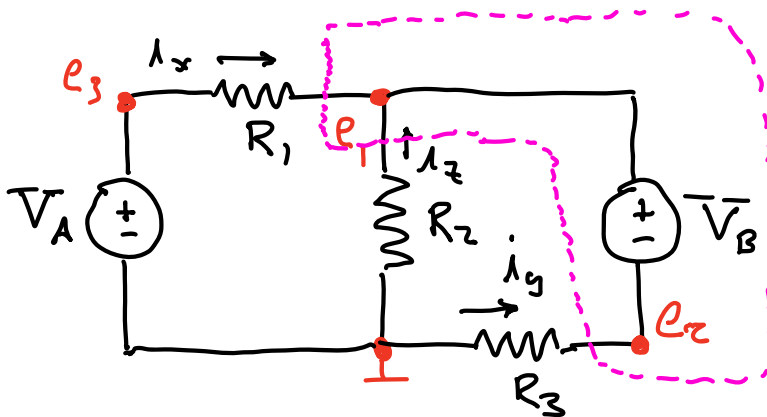

- V_B is between 2 non-ref nodes (1, 2).
- We cannot express I_y in terms of e_1, e_2 , making KCL at e_1, e_2 in terms of e_1, e_2 tricky.

"supernode" encompassing nodes 1, 2.

Again define $G_1 = 1/R_1$, $G_2 = 1/R_2$, $G_3 = 1/R_3$

- We have 2 unknown node voltages ($e_3 = V_A$) so need 2 equations:

①

$$e_1 - e_2 = V_B$$

{ floating voltage source gives us one relation directly by KVL }

$$\text{KVL } e_1 - V_B - e_2 = 0$$

- To get our second equation we can do KCL into the "supernode" encompassing nodes 1, 2. (illustrated by the dotted region)

\Rightarrow KCL holds not only at a node but into any closed surface as it is a reflection of conservation of charge.

②

$$\text{Supernode KCL: } I_x + I_y + I_z = 0$$

Expressed in terms of unknown node voltages:

$$G_1 \cdot (V_A - e_1) - G_3 \cdot e_2 - G_2 \cdot e_1 = 0$$

Solving these two simultaneous equations:

$$\begin{bmatrix} G_1 + G_2 & G_3 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V_A \\ \bar{V}_B \end{bmatrix}$$

$$\begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \frac{1}{-G_1 - G_2 - G_3} \begin{bmatrix} -1 & -G_3 \\ -1 & G_1 + G_2 \end{bmatrix} \begin{bmatrix} G_1 V_A \\ \bar{V}_B \end{bmatrix}$$

$$\begin{cases} e_1 = \frac{G_1 \bar{V}_A + G_3 \bar{V}_B}{G_1 + G_2 + G_3} = \frac{R_2 R_3 \bar{V}_A + R_1 R_2 \bar{V}_B}{R_2 R_3 + R_1 R_3 + R_1 R_2} \\ e_2 = \frac{G_1 \bar{V}_A - G_1 \bar{V}_B - G_2 \bar{V}_B}{G_1 + G_2 + G_3} = \frac{R_2 R_3 \bar{V}_A - R_2 R_3 \bar{V}_B - R_1 R_3 \bar{V}_B}{R_2 R_3 + R_1 R_3 + R_1 R_2} \end{cases}$$

From here we can easily find any other voltage or current!

Supernode Summary:

- For each independent voltage source between non-reference nodes, we lose 2 KCL equations for those 2 nodes
 - we recover 1 equation because we know the voltage difference between the two nodes (1)
 - we recover another equation by writing KCL for the supernode encompassing the two nodes (2)
- ⇒ We thus retain the exact number of independent eqns. needed to solve for unknown node voltages!

Other modifications:

- Additional tricks/modifications sometimes needed for other special cases, such as with "dependent sources"
- However we will always be able to recover enough independent equations to match our unknowns!


General Summary:

- Nodal Analysis always works for finding a set of independent equations needed to "solve" a circuit, and is unambiguous
 \Rightarrow For linear networks we can Always find a solution provided we haven't specified an "impossible" network (like having different voltage sources in parallel).
- For this reason, nodal analysis is often the "go to" method for solving circuits.
- Some reference selections yield equations that are easier to solve

Simplifications: Sometimes we combine nodal analysis with circuit simplifications (e.g. to reduce the number of nodes).

Consider combining elements to make a system simpler.

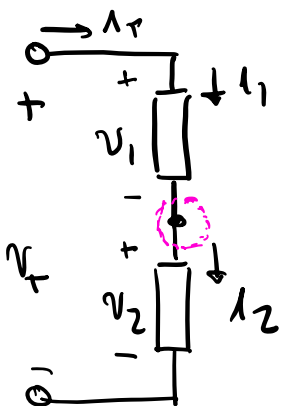Series: Two elements are in series if they share the same current.




By KVL, $V_T = V_1 + V_2$

By KCL, $I_1 = I_2 (= I_T)$

\therefore elements are in series!

How do resistors in series act?

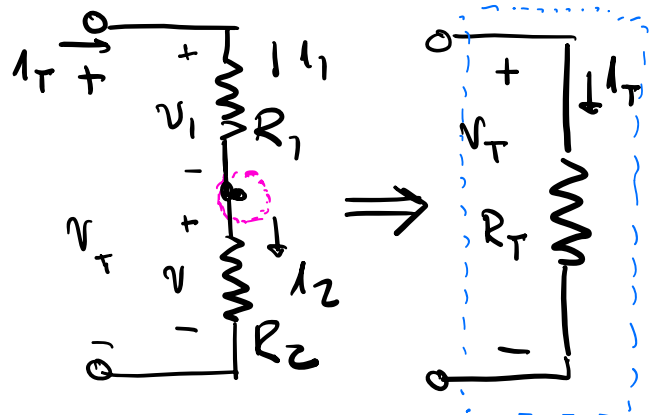

$$V_T = V_1 + V_2 = I_1 R_1 + I_2 R_2 \\ = I_T (R_1 + R_2)$$

$$\therefore \boxed{\frac{V_T}{I_T} = R_1 + R_2}$$


Resistors in series

Together 2 resistors R_1, R_2 in series act like a resistor $R_T = R_1 + R_2$

(R_T is a resistor that draws the same current between the end nodes as the original chain of resistors would)


In general, for N resistors in series $R_T = \sum_{i=1}^N R_i$

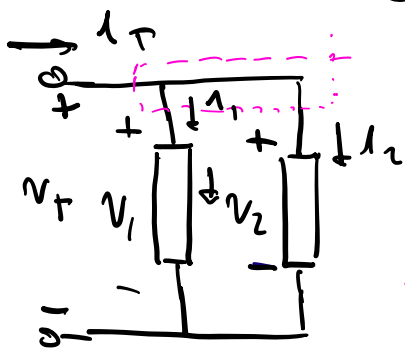Parallel: Two elements are in parallel if they share the same voltage (i.e. are connected between the same two nodes)



By KVL
 $V_1 = V_2 (=V_T)$
 elements are in parallel

By KCL
 $I_T = I_1 + I_2$

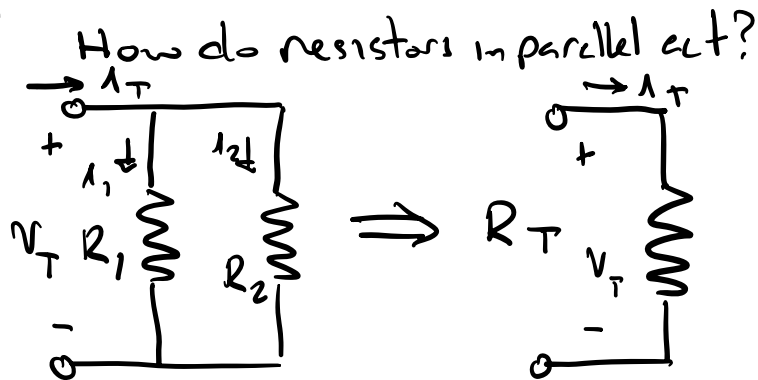

Define
 $G_1 = 1/R_1, G_2 = 1/R_2$

$I_1 = G_1 V_1 = G_1 V_T$ $I_T = I_1 + I_2 = (G_1 + G_2) V_T$
 $I_2 = G_2 V_2 = G_2 V_T$ $G_T = \frac{I_T}{V_T} = G_1 + G_2$

or

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2}$$


Resistors in parallel
 (sometimes written as $R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$)

For N resistors in parallel

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}} = \frac{1}{\sum_{j=1}^N \frac{1}{R_j}}$$

We can sometimes use series + parallel combinations to simplify our circuit before solving (reducing # nodes +/or branches to solve)

Example 3:

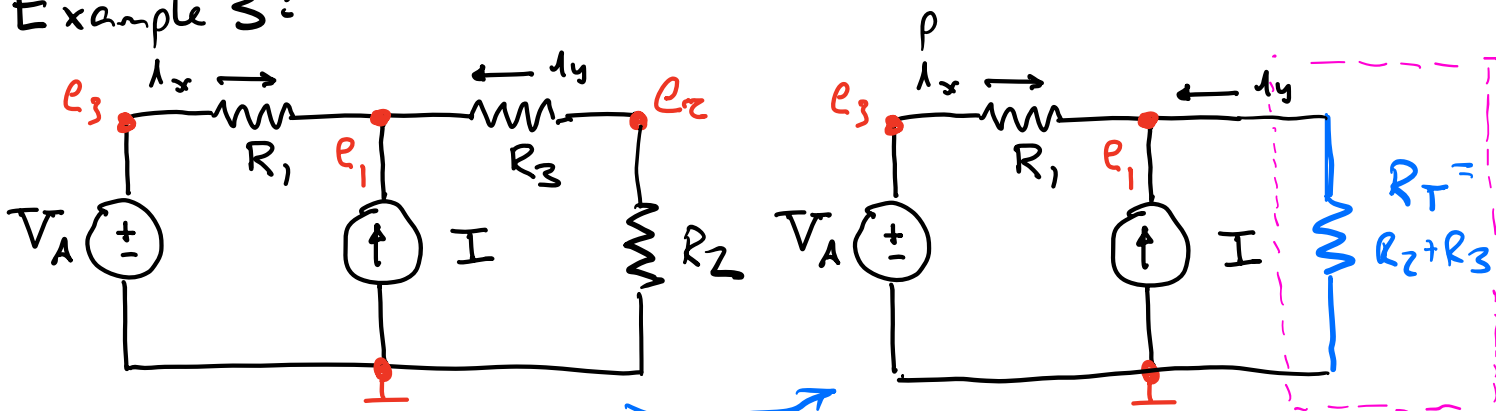

Simplify w series combination

Solve for e_1 by KCL @ e_1 :

$$(V_A - e_1) \frac{1}{R_1} + I - e_1 \cdot \frac{1}{R_2 + R_3} = 0$$

$$\therefore e_1 \left[\frac{1}{R_1} + \frac{1}{R_2 + R_3} \right] = \frac{V_A}{R_1} + I$$

$$e_1 \left[R_2 + R_3 + R_1 \right] = V_A \cdot (R_2 + R_3) + I R_1 (R_2 + R_3)$$

$$e_1 = V_A \cdot \frac{R_2 + R_3}{R_1 + R_2 + R_3} + \frac{I \cdot R_1 (R_2 + R_3)}{R_1 + R_2 + R_3}$$

Now that we know e_1 , we can find other variables, e.g.

$$I_y = -\frac{e_1}{R_2 + R_3} = -\frac{V_A}{R_1 + R_2 + R_3} - I \cdot \frac{R_1}{R_1 + R_2 + R_3}$$

From the original circuit

$$e_2 = -I_y \cdot R_2 \quad \therefore e_2 = V_A \cdot \frac{R_2}{R_1 + R_2 + R_3} + I \cdot \frac{R_1 R_2}{R_1 + R_2 + R_3}$$