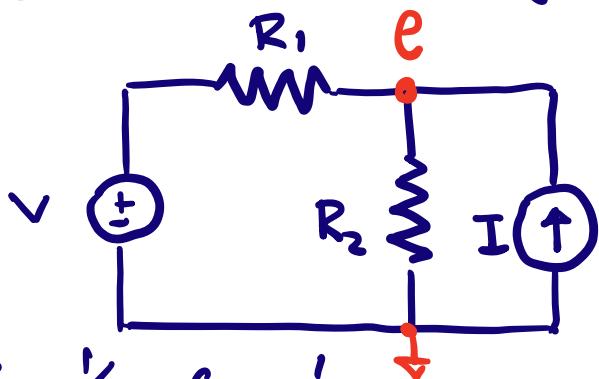


Consider nodal analysis of the following circuit:



$$G_1 = \frac{1}{R_1}, G_2 = \frac{1}{R_2}$$

KCL @ node e:

$$(e - V)G_1 + eG_2 - I = 0$$

$$(G_1 + G_2)e = I + G_1 V$$

$$e = \frac{1}{G_1 + G_2} \cdot I + \frac{G_1}{G_1 + G_2} V$$

Could also express as:

$$e = \frac{R_1 R_2}{R_1 + R_2} I + \frac{R_2}{R_1 + R_2} V$$

note that  $e$  is a linear combination of  $I, V$  with weights that depend upon the circuit components

In the general (many node) case, we would get (from nodal analysis):

$$G \cdot e = S$$

 $\Rightarrow$ 

$$e = G^{-1} \cdot S$$

Conductance matrix

node voltage vector


Linear sum of sources vector

The node voltages are all linear combinations of the input sources (indep.  $V, I$  sources).

A characteristic of networks constructed of linear resistors and independent sources is that there is a linear response of network voltages and currents (outputs) to the independent sources (inputs)


Linearity requires and implies two properties:

1. Homogeneity:

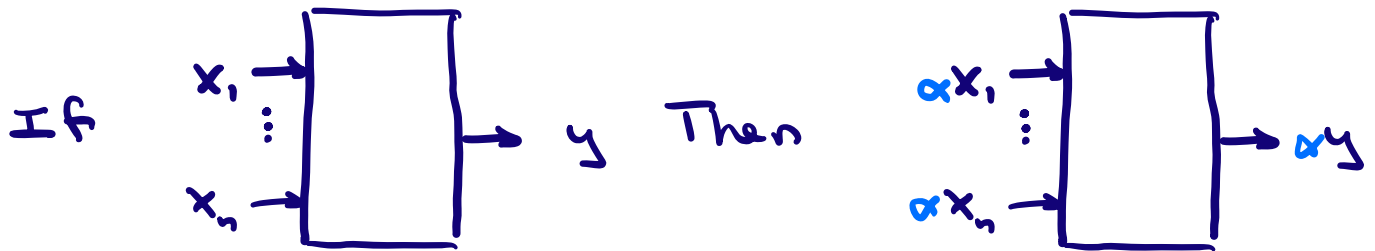


Scaling inputs gives a proportionally scaled output

2. Superposition:

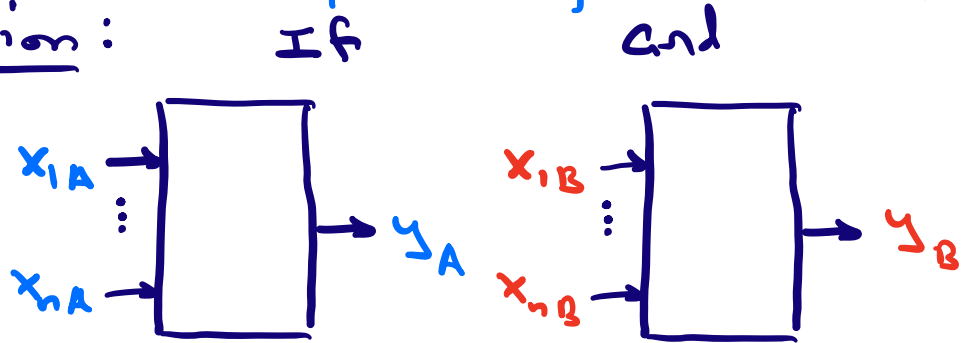


then

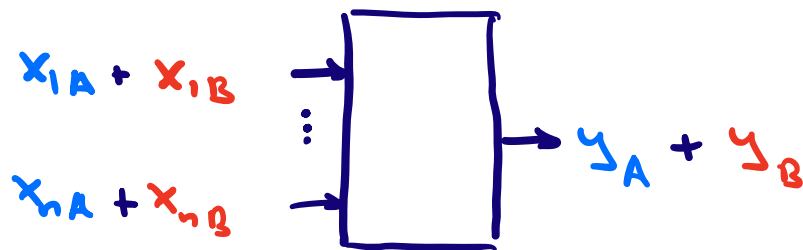


A sum of inputs yields a response that is the sum of the responses to the individual inputs

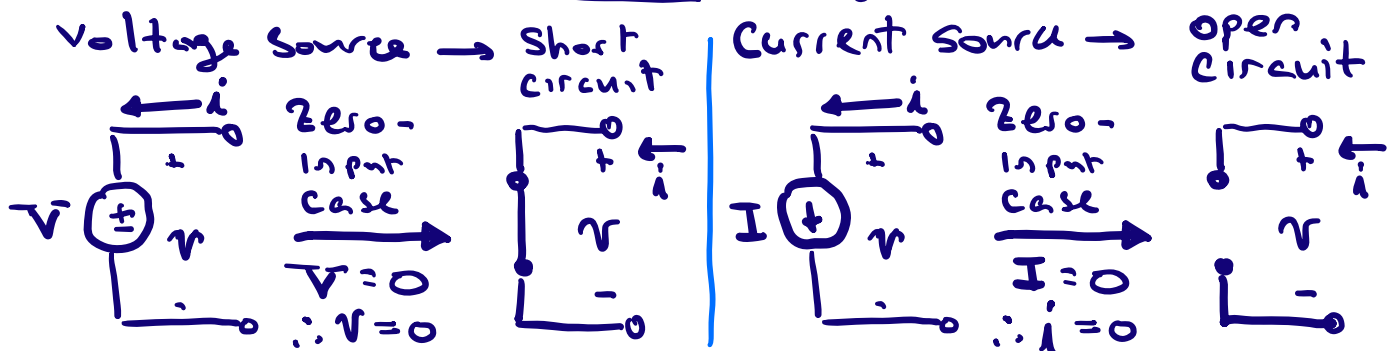Our inputs are independent voltage + current sources




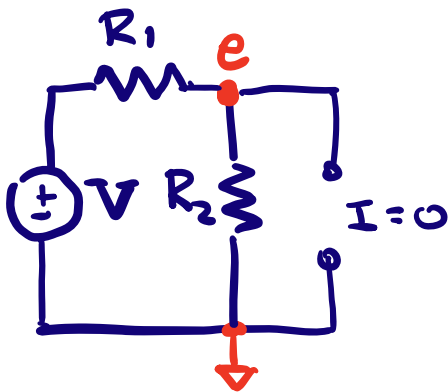Looking at our example, let's find the response to the individual inputs and superpose them:




$$e = \frac{R_2}{R_1 + R_2} \cdot V$$

V-source only

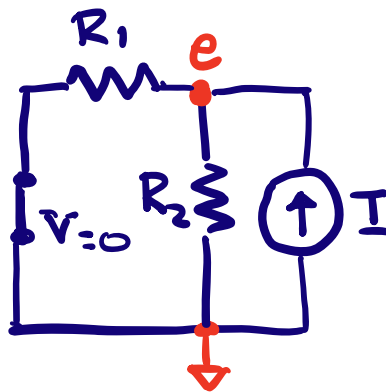

$$e = \frac{R_1 R_2}{R_1 + R_2} \cdot I$$

I-source only

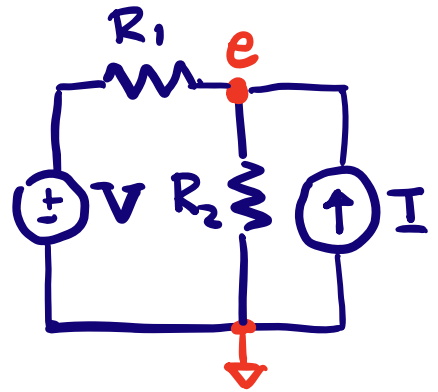


$$e = \frac{R_2}{R_1 + R_2} \cdot V + \frac{R_1 R_2}{R_1 + R_2} \cdot I$$

Superposition

The total response (by superposition) to both V, I is as found before using nodal analysis.

Demo:

Distributed resistor network (Jello)

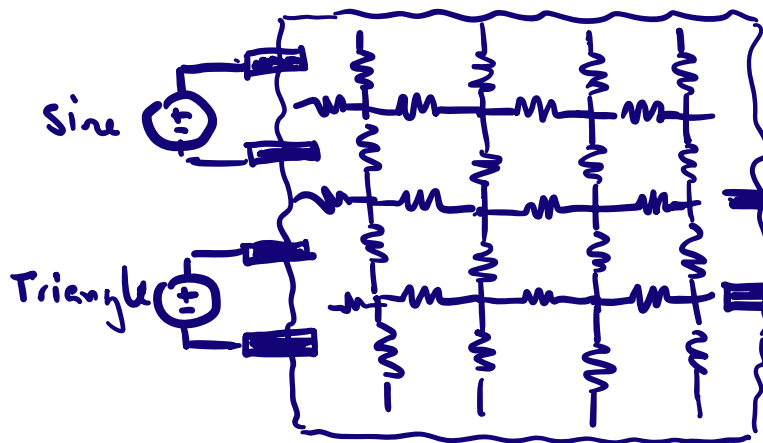


Look for Superposition + homogeneity @ output

- Linearity + superposition are often used to find the response to multiple inputs
- They also enable a powerful modeling method!

Let's see how superposition can help simplify analysis

Consider the following circuit:

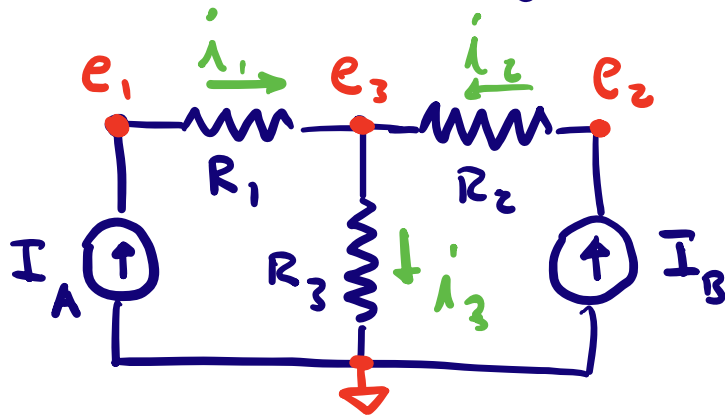


Fun fact:

This circuit shows up in real life for modeling the heat transfer of multiple devices mounted to the same heat sink. The node potentials represent the temperature rises at different places in the system.

Consider solving for node potentials  $e_1, e_2, e_3$  using nodal analysis. There are 4 nodes, so this gives a  $3 \times 3$  set of eqns.

However, we can solve more quickly by superposing the responses to  $I_A, I_B$  individually:

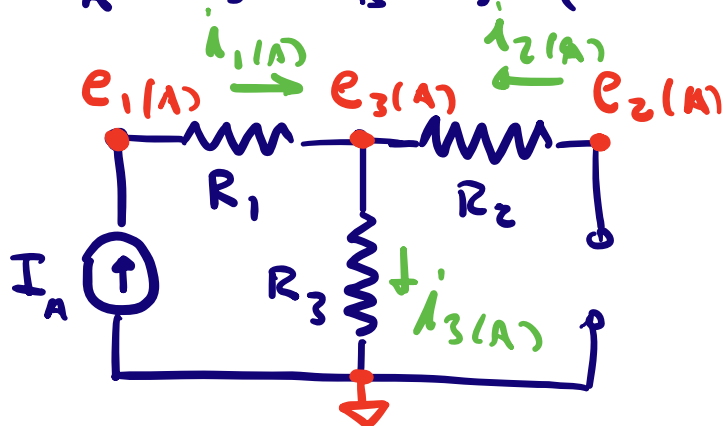- $I_A$  only ( $I_B = 0$ ; replace  $I_B$  with an open):



$$i_1(A) = i_3(A) = I_A$$

$$i_2(A) = 0$$


Note:  $R_1, R_3$  are in series here because they share the same current!

$$\therefore e_3(A) = i_3(A) R_3 = I_A R_3$$

$$e_2(A) = e_3(A) + i_2(A) R_2 = I_A R_3$$

$$e_1(A) = e_3(A) + i_1(A) R_1 = I_A (R_1 + R_3)$$

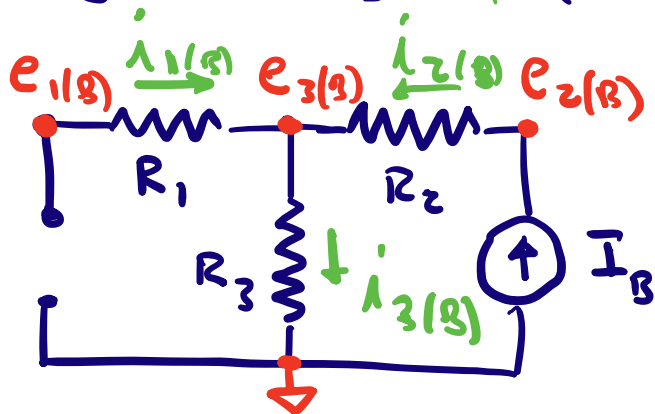- $I_B$  only ( $I_B = 0$ ; replace  $I_A$  with an open):



$$i_2(B) = i_3(B) = I_B$$

$$i_1(B) = 0$$


note:  $R_2, R_3$  are in series here because they share the same current!

$$\therefore e_3(B) = i_3(B) \cdot R_3 = I_B \cdot R_3$$

$$e_2(B) = e_3(B) + i_2(B) \cdot R_2 = I_B (R_2 + R_3)$$

$$e_1(B) = e_3(B) + i_1(B) \cdot R_1 = I_B \cdot R_3$$

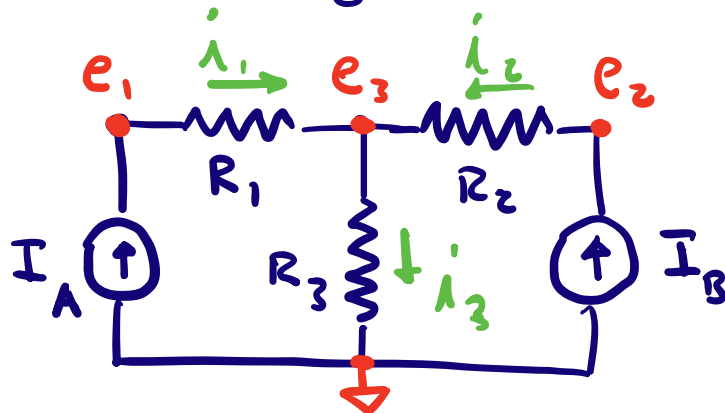By superposition we get the total solution:




$$e_3 = e_{3(A)} + e_{3(B)} = I_A R_3 + I_B R_3$$

$$e_2 = e_{2(A)} + e_{2(B)} = I_A R_3 + I_B (R_2 + R_3)$$

$$e_1 = e_{1(A)} + e_{1(B)} = I_A (R_1 + R_3) + I_B R_3$$

⇒ We get the answer easily, and can nicely see the contribution of each input ( $I_A, I_B$ ) to the node voltages.

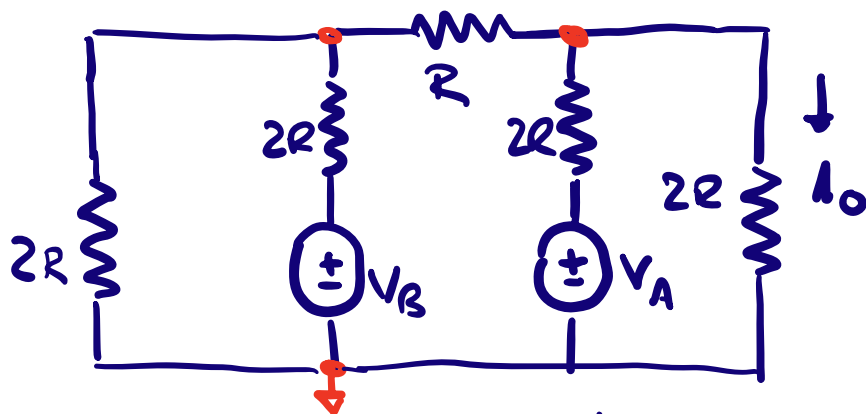Another Example: A circuit with 2 voltage inputs  $V_A, V_B$  driving a current output  $I_0$ :




Fun Fact:  
much expanded versions of this circuit are common in D-to-A converters (DACs)

We could use nodal analysis to solve for the 2 unknown node potentials (2x2 system of eqns) then solve for  $I_0$

However, superposition of the responses to the individual inputs ( $V_A, V_B, V_C$ ) is both faster and gives insight into circuit operation

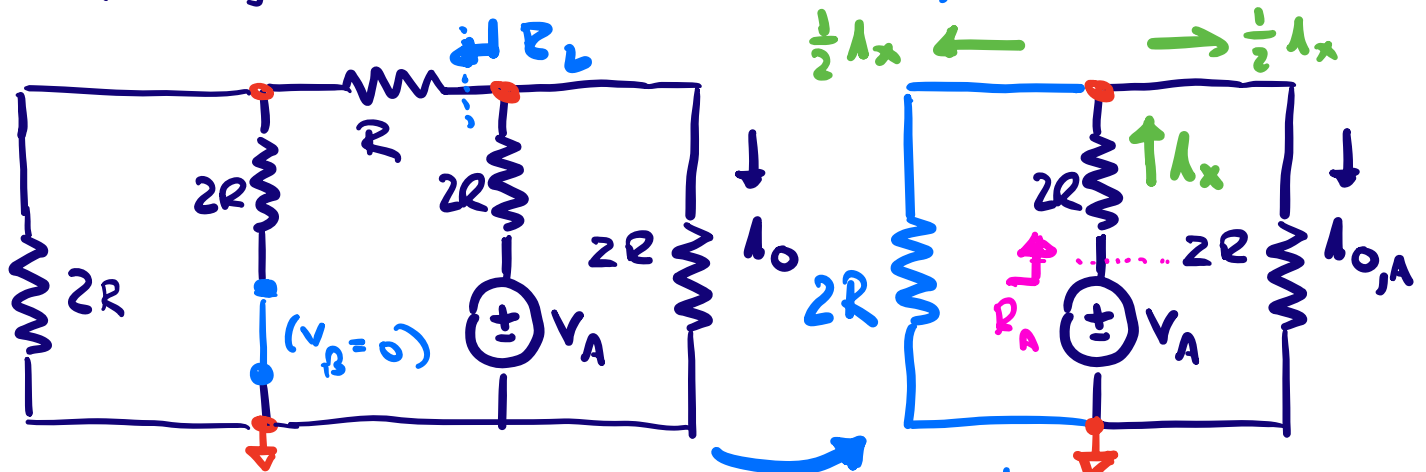
$V_A$  only ( $V_B$  set to 0  $\rightarrow$  replaced by short circuit)



Simplify: replace left part of circuit with  $R_L = 2R$


What net resistance does  $V_A$  "see"?
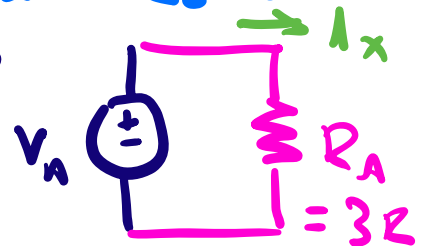
$$R_A = 3R \therefore I_x = \frac{V_A}{3R}$$



By current division  $I_{0,A} = \frac{1}{2} I_x = \frac{1}{2} \frac{V_A}{3R}$

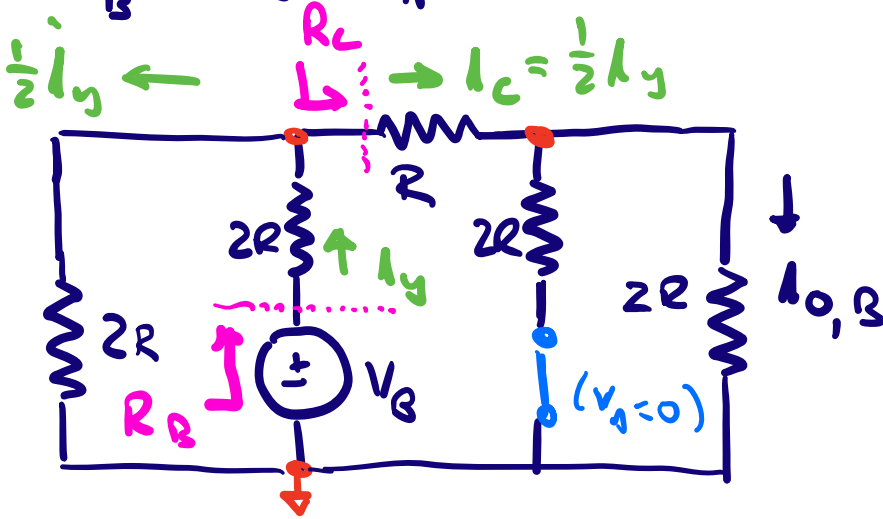$V_B$  only ( $V_A$  set to 0  $\rightarrow$  replaced by short circuit)



What net resistance does  $V_B$  "see"?

$$R_B = 3R \quad \therefore i_y = \frac{V_B}{3R}$$


what net resistance of right-hand branch?

$$R_C = 2R \quad \therefore \text{by current division } i_c = \frac{1}{2} i_y$$

what is  $i_{o,B}$ ?

$$\text{By current division } i_{o,B} = \frac{1}{2} i_c = \frac{1}{4} i_y = \frac{1}{4} \frac{V_B}{3R}$$

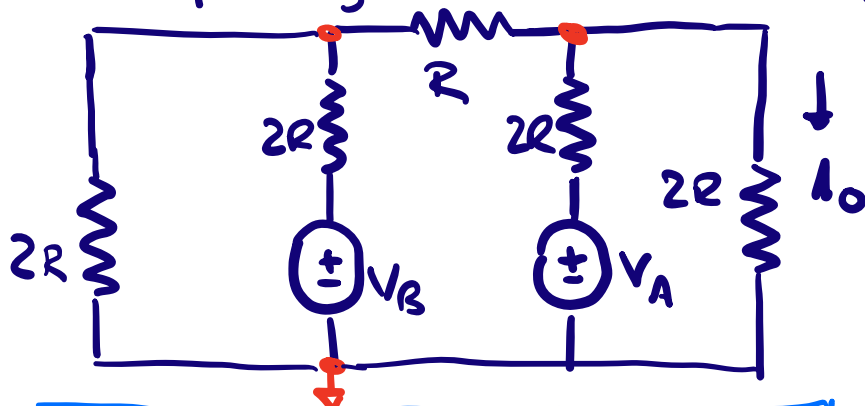Superposing our two solutions, for the original circuit



$$i_o = \frac{1}{3R} \left[ \frac{1}{2} V_A + \frac{1}{4} V_B \right]$$

weighted  
response  
from  
 $V_A, V_B$