

Consider a winding (e.g. a coil of wire) with a current in it. The magnetic flux linking the winding owing to the current is proportional to the current (with a proportionality constant called inductance):

$$\lambda = L \cdot i_L$$


flux linkage \rightarrow inductance \leftarrow current

L in Henrys, H
(volt-sec/Ampere)

The time derivative of the flux linkage is voltage v_L across the winding:

$$\frac{d\lambda}{dt} = v_L = \frac{d}{dt} \{ L i \} = L \frac{di_L}{dt}$$

$$\Rightarrow v_L = L \frac{di_L}{dt}$$

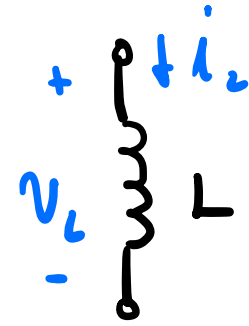

(note the associated variables convention between v_L, i_L)

Inductors Store Energy:

$$W_m = \int_{-\infty}^t i_L(t) v_L(t) dt = \int_{-\infty}^{\infty} i_L \cdot \left(L \frac{di_L}{dt} \right) dt = \int_0^{I_L} i_L \cdot L di_L$$

$$\Rightarrow W_m = \frac{1}{2} L I_L^2$$

- The energy is stored in the magnetic field
- Because of this, circuits with inductors exhibit dynamic behavior and are described with differential equations

State Property:

$$v_L = L \frac{di_L}{dt} \therefore$$

$$i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(\tau) d\tau$$


or for incremental Δt :

$$i_L(t + \Delta t) = i_L(t) + \frac{1}{L} v_L(t) \Delta t$$

\therefore As long as $v_L(t) < \infty$, $i_L(t)$ must be continuous (cannot change instantly): $i_L(t^+) = i_L(t^-)$

* See demo of what happens when we try to instantaneously open-circuit an inductor with current in it.

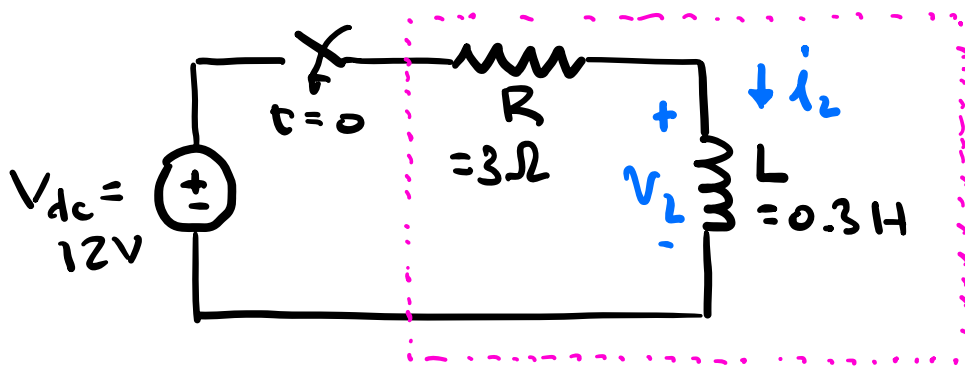A Simple Example: Lets model the time response of the field winding of an automotive alternator (generator):



@ $t=0$ the switch closes. What is $i_L(t)$ for $t \geq 0$?

$i_L(t) = 0$ for $t < 0$. Since no ∞ voltage @ $t=0$ $i_L(0^+) = i_L(0^-) = 0$

KVL for $t > 0$:

$$V_{dc} - i_L R - L \frac{di_L}{dt} = 0 \quad \therefore \quad i_L + \frac{L}{R} \frac{di_L}{dt} = \frac{V_{dc}}{R} \quad *$$

This is a first-order linear, constant-coefficient differential equation (LCCDE).

This is very like our first-order differential equation for capacitor circuits, but with time constant $\tau = L/R$ rather than $\tau = RC$.


The formal solution approach:

$$i_L(t) = \underbrace{i_{L,p}}_{\substack{\text{particular solution} \\ i_{L,p} \text{ is any solution to } *}} + \underbrace{i_{L,h}}_{\substack{\text{homogeneous, or "natural" solution} \\ \text{is the solution to the homogeneous differential equation}}} \\ \underbrace{\uparrow}_{\text{Total solution}} \quad \underbrace{\uparrow}_{i_L + \frac{L}{R} \frac{di_L}{dt} = 0 \quad **}$$

This differential equation describes the undriven system (i.e. with $V_{dc} = 0$)

Note: the homogeneous solution has an arbitrary scale constant.

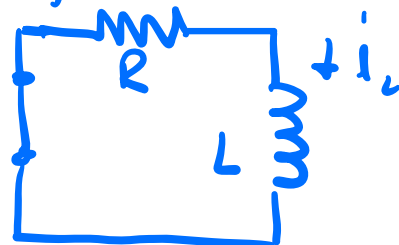We pick the scale constant such that the total solution matches the initial condition.



• Particular Solution to $i_L + \frac{L}{R} \frac{di_L}{dt} = \frac{V_{dc}}{R}$

• Can guess any solution that will work.

• Since the right side (related to the drive input) is constant, guessing a constant is a good idea (since derivatives of a constant are zero):

$$V_{c,p} = V_{dc}/R \quad \checkmark$$

• General homogeneous solution to $i_L + \frac{L}{R} \frac{di_L}{dt} = 0$

• LCCDE's always have exponentials as solutions (since exponentials replicate under differentiation). \therefore

guess

guess: $V_{c,h} = A e^{st}$

• A is arbitrary scale constant
• find value(s) of S that work. A 1st order eqn will only have one value of S

Substituting in:

$$A e^{st} + \frac{L}{R} \cdot s \cdot A e^{st} = 0 \quad \therefore \quad \boxed{1 + \frac{L}{R} s = 0}$$

This is the "characteristic equation" that gives us $s = -R/L$

$$\therefore V_{c,h} = A e^{-\left(\frac{R}{L}\right)t} = A e^{-t/\tau} \quad \text{where } \tau = L/R \text{ (units seconds)}$$

• Total solution form

$$\begin{aligned} V_c(t) &= V_{c,p} + V_{c,h} \\ &= V_{dc}/R + A e^{-t/\tau} \quad (\tau = L/R) \end{aligned}$$

To find A, apply initial condition:

$$i_L(0^+) = 0 = \frac{V_{dc}}{R} + A e^{-0/\tau} \quad \Rightarrow \quad A = -\frac{V_{dc}}{R}$$


$$\therefore \boxed{i_L(t) = \frac{V_{dc}}{R} - \frac{V_{dc}}{R} e^{-t/\tau} \quad \text{for } t > 0}$$

where $\tau = L/R$

Circuits Inductors and First-Order Systems (4)


For our system $V_{dc} = 12V$, $L = 0.3H$, $R = 3\Omega$
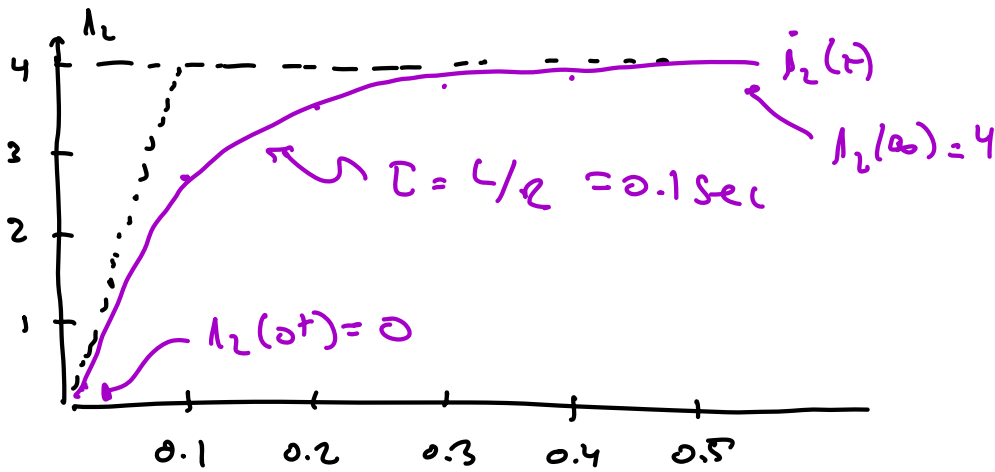
$$i_L(t) = 4(1 - e^{-0.1t}) \text{ for } t > 0$$




time t	$\frac{-t}{\tau}$
0	1
$1 \cdot \tau$	$\frac{1}{e} \approx 0.37$
$2 \cdot \tau$	$\frac{1}{e^2} \approx 0.14$
$3 \cdot \tau$	0.05
$4 \cdot \tau$	0.018
$5 \cdot \tau$	0.006

Another example: ($i_L(0^-) = 0A$)

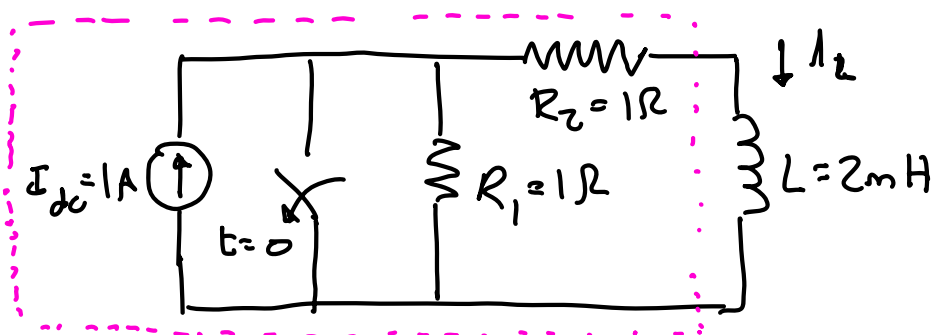

find $i_L(t)$, $t > 0$

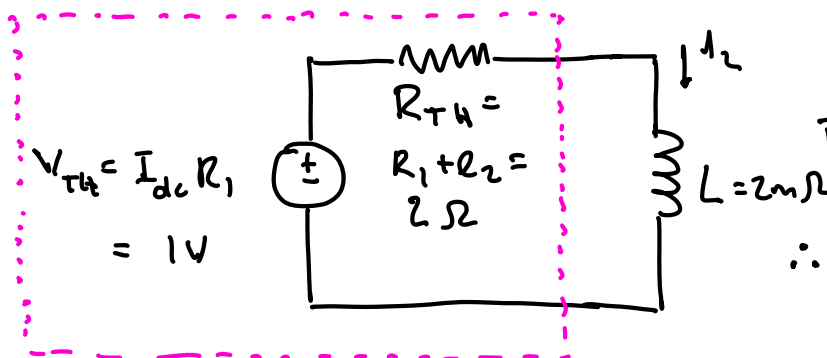For $t > 0$ we can replace the resistor/source network with a Thevenin equivalent:



This circuit has the same form as our first example!

$$\tau = L/R_{TH} = 1ms$$

$$\therefore i_L(t) = \frac{V_{TH}}{R_{TH}} (1 - e^{-t/\tau})$$

Because we can always reduce the resistor + source network to a Thevenin equivalent, we can always solve easily for any 1st order inductor system, we will always get a time constant

$\tau = L/R_{TH}$ where R_{TH} is the Thevenin eq. resistance of the network connected to the inductor.

Add some insight:


In both resistor/inductor and resistor/capacitor cases with constant inputs we get a response from an initial condition to a final value. The final value is the dc steady-state response (a constant current or voltage).

Previously we determined the final value from the differential equation. However, we can figure it out directly from the circuit!


For an inductor $v_L = L \frac{di_L}{dt}$. However, once we're approaching steady state (e.g. as $t \rightarrow \infty$) then $di_L/dt \rightarrow 0$. $\therefore v_L \rightarrow 0$.

So, in dc steady state, an inductor looks like a short circuit! We can figure out the steady state value by replacing the inductor with a short!

Reconsider our first example:

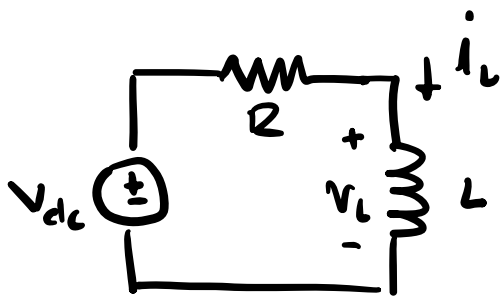

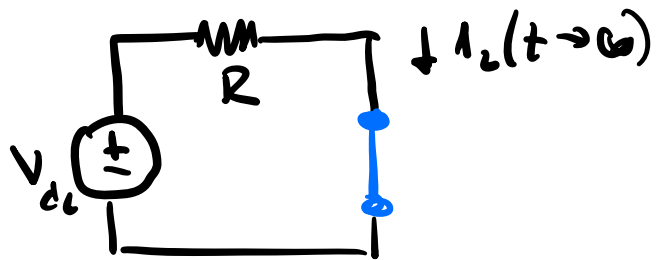as $t \rightarrow \infty$
we get to
dc steady
state:




We expect a steady-state solution of $i_L(\infty) = V_{dc}/R$, which is exactly what we got from the differential equation!

(Likewise, in a capacitor circuit we would replace the capacitor with an open circuit to find the dc steady-state response.)

One more example:

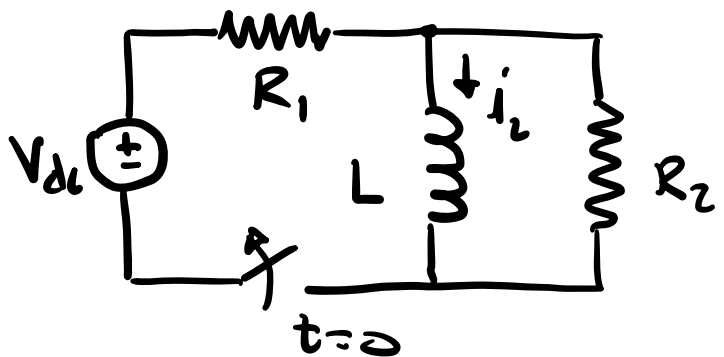
switch has been closed a long time and opens @ $t=0$.



Circuits

Inductors and first-order systems (6)

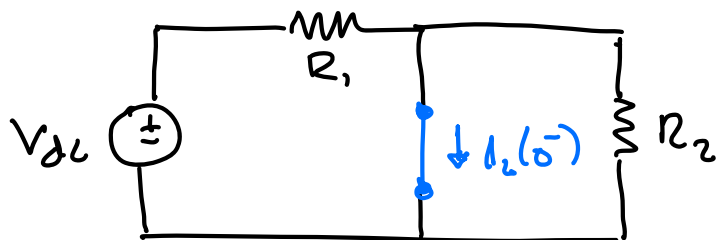① @ $t = 0^-$ (before switch opens) we're in steady state




$$i_L(0^-) = \frac{V_{dc}}{R_1}$$

Since no ∞ voltage when switch opens


$$i_L(0^+) = i_L(0^-) = \frac{V_{dc}}{R_1}$$

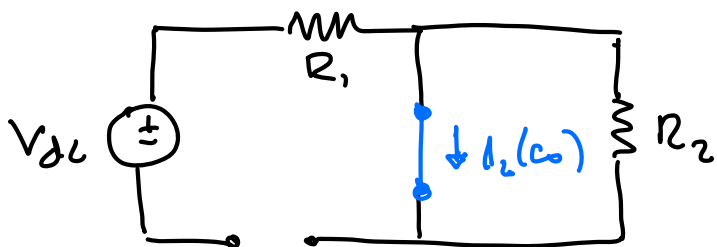② as $t \rightarrow \infty$ (long after switch opens) we're in steady state



$$i_L(t \rightarrow \infty) = 0$$

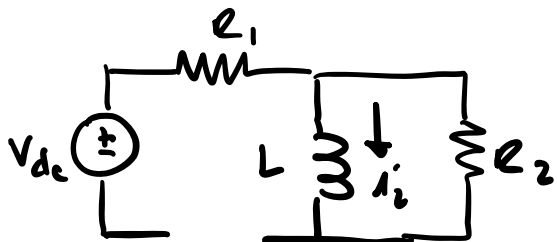③ The transition from the initial condition @ $t=0$ to the final value @ $t=\infty$ must have a time constant of L/R_{Th}



$$R_{Th} = R_2 \Rightarrow \tau = L/R_{Th} = L/R_2$$

$$\therefore i_L(t) = \begin{cases} V_{dc}/R_1 & t \leq 0 \\ V_{dc}/R_1 \cdot e^{-t \cdot R_2/L} & t \geq 0 \end{cases}$$

