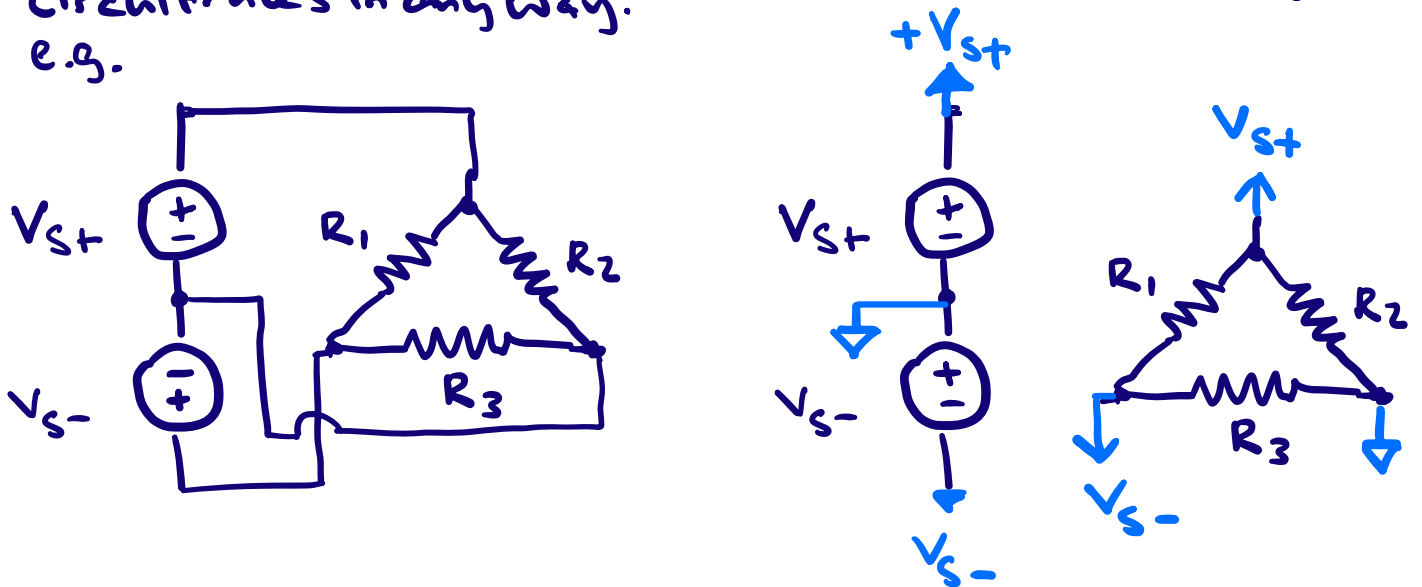


# Circuits Op Amp Comparator, Oscillator ①

## Aside / Reminder: Voltage Bus Notation


We often introduce symbols to convey node connections without explicitly drawing them. This often simplifies diagrams (esp. for power, gnd, etc.) but does not change circuit rules in any way.

e.g.



Amplifiers are a type of device that serves an important need in circuits and has many applications. They may be thought of as three-part devices with a control part, a power part and an output part.



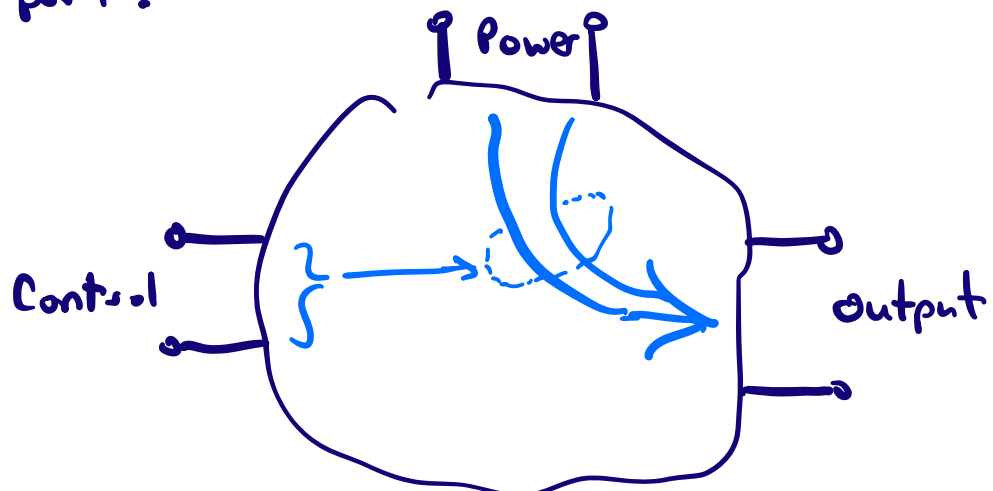
Amplifiers use a small quantity (voltage, current, power) at the control part to deliver a large quantity from a power part to the output part:



The need for amplification is so common that engineers have developed a class of electronic building blocks that realize this function: The Operational Amplifier, or Op-Amp

The symbol for an op-amp:

model As:

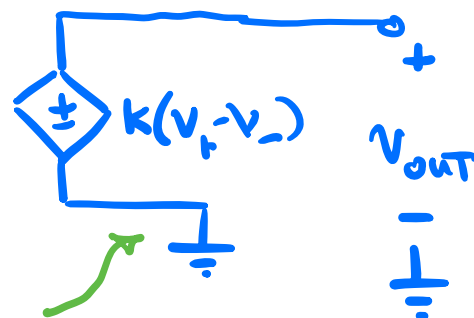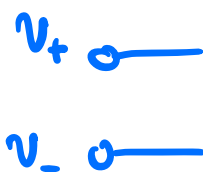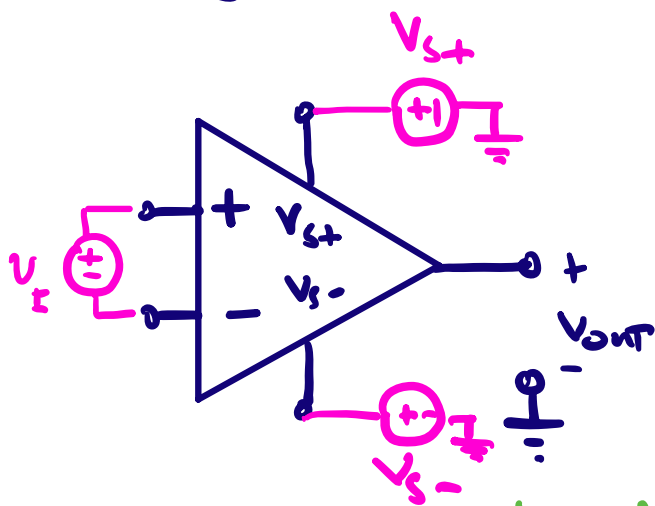


In reality, dependent source may be referenced to  $V_{s-}$ , but this doesn't change the result significantly because  $k$  is BIG (ideally  $k \rightarrow \infty$ )

- A practical op amp has an "open-loop gain"  $k$  that is very large:  $10^5 - 10^6$  in practice. Ideally we treat as  $k \rightarrow \infty$
- In practice, the output voltage  $V_{out}$  is constrained to remain within the range of the power supply, i.e. between  $(V_{s-}, V_{s+})$  or an even narrower range, e.g.  $(V_{s-} - \Delta V, V_{s+} + \Delta V)$

e.g., if


$$\begin{aligned} V_{s+} &= +15V \\ V_{s-} &= -15V \\ \Delta V &= 3V \end{aligned}$$

$V_{out}$  in  $(-12, 12) V$  range

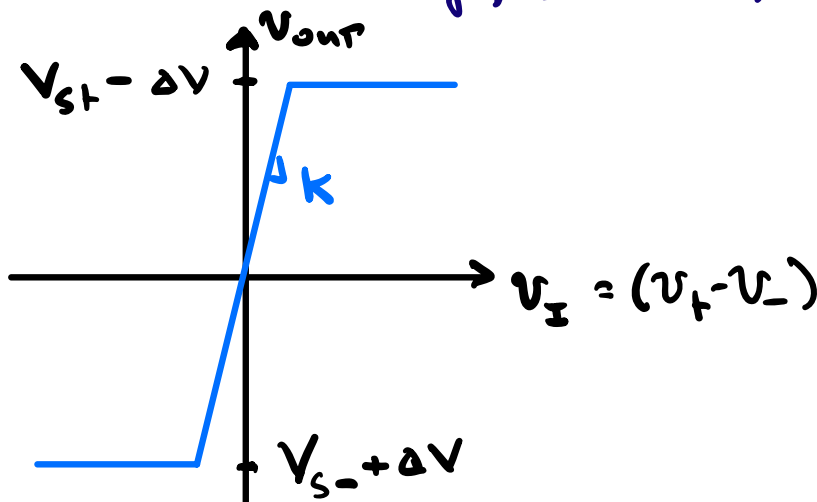


One way we can use an op-amp is as a comparator. (there are special versions designed specifically for use as comparators, though we can do this function with most op amps).

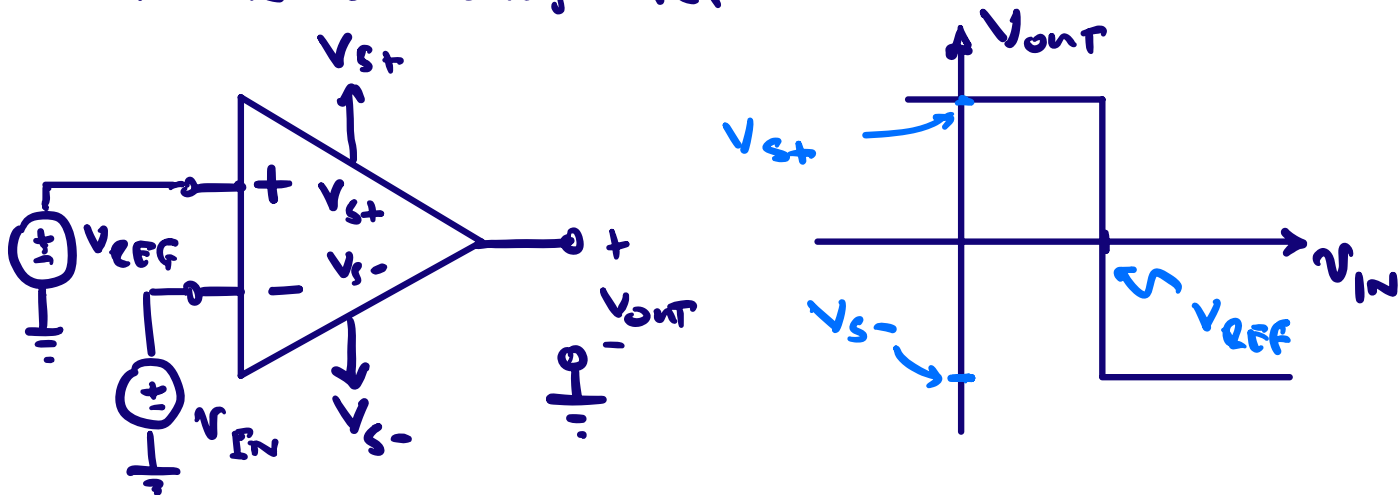Suppose we want to compare some "input" voltage  $V_{IN}$  to a "reference" voltage  $V_{REF}$ :



Our comparator can tell us whether or not our input signal is greater than or less than the reference voltage.

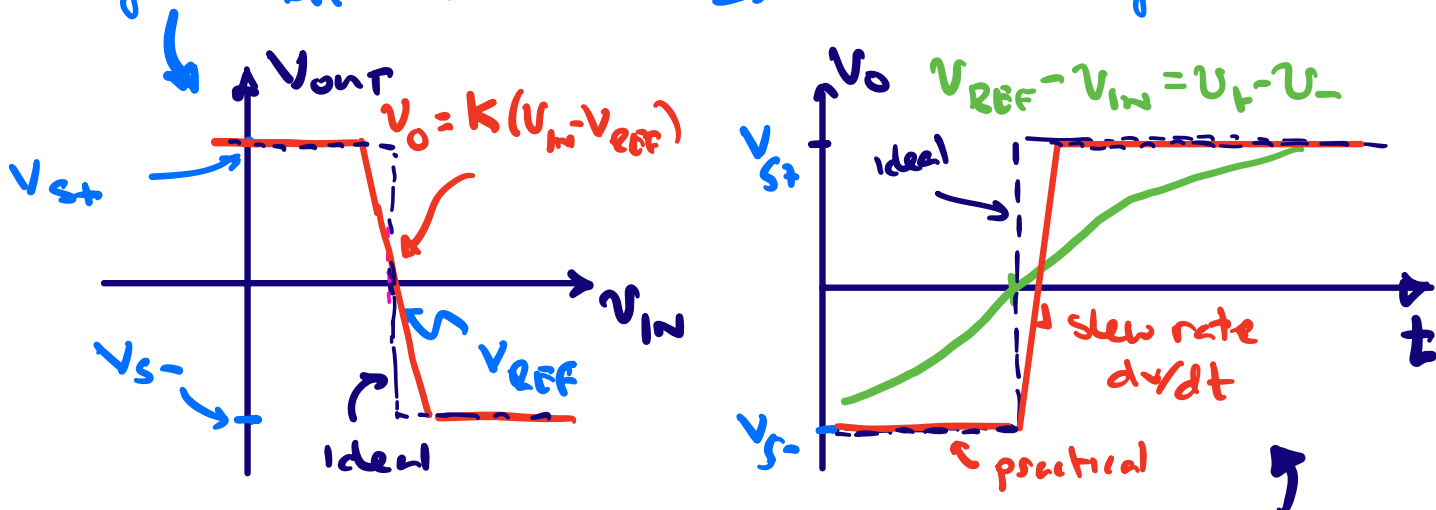In reality the output transitions over a small but nonzero range of  $V_{REF} - V_{IN}$  (but  $k$  is big so transition range is small)





In reality, the speed with which the output can switch is finite, with a limiting "slew rate" in output voltage that depends on the difference between  $V_{+}, V_{-}$  up to a practical maximum that depends on the device.

# Circuits
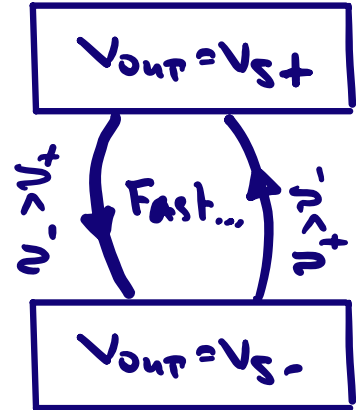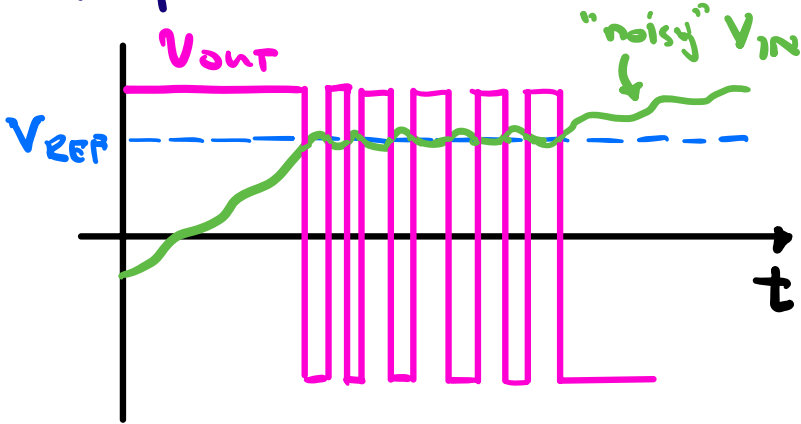
# Op Amp Comparator Oscillator ④


A problem with comparator circuits is that the output can "chatter" back and forth for input voltages near the reference voltage (such that  $V_+$  is very close to  $V_-$ ), especially in the presence of noise:



Such chatter can cause problems for circuits that try to use  $V_{out}$ .

We can fix the chattering problem with "positive feedback" that causes hysteresis in the switching.

See demo


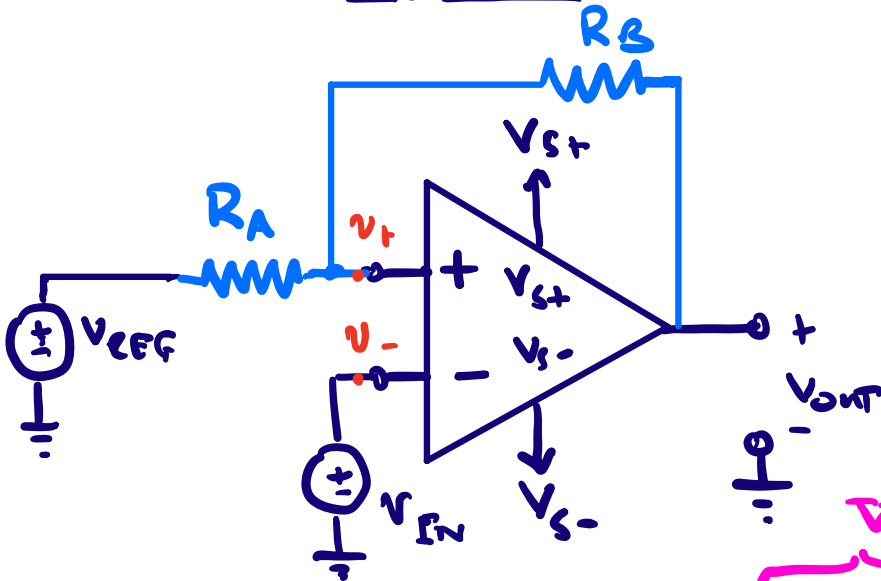


If  $V_{out} = V_{S+} \iff V_{IN} < V_{REF} \cdot \frac{R_B}{R_A + R_B} + V_{S+} \cdot \frac{R_A}{R_A + R_B}$

If  $V_{out} = V_{S-} \iff V_{IN} > V_{REF} \cdot \frac{R_B}{R_A + R_B} + V_{S-} \cdot \frac{R_A}{R_A + R_B}$


Circuits

Op Amp Comparator Oscillator (5)

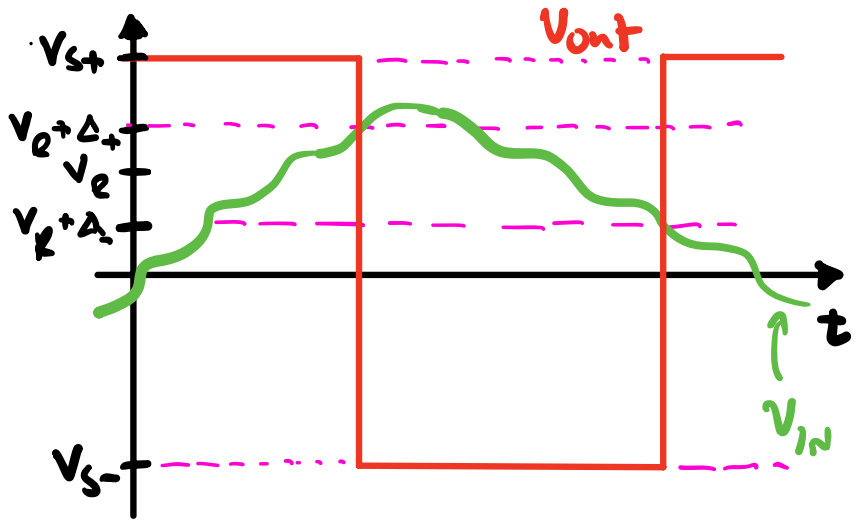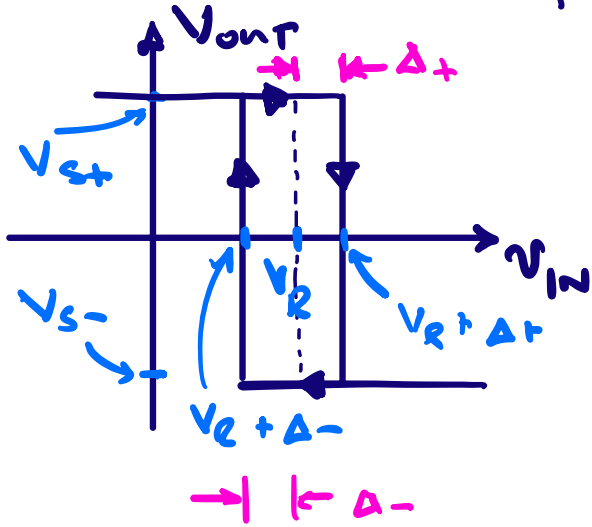


The transition threshold is different for positive- and negative-going transitions, so we do not get chattering at the boundary! (Positive feedback provides hysteresis.)

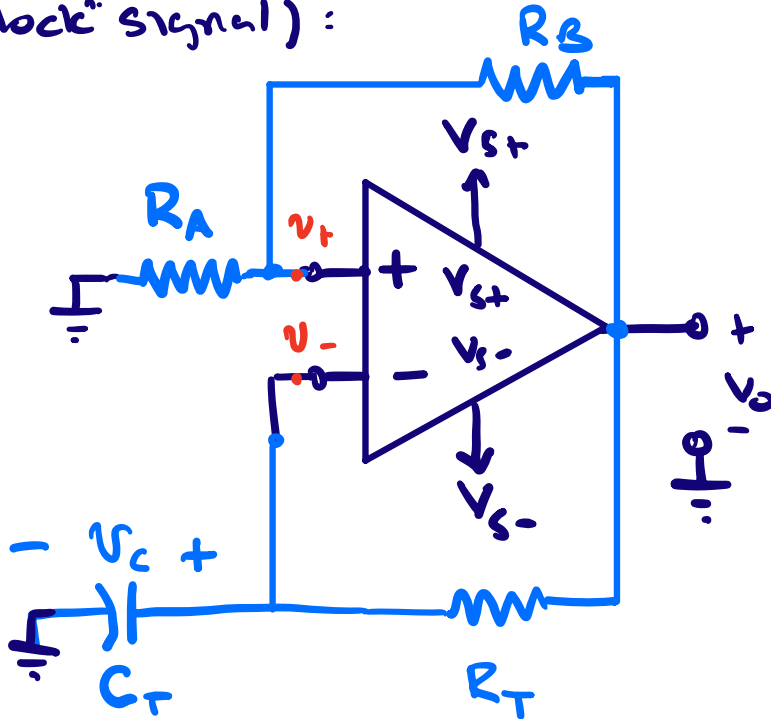We can also use hysteresis (with both +ve and -ve feedback) to build an oscillator. (e.g. to generate a "clock" signal):



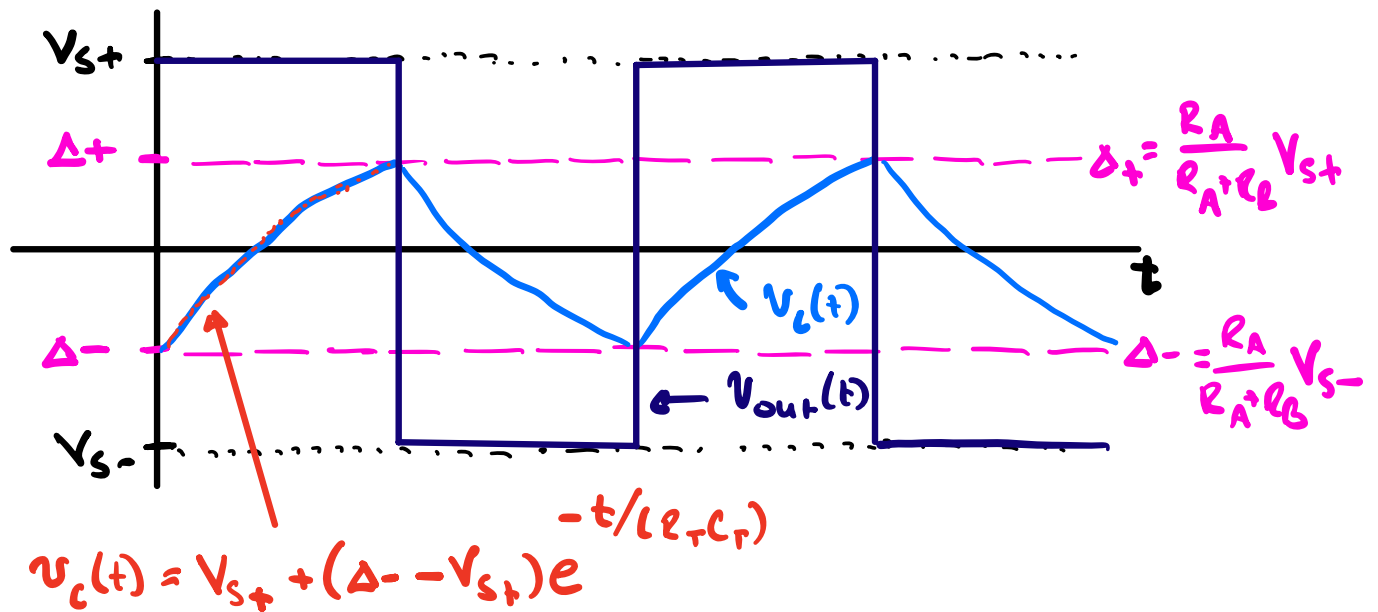Consider  $V_o, V_c$  as a function of time



The oscillation period is related to the output saturation voltages (here  $V_{s+}, V_{s-}$ ), hysteresis band size  $\Delta_+ - \Delta_-$  (determined by  $R_A, R_B$ ) and the time constant  $R_T C_T$