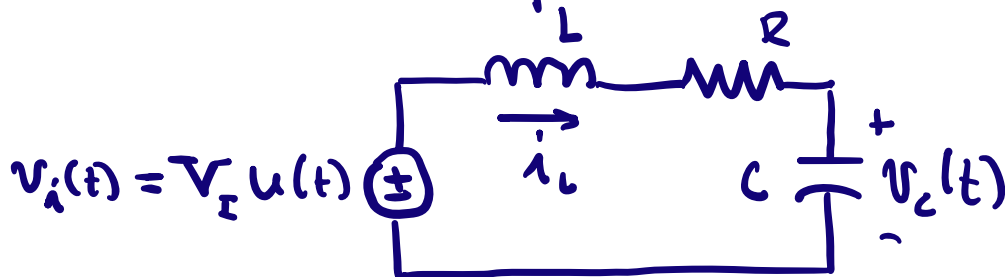


Today let's expand our previous discussion to look at the time-domain behavior of damped second-order circuits.

Consider as an example a "series RLC" circuit:




For this case, we get as initial conditions:  $i_L(0^-) = i_L(0^+) = 0$   
 $V_C(0^-) = V_C(0^+) = 0$

This circuit has two independent energy storage elements. It will thus be represented by a second-order differential equation, and have a response that comprises


- ① A particular response, which we can determine as the dc steady-state response
- ② A natural response having (up to) two natural frequencies and two scaling constants that are determined by the two initial conditions.

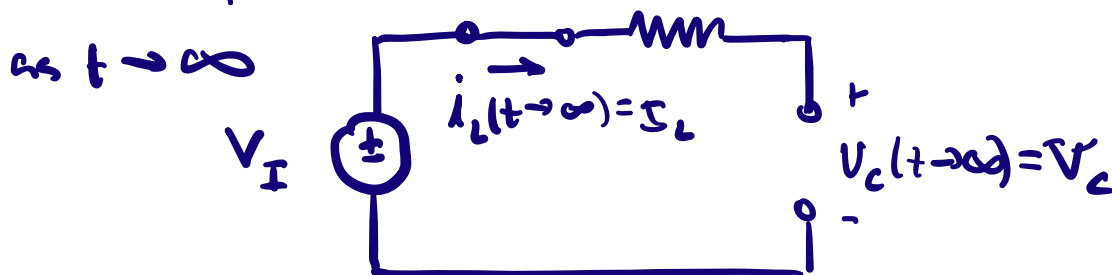Since our input for  $t > 0$  is constant, we already know how to find a particular solution. It is the dc steady-state response.



$$I_L = 0 \quad V_C = V_I$$

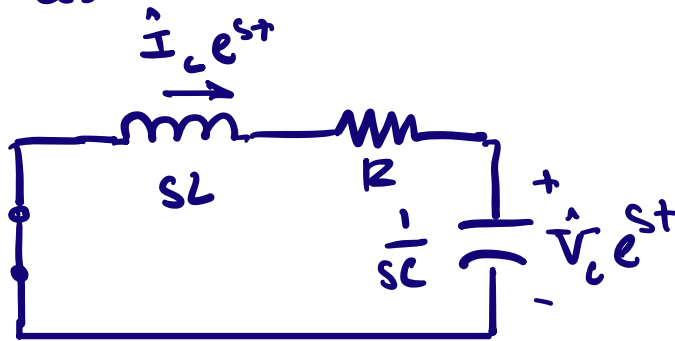We can easily find the form of the natural response by looking at the undriven circuit ( $V_i \rightarrow 0$ ) in terms of impedances:



$$\hat{i}_c e^{st} \left[ sL + R + \frac{1}{sC} \right] = 0$$

$$\hat{i}_c \left[ s^2 LC + sCR + 1 \right] = 0$$


$\therefore$  for  $\hat{i}_c \neq 0$  we require  $s^2 LC + sCR + 1 = 0$

Characteristic eqn: 
$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

The solutions  $s_1, s_2$  to the characteristic equation give the natural response (with scaling constants  $A_1, A_2$ ):

$$v_{c,h} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

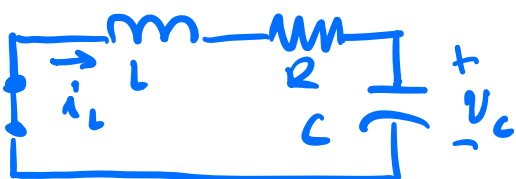Aside: We could also determine the characteristic equation by directly analyzing the circuit in the time domain and guessing solutions of the form  $Ae^{st}$ :



$$\text{KVL: } L \frac{di_L}{dt} + R \cdot i_L + v_c = 0$$

$$\text{and } i_L = i_C = C \frac{dv_c}{dt}$$

## Circuits

## Damped Second-Order Circuits (3)

$$\therefore LC \frac{d^2 v_c}{dt^2} + RC \frac{dv_c}{dt} + v_c = 0$$

Homogeneous differential eqn.

guessing  $v_{c,h} = Ae^{st}$  gives

$$LCs^2 Ae^{st} + RCs Ae^{st} + Ae^{st} = 0$$

$$LCs^2 + RCs + 1 = 0$$

$$\text{or } s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 \quad \text{Characteristic equation}$$

For this system, the natural frequencies  $s$  ( $= s_1, s_2$ ) are:

$$s = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\text{Defining } \alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

called "exponential damping coefficient"

called "undamped natural frequency"

(We use these substitutions to put our equations into a "standard form that applies to all kinds of second-order circuits and systems")

$$\text{we get } s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


The exact form of our solution depends on the relative values of  $\alpha, \omega_0$ .  $s_1, s_2$  may be real or complex.

# Circuits

# Damped Second-Order Circuits (4)

Three cases are possible, each with natural frequencies  $s_1, s_2$  at different places in the complex plane


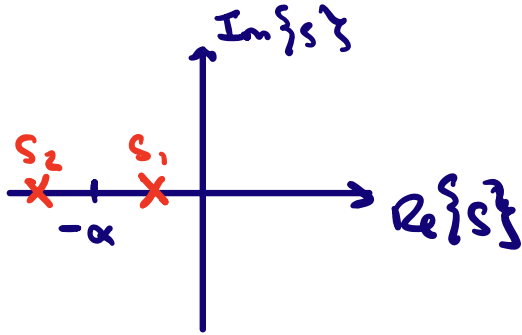
(A) For  $\alpha > \omega_0$  "overdamped case"  $\{s_1, s_2 \text{ real, negative}\}$



$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$


$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$
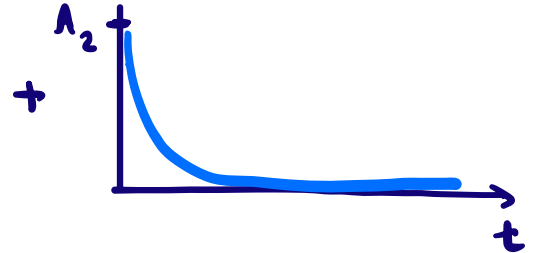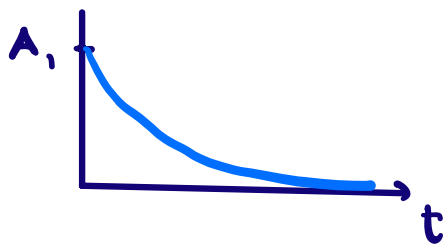
$$v_{c,h}(t) = A_1 e^{-(\alpha - \sqrt{\alpha^2 - \omega_0^2})t} + A_2 e^{-(\alpha + \sqrt{\alpha^2 - \omega_0^2})t}$$



Natural response is a pair of decaying exponentials


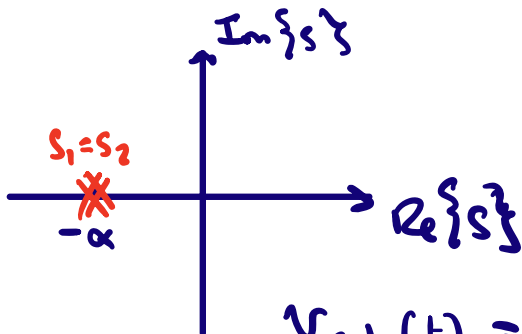
(B) For  $\alpha = \omega_0$  "critically-damped case"  $\{s_1, s_2 \text{ equal, real + negative}\}$



$$s_1 = s_2 = -\alpha$$

Easy to validate that this expression satisfies the homogeneous diff. eq.
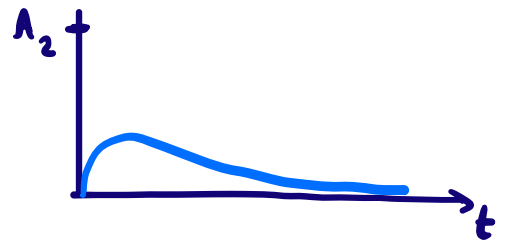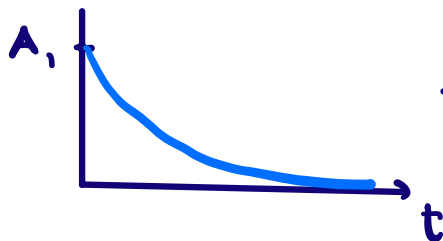
$$v_{c,h}(t) = A_1 e^{-\alpha t} + A_2 t e^{-\alpha t}$$




# Circuits

## Damped Second-Order Circuits (5)

(C) For  $\alpha < \omega_0$  "underdamped case"  $\{s_1, s_2 \text{ complex}\}$

$$s_{1,2} = -\alpha \pm j \sqrt{\omega_0^2 - \alpha^2}$$

$$= -\alpha \pm j \omega_d$$

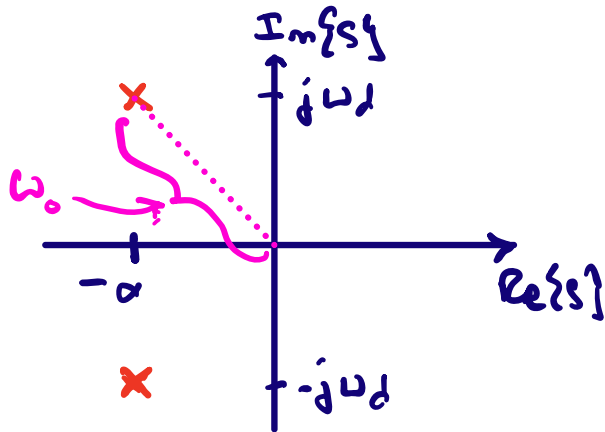

$\omega_d \triangleq \sqrt{\omega_0^2 - \alpha^2}$   
 is the "damped natural frequency"  
 ( $\omega_0 = \sqrt{\omega_d^2 + \alpha^2}$ )

$$\therefore v_{c,h}(t) = A_1 e^{-\alpha t} e^{j\omega_d t} + A_2 e^{-\alpha t} e^{-j\omega_d t}$$


OR  $v_{c,h}(t) = B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)$

OR  $v_{c,h}(t) = C_1 e^{-\alpha t} \cos(\omega_d t + C_2)$

In the underdamped case, our natural response is a decaying sinusoid:

$\omega_d$  "damped natural frequency" is the oscillation angular frequency

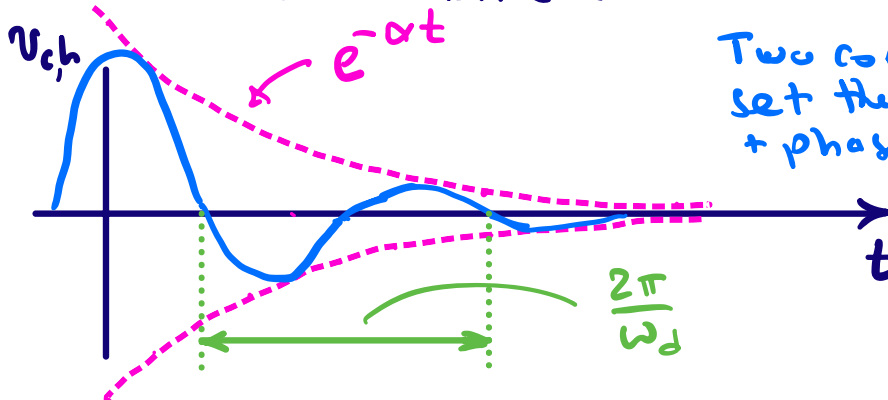$\alpha$  "exponential damping coefficient" is the decay rate of oscillation (i.e. of the envelope)




Two coeffs (e.g.  $B_1, B_2$ ) set the magnitude + phase of the oscillation to meet initial conditions

# Circuits
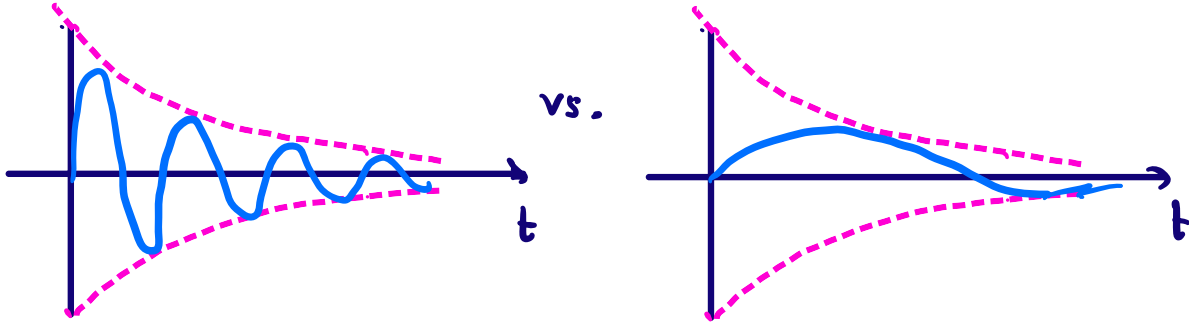
# Damped Second-Order Circuits (6)

The relative rate at which the natural response oscillates + decays determines a lot about the system response, e.g.



To characterize this, we define circuit "quality factor"

Quality Factor

$$Q_0 \triangleq \frac{1}{2} \cdot \frac{\omega_0}{\alpha}$$

Quality factor often appears as a metric

Tells us how quickly the natural response oscillates as compared to how it decays:

$Q_0 < \frac{1}{2}$  overdamped (exponential decay only)

$Q_0 \sim 1$  oscillates but damps quickly


$Q_0 \gg 1$  highly oscillatory

writing the characteristic equation in terms of  $\omega_0, Q_0$ :

$$s^2 + \frac{\omega_0}{Q_0} s + \omega_0^2 = 0$$

We can identify behavior directly from the characteristic equation!

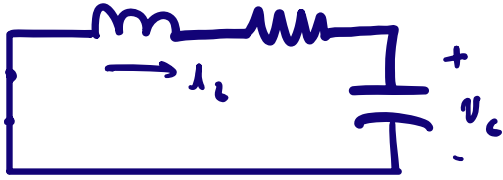In circuit terms: For the series RLC circuit



$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q_0 = \frac{\sqrt{L/C}}{R} = \frac{z_0}{R}$$

where  $z_0 = \sqrt{\frac{L}{C}}$  is the

"characteristic impedance"

So we will have

- high- $Q$  (highly oscillatory) behavior when  $R \ll \sqrt{\frac{L}{C}}$
  - oscillation with rapid damping for  $R \approx \sqrt{\frac{L}{C}}$
  - overdamped exponential decay only for  $R > 2\sqrt{\frac{L}{C}}$
- \* So just by comparing circuit values  $\sqrt{\frac{L}{C}}$ ,  $R$  we can tell how oscillatory the response will be.

The details are different for other circuits, e.g. parallel RLC, but usually boil down to comparisons between  $\sqrt{\frac{L}{C}}$  and  $R$ .

- \* we can also identify circuit characteristics from waveforms, e.g. for high  $Q$  ( $Q_0 > 5$ ) case

$$\Rightarrow \omega_d \approx \omega_0 = \frac{1}{\sqrt{LC}} \rightarrow \text{look at natural response oscillation frequency.}$$

$$\Rightarrow \text{oscillations decay (to } \approx 4\% \text{ of initial) in } Q_0 \text{ cycles (so count oscillations to estimate } Q_0 \text{).}$$

See demo circuit for example behavior!

Putting this all together:

Given an "arbitrary" LRC circuit, we can get a response to a constant (or "step") input and initial conditions

- ① Steady-state dc response ("particular response") from the method at the bottom of p. 1
- ② To get the form of the natural (homogeneous) response, find the characteristic equation + solve for natural frequencies  $s_1, s_2$

[All  $v$ 's,  $i$ 's in the circuit respond with the same natural frequencies!]

Response might be

- ① overdamped
- ② critically damped
- ③ underdamped

We can identify the expected behavior by:

- A. Looking at circuit values  $R, \sqrt{L/C}, 1/\sqrt{LC}$
- B. Looking at characteristic equation in terms of  $\zeta, \omega_0$

- ③ Add particular response + natural response, and apply initial conditions to find the scaling constants in the natural response.

