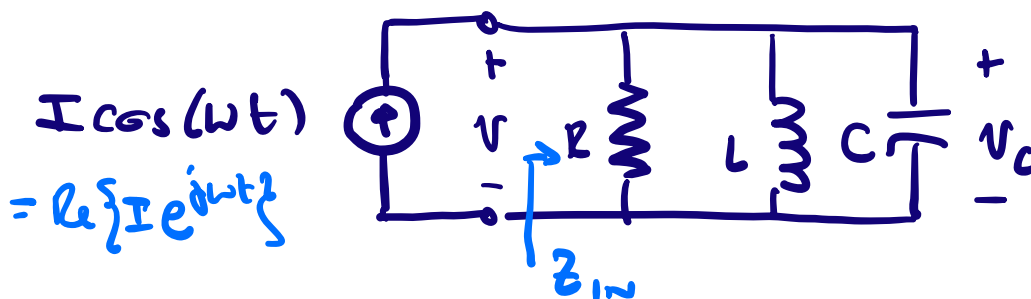


We have seen that second-order RLC circuits can have interesting response properties. Let's further consider their behavior under sinusoidal drive conditions.

Resonance in a second-order circuit can be defined as when the voltage and current at the network input terminals are in phase (i.e. the load impedance seen by the source is resistive.) {Resonance implies a sinusoidal drive of the network.}

One gets maximum amplitude responses in a second-order system for a frequency at or near resonance. The maximum response frequency tends to converge on the resonant frequency as damping becomes lighter, as shown below.

Example: Parallel Resonant Circuit



$$\text{Admittance } Y = 1/Z = \frac{1}{R} + \frac{1}{sL} + sC$$

$$\Rightarrow Z_{in} = \frac{1}{\frac{1}{R} + \frac{1}{sL} + sC}$$

For sinusoidal drive,  $s = j\omega$

$$\therefore Z_{in} = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{1}{\frac{1}{R} + j(\omega C - \frac{1}{\omega L})}$$


$$|Z_{in}| = \frac{1}{\sqrt{(\frac{1}{R})^2 + (\omega C - \frac{1}{\omega L})^2}} \quad \angle Z_{in} = -\text{ATAN} \left[ \frac{\omega C - \frac{1}{\omega L}}{1/R} \right]$$

# Circuits Resonance and Second-Order Systems (2)

Let's consider the input impedance  $Z_{in}$  graphically:

@  $\omega$  small,  $\omega L \ll R, \frac{1}{\omega C} \rightarrow$  inductor determines  $Z_{in}$

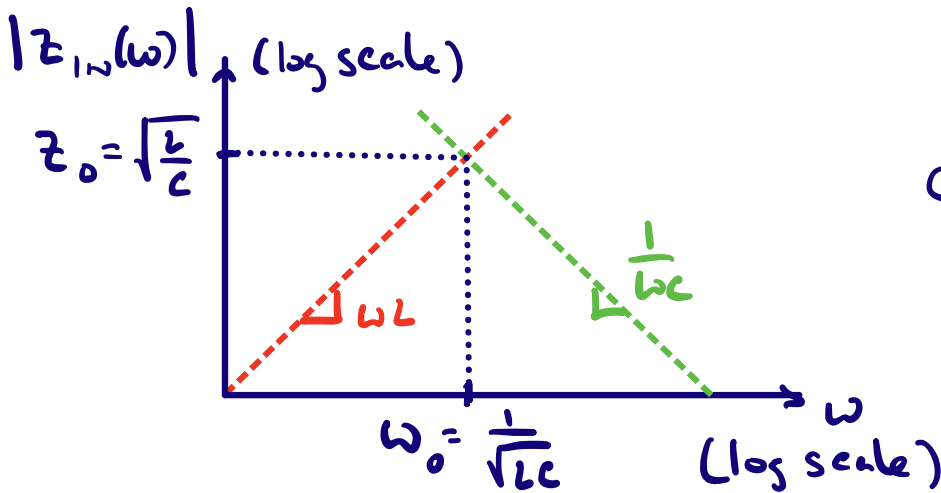@  $\omega$  big  $\frac{1}{\omega C} \ll R, \omega L \rightarrow$  capacitor determines  $Z_{in}$



@ low  $\omega$   
 $Z_{in} \approx j\omega L$

@ high  $\omega$   
 $Z_{in} \approx -j \frac{1}{\omega C}$

at some intermediate frequency, the low- and high-frequency asymptotes meet!

$$|Z_L| = |Z_C|$$

Asymptotes meet at the "undamped natural frequency"  $\omega_0$ !

$$\omega L = \frac{1}{\omega C} \text{ happens at } \omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

The impedance magnitudes of the inductor + capacitor (and associated asymptotes) are equal @  $\omega = \omega_0$

$$|Z_L| = \omega_0 L = |Z_C| = \frac{1}{\omega_0 C} = \sqrt{\frac{L}{C}} = Z_0$$

The impedance magnitudes of both the inductor and capacitor @  $\omega = \omega_0$  are both equal to the "characteristic impedance"  $Z_0$

Note: @  $\omega = \omega_0$   $|I_L| = \frac{|V_C|}{\omega_0 L}$

$$\Rightarrow \omega_0 L = Z_0 = \frac{|V_C|}{|I_L|}$$

$Z_0$  equals the ratio of the capacitor voltage to inductor current @  $\omega = \omega_0$

# Circuits Resonance and Second-Order Systems (3)


At  $\omega = \omega_0$ ,  $Z_{IN} = R$  ( $|Z_{IN}| = R$ , &  $Z_{IN} = \textcircled{0}$ )

$\therefore$  we are at resonance! At resonance, all drive current  $I$  goes into  $R$ . The inductor and capacitor currents cancel!


What happens near  $\omega = \omega_0$  depends upon the relative values of  $Z_0, R$

$R \ll Z_0$

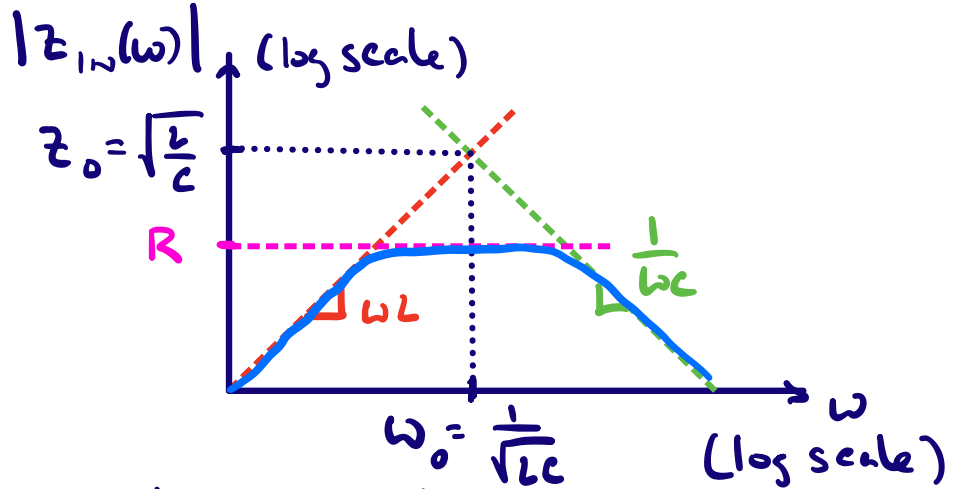
(note: circuit is overdamped for  $R < \frac{1}{2} Z_0$ )



$R \sim Z_0$   
"low Q"

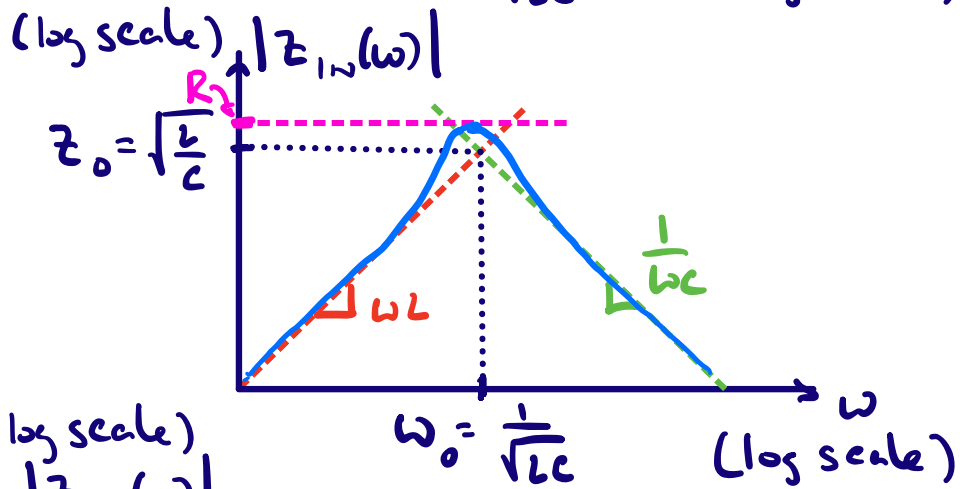

$R \gg Z_0$   
"high Q"

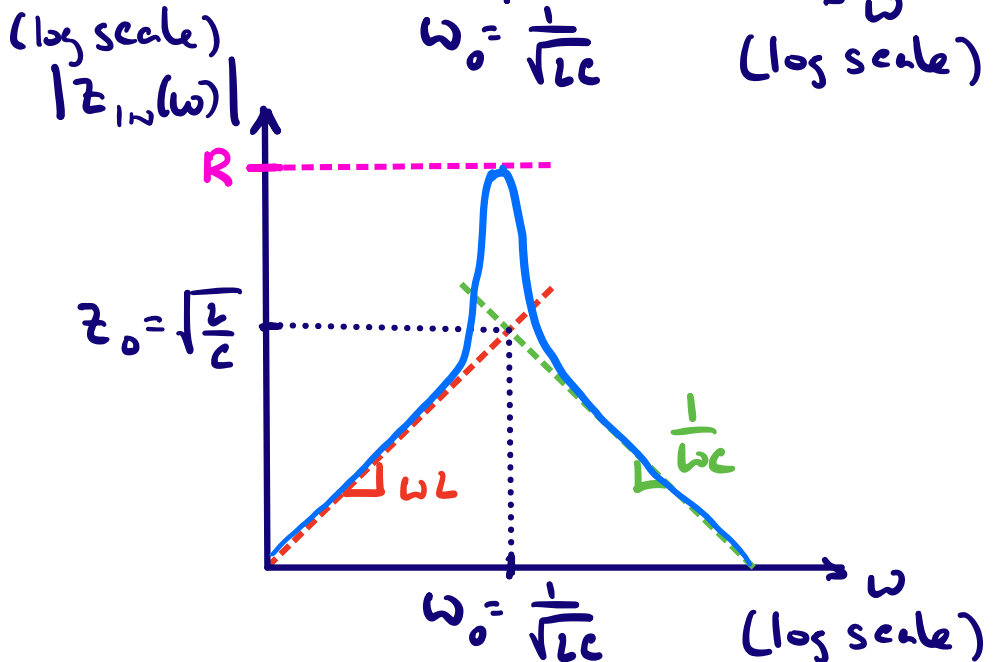

# Circuits Resonance and Second-Order Systems (4)

We sometimes refer to the "quality factor"  $Q_0$  of a second-order circuit, calculated from the characteristic equation expressed in a standard form:

$$s^2 + 2\alpha s + \omega_0^2 = 0 \quad \text{or} \quad s^2 + \left(\frac{\omega_0}{Q_0}\right)s + \omega_0^2 = 0$$

Where  $\omega_0 \triangleq$  undamped natural frequency

$\alpha \triangleq$  exponential damping coefficient

$Q_0 \triangleq$  circuit quality factor

$\omega_d \triangleq$  damped natural frequency

$$Q_0 \triangleq \frac{1}{2} \frac{\omega_0}{\alpha}$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$


In our circuit :

$$Z_{in}(s) = \frac{sL}{s^2LC + s\frac{L}{R} + 1} = \frac{1}{C} \cdot \frac{s}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

characteristic eqn:


$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$
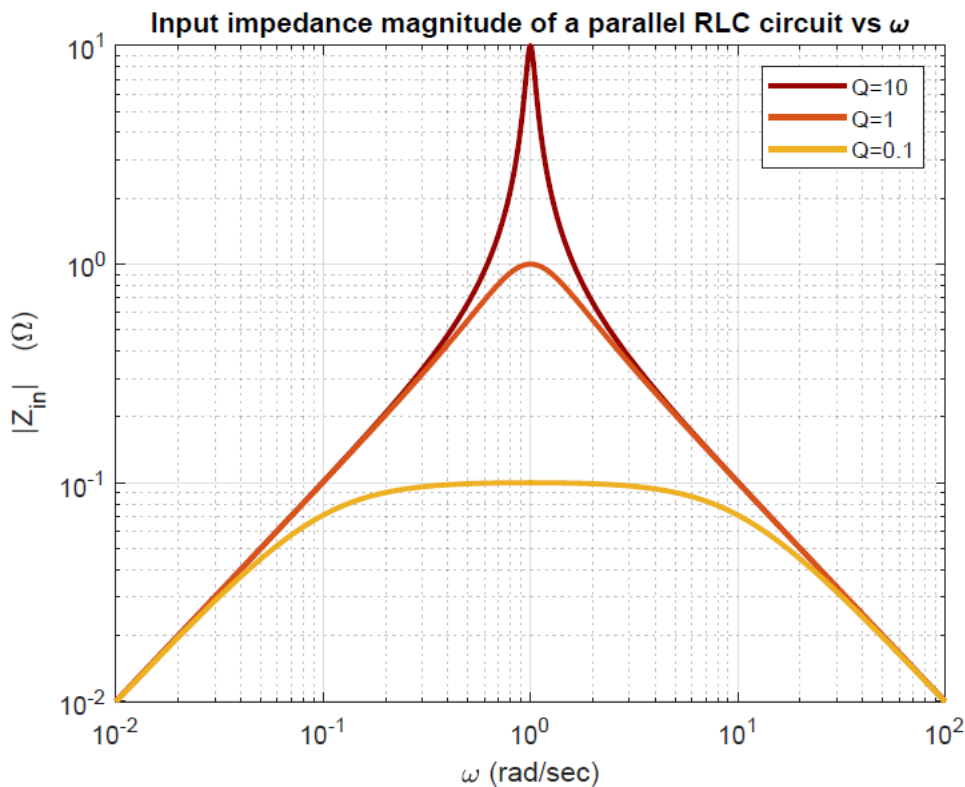
$$\therefore \omega_0 = \frac{1}{\sqrt{LC}} \quad \alpha = \frac{1}{2RC} \quad \text{and} \quad Q_0 = \frac{R}{\sqrt{L/C}} = \frac{R}{Z_0}$$




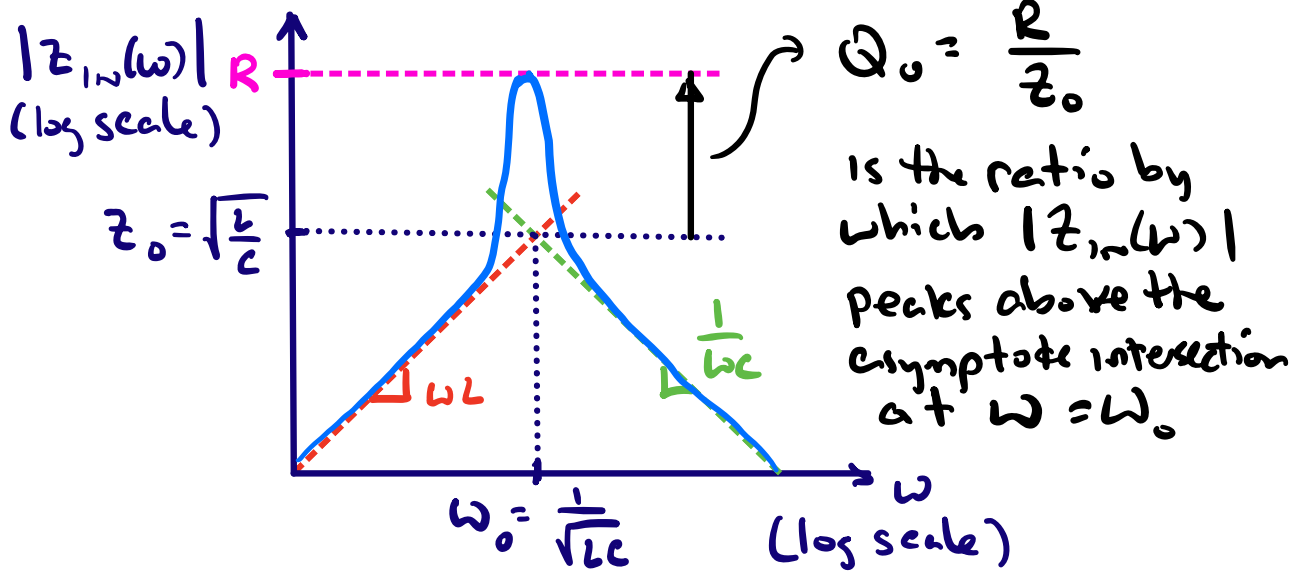Example:  
 $L = 1 \text{ H}$   
 $C = 1 \text{ F}$   
 $R =$   
 $(0.1, 1, 10)$   
 $\Omega$

One reason we might express things in terms of  $Q_0$  is that  $Q_0$  expresses the amount of peaking and the frequency range over which peaking occurs in the transfer function



Also,  $Q_0$  reflects the fractional width in frequency the fractional "bandwidth" over which the peaking occurs. We consider the range of frequency over which  $|Z_{in}|$  is  $\geq \frac{1}{\sqrt{2}} R$ . This is the "half-power" bandwidth.

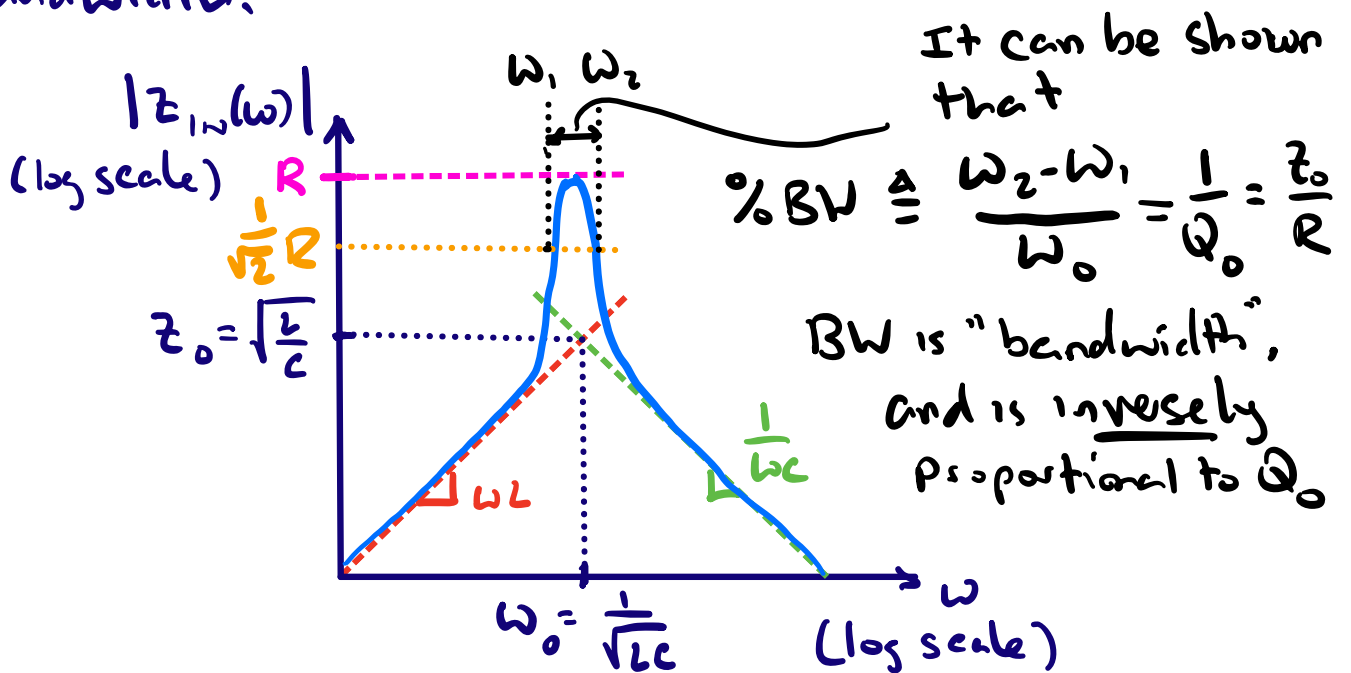

So  $Q_0$  gives the amount of peaking and bandwidth of peaking in  $|Z_{in}(\omega)|$ ! More peaking  $\rightarrow$  narrower BW

# Circuits Resonance and Second-Order Systems (6)

Note that these sinusoidal excitation characteristics relate back to the time-domain natural responses and to the natural frequencies s "poles" where  $Z_{IN}(s) \rightarrow \infty$

characteristic eqn:

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

gives natural frequencies


$$s_{1,2} = -\alpha \pm j\omega_d$$

where  $\alpha = \frac{1}{2RC}$ ,  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$  for  $\begin{cases} \omega_0 \triangleq \frac{1}{\sqrt{LC}} \\ \tau_0 \triangleq \sqrt{\frac{L}{C}} \end{cases}$

If  $R < \frac{1}{2}\tau_0$  gives  $s_1, s_2$  on real axis "overdamped"

$R = \frac{1}{2}\tau_0$  gives  $s_1, s_2 = \text{end}$  on real axis "critically damped"

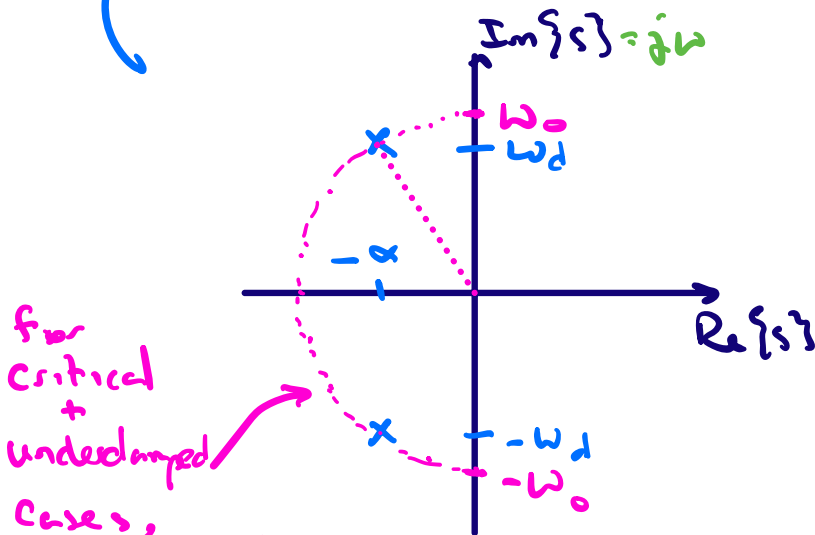$R > \frac{1}{2}\tau_0$  gives  $s_1, s_2$  in complex plane "underdamped"




For critical + underdamped cases, at constant  $L, C$ ,  $\omega_0 = \frac{1}{\sqrt{LC}}$  is constant, pole locations vary with  $R$  on a circle of radius  $\omega_0$   
 $\omega_0 = \sqrt{\alpha^2 + \omega_d^2}$

Natural Responses

overdamped  $R < \frac{1}{2}\tau_0$



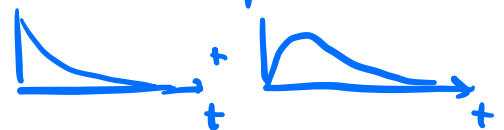critically damped  $R = \frac{1}{2}\tau_0$




underdamped  $R \sim \tau_0$  poles  $\sim 45^\circ$  to real axis

"low Q"



underdamped  $R \gg \tau_0$  poles near  $j\omega$  axis

"high Q"

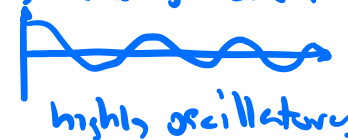

highly oscillatory

where "high Q" is  $Q_0 = \frac{R}{\sqrt{L/C}} = \frac{R}{\tau_0} \gg 1$

# Circuits Resonance and Second-Order Systems (7)

Note that Quality factor has a more general definition and can be applied to any sinusoidally-driven LTI network:


We can define the quality factor of a sinusoidally-driven system as

$$Q \triangleq 2\pi \frac{\text{Peak energy stored over a cycle}}{\text{Total energy dissipated in a cycle}}$$

Essentially,  $Q$  is a dimensionless measure of how much energy we are dissipating in a circuit as compared to how much energy we are storing, with higher  $Q$  meaning lower fractional dissipation.

High  $Q \leftrightarrow$  low % dissipation

Example: a parallel RC circuit

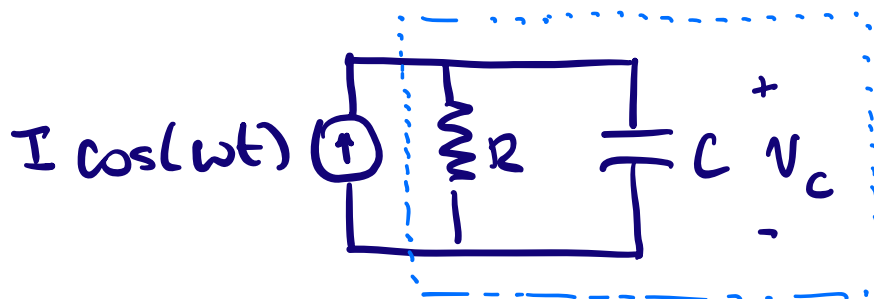

$V_c(t)$  will be a sinusoidal voltage with some frequency-dependent amplitude  $V$


$$\therefore \text{peak energy stored} = \frac{1}{2} C V_c^2$$

$$\text{energy dissipated in } R = \underbrace{\left( \frac{1}{2} \frac{V_c^2}{R} \right)}_{\text{Average power}} \underbrace{\left( \frac{2\pi}{\omega} \right)}_{\text{length of one period } T}$$

$$\therefore Q = 2\pi \frac{\frac{1}{2} C V_c^2}{\frac{1}{2} \frac{V_c^2}{R} \cdot \frac{2\pi}{\omega}} = \omega RC$$
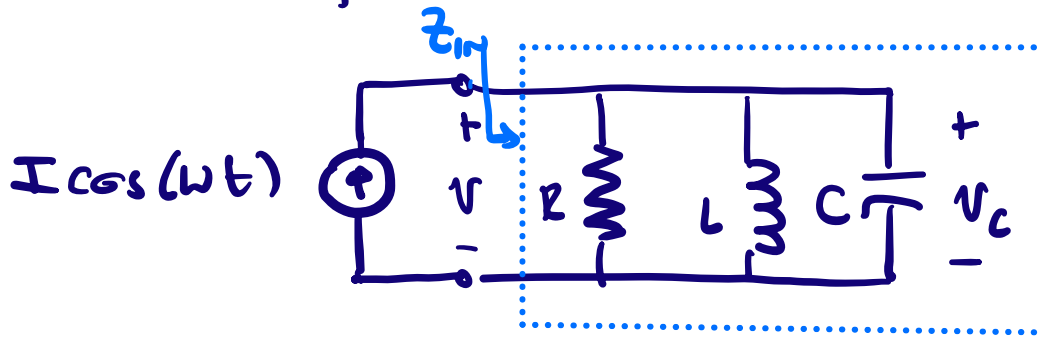
# Circuits Resonance and Second-Order Systems (8)

We can find quality factor for an RLC circuit such as our "parallel" resonant circuit



The quality factor  $Q$  will be a function of frequency

However, it is often of interest to find the quality factor at resonance (i.e., at the resonant frequency  $\omega_0$ ). Let's call this specific value  $Q_0$

$$Q_0 \triangleq Q(\omega) \Big|_{\omega=\omega_0} = \text{The quality factor at the frequency where } z_{in} \text{ is resistive}$$

If we work it out, we will find that

$$Q(\omega) \Big|_{\omega=\omega_0} = Q_0 = \frac{R}{Z_0}$$

So when we are describing the "quality factor" of a second-order resonant circuit, we generally mean the quality factor at resonance!

$$\therefore Q_0 = 2\pi \frac{\text{Peak energy stored in } L, C}{\text{Energy dissipated in } R \text{ over a cycle}} \quad @ \omega = \omega_0$$