


# Circuits Second-Order Circuits and Filtering ①

Let's consider a series RLC circuit driven with a sinusoidal voltage input:

$$v_i(t) = V_I \cos(\omega t + \phi_I) = \operatorname{Re} \{ V_I e^{j\phi_I} e^{j\omega t} \}$$

or
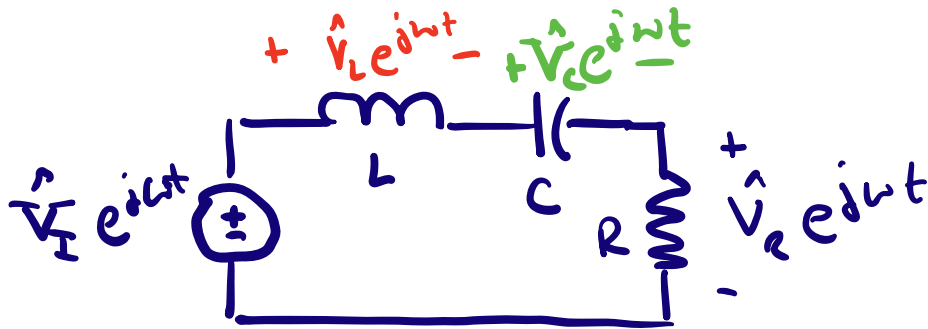
$$= \operatorname{Re} \{ \hat{V}_I e^{j\omega t} \} \quad \text{where } \hat{V}_I = V_I e^{j\phi_I}$$



Let's first consider the transfer function from the input voltage to the resistor voltage

$$\frac{\hat{V}_R}{\hat{V}_I} = H_R(s) = \frac{R}{R + sL + 1/sC} = \frac{R s C}{s^2 L C + s C R + 1}$$

$$= \frac{R}{L} \cdot \frac{s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

The characteristic equation is:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

matching this to  $s^2 + 2\alpha s + \omega_0^2 = s^2 + \left(\frac{\omega_0}{Q_0}\right)s + \omega_0^2 = 0$

undamped natural frequency  $\omega_0 = \frac{1}{\sqrt{LC}}$

exponential damping coeff.  $\alpha = \frac{R}{2L}$

circuit quality factor  $Q_0 = \frac{\sqrt{L/C}}{R} = \frac{Z_0}{R}$

for characteristic impedance  $Z_0 = \sqrt{\frac{L}{C}}$

# Circuits Second-Order Circuits and Filtering (2)

@  $s = j\omega$  (sinusoidal input):

$$H_R(\omega) = \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC}$$

$$|H_R(\omega)| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} \quad \angle H_R(\omega) = \frac{\pi}{2} - \text{ATAN} \left\{ \frac{\omega RC}{1 - \omega^2 LC} \right\}$$

$\therefore$  In sinusoidal steady state:



$$v_R(t) = \frac{\omega RC V_I}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} \cdot \cos\left(\omega t + \phi_I + \frac{\pi}{2} - \text{ATAN} \left\{ \frac{\omega RC}{1 - \omega^2 LC} \right\}\right)$$

Let's consider the magnitude + phase of  $H_R(\omega)$  over frequency.

Frequency	$ H_R(\omega) $	$\angle H_R(\omega)$
$\left\{ \begin{array}{l} \omega \ll \frac{1}{\sqrt{LC}} \\ \omega \ll \frac{1}{RC} \end{array} \right.$	$\approx \omega RC$	$= \frac{\pi}{2}$
$\omega = \frac{1}{\sqrt{LC}}$	1	$\ominus$
$\left\{ \begin{array}{l} \omega \gg \frac{1}{\sqrt{LC}} \\ \omega \gg \frac{1}{RC} \end{array} \right.$	$\approx \frac{R}{\omega L}$	$= -\frac{\pi}{2}$

Asymptotes intersect @  $\omega RC = \frac{R}{\omega L} \rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$   
 at a value  $\frac{R}{\sqrt{LC}} = \frac{R}{Z_0}$

Circuits Second-Order Circuits and Filtering  
 for All values of R, L, C  $|H_c(\omega)|$  peaks at 1.

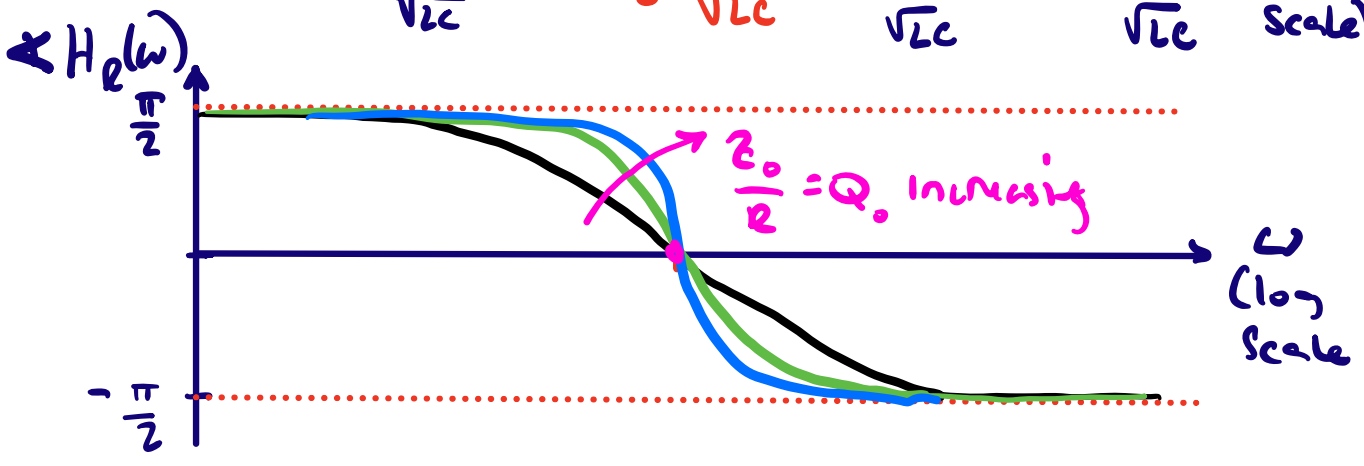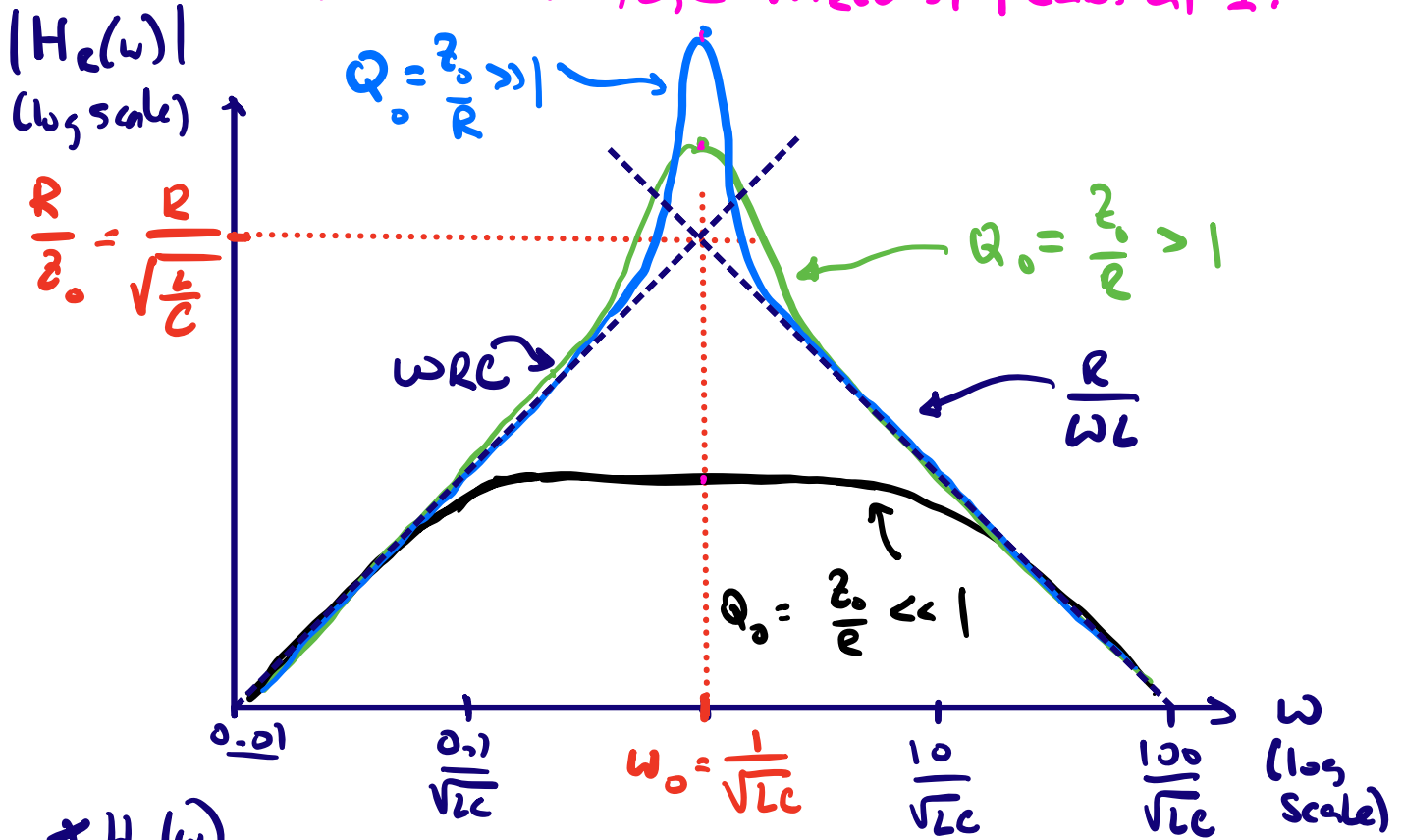


The peaking / sharpness in  $H_c(\omega)$  is reflected in the degree of damping in the natural response.  
 (see demo)

- overdamped  $Q_0 < \frac{1}{2}$   $\leftrightarrow$
- critically damped  $Q_0 = \frac{1}{2}$   $\leftrightarrow$
- underdamped  $Q_0 > \frac{1}{2}$   $\leftrightarrow$
- very underdamped  $Q_0 \gg \frac{1}{2}$   $\leftrightarrow$


Circuits Second-Order Circuits and Filtering  
 Consider our circuit as a filter, where  $V_I$  is the input and  $V_R$  is the output:

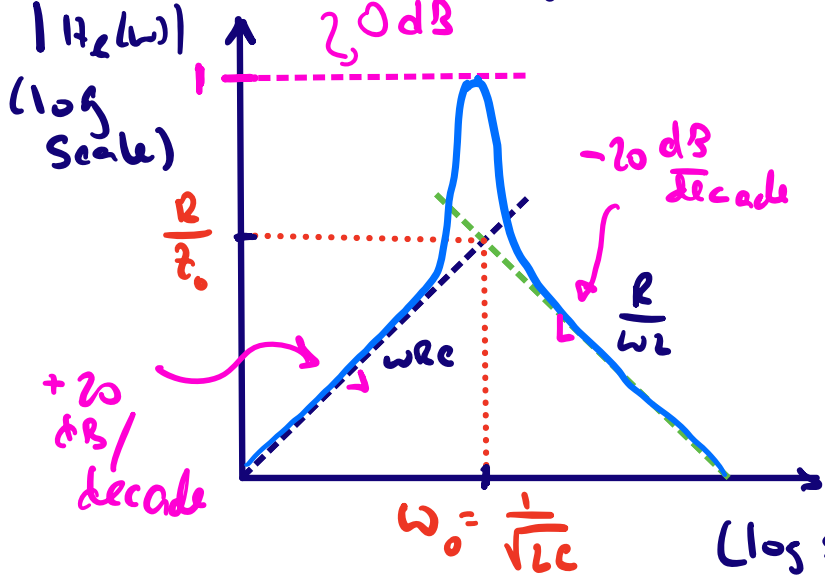$H_R(\omega)$  passes frequencies near  $\omega = \omega_0$ , and attenuates frequencies far above or far below  $\omega_0$



This is a "bandpass" filter.  
 (e.g. can be used to pass signals from a radio station transmitting @  $\omega = \omega_0$ , while attenuating signals from stations at other frequencies)

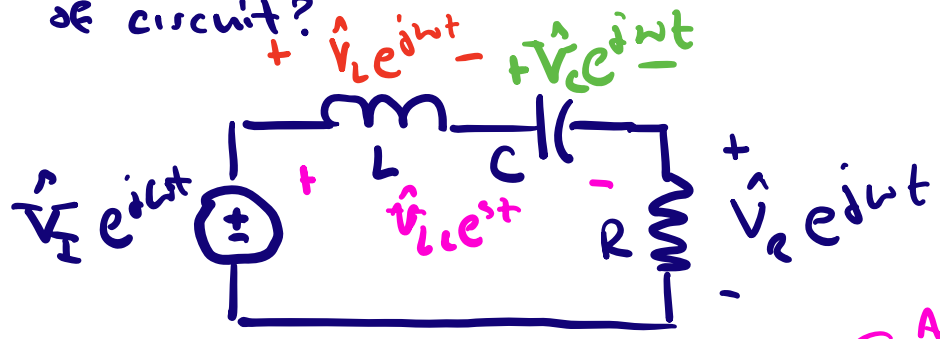Can we build other kinds of filters with this kind of circuit?



$$H_{LC}(s) = \frac{\hat{V}_{LC}}{\hat{V}_I} = 1 - H_R(s)$$

All of the input except  $V_R$ . This is a bandstop filter! Blocks signals near  $\omega = \omega_0$

$$H_C(s) = \frac{\hat{V}_C}{\hat{V}_I} = \frac{1}{\frac{1}{sC} + sL + R} = \frac{1}{LC} \cdot \frac{1}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$H_L(s) = \frac{\hat{V}_L}{\hat{V}_I} = \frac{sL}{\frac{1}{sC} + sL + R} = 1 \cdot \frac{s^2}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

# Circuits Second-Order Circuits and Filtering

5

\* Note that all transfer functions  $H_x(s)$  in the system have the same denominator, and hence all have the same characteristic equation and the same natural frequencies. (with the same form of the natural response).

$\Rightarrow \omega_0, \varphi_0, \zeta_0, \alpha, \omega_d$ , etc. are the same

What is different about different transfer functions is the numerator of  $H(s)$ . The numerator determines important aspects of how an input is reflected in the output.

Consider the transfer function from  $V_E$  to  $V_C$


$$H_c(\omega) = H_c(s) \Big|_{s=j\omega} = \frac{1}{LC} \cdot \frac{1}{(\frac{1}{LC} - \omega^2) + j\omega R/L}$$

$$H_c(\omega) = \frac{1}{(1 - \omega^2 LC) + j\omega RC}$$

$$|H_c(\omega)| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

$$\angle H_c = -\text{ATAN}\left(\frac{\omega RC}{1 - \omega^2 LC}\right)$$

Frequency	$ H_c(\omega) $	$\angle H_c(\omega)$
$\omega \ll \frac{1}{\sqrt{LC}}$	$\approx 1$	$= 0$
$\omega \ll \frac{1}{RC}$		
$\omega = \frac{1}{\sqrt{LC}}$	$= \frac{\sqrt{LC}}{R}$	$= -\frac{\pi}{2}$
$\omega \gg \frac{1}{\sqrt{LC}}$		
$\omega \gg \frac{1}{RC}$	$\approx \frac{1}{\omega^2 LC}$	$\approx -\pi$

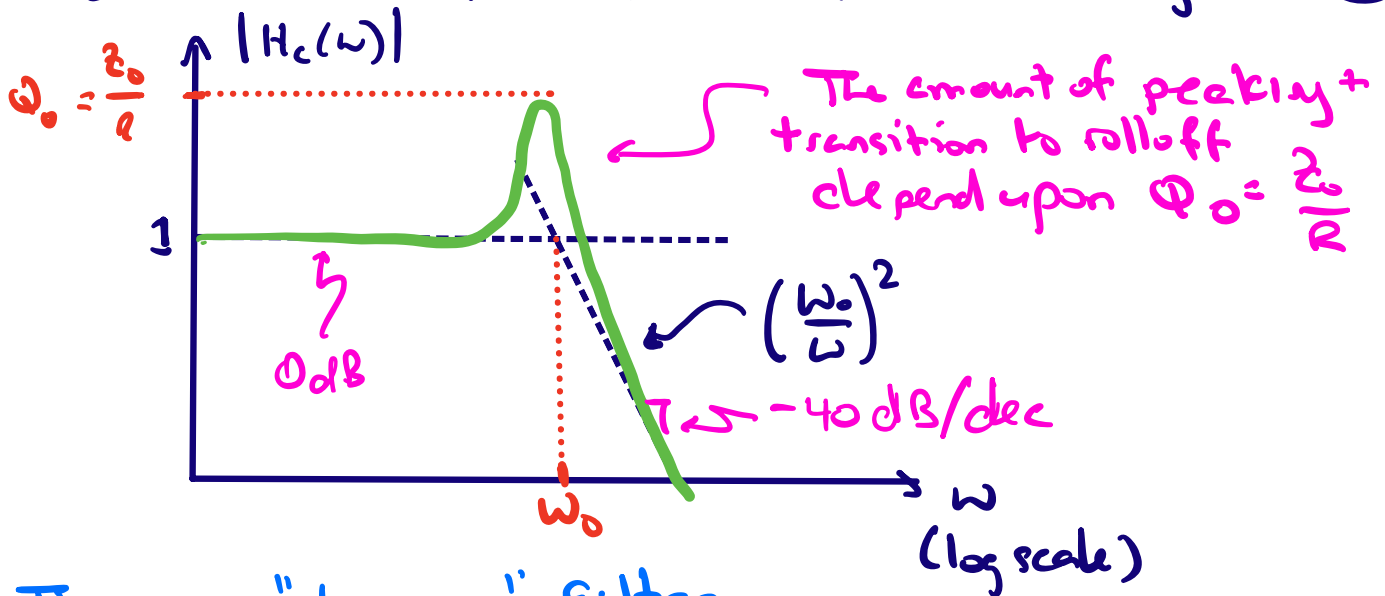

This is a "lowpass" filter

\*Having 2 energy storage elements gives us a fast rolloff (or  $1/\omega^2$  or  $-40 \text{ dB/decade}$ )

If we calculated  $H_c(\omega)$ , the transfer function from input to inductor voltage, we would get a high-pass filter with similar peaking + fast rolloff.