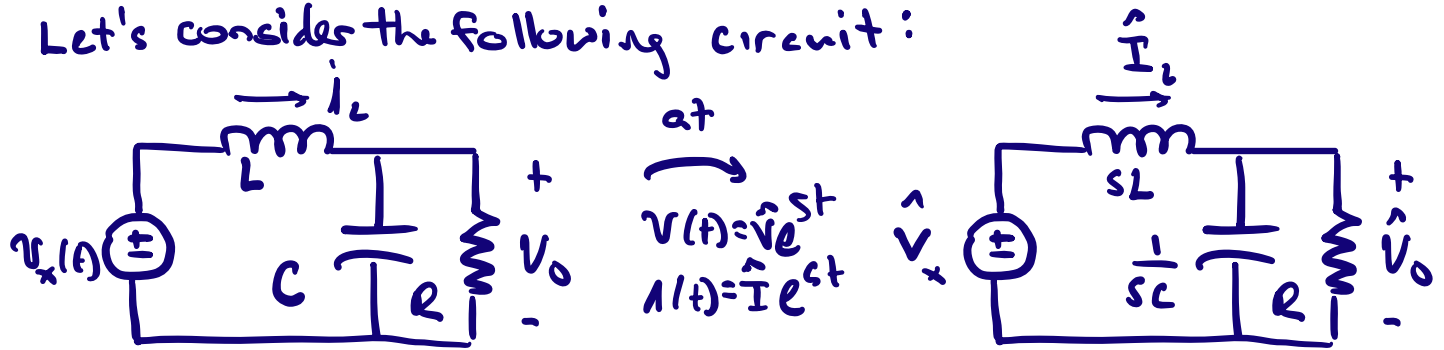


# Circuits

# Forced + Natural Responses

①

Let's consider the following circuit:



$$R \parallel \frac{1}{sC} = \frac{\frac{1}{sC} \cdot R}{\frac{1}{sC} + R} = \frac{R}{sCR + 1}$$

$$\therefore \frac{\hat{V}_o}{\hat{V}_x} = \frac{\frac{R}{sCR + 1}}{\frac{R}{sCR + 1} + sL} = \frac{R}{s^2LCR + sL + R} = \frac{1}{s^2LC + s\frac{L}{R} + 1}$$

$$\therefore H(s) = \frac{\hat{V}_o}{\hat{V}_x} = \frac{1}{s^2LC + s\frac{L}{R} + 1} = \frac{1}{LC} \cdot \frac{1}{s^2 + \frac{1}{RC}s + \frac{1}{LC}}$$

For sinusoids  $v_x(t) = V \cos(\omega t + \phi) = \text{Re} \left\{ \underbrace{V e^{j\phi}}_{\hat{V}_x} \underbrace{e^{j\omega t}}_{s=j\omega} \right\}$

$$s = j\omega \quad H(\omega) \triangleq H(s) \Big|_{s=j\omega} = \frac{1}{(1 - \omega^2 LC) + j\omega L/R}$$

where  $|H(\omega)| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\omega L/R)^2}}$

$$\angle H(\omega) = -\text{ATAN} \left\{ \frac{\omega L/R}{1 - \omega^2 LC} \right\}$$

and for sinusoidal steady state we get

$$v_o(t) = \text{Re} \left\{ H(\omega) \hat{V}_x e^{j\omega t} \right\} = |H(\omega)| V \cos(\omega t + \phi + \angle H(\omega))$$

# Circuits

# Forced + Natural Responses

(2)

Lets look at  $|H(\omega)|$  on a log-log plot

where we define:

$$|H(\omega)| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\frac{\omega L}{R})^2}}$$

$$\omega_0 \triangleq \frac{1}{\sqrt{LC}} \quad z_0 \triangleq \sqrt{\frac{L}{C}}$$

$$Q_0 = \frac{R}{\sqrt{L/C}} = \frac{R}{z_0}$$

Three frequency ranges / key values:

$$\left. \begin{array}{l} \omega \ll \frac{1}{\sqrt{LC}} (= \omega_0) \\ \text{and } \omega \ll \frac{R}{L} (= \frac{R\omega_0}{z_0}) \end{array} \right\}$$


$$|H(\omega)| \approx 1$$

$$\text{@ } \omega = \frac{1}{\sqrt{LC}} (= \omega_0)$$

$$|H(\omega)| = \frac{R}{\omega_0 L} = \frac{R}{z_0} = Q_0$$

$$\omega \gg \frac{1}{\sqrt{LC}} (= \omega_0)$$

$$|H(\omega)| \approx \frac{1}{\omega^2 LC} = \frac{\omega_0^2}{\omega^2}$$

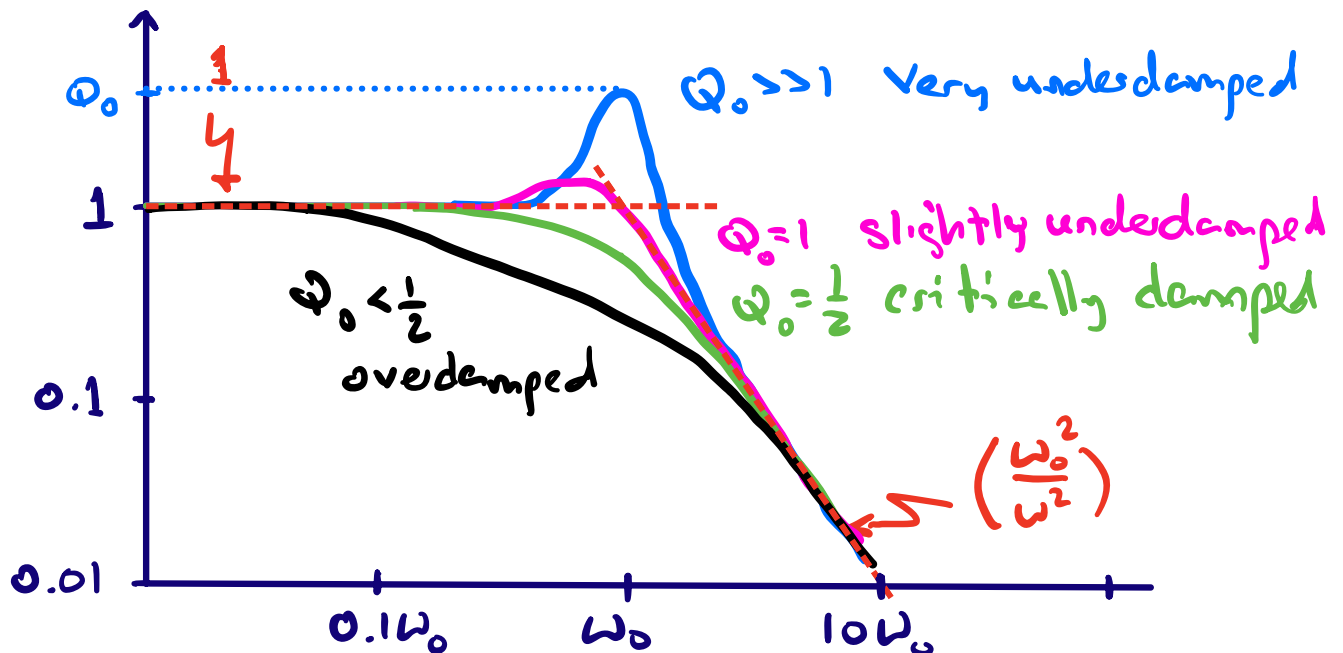

# Circuits

# Forced + Natural Responses

3

We have a low-pass filter:

passes voltages for frequencies  $\omega \ll \omega_0$

attenuates voltages for frequencies  $\omega \gg \omega_0$

peaking near  $\omega = \omega_0$  depends on  $Q_0 = R/Z_0$

Natural Response:  $\hat{V}_o e^{st} = H(s) \hat{V}_x e^{st}$


when can  $\hat{V}_o$  be nonzero for  $\hat{V}_x = 0$  (no drive)?

only if the denominator of  $H(s) \rightarrow 0$

$$s^2 + \frac{1}{RC} s + \frac{1}{LC} = 0$$

Natural response  $Ae^{st}$  for  $s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$


3 possible cases

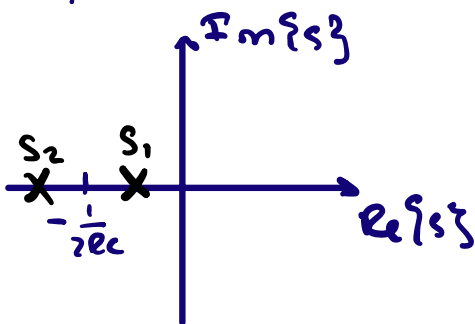

overdamped

$$\frac{1}{\sqrt{LC}} < \frac{1}{2RC}$$


or  $R < \frac{1}{2} Z_0$

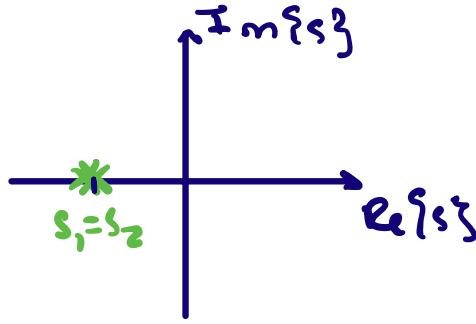

critically damped

$$\frac{1}{\sqrt{LC}} = \frac{1}{2RC}$$

$$R = \frac{1}{2} Z_0$$

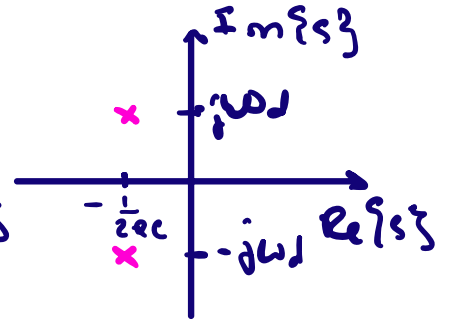

underdamped

$$\frac{1}{\sqrt{LC}} > \frac{1}{2RC}$$

$$R > \frac{1}{2} Z_0$$

$s_{1,2}$  real

$$v_{o,h} = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$s_{1,2}$  real, equal

$$v_{o,h} = (A_1 + t A_2) e^{s t}$$

$s_1, s_2$  complex

$$v_{o,h} = A_1 e^{\sigma t} \cos(\omega_d t + A_2)$$

where  $\sigma = -\frac{1}{2RC}$


$$\omega_d = \sqrt{\frac{1}{LC} - \left(\frac{1}{2RC}\right)^2}$$

# Circuits


# Forced + Natural Responses

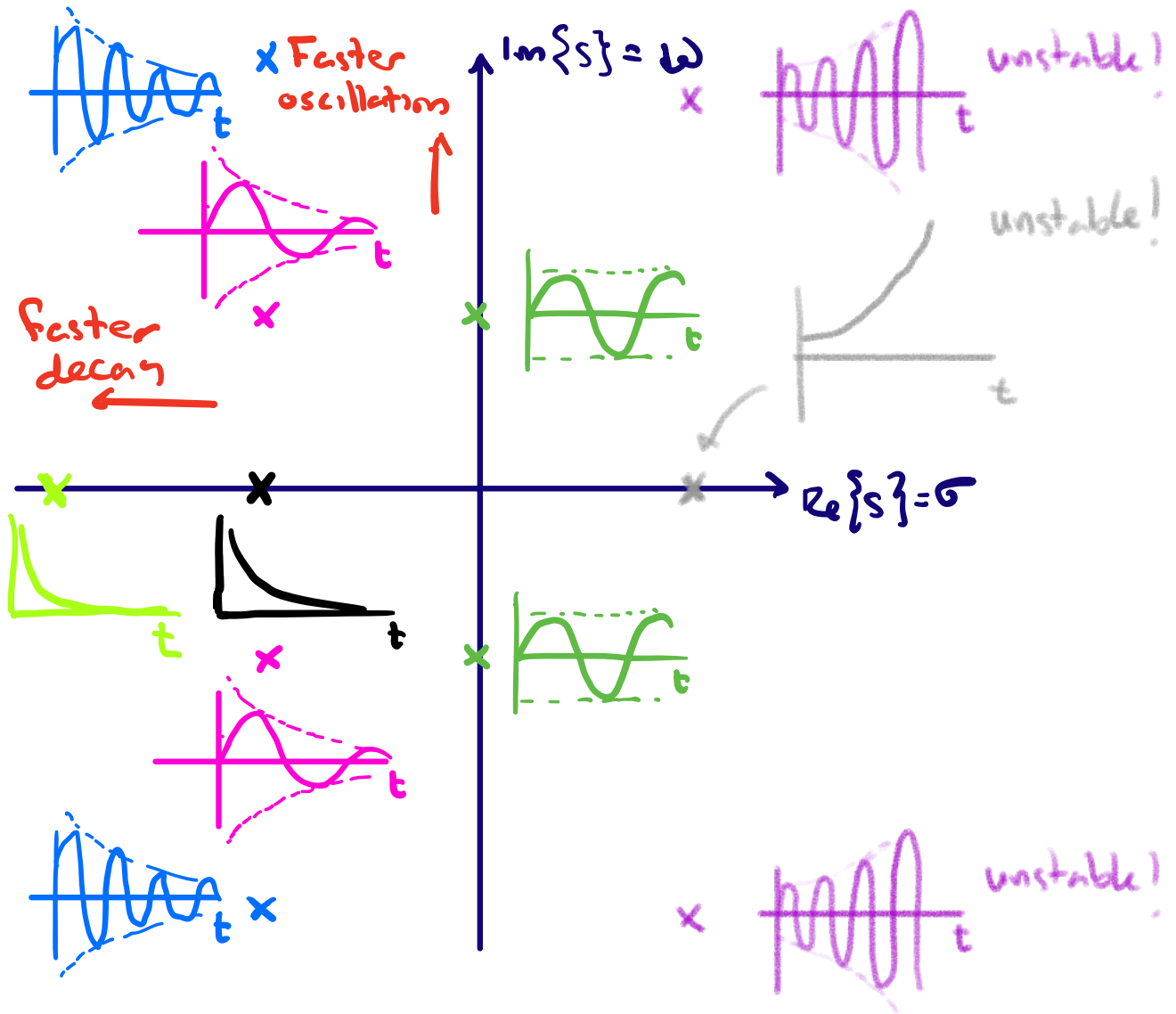(4)

Note how the natural frequency locations:  $s = \sigma + j\omega$  affect the natural response time wave form:



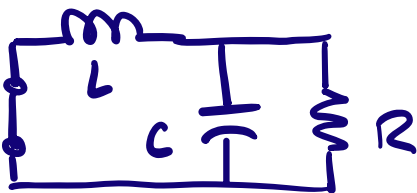Note that this is a "parallel resonant" circuit: when there is no drive, ( $V_x = 0$ ),  $L, R, C$  are in parallel!



$$Q_0 = \frac{R}{\sqrt{L/C}}$$


more oscillatory ↑

So becomes less damped as  $R \uparrow$  as less energy removed by  $R$  each cycle

\*The natural response relates directly to the peaking in the driven (forced) response.

How might this kind of circuit be used?

Consider a "buck" power converter

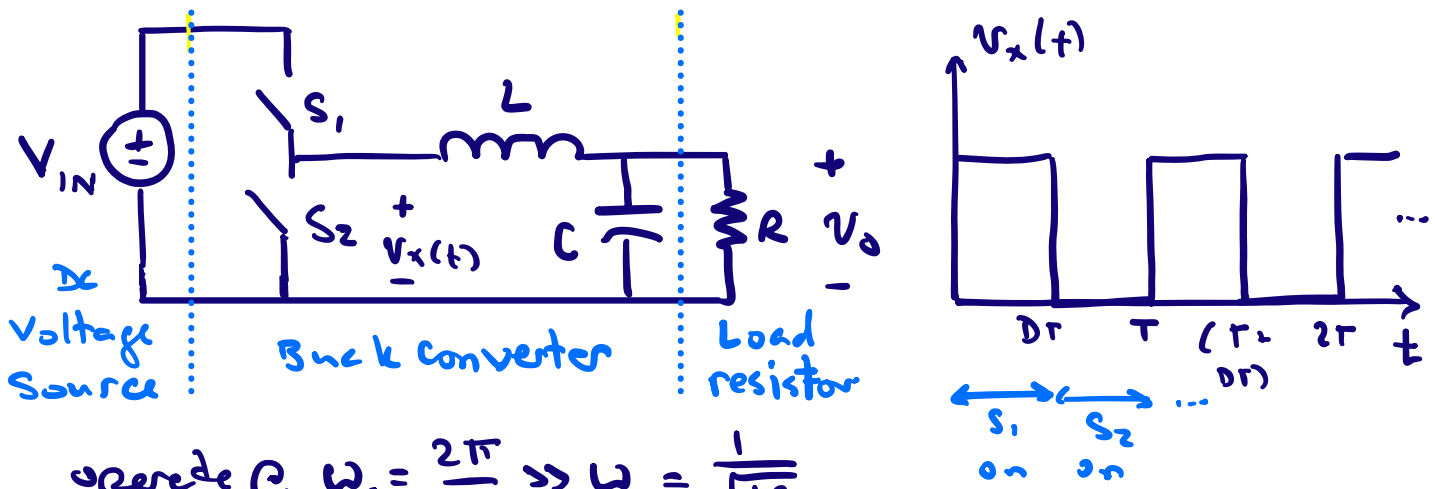


operates @  $\omega_s = \frac{2\pi}{T} \Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$

Switches  $S_1$  and  $S_2$  are alternately turned on and off with period  $T = 2\pi/\omega_s$ , creating a "square wave" voltage  $V_x$ . This is filtered by the LC network such that the load resistor receives a low-pass filtered (approximately dc) voltage equal to the average of  $V_x(t)$ ,  $\langle V_O \rangle = \langle V_x \rangle = DV_{IN}$ . This converts a high supply voltage  $V_{IN}$  to a low output voltage  $V_O$ .

⇒ This general type of converter appears in most computer power supplies!

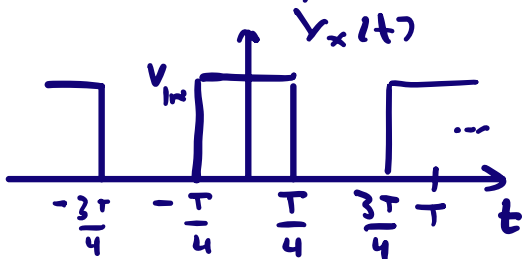How can we understand the details of the filtering action? Consider  $D = 0.5$ : As you will see in 6.300, a square wave can be represented as a sum of a constant plus harmonically-related sinusoids:



$$V_x(t) = \frac{V_{IN}}{2} + \frac{2V_{IN}}{\pi} \cos(\omega_s t) + \frac{2V_{IN}}{3\pi} \cos(3\omega_s t + \pi) + \dots$$

$$V_x = \frac{V_{IN}}{2} + \sum_{k=0}^{\infty} \frac{2V_{IN}}{(2k+1)\pi} \cos((2k+1)\omega_s t + \pi^k)$$

# Circuits

# Forced + Natural Responses

(6)

After natural response dies away we get the Steady-State (forced) response (by superposition)

$$V_o(t) = \left\{ \frac{V_{in}}{2} \cdot |H(\omega)| \right\} + \left\{ \sum_{k=0}^{\infty} |H((2k+1)\omega_s)| \cdot \frac{2V_{in}}{(2k+1)\pi} \cos((2k+1)\omega_s t + \pi^k + \angle H((2k+1)\omega_s)) \right\}$$


dc component of output voltage  
 ↓  
 Small ripple component

$$\approx \frac{V_{in}}{2} \quad \text{if } \omega_s \gg \omega_0$$

See demo for validation!

What will our (periodic steady state) waveforms look like?

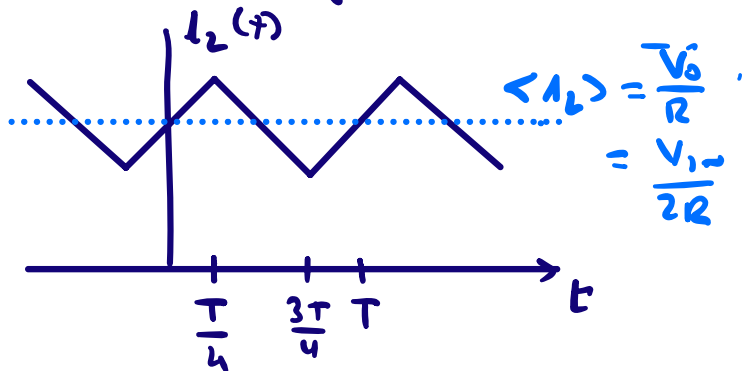If  $V_o(t)$  is almost constant (due to filtering)  $i_L(t)$  is a triangular wave



- \* The dc component of  $i_L$  goes through  $R$  only (capacitor is a dc open)
- \* most of the triangular ripple current goes through  $C$  as  $\frac{1}{\omega_s C} \ll R$

\* We could've also calculated  $i_L(t)$  from  $H_z(s) = \frac{\hat{I}_L}{\hat{V}_x}$  using superposition.

\* since the capacitor takes most of the ripple current, we could also approximately calculate the ripple voltage as  $V_{o,ac} = \frac{1}{C} \int i_{L,ac} dt$

# Circuits


## Forced + Natural Responses

⑦

When would we see the natural response in our buck converter system?

- ① At startup of the circuit
- ② after a change (e.g. step) in the input voltage
- ③ after a change in the load resistance

e.g. -

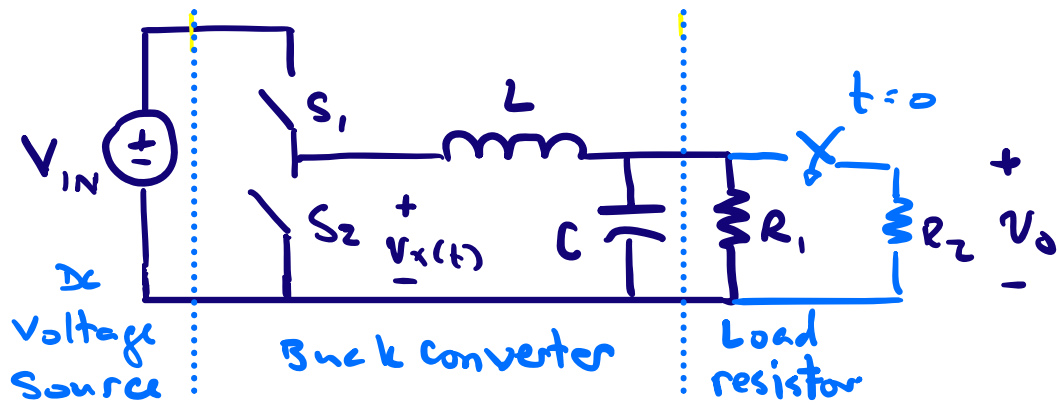

$R$  changes from  $R_1$  to  $R_1 \parallel R_2$  at  $t = 0$ .

See demo