

6.200 Circuits and Electronics

Week 5 Recitation: Dependent Sources


No new hardware kit this week. No pre-lab either (but yes lab on Friday).

PCB people: boards are in! Take them today if you want, or we'll have them in lab.


Student in class needs copies of notes from a paid note-taker. das-student@mit.edu

Dependent Sources

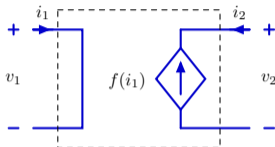
A *dependent* source produces a voltage or current whose value depends on another voltage or current elsewhere in a circuit.




CCCS
 $v_1 = 0$
 $i_2 = -f(i_1)$

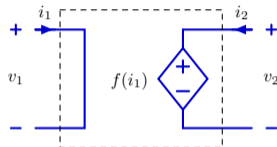

CCVS
 $v_1 = 0$
 $v_2 = f(i_1)$

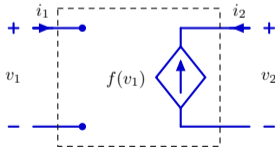

VCCS
 $i_1 = 0$
 $i_2 = -f(v_1)$

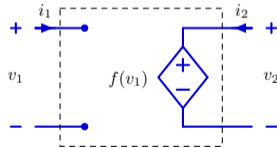

VCVS
 $i_1 = 0$
 $v_2 = f(v_1)$

Why Do We Care?

Everything we've talked about here so far is a way of *modeling* physical systems. Some kinds of devices can sometimes be modeled as dependent sources:


- A Bipolar Junction Transistor (BJT) can* be modeled as a CCCS.
- A MOSFET can* be modeled as a VCCS.
- An operational amplifier (op-amp) can* be modeled as a VCVS.

*under certain circumstances

We'll see some of these devices in the upcoming labs!

Solving With Dependent Sources

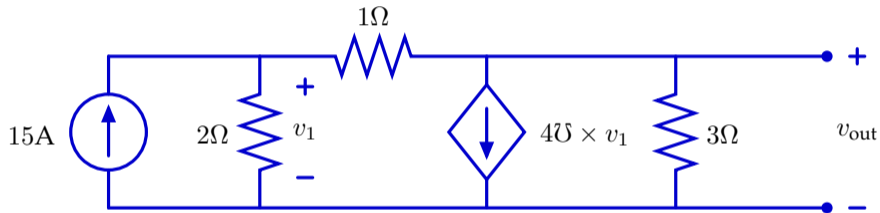We need to be careful with superposition and Thévenin/Norton, but other solution/simplification methods still work fine. Let's solve this one with the node method:



Superposition

In a network consisting of only* constant resistors, ideal independent voltage and current sources, **and linear dependent sources**, the solution for *any* branch current or branch voltage will be a linear combination of the strengths of the independent sources.

A dependent source is **linear** if $f(x) = kx$ for some constant k .

Approach: solve for each *independent* source's contribution to the solution separately by zeroing out the other *independent* source values and solving.

DON'T ZERO OUT THE DEPENDENT SOURCES!!!!!!!!!!
DON'T ZERO OUT THE DEPENDENT SOURCES!!!!!!!!!!
DON'T ZERO OUT THE DEPENDENT SOURCES!!!!!!!!!!

* we'll add more to this list later

Superposition

DON'T ZERO OUT THE DEPENDENT SOURCES!!!!!!!!!!

Superposition

DON'T ZERO OUT THE DEPENDENT SOURCES!!!!!!!!!!

Superposition

DON'T ZERO OUT THE DEPENDENT SOURCES!!!!!!!!!!


Superposition

**DON'T ZERO OUT THE DEPENDENT
SOURCES!!!!!!!!!!**




Superposition

**DON'T ZERO OUT THE
DEPENDENT SOURCES!!!!!!!!!!**

Superposition: Example

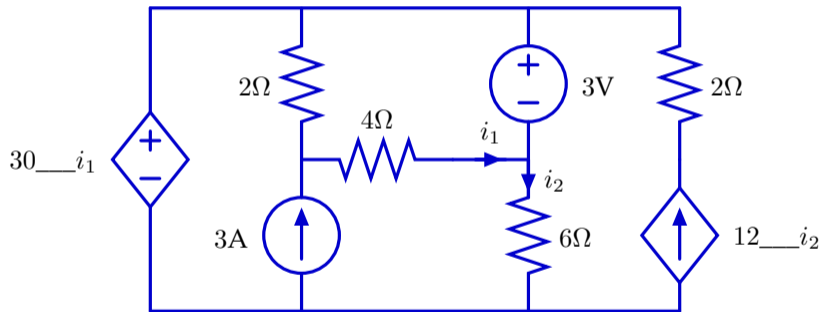

Thévenin/Norton

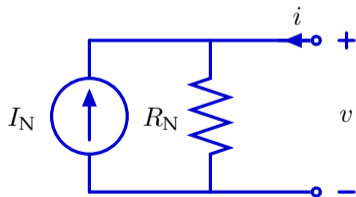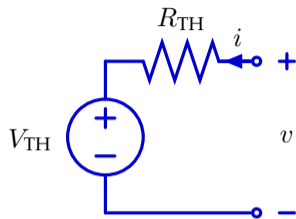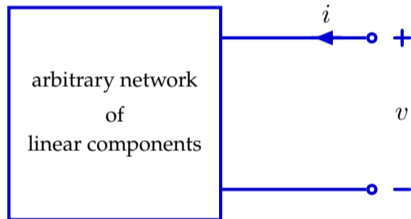

Equivalents: Example

