

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.200 – Circuits & Electronics
Spring 2024

Quiz #1

13 March 2024

Name: _____

MIT Kerberos Username: _____


Recitation Time: 11 12 1

- There are 15 pages in this quiz, including this cover page.
- Please put your name and Kerberos ID in the spaces provided above, and circle the time of your recitation.
- Please do not remove any pages from this quiz.
- Do your work for each question within the boundaries of that question, or on the back of the preceding page. *When finished with each part, clearly write your answer for that part into the corresponding answer box or graph.*
- Make sure all work is on pages with QR codes, and **do not write on the QR codes.**
- *All numerical answers require proper units.*
- *In order to guarantee receipt of full credit, all answers should be justified by supporting math and/or explanations.*
- This is a closed-book quiz, but calculators and a single two-sided page of notes are allowed.
- Good luck!

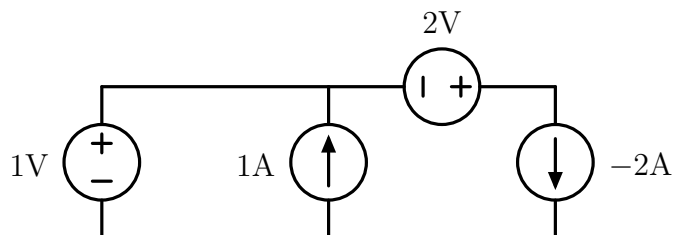Problem 1: Miscellany – 35%


All parts of this problem are independent of the other parts.

- (1A) Determine the power sourced (provided) by each of the four sources in the circuit shown below. If a source sinks (receives) power, then consider its sourced power to be negative. *Proper units are required.*




1 V Source:	1 A Source:
2 V Source:	-2 A Source:

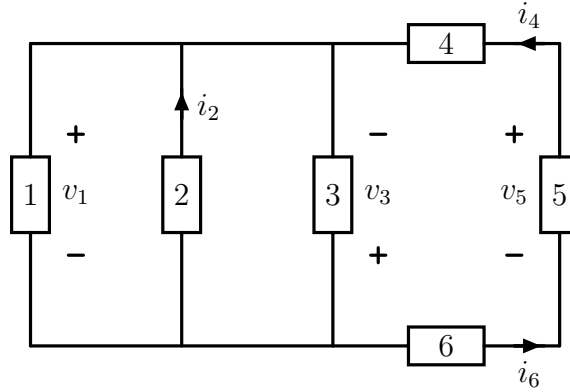- (1B) The circuit shown below comprises six branches with partially labeled branch voltages and currents. Add the missing labels to the circuit diagram according to the passive sign convention. A brute-force analysis of the circuit would require the use of six equations obtained from KCL and KVL. Provide six such equations that are necessary and sufficient to carry out a brute-force analysis.




Eqn #1:	Eqn #2:
Eqn #3:	Eqn #4:
Eqn #5:	Eqn #6:

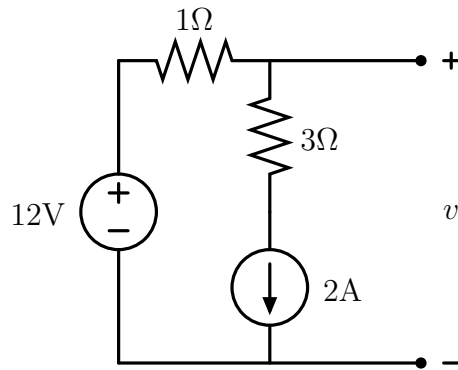(1C) Determine the voltage v in the circuit shown below. *Proper units are required.* If the voltage cannot be determined, enter “N/A” in the answer box.




$v =$

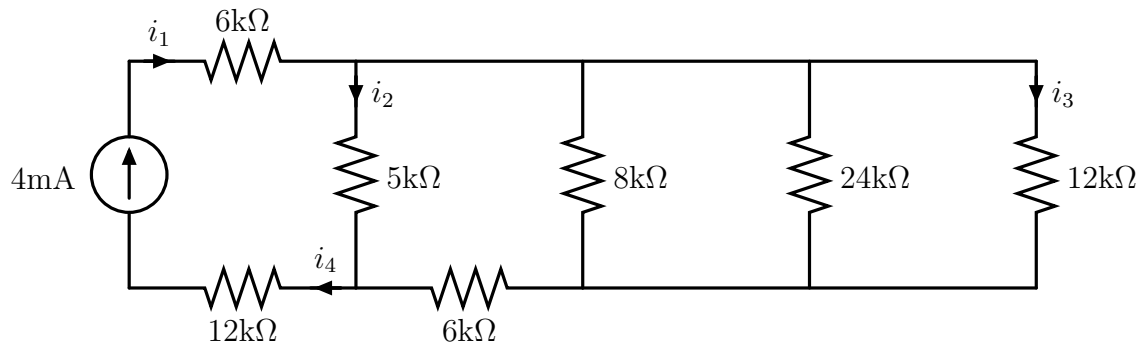- (1D) The circuit shown below has four labeled currents. Determine numerical values for all four currents. *Proper units are required.*



$i_1 =$	$i_2 =$
$i_3 =$	$i_4 =$


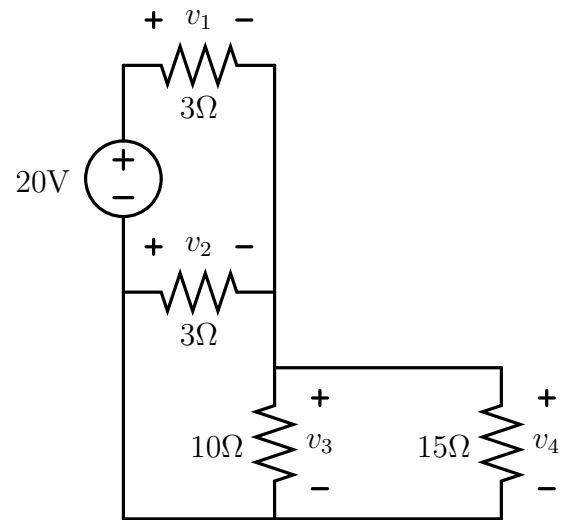
- (1E) The circuit shown below has four labeled voltages. Determine numerical values for all four voltages. *Proper units are required.*



$v_1 =$	$v_2 =$
$v_3 =$	$v_4 =$

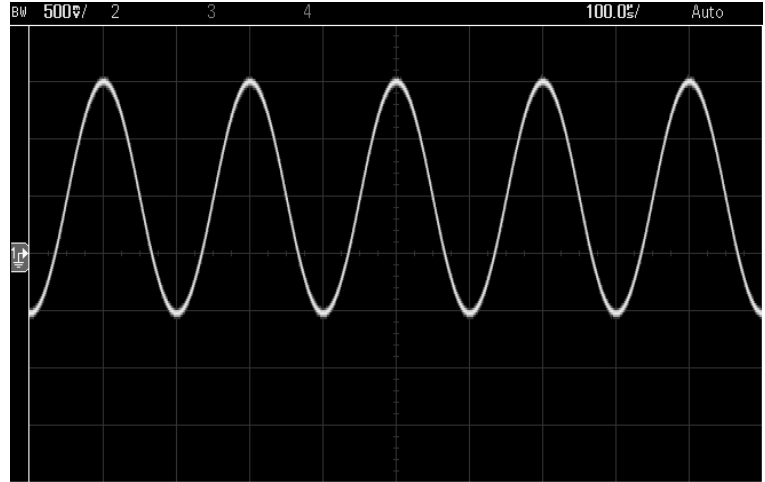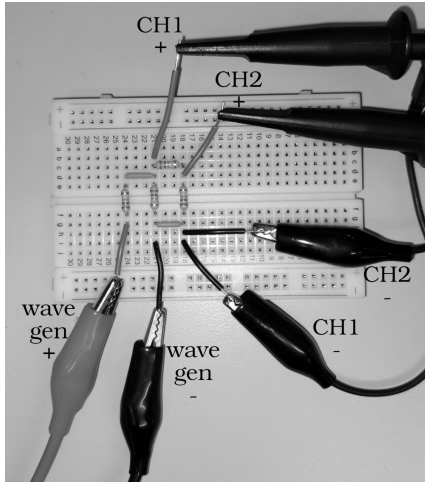Problem 2: Measurements – 15%


The top figure below shows a photograph of a circuit built on a protoboard. The resistance of each of the four resistors in the circuit is $22\text{ k}\Omega$. The oscilloscope image shows the voltage measured on Channel 1.



Given this measurement, determine the amplitude and frequency of the sine wave produced by the signal generator. *Proper units are required.*


Amplitude:	Frequency:
------------	------------

In addition, on the axes given below, sketch the waveform measured by Channel 2. The voltage from Channel 1 has been reproduced in light grey for reference.

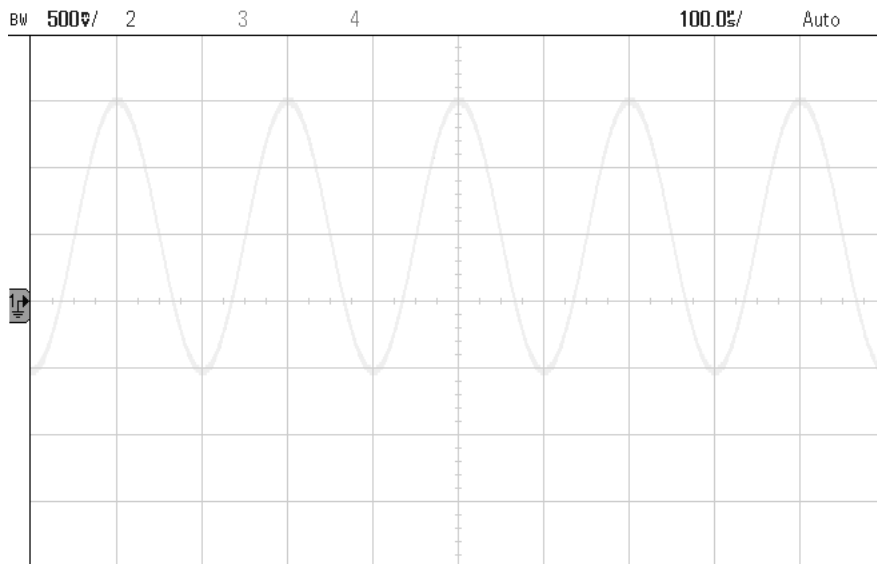

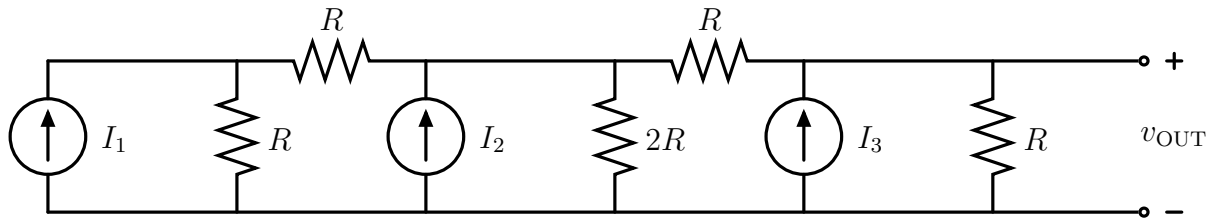Problem 3: Multiple Sources – 14%

This problem concerns the circuit shown below, comprising three current sources and five resistors. The circuit has one port labeled with the voltage v_{OUT} .



(3A) Determine v_{OUT} in terms of I_1 , I_2 , I_3 and R .


$v_{\text{OUT}} =$

(3B) Draw and clearly label the Thévenin and Norton equivalents for the original circuit when viewed from the port labeled v_{OUT} .

Thévenin:
Norton:

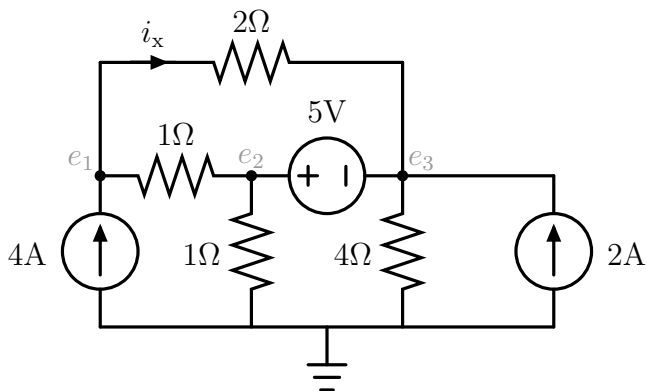Problem 4: Node Analysis – 20%

Consider the network shown below. The objective of this problem is to use nodal analysis to determine the current i_x flowing through the 2Ω resistor. To do so, follow the steps outlined below. *To receive partial credit, please clearly explain your approach including the equations you are using for part (4A).*



- (4A) Write two node equations that can be solved for the unknown node voltages e_1 and e_2 . *Proper units are required.*

Equation 1:

Equation 2:

(4B) Determine the values of e_1 , e_2 and e_3 . *Proper units are required.*

e_1 :
e_2 :
e_3 :

(4C) Determine the current i_x flowing through the 2Ω resistor. *Proper units are required.*

If you were unable to determine numerical values for e_1 , e_2 and e_3 , then provide symbolic expressions for partial credit.

$i_x:$

(4D) Determine the power dissipated in the 2Ω resistor. *Proper units are required.*


If you were unable to determine numerical values for e_1 , e_2 and e_3 , then provide symbolic expressions for partial credit.

Power:

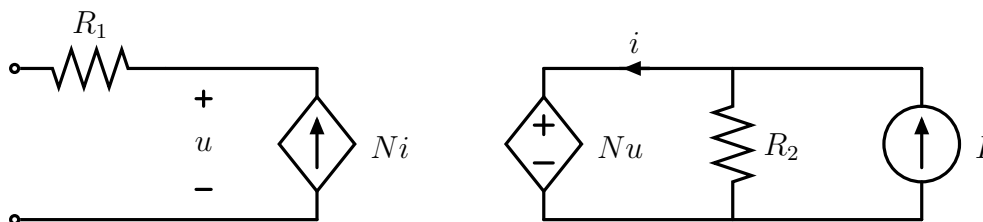Problem 5: Dependent Sources – 16%


With one exception, all parts of this problem are independent of the other parts. The one exception is that Parts (C) and (D) consider the same circuit.

- (5A) Determine the Thévenin equivalent, as viewed from the open port, of the circuit shown below. Make sure to clearly label the open port in the Thévenin equivalent.



Thévenin:

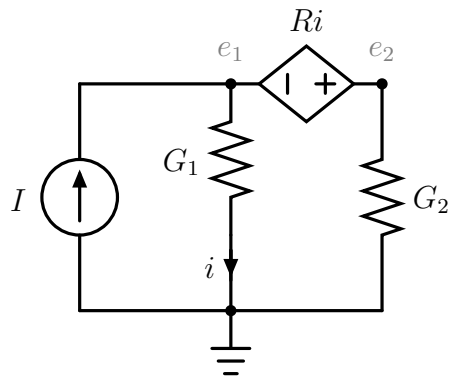- (5B) Determine the two unknown node voltages e_1 and e_2 in the circuit shown below. Note that the two resistors in the circuit are labeled with their *conductances* as opposed to their resistances.



$$e_1 =$$

$$e_2 =$$