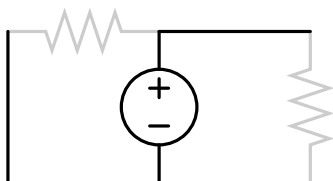



Name: answers

Kerberos Username: _____


are the grey components
connected in series, in parallel,
or neither?




parallel

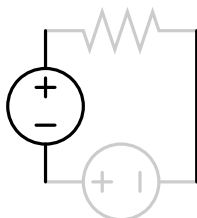


series

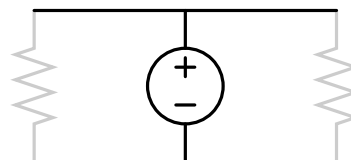


parallel

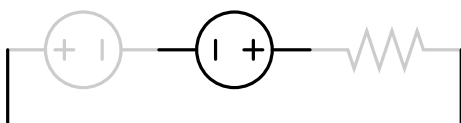


series

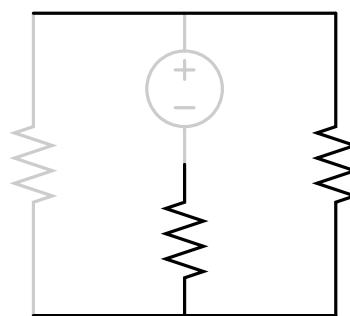


neither

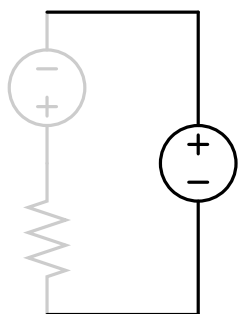


series

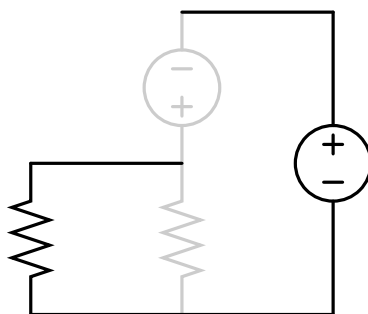

neither

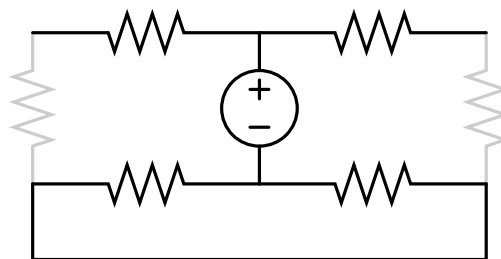

neither

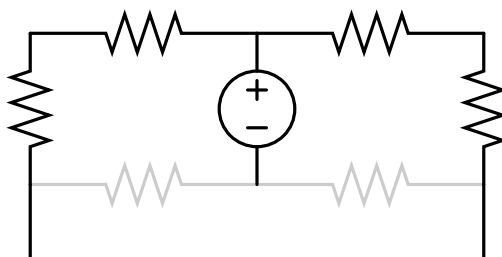

parallel