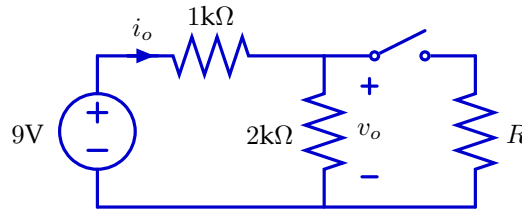


Name: _____


Kerberos Username: _____

when the switch is closed,
does v_o increase, decrease,
or stay the same?
does i_o increase, decrease,
or stay the same?
does the result depend
on R ?




v_o decreases.

switch open:

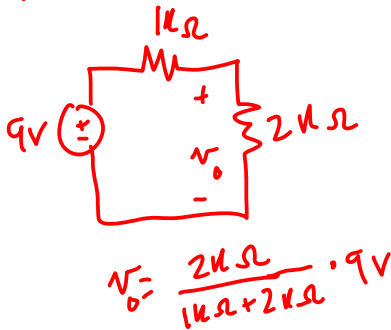


switch closed:

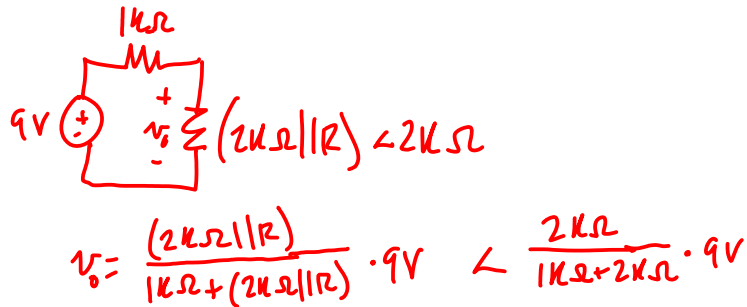

i_o increases.

switch open:

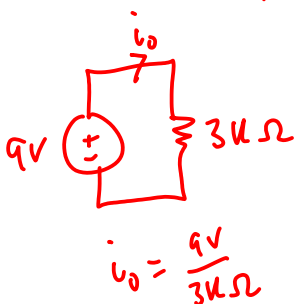

switch closed

