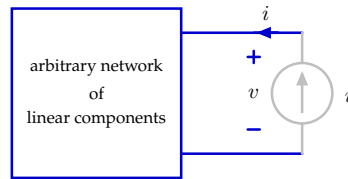


For any linear network containing only voltage sources, current sources, and resistors, the relationship between i and v at any pair of terminals will be a straight line in the v - i plane. To see this, consider connecting an independent current source to the circuit and analyzing with superposition to find the relationship between i and v :



The solution for v will always have the following form:

$$v = \underbrace{\sum_m \alpha_m V_m}_{\text{one term for each internal independent VSrc}} + \underbrace{\sum_k \beta_k I_k}_{\text{one term for each internal independent ISrc}} + \underbrace{R_{\text{eq}}}_{\text{equivalent resistance with all internal sources zeroed out}} \times i$$

This relationship holds *regardless of what is connected to those terminals*.

We can replicate this relationship with either of two relatively-simple networks:

