

A *dependent source* produces a voltage or current whose value depends on another voltage or current elsewhere in a circuit.







