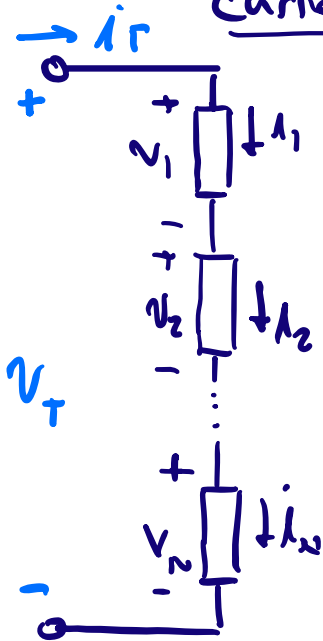


Circuits

Series, parallel, v & i dividers, examples ①

Series: Elements are in series iff they share the same current



$$i_T = i_1 = i_2 = \dots = i_N$$


$$v_T = v_1 + v_2 + \dots + v_N$$

For resistors in series, we get a resistance for the whole "chain" of:

$$\frac{v_T}{i_T} = R_T = \sum_{i=1}^N R_i$$

e.g. 2 resistors R_1, R_2 in series form a net resistance $R_T = R_1 + R_2$

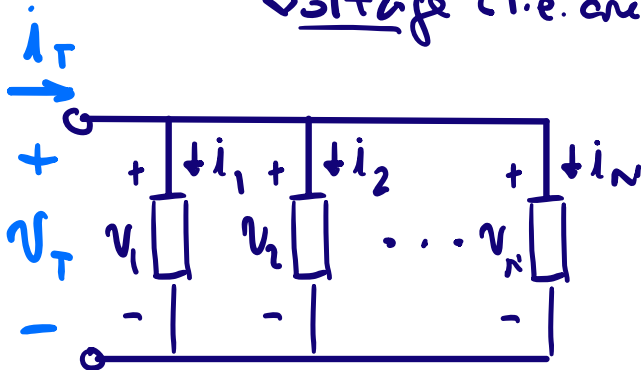Parallel: Elements are in parallel if they share the same voltage (i.e. are connected between the same nodes)



$$v_T = v_1 = v_2 = \dots = v_N$$

$$i_T = i_1 + i_2 + \dots + i_N$$

For resistors in parallel we get a net resistance for the whole parallel group of:

$$\frac{v_T}{i_T} = R_T = \frac{1}{G_1 + G_2 + \dots + G_N} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}}$$

e.g. 2 resistors R_1, R_2 in parallel gives a net resistance:

$$R_T = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} \triangleq R_1 || R_2$$

Circuits


Series, parallel, v & i dividers, examples (2)

- we often combine series resistors into a single resistor to reduce # of nodes and simplify analysis of a network. Once we've done this and found the voltage V_T across the whole resistor "chain", how can we find the voltages across individual resistors?

Voltage dividers:

Suppose we have a set of resistors in series with a total voltage V_T across the series "chain". How can we find the voltages across the individual resistors in terms of the total voltage?

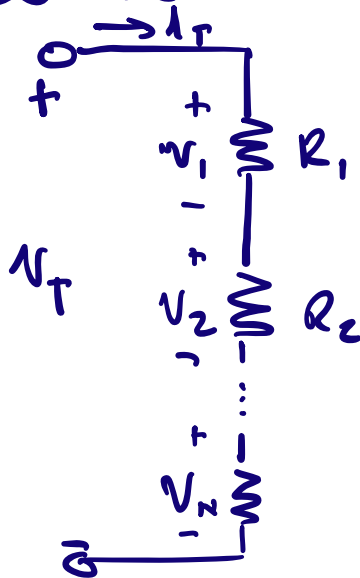Consider N resistors $R_1, R_2, \dots, R_N$ in series:



$$V_j = I_T \cdot R_j$$


$$V_T = V_1 + \dots + V_N$$

$$= I_T \cdot (R_1 + \dots + R_N)$$

$$\therefore \frac{V_j}{V_T} = \frac{R_j}{R_1 + \dots + R_N}$$

So resistors in series share the total voltage according to their fraction of the total resistance. Voltage "divides" proportional to the fractional resistance

e.g. for 2 resistors:

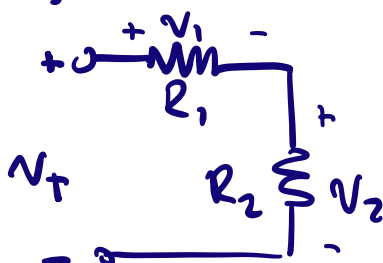


$$V_2 = \frac{R_2}{R_1 + R_2} V_T \quad V_1 = \frac{R_1}{R_1 + R_2} \cdot V_T$$

Circuits

Series, parallel, v & i dividers, examples (3)

A Series resistor chain is often used as a "voltage divider" to provide a scaled-down version of a large voltage.

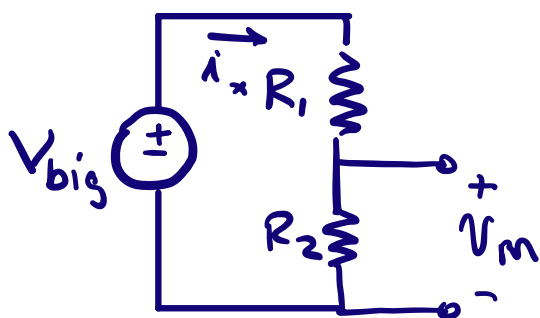Suppose we had a large power supply voltage V_{big} that could be as large as 10,000 V. We might want to monitor that voltage, but we might have monitoring circuitry that can only take a voltage input V_m that is less than 10 V. We could use a voltage divider to make V_m a scaled-down replica of V_{big} :



$$V_m = \frac{R_2}{R_1 + R_2} \cdot V_{big}$$

To make $V_m = 10 \text{ V}$ @ $V_{big} = 10,000 \text{ V}$

$$\frac{R_2}{R_1 + R_2} = \frac{10}{10,000} = 1 \times 10^{-3} = 0.001$$

If $R_1 + R_2 = 10 \text{ M}\Omega$, $R_2 = 10 \text{ k}\Omega$

$$\therefore R_1 = 10 \text{ M}\Omega - 10 \text{ k}\Omega = 9.99 \text{ M}\Omega$$

How much power do we dissipate?

power dissipated in a component x : $P_x = V_x \cdot i_x$



For a resistor $i_x = V_x / R_x \therefore P_x = V_x^2 / R_x$

$\therefore$ Total power in R_1, R_2 is $P_{TOT} = V_{big}^2 / (R_1 + R_2)$

$$= (10,000^2) / 10^7 = 10 \text{ W!}$$

The power in R_2 is $P_2 = \frac{V_m^2}{R_2} = \frac{(10)^2}{10^4} = 0.01 \text{ W}$

All the rest is dissipated in R_1

In practice we'd likely build R_1 from a series chain of resistors both to get the exact value and to handle the power.


Circuits

Series, parallel, v & i dividers, examples ④

Current Divider: Calculate how current splits among a set of paralleled resistors.

Suppose we have a set of paralleled resistors carrying a total current i_T . Let's find how this current distributes (divides) among the resistors

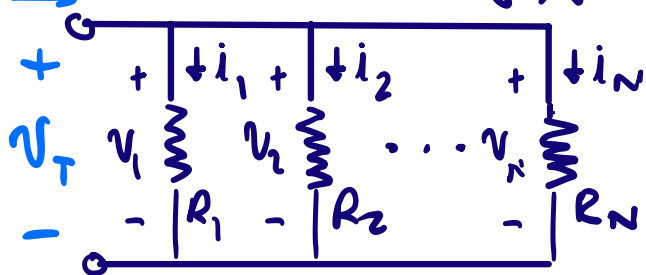Resistors $R_j, j=1..N$ where $G_j = \frac{1}{R_j}$



$$i_j = v_T \cdot G_j$$

$$i_T = i_1 + i_2 + \dots + i_N$$

$$= v_T \cdot (G_1 + G_2 + \dots + G_N)$$

The j^{th} branch current over the total current is thus:

$$\frac{i_j}{i_T} = \frac{G_j}{G_1 + \dots + G_N} \quad \text{or} \quad i_j = \frac{G_j}{G_1 + \dots + G_N} \cdot i_T$$

So resistors in parallel split current according to their fraction of the total conductance.
Current "divides" based on fractional conductance.

Expressed in terms of resistances, this gives us:


$$\frac{i_j}{i_T} = \frac{1/R_j}{1/R_1 + \dots + 1/R_N}$$

so the smaller an individual resistor is, the greater fraction of the current it draws.

Circuits

Series, parallel, v & i dividers, examples ⑤

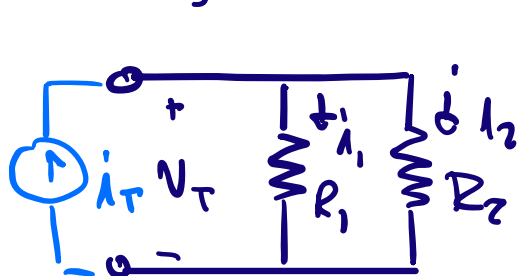Consider current division of a total current i_T among 2 resistors R_1, R_2 in parallel




$$i_1 = \frac{1/R_1}{1/R_1 + 1/R_2} i_T = \frac{R_2}{R_1 + R_2} i_T$$

$$i_2 = \frac{1/R_2}{1/R_1 + 1/R_2} i_T = \frac{R_1}{R_1 + R_2} i_T$$

So expressed in terms of resistances, the current divider relationship for parallel resistors is "opposite" to that of the voltage divider relationship for series resistors.


Series/Parallel resistor combinations and dividers appear so frequently, and are so useful that they are worth memorizing.

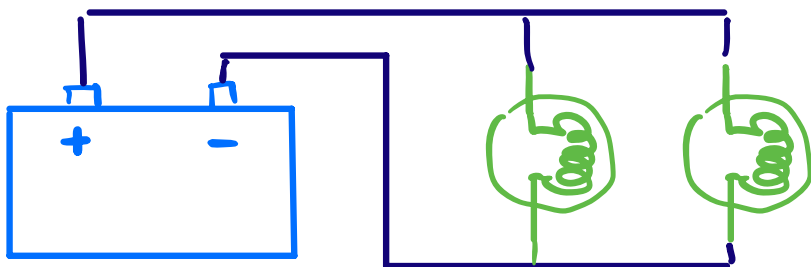Example: Consider a battery feeding two lights:



model the battery as having an "open circuit" voltage V_B in series with an "internal resistance" R_B : $V_B = 12V$, $R_B = 0.1\Omega$

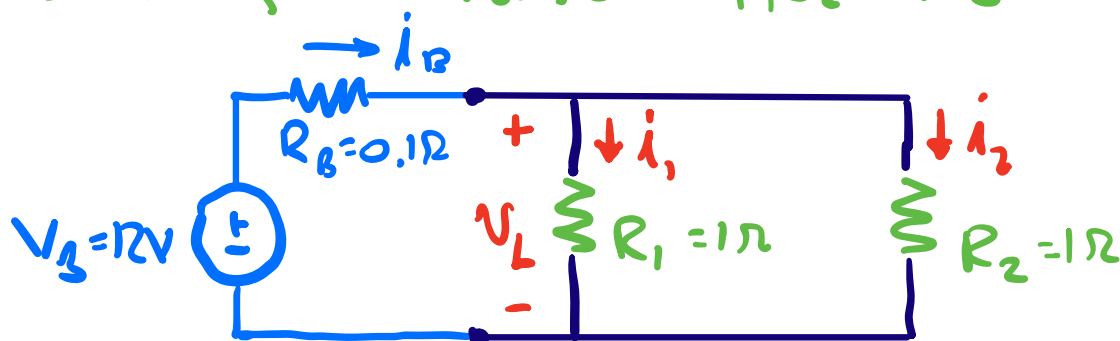model the lights as resistors $R_1, R_2 = 1\Omega$




Circuits

Series, parallel, v & i dividers, examples ⑥

- Suppose we want to know the voltage at the lights:

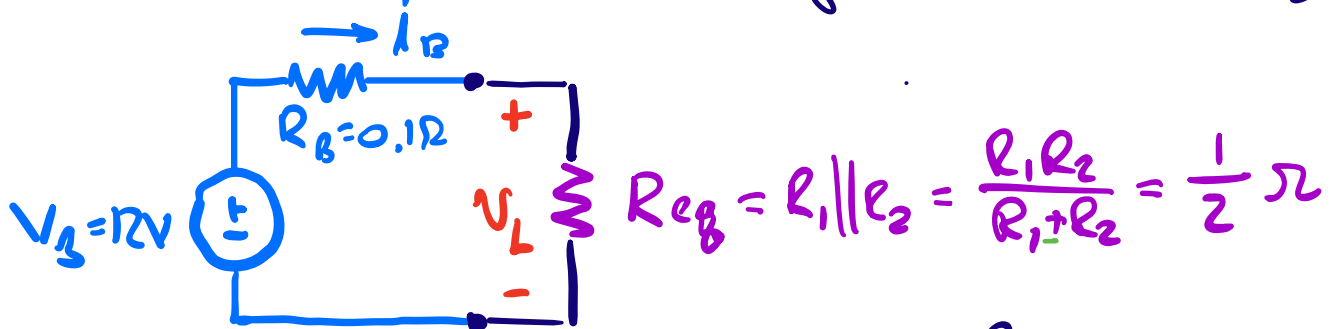We can quickly simplify the circuit (by parallel resistor combination) and then use voltage division to find V_L :



$$\text{By voltage division from } V_B: V_L = \frac{R_{eq}}{R_{eq} + R_B} \cdot V_B$$
$$= \frac{0.5}{0.6} \cdot 12 = 10V$$

- What is the battery current, i_B ?

The total series resistance is $R_T: R_B + R_{eq} = 0.6 \Omega$

$$\therefore i_B = \frac{V_B}{R_T} = \frac{12V}{0.6\Omega} = 20A$$

- How does i_B divide between the two lights?

Current division!

$$i_1 = \frac{R_2}{R_1 + R_2} \cdot i_B = \left(\frac{1}{2}\right)(20) = 10A$$

$$i_2 = \frac{R_1}{R_1 + R_2} \cdot i_B = 10A \quad (\text{current splits equally})$$

Note: This is expected by symmetry (equal resistances). If R_1 were smaller than R_2 , you'd expect R_1 to get a greater fraction of the total current.