
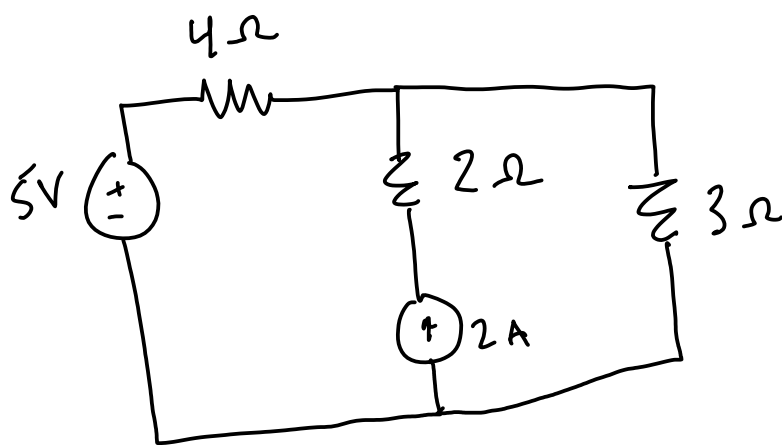


"Brute-force" method

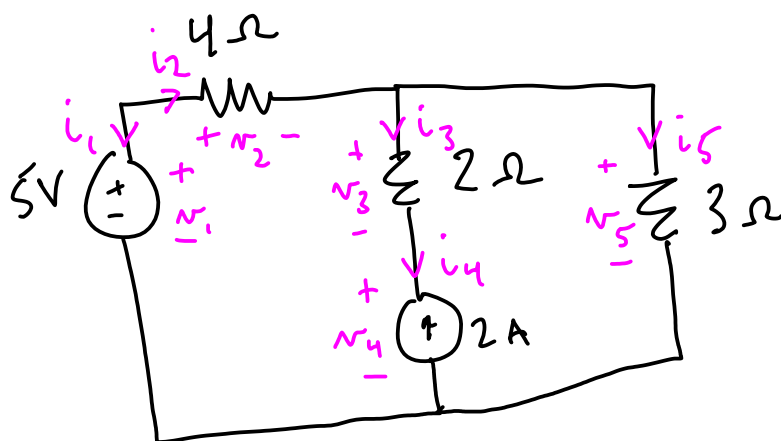goal: Solve for all branch voltages and currents




- 1) Label each branch variable with a name and direction (arbitrary but consistent with our convention that the current variable is defined to be flowing into the "+" side of the voltage variable)



in a circuit with B branches and N nodes, we'll have:

- B constitutive (component) equations
- $N-1$ linearly-independent KCL equations
- $B-N+1$ linearly-independent KVL equations

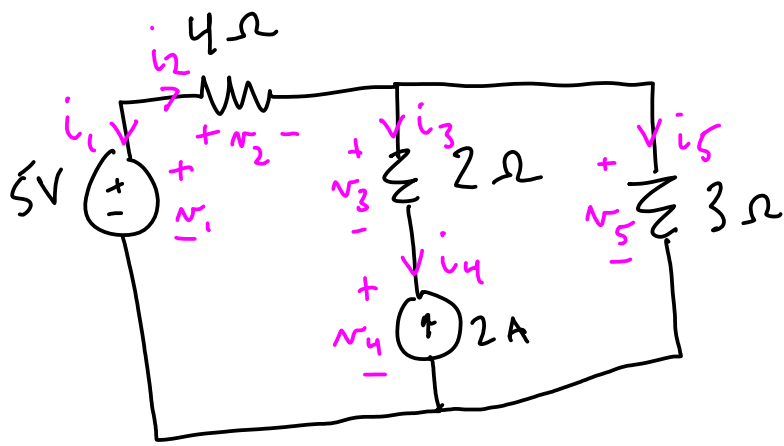$2B$ total equations for our $2B$ unknowns



Constitutive equations:

$$v_1 = 5V$$

$$v_2 = i_2 \cdot 4\Omega$$


$$v_3 = i_3 \cdot 2\Omega$$

$$i_4 = -2A$$

$$v_5 = i_5 \cdot 3\Omega$$



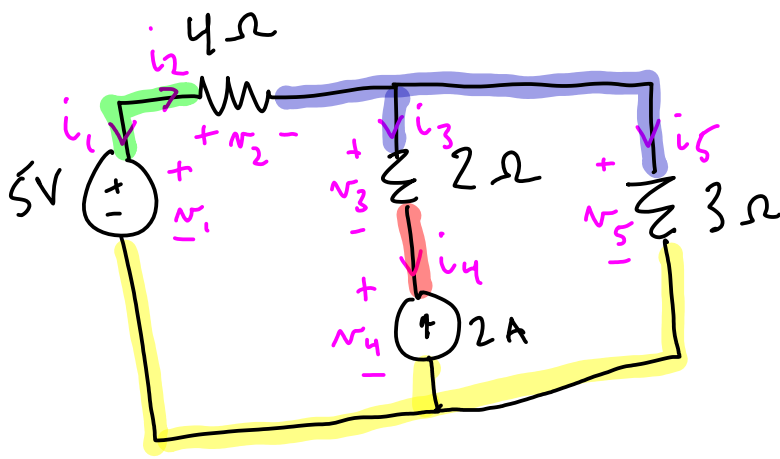it might be tempting to try to say something about v_4 here, but we can't (yet) because the current source doesn't constrain v_4 at all




we have 4 nodes, so we'll have 3 ^{$(N-1)$} linearly-independent KCL equations. pick any 3 nodes.

green node: $i_1 + i_2 = 0$
(top-left)

blue node: $i_2 = i_3 + i_5$
(top-right)

red node: $i_3 = i_4$
(middle)

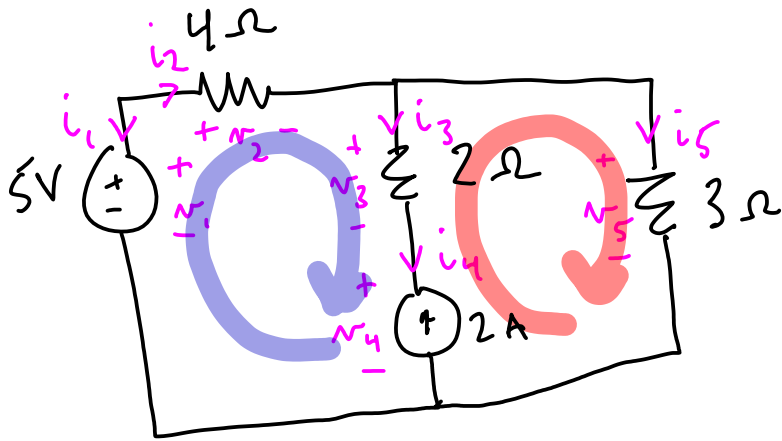

need 2 linearly-independent KVL equations.
 one general method: pick the smallest enclosed regions that span the whole circuit

blue loop: $v_1 = v_2 + v_3 + v_4$
 (left)

red loop: $v_4 + v_3 = v_5$
 (right)

↑ this works if the circuit is planar (2-D with no wires jumping over each other)

now we have 10 equations in 10 unknowns, so we can solve:

```
1 import sympy
2
3 syms = sympy.symbols('v1, v2, v3, v4, v5, i1, i2, i3, i4, i5')
4 v1, v2, v3, v4, v5, i1, i2, i3, i4, i5 = syms
5
6 constitutive = [
7     v1 - 5,
8     v2 - i2 * 4,
9     v3 - i3 * 2,
10    i4 + 2,
11    v5 - i5 * 3
12 ]
13
14 kcl = [
15     i1 + i2,
16     i2 - i3 - i5,
17     i3 - i4,
18 ]
19
20 kvl = [
21     v1 - v2 - v3 - v4,
22     v4 + v3 - v5
23 ]
24
25 result = sympy.solve([*constitutive, *kvl, *kcl], syms)
26
27 units = {'v': 'V', 'i': 'A'}
28
29 for var in syms:
30     print (f"{var} = {result[var]}{units[var.name[0]]}")
```

~
~
v1 = 5V
v2 = -4/7V
v3 = -4V
v4 = 67/7V
v5 = 39/7V
i1 = 1/7A
i2 = -1/7A
i3 = -2A
i4 = -2A
i5 = 13/7A

yay!



if this approach feels algebraically painful, fear not! we'll find simpler ways to solve circuits over the coming weeks!