

6.002 - Lecture 9B

Power Electronics

“Power electronics” does not necessarily mean “powerful electronics”. Rather it refers to electronics designed to process power/energy as opposed to electronics that process signals/information.

Boost Converter

- Power Electronics
- Energy Processing
- Boost Converter Example
- LC Network Review
- LC Network Application

Power electronics concerns include:


- efficiency and temperature rise;
- power density;
- regulation of output voltage or current; and
- response bandwidth in the presence of source and load variations.

As a consequence of the concern for efficiency, power electronics involve (to first order) only ideally lossless devices:


- capacitors and inductors acting as energy stores;
- transistors and diodes acting as switches to direct energy flow;
- transformers for isolation and voltage and current transformation.

To learn more, consider 6.131 and/or 6.334.

Boost Converter?

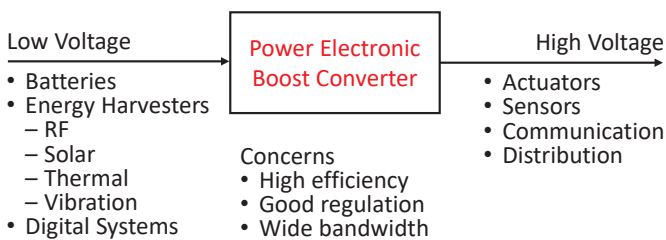




Single-Use Camera

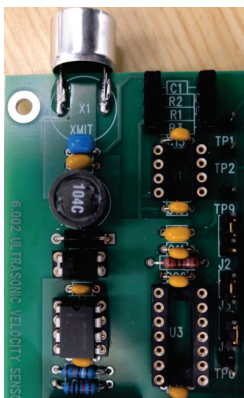

6.002 Ultrasound Boost Converter

Hansen, Martin and Perreault
DOI:10.1109/TPEL.2019.2900021


Ofori-Tenkorang,
PhD Thesis, MIT, 1997

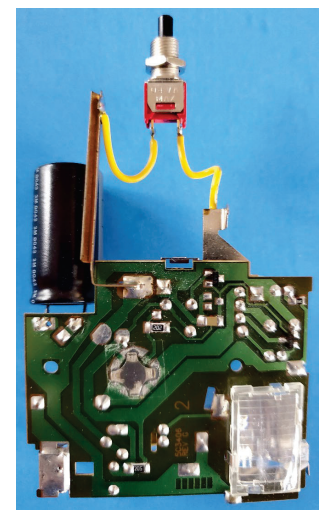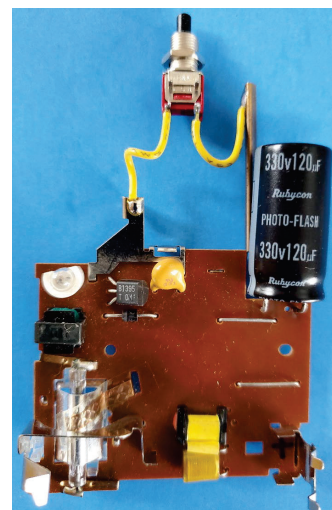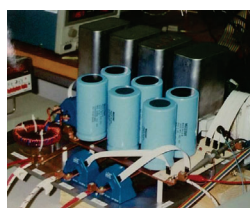



Kodak Camera

Simplified Camera Flash Circuit

Voltage Pump (Boost Converter)


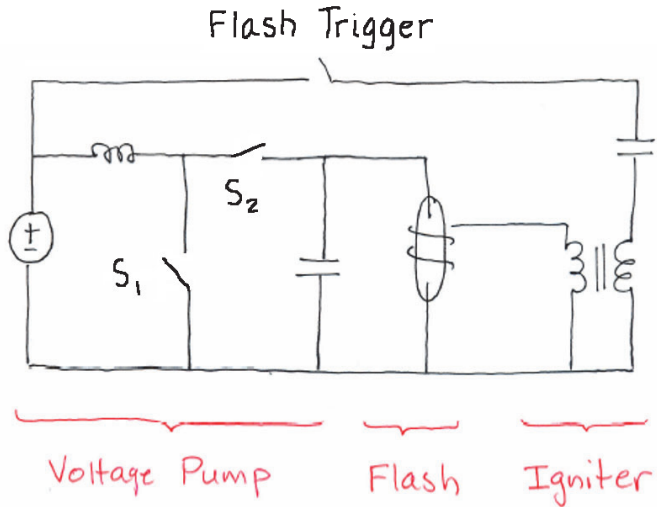


Typical Operation: 1.5 V @ Battery
 300 V @ Capacitor
 10 kV @ Igniter

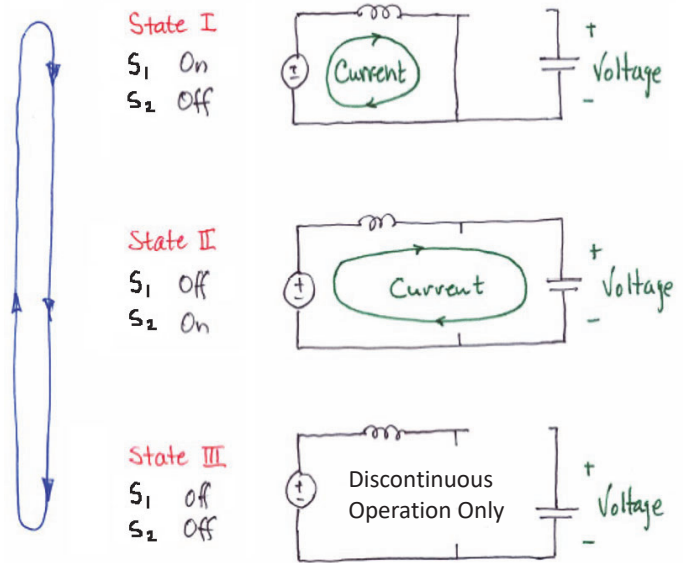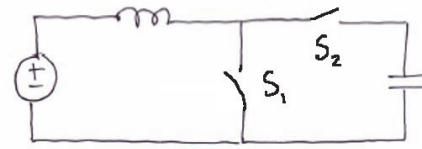


State I

State II

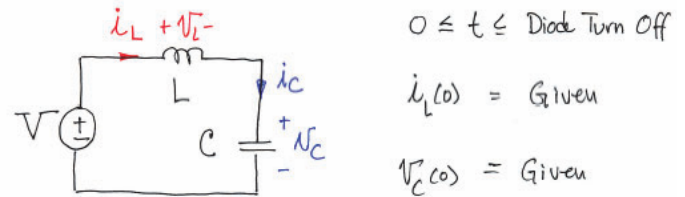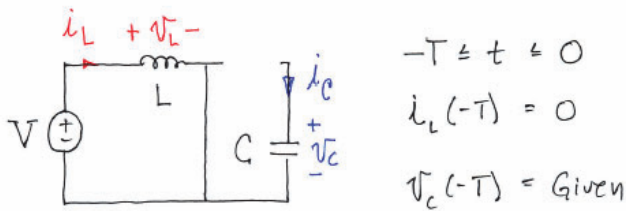

$$V = v_L = L \frac{di_L}{dt} \Rightarrow i_L(t) = \frac{V}{L}(t+T)$$
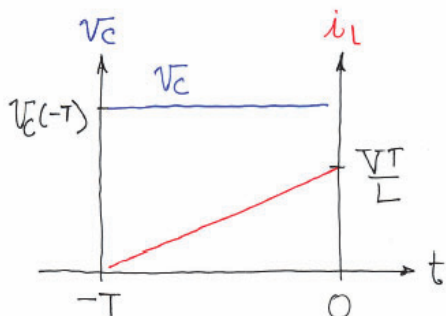
$$0 = i_C = C \frac{dv_C}{dt} \Rightarrow v_C(t) = v_C(-T)$$



$$V = LC \frac{d^2 v_C}{dt^2} + v_C \quad \& \quad i_C = C \frac{dv_C}{dt}$$

$$v_C = V + A \sin\left(\frac{t}{\sqrt{LC}}\right) + B \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_L = C \frac{dv_C}{dt} = \sqrt{\frac{C}{L}} A \cos\left(\frac{t}{\sqrt{LC}}\right) - \sqrt{\frac{C}{L}} B \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$$v_C = V + \sqrt{\frac{L}{C}} i_L(0) \sin\left(\frac{t}{\sqrt{LC}}\right) + (v_C(0) - V) \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_L = i_L(0) \cos\left(\frac{t}{\sqrt{LC}}\right) - \sqrt{\frac{C}{L}} (v_C(0) - V) \sin\left(\frac{t}{\sqrt{LC}}\right)$$


All States Together

State II Review:


$\phi = \text{Positive}$

$$V_c(t) = V + \sqrt{(V_c(0)-V)^2 + \frac{L}{C} i_L^2(0)} \cos\left(\frac{t}{\sqrt{LC}} - \tan^{-1}\left(\sqrt{\frac{L}{C}} \frac{i_L(0)}{V_c(0)-V}\right)\right)$$
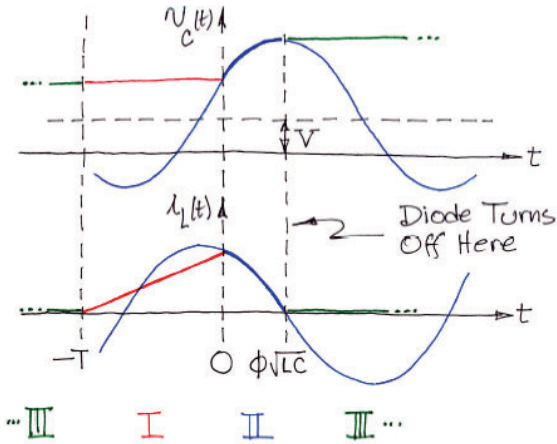
$$i_L(t) = -\sqrt{\frac{C}{L}(V_c(0)-V)^2 + i_L^2(0)} \sin\left(\frac{t}{\sqrt{LC}} - \tan^{-1}\left(\sqrt{\frac{L}{C}} \frac{i_L(0)}{V_c(0)-V}\right)\right)$$



(Lossless) Cycle Analysis

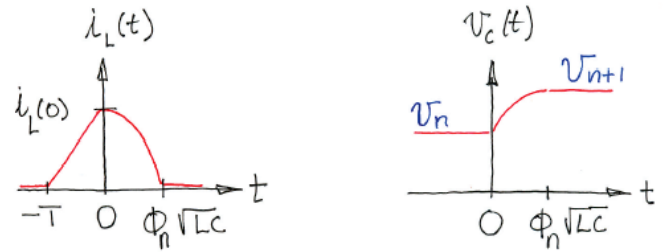

$$V_{n+1} = V + \sqrt{(V_n - V)^2 + \frac{L}{C} i_L^2(0)}$$

$$= V + \sqrt{(V_n - V)^2 + \frac{V^2 T^2}{LC}}$$

$$(V_{n+1} - V)^2 = (V_n - V)^2 + \frac{V^2 T^2}{LC} \quad (V_0 - V)^2 = 0$$

$$V_n = V + V \sqrt{\frac{n T^2}{LC}}$$

Cycle Analysis Via Energy

Conservation: $\Delta W_C = -\Delta W_B + W_L$

Capacitor: $\Delta W_C = \frac{1}{2} C V_{n+1}^2 - \frac{1}{2} C V_n^2$

Inductor: $W_L = \frac{1}{2} L i_L^2(0)$

Battery: $-\Delta W_B = V \Delta Q$


Charge: $\Delta Q = C V_{n+1} - C V_n$

$$\frac{C}{2} V_{n+1}^2 - \frac{C}{2} V_n^2 = C V V_{n+1} - C V V_n + \frac{L}{2} i_L^2(0)$$


$$V_{n+1}^2 - 2V V_{n+1} + V^2 = V_n^2 - 2V V_n + V^2 + \frac{L}{C} i_L^2(0)$$

$$(V_{n+1} - V)^2 = (V_n - V)^2 + \frac{L}{C} i_L^2(0) \quad \dots \text{As Before!}$$

Demo

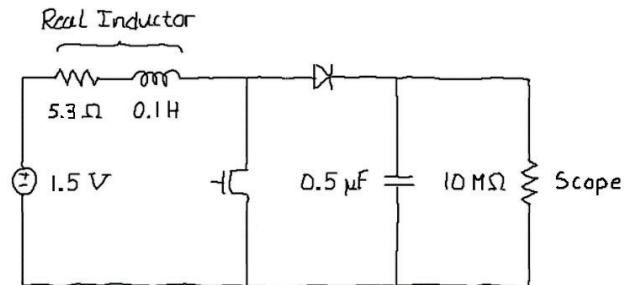


MOSFET Switching

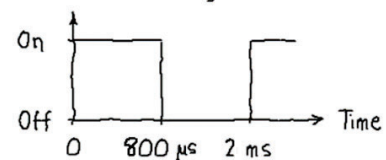

- Transistor Rating = 50V
- Capacitor Rating = 100V
- Diode Rating = 100V
- Inductor Rating = ?

Operation


First two switching cycles

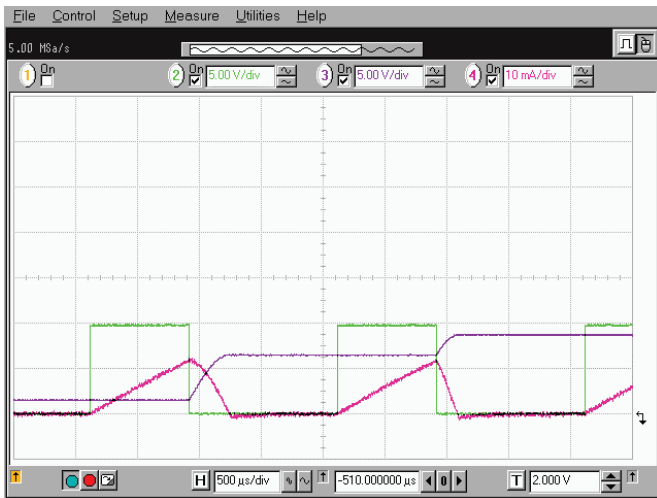

Green: S1 switch state (high = on and low = off)
Red: inductor current (10 mA/division)
Purple: capacitor voltage (5 V/division)

Operation

First fifty switching cycles

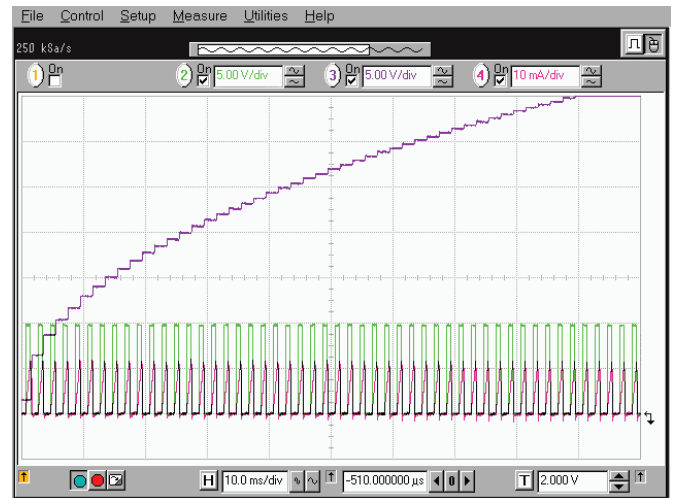

Green: S1 switch state (high = on and low = off)
Red: inductor current (10 mA/division)
Purple: capacitor voltage (5 V/division)

Simulation

This simulation omits all losses:
inductor, scope, transistor and diode.

