
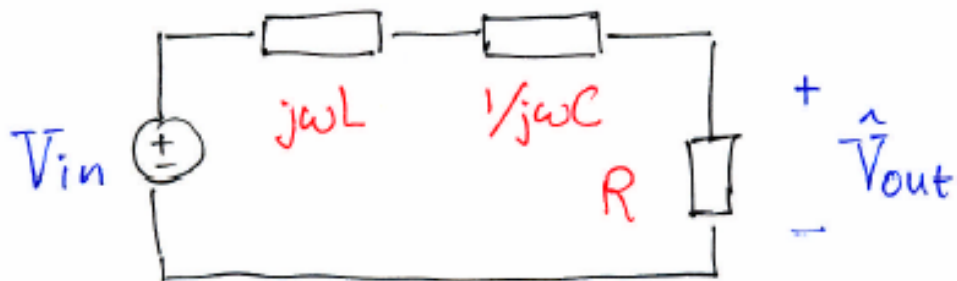


6.200 - Lecture 11A

Filtering:

- Completion of Last Lecture
- Simple Filtering Objectives
(LPF , HPF , BPF , BSF)
- Simple Synthesis
 - Without Op Amps
 - With Op Amps
- Logarithmic Bode Plots

Series RLC Example

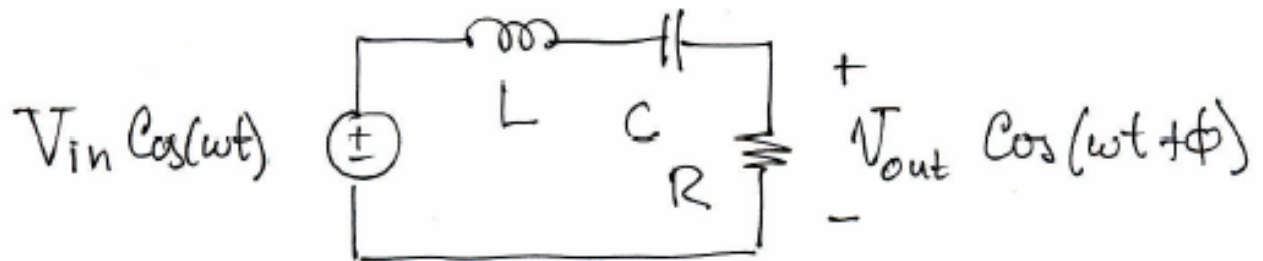


$$\hat{V}_{out} = \frac{R}{R + j\omega L + 1/j\omega C} \hat{V}_{in} = \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC} \hat{V}_{in}$$

$$V_{out} = |\hat{V}_{out}| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} V_{in}$$

$$\phi = \angle \hat{V}_{out} = \tan^{-1} \left(\frac{1 - \omega^2 LC}{\omega RC} \right)$$

Magnitude: Series RLC

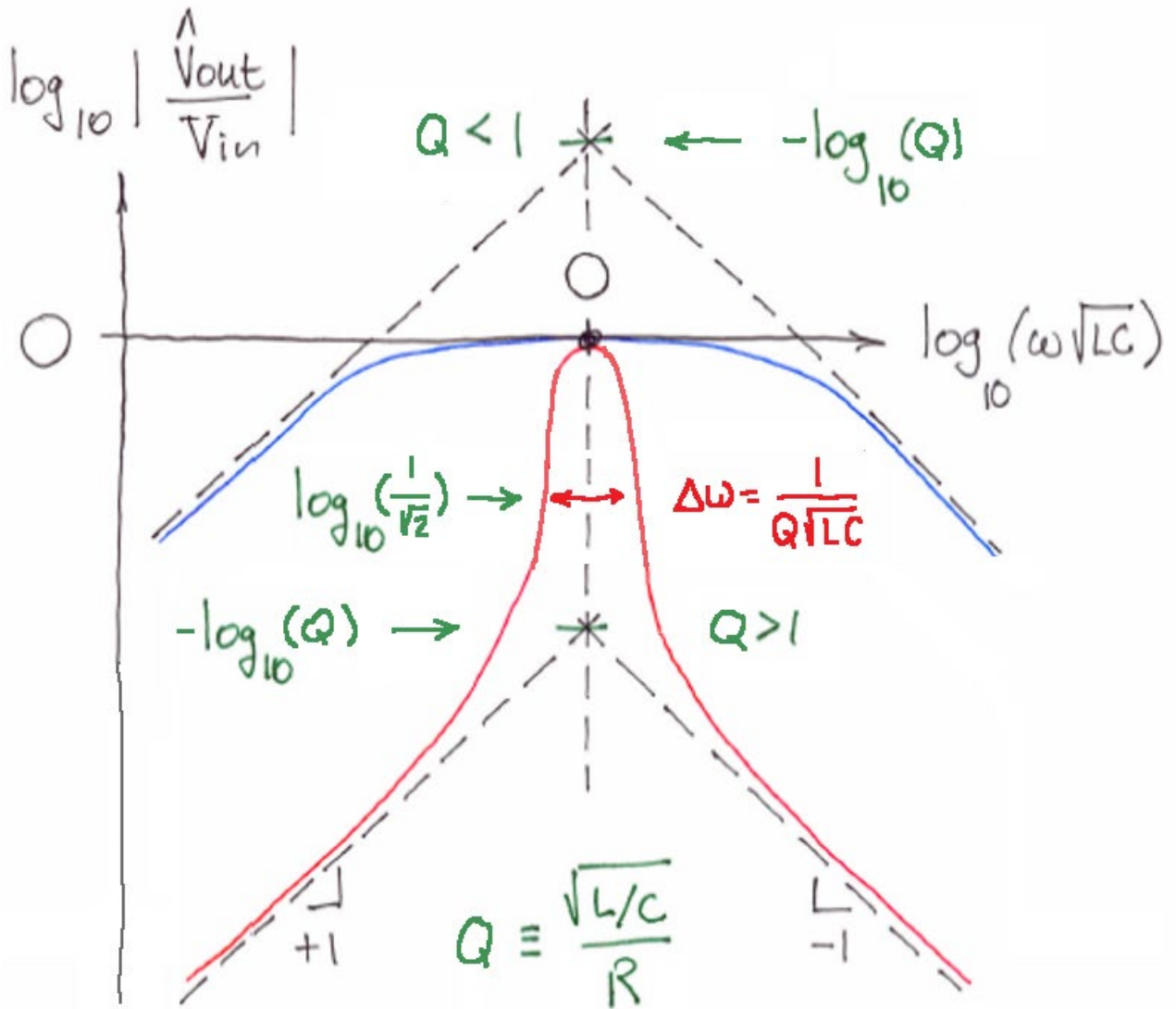



Low Frequency

$$\frac{|\hat{V}_{out}|}{V_{in}} \sim \omega RC = \frac{\omega\sqrt{LC}}{Q}$$

High Frequency





$$\frac{|\hat{V}_{out}|}{V_{in}} \sim \frac{R}{\omega L} = \frac{1}{\omega\sqrt{LC}Q}$$

Phase: Series-LC


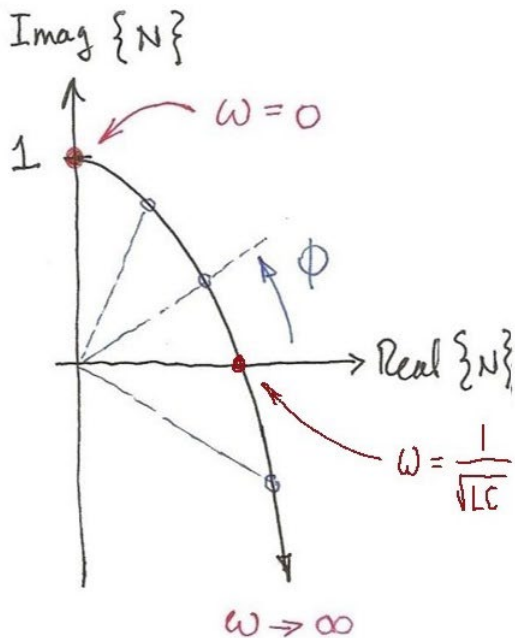
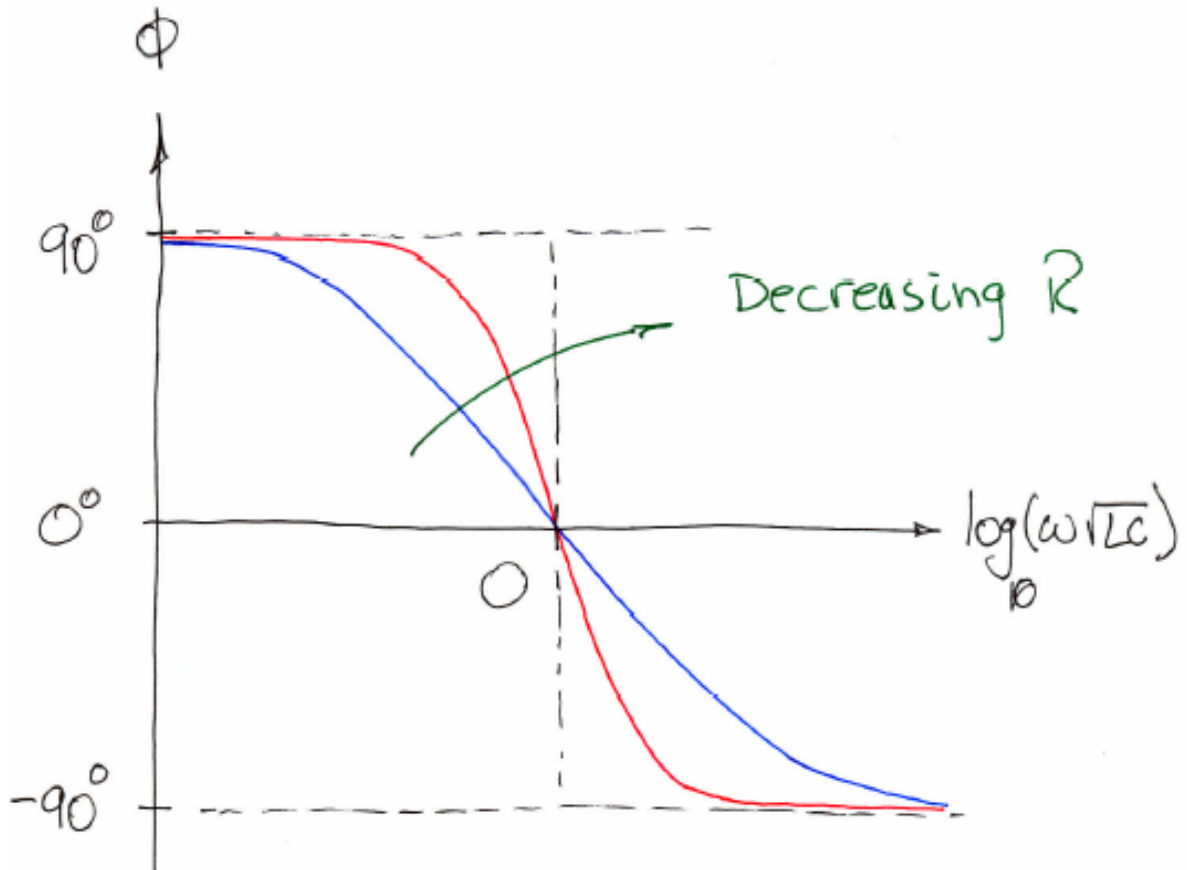


$$\begin{aligned}
 \phi &= \angle \left| \frac{\hat{V}_{out}}{V_{in}} \right| \\
 &= \angle \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC} \\
 &= \angle \frac{j\omega RC (1 - \omega^2 LC - j\omega RC)}{(1 - \omega^2 LC)^2 + (\omega RC)^2} \\
 &= \angle j(1 - \omega^2 LC) + \omega RC \\
 &= \angle N
 \end{aligned}$$




Simple Filtering Objectives

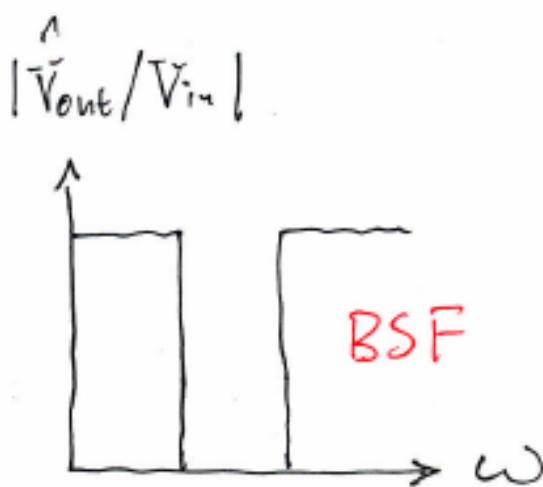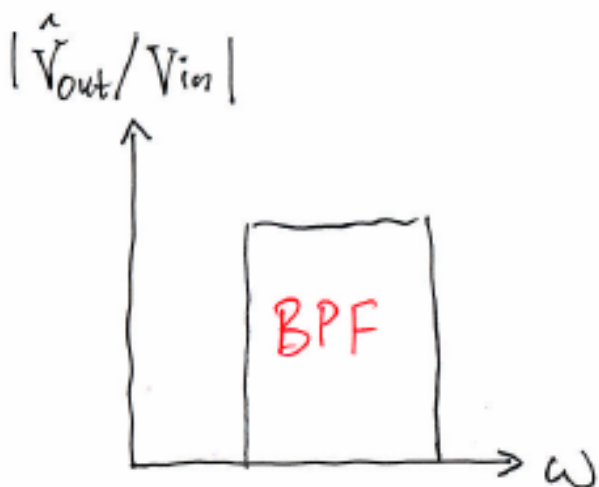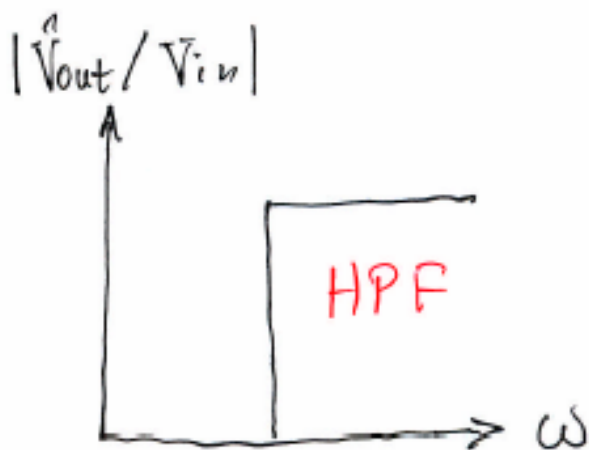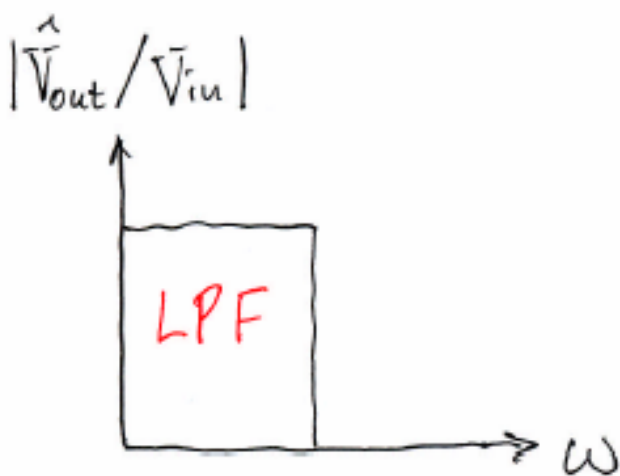




Simple Filtering Synthesis

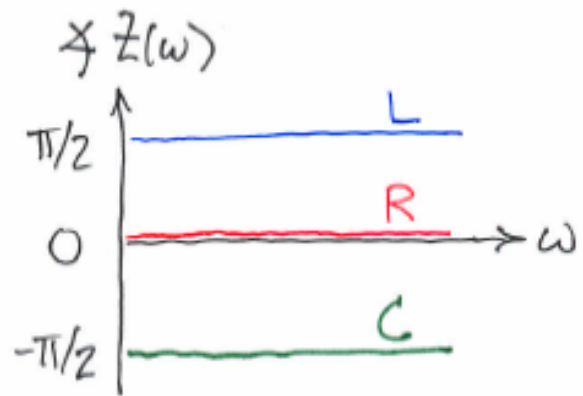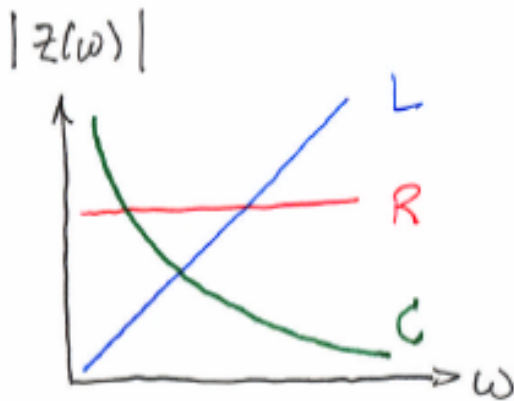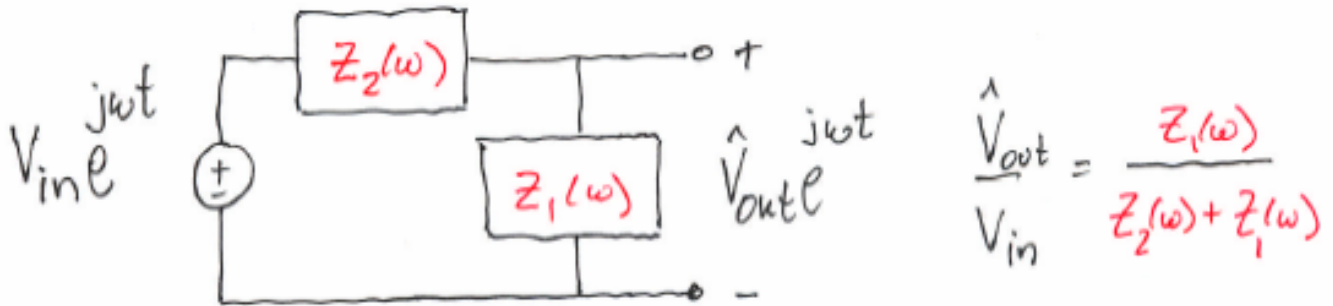

LPF:

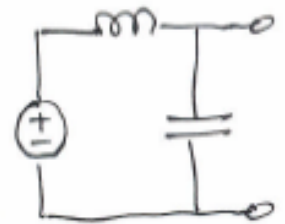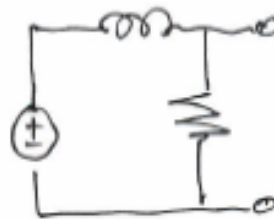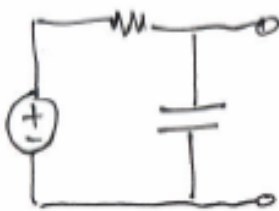

HPF:

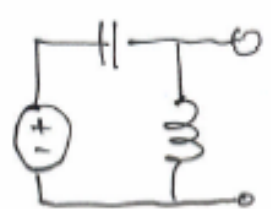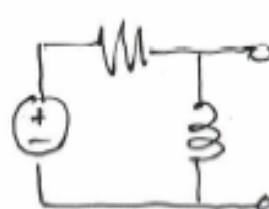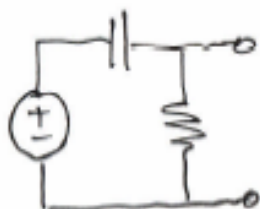


RC & RL Low-Pass Filters

$$V_{in} \begin{array}{c} \text{---} \\ | \\ \text{---} \\ \oplus \\ | \\ \ominus \end{array} \begin{array}{c} \text{---} \\ | \\ \text{---} \\ \oplus \\ | \\ \ominus \end{array} \begin{array}{c} \text{---} \\ | \\ \text{---} \\ \oplus \\ | \\ \ominus \end{array} \begin{array}{c} \text{---} \\ | \\ \text{---} \\ \oplus \\ | \\ \ominus \end{array} \hat{V}_{out} = \frac{1/j\omega C}{R + 1/j\omega C} V_{in} = \frac{V_{in}}{j\omega RC + 1}$$

$$V_{in} \begin{array}{c} \text{---} \\ | \\ \text{---} \\ \oplus \\ | \\ \ominus \end{array} \begin{array}{c} \text{---} \\ | \\ \text{---} \\ \oplus \\ | \\ \ominus \end{array} \begin{array}{c} \text{---} \\ | \\ \text{---} \\ \oplus \\ | \\ \ominus \end{array} \begin{array}{c} \text{---} \\ | \\ \text{---} \\ \oplus \\ | \\ \ominus \end{array} \hat{V}_{out} = \frac{R}{R + j\omega L} V_{in} = \frac{V_{in}}{j\omega L/R + 1}$$

Both $\Rightarrow \hat{V}_{out}/V_{in} \equiv H(j\omega) = \frac{1}{j\omega\tau + 1} \quad \tau = RC, L/R$


$$\text{Gain} = |H| = \frac{1}{\sqrt{\omega^2\tau^2 + 1}}$$

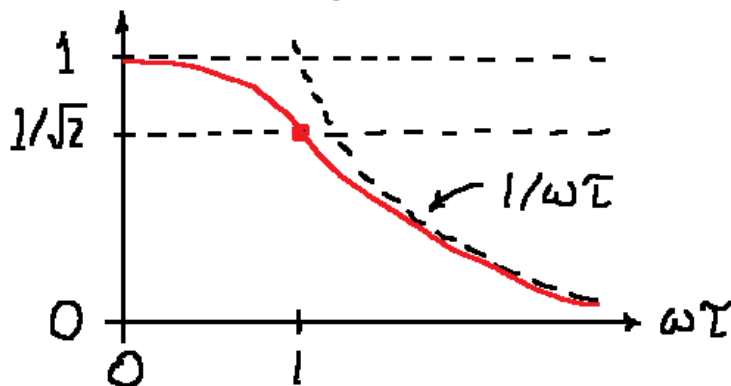


Together, the gain and phase plots are termed a Bode plot.

$$\angle H = \angle 1 - j\omega\tau = \angle N$$
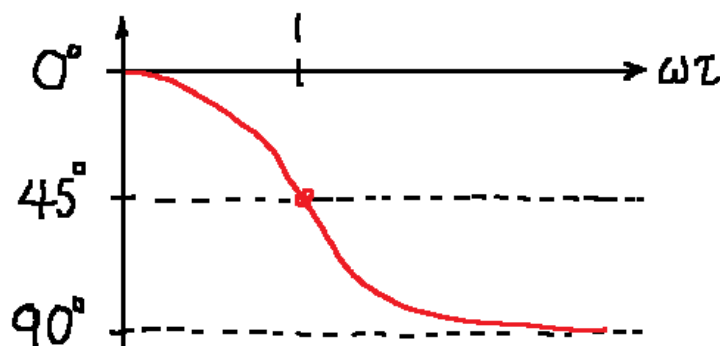
$$\text{Phase} = \angle H = \tan^{-1}(-\omega\tau)$$



$\text{Im}\{N\}$

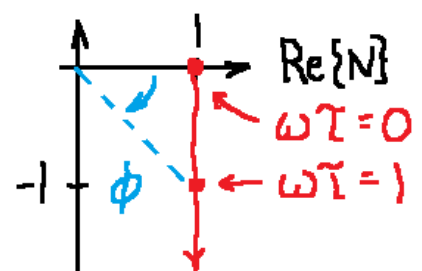

Bels [B] & deciBels [dB]

Base 10 logarithmic scales are often used to show features of $H(j\omega)$ with clarity over a wide range of frequency and amplitude.

The argument of a logarithm should be unitless, so logarithmic scales are scales that are defined relative to a reference. The Bel unit of measurement expresses relative power such that two signals whose strengths differ by 1 Bel [B] have a power ratio of 10. Two signals whose strengths differ by 1 deciBel [dB] have a power ratio of $10^{0.1}$. Thus, there are ten 1 dB steps in 1 B. The use of dB is much more common.

The reference for a logarithmic scale must be specified. If left unspecified, a good assumption is 1 W for the reference. Or, the reference could be specified with extra letters. For example, dBW and dBm use 1 W and 1 mW, respectively for a reference.


dB For Signals

Generally, Power (P) \sim Signal² (S^2)

$$\Rightarrow \text{Power Gain} = 10 \log_{10} \left(\frac{P}{P_{\text{Ref}}} \right) \text{ dB}$$

$$= 10 \log_{10} \left(\frac{S^2}{S_{\text{Ref}}^2} \right) \text{ dB}$$

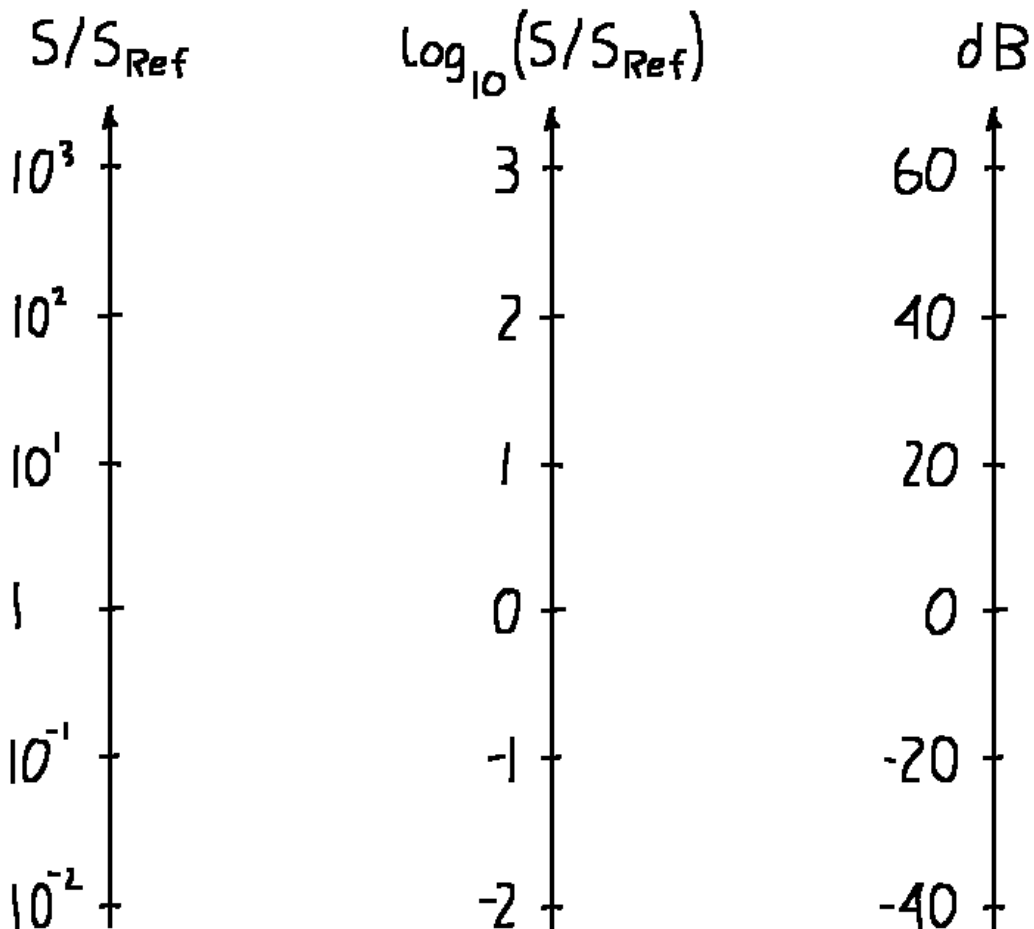
$$= 20 \log_{10} \left(\frac{S}{S_{\text{Ref}}} \right) \text{ dB}$$





Logarithmic Gain Plot

Gain asymptotes often take the form $(\omega\tau)^n$

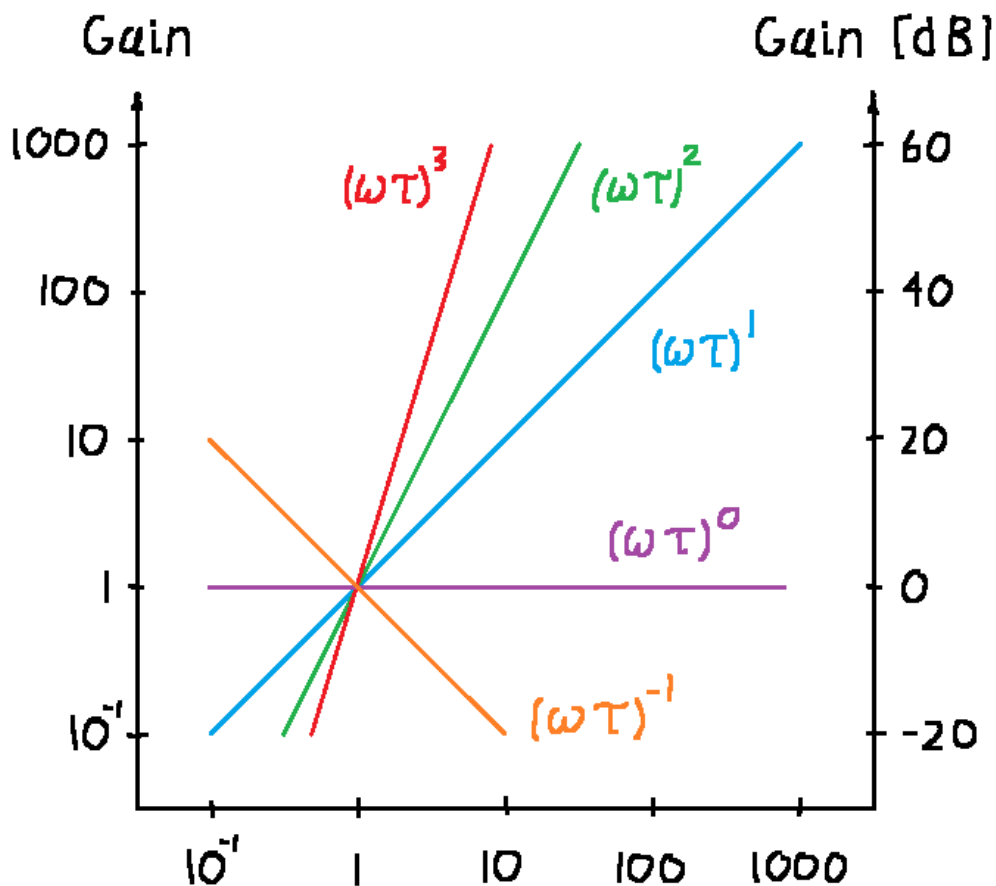- $\log_{10}((\omega\tau)^n) = n \cdot \log_{10}(\omega\tau)$
⇒ n decades per decade
- $20 \log_{10}((\omega\tau)^n) = 20 n \cdot \log_{10}(\omega\tau)$
⇒ $20 n$ dB per decade



Low-Pass Filter Bode Plot

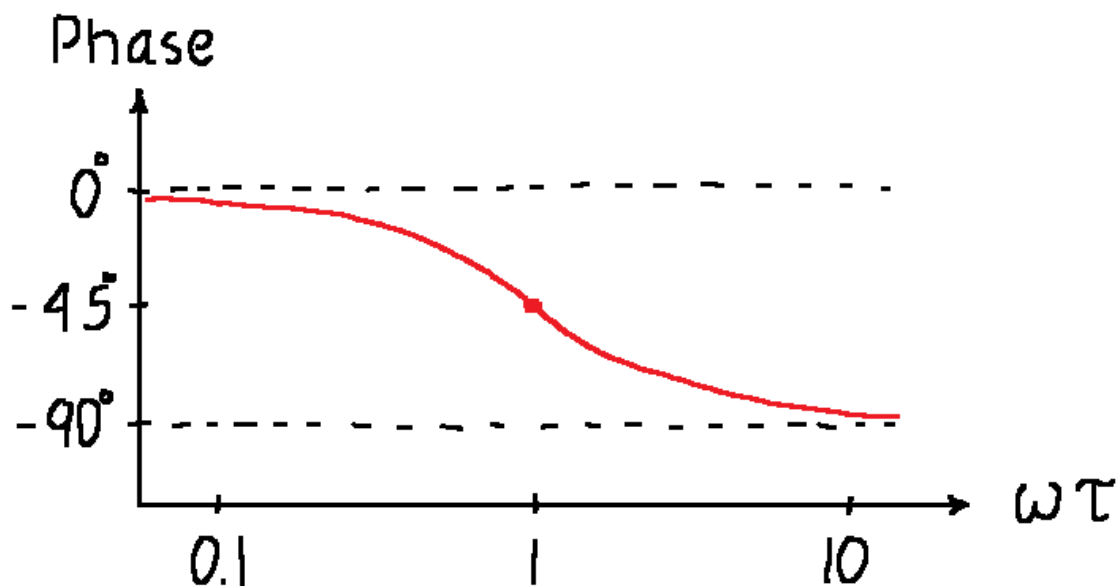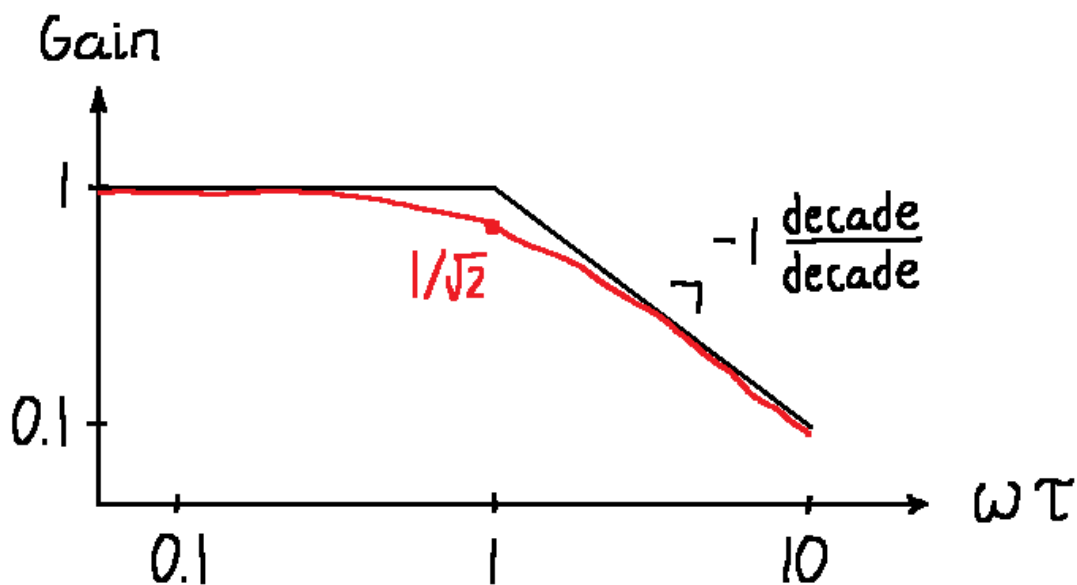


RC & RL High-Pass Filter

$$V_{in} \begin{array}{c} \text{---} | \text{---} \\ | \\ \oplus \text{---} C \text{---} \\ | \\ \ominus \end{array} \begin{array}{c} \oplus \\ | \\ \ominus \end{array} \begin{array}{c} | \\ | \\ \oplus \text{---} R \text{---} \\ | \\ \ominus \end{array} \hat{V}_{out} = \frac{R}{R + 1/j\omega C} V_{in} = \frac{j\omega RC V_{in}}{j\omega RC + 1}$$

$$V_{in} \begin{array}{c} \oplus \text{---} R \text{---} \\ | \\ \oplus \text{---} L \text{---} \\ | \\ \ominus \end{array} \hat{V}_{out} = \frac{j\omega L}{R + j\omega L} V_{in} = \frac{V_{in} j\omega L/R}{j\omega L/R + 1}$$


$$\text{Both} \Rightarrow \hat{V}_{out}/V_{in} \equiv H(j\omega) = \frac{j\omega\tau}{j\omega\tau + 1} \quad \tau = RC, L/R$$

$$\text{Gain} = |H| = \frac{\omega\tau}{\sqrt{\omega^2\tau^2 + 1}}$$

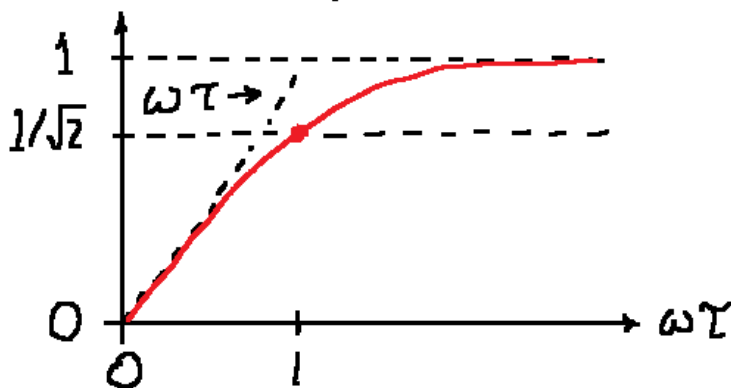

$$\text{Phase} = \angle H = \tan^{-1}(1/\omega\tau)$$


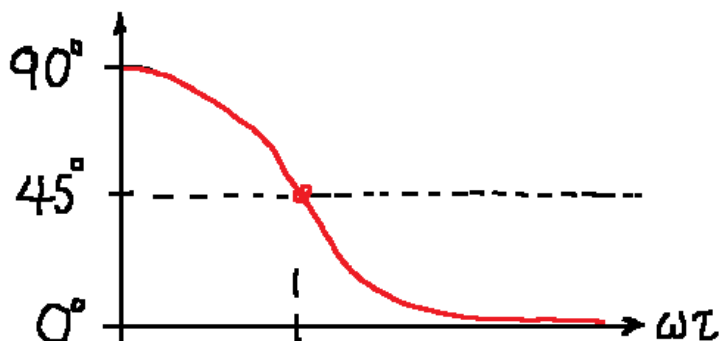
$$\angle H = \angle \frac{j\omega\tau}{j\omega\tau + 1}$$




$$= \angle j\omega\tau(1 - j\omega\tau)$$

$$= \angle \omega\tau + j$$

High-Pass Filter Bode Plot

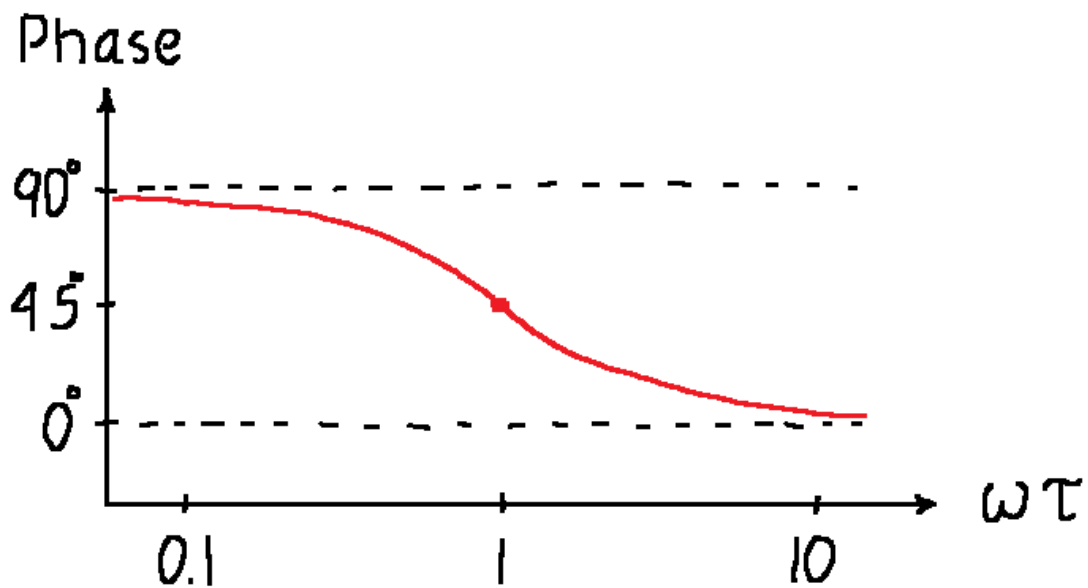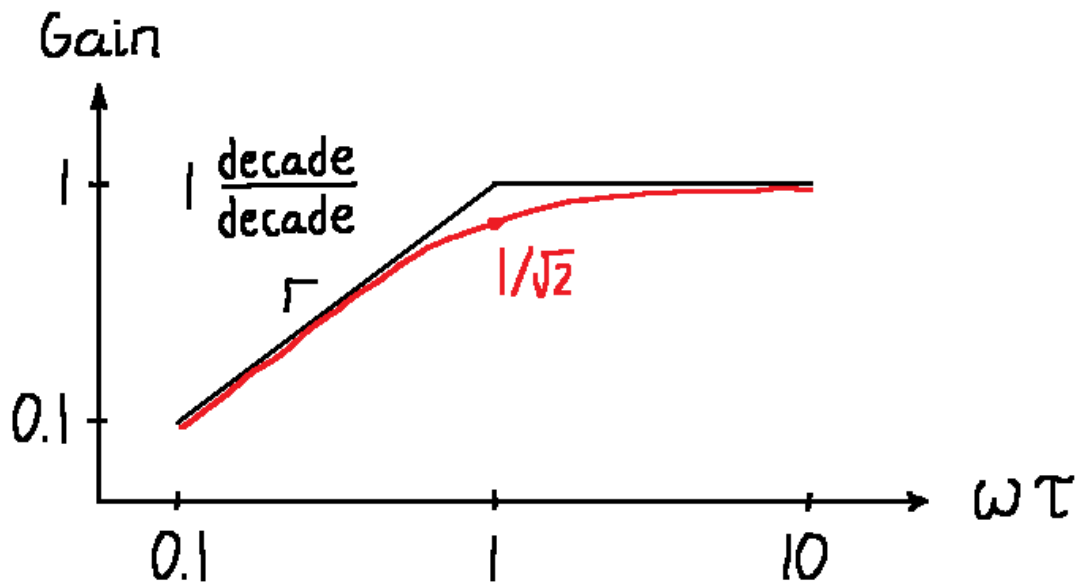

Loaded Filter

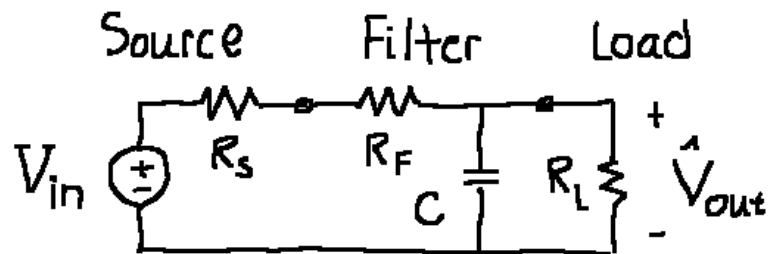


V_{th} R_{th} C R_L \hat{V}_{out}

$$= \frac{V_{th}}{j\omega R_{th}C + 1} \neq \frac{V_{in}}{j\omega R_F C + 1}$$


$$V_{th} = \frac{R_L}{R_s + R_F + R_L} V_{in} \quad \& \quad R_{th} = R_L \parallel (R_s + R_F)$$

Problem: the filter gain and phase are both modified by R_s and R_L .

Solution: use op-amp buffering.

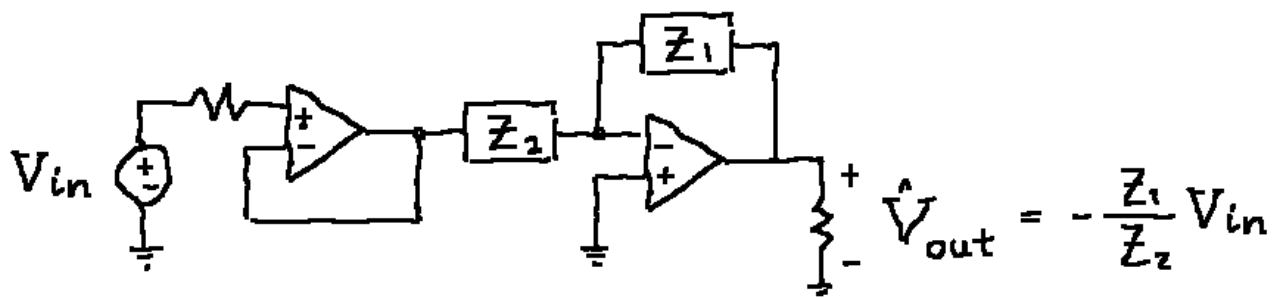

Op-Amp Filter

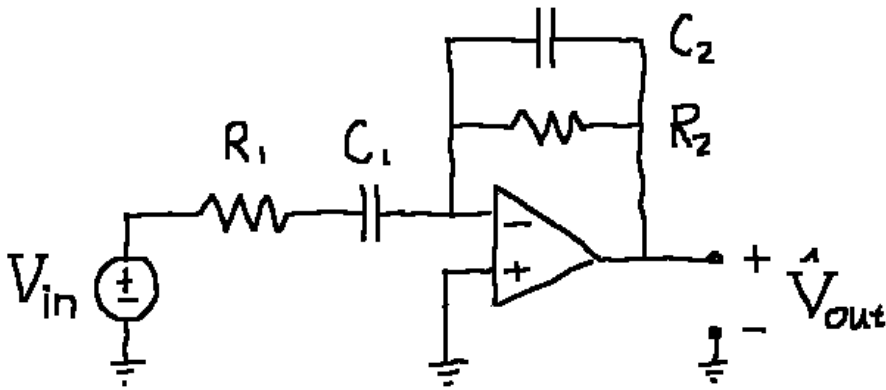

$$\begin{aligned} H(j\omega) &= \frac{\hat{V}_{out}}{V_{in}} = - \frac{R_2 / j\omega C_2}{(R_2 + 1/j\omega C_2)(R_1 + 1/j\omega C_1)} \\ &= - \frac{j\omega C_1 R_2}{(j\omega C_2 R_2 + 1)(j\omega C_1 R_1 + 1)} \end{aligned}$$

Asymptotes: Assume $R_1 C_1 > R_2 C_2$

$$\text{Low } \omega \Rightarrow H \approx -j\omega C_1 R_2$$

$$\text{High } \omega \Rightarrow H \approx -1/j\omega C_2 R_1$$

$$\text{Mid } \omega \Rightarrow H \approx -R_2/R_1$$

Op-Amp Filter Bode Plot

