
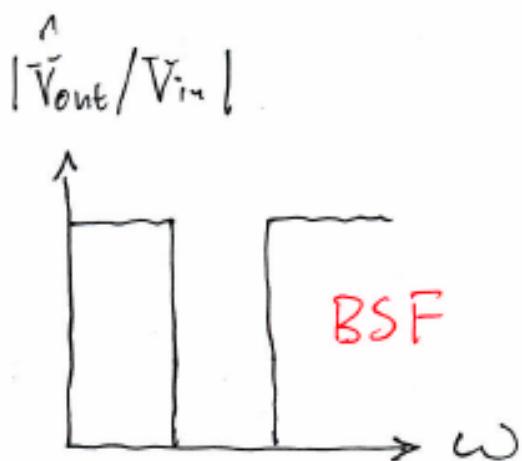
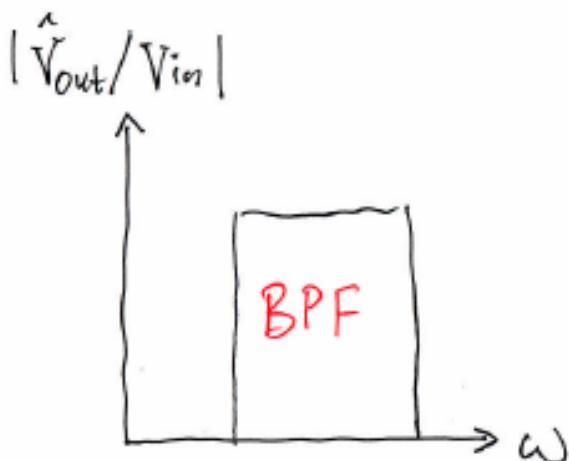
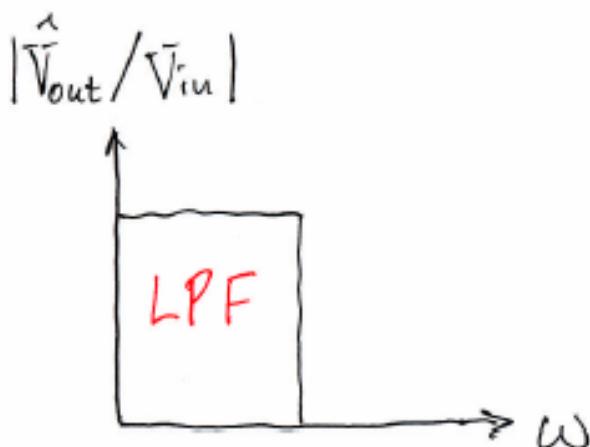


6.002 - Lecture 11B






Filtering:

- Review Simple Objectives
(LPF , HPF , BPF , BSF)
- Review Simple Synthesis
- LC Resonators
- Tesla Coil


Simple Filtering Objectives

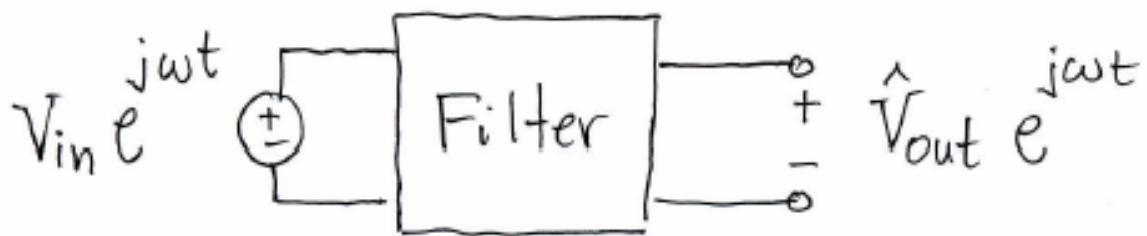





Simple Filtering Synthesis

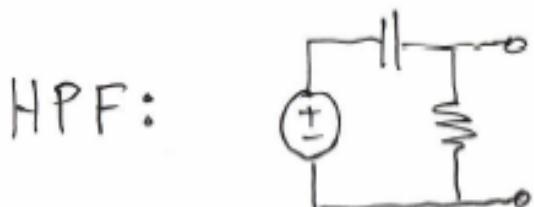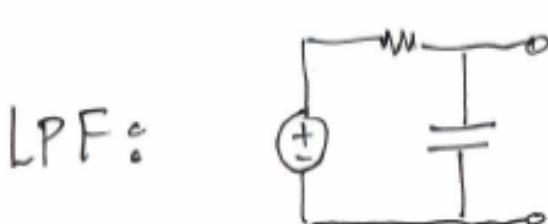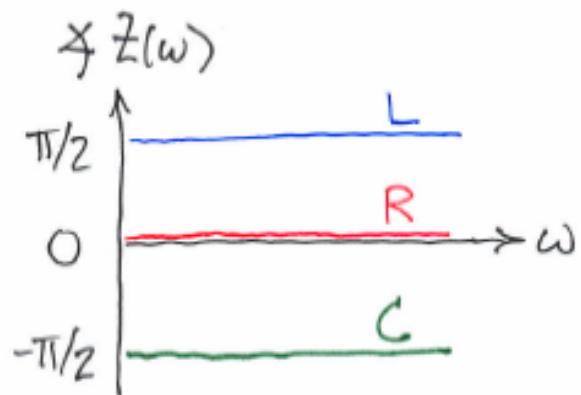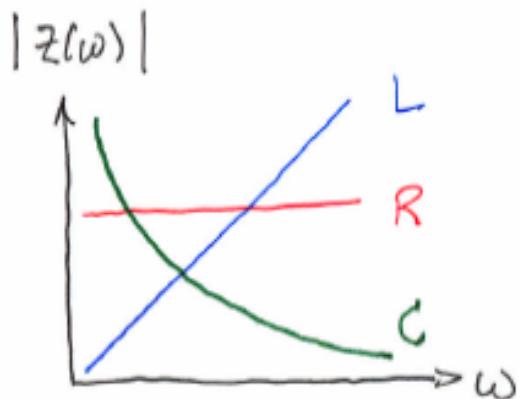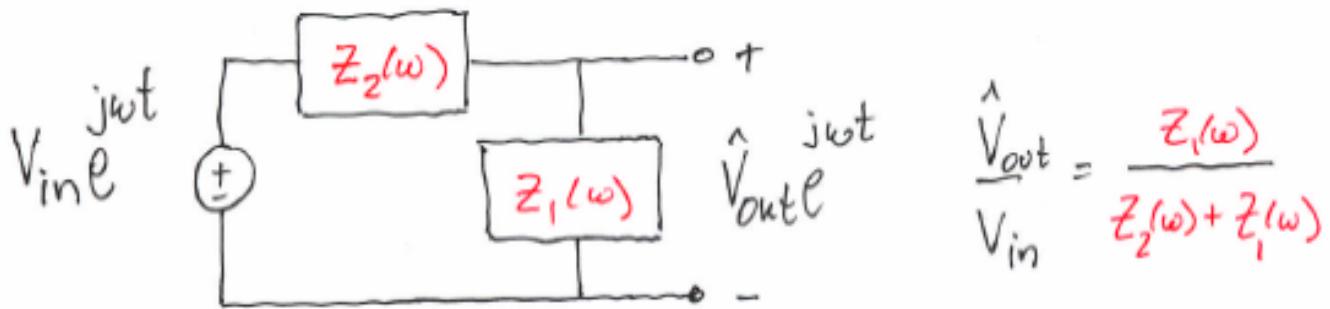


Parallel LC Resonator

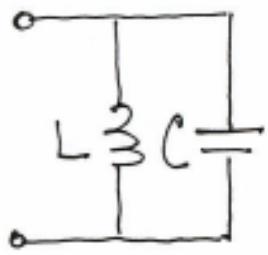

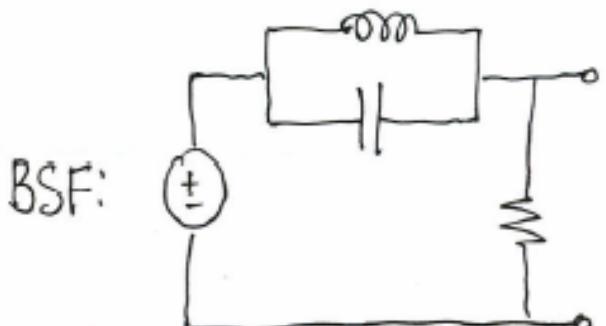
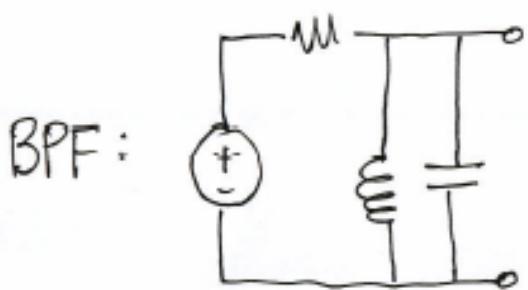
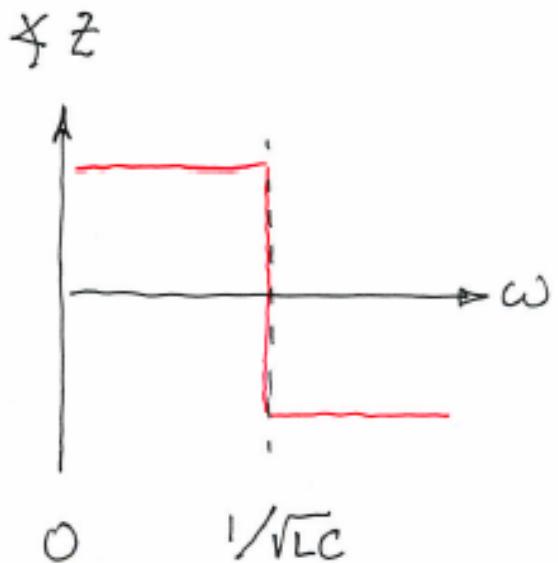
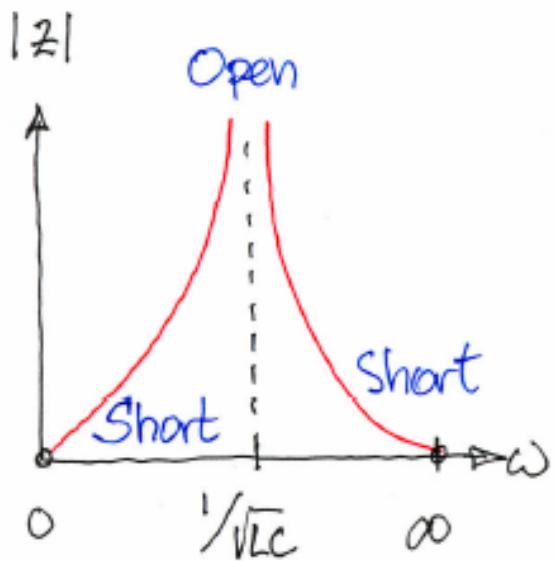
$$Z = \frac{j\omega L \cdot \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega L}{1 - \omega^2 LC}$$





Series LC Resonator

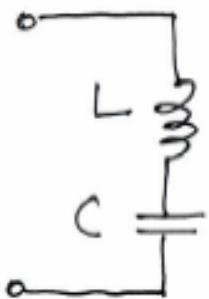
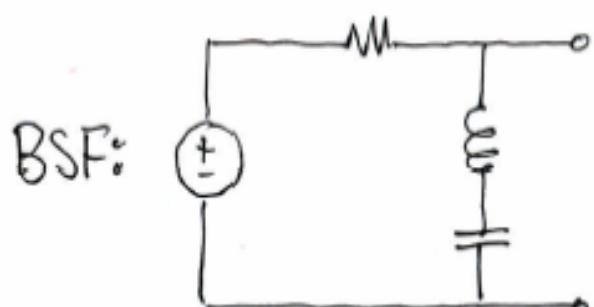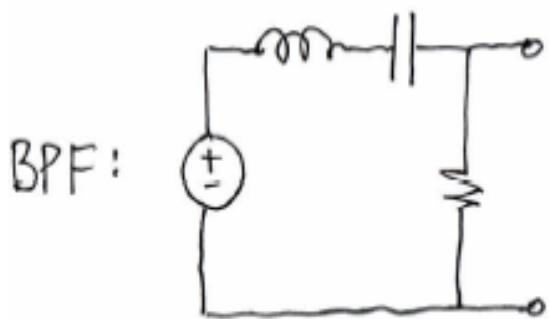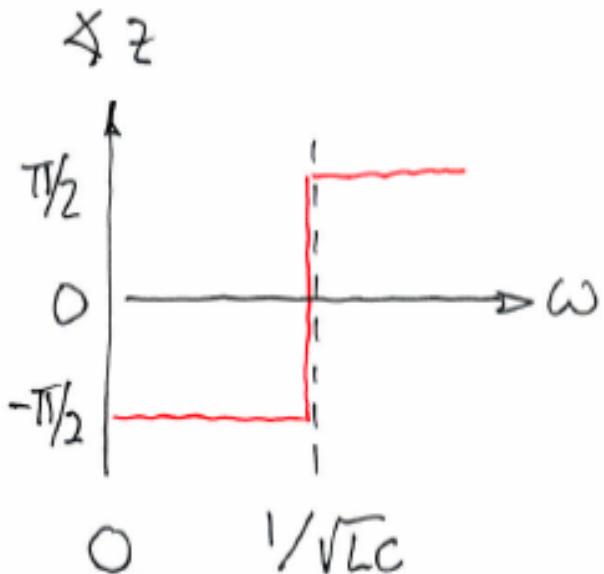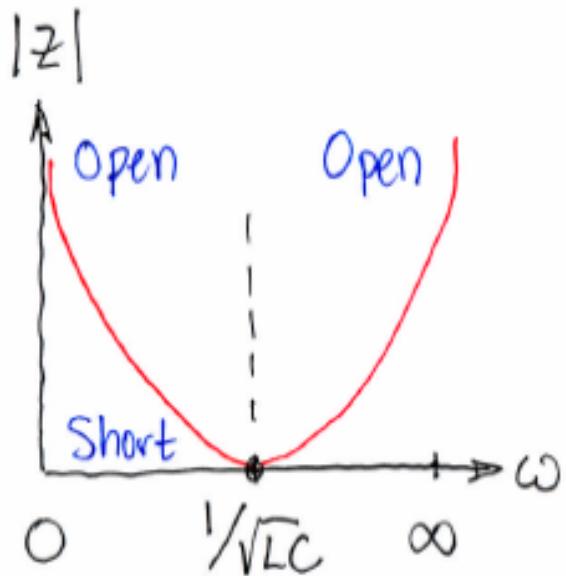
$$Z = j\omega L + \frac{1}{j\omega C} = \frac{1 - \omega^2 LC}{j\omega C}$$



Theory: Series-LC BPF

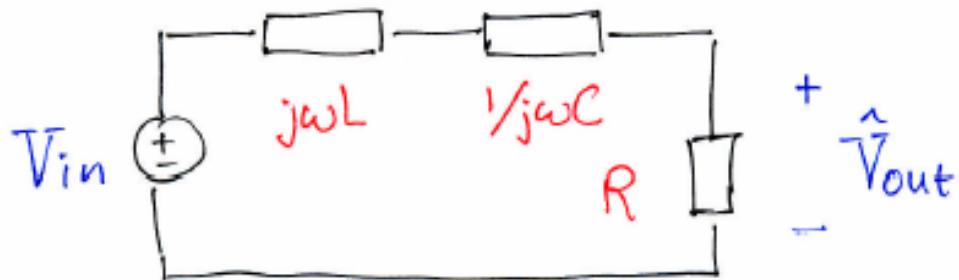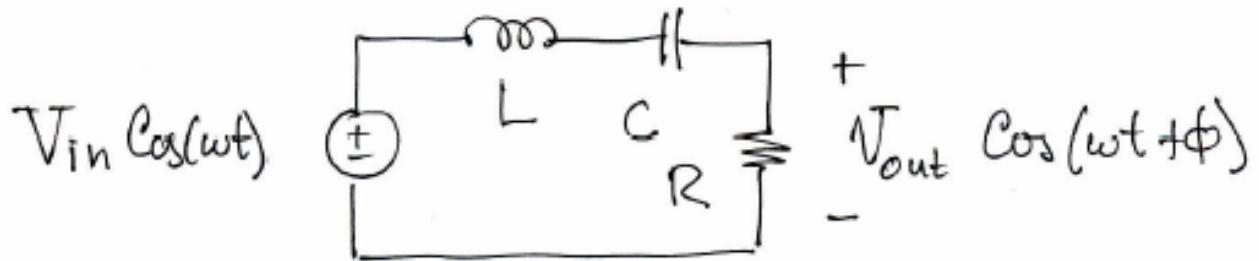


$$\hat{V}_{out} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} \hat{V}_{in} = \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC} \hat{V}_{in}$$

$$V_{out} = |\hat{V}_{out}| = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}} \hat{V}_{in}$$

$$\phi = \arg \hat{V}_{out} = \tan^{-1} \left(\frac{1 - \omega^2 LC}{\omega RC} \right)$$

Theory: Series-LC BPF

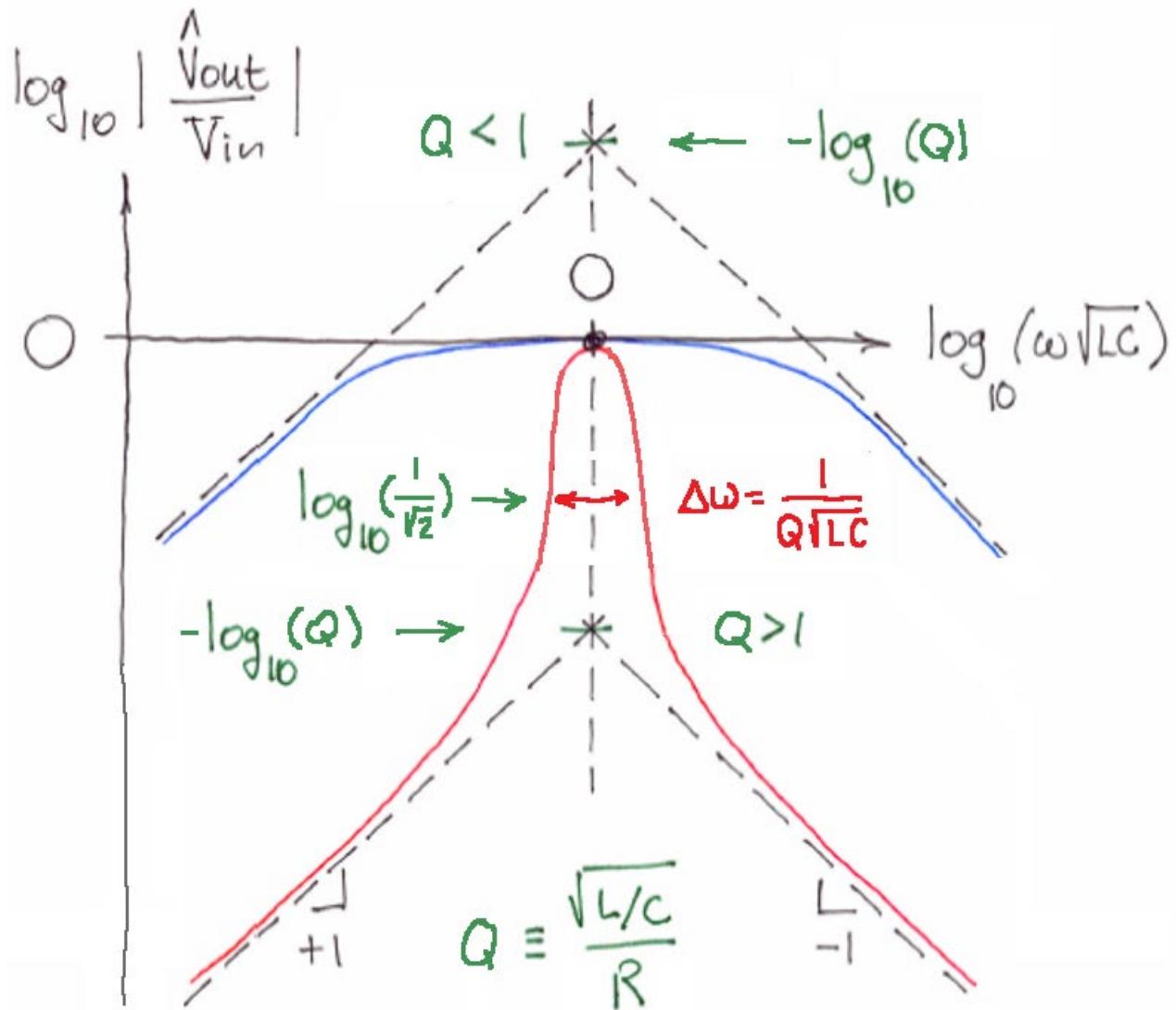



Low Frequency

$$\left| \frac{\hat{V}_{\text{out}}}{V_{\text{in}}} \right| \sim \omega R C = \frac{\omega \sqrt{LC}}{Q}$$

High Frequency


$$\left| \frac{\hat{V}_{\text{out}}}{V_{\text{in}}} \right| \sim \frac{R}{\omega L} = \frac{1}{\omega \sqrt{LC} Q}$$

Theory: Series-LC BPF

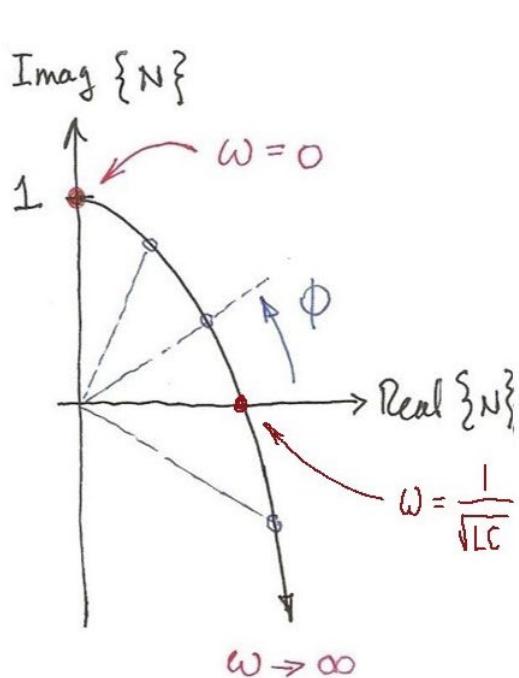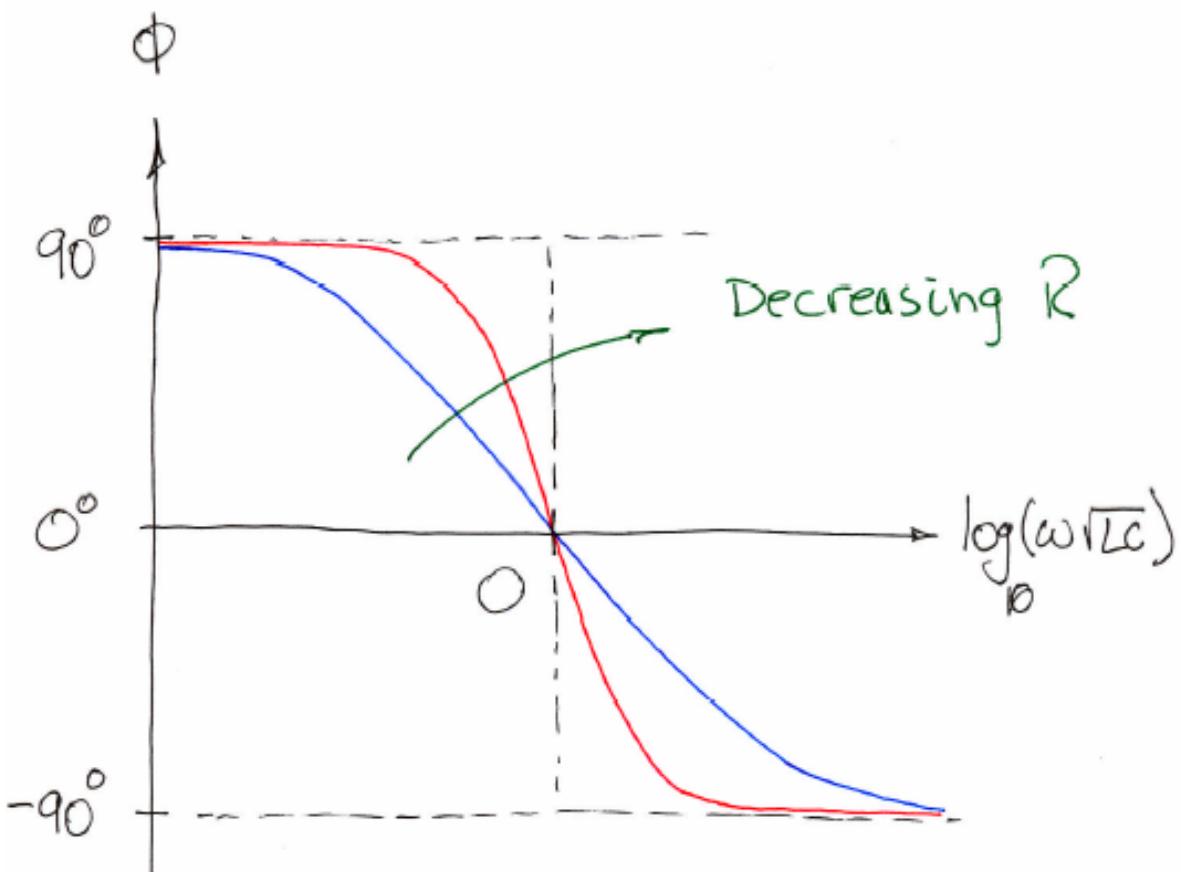



$$\begin{aligned}
 \phi &= \arg \left| \frac{\hat{V}_{out}}{V_{in}} \right| \\
 &= \arg \frac{j\omega RC}{1 - \omega^2 LC + j\omega RC} \\
 &= \arg \frac{j\omega RC (1 - \omega^2 LC - j\omega RC)}{(1 - \omega^2 LC)^2 + (\omega RC)^2} \\
 &= \arg j (1 - \omega^2 LC) + \omega RC \\
 &\equiv \arg N
 \end{aligned}$$

RLC Demos

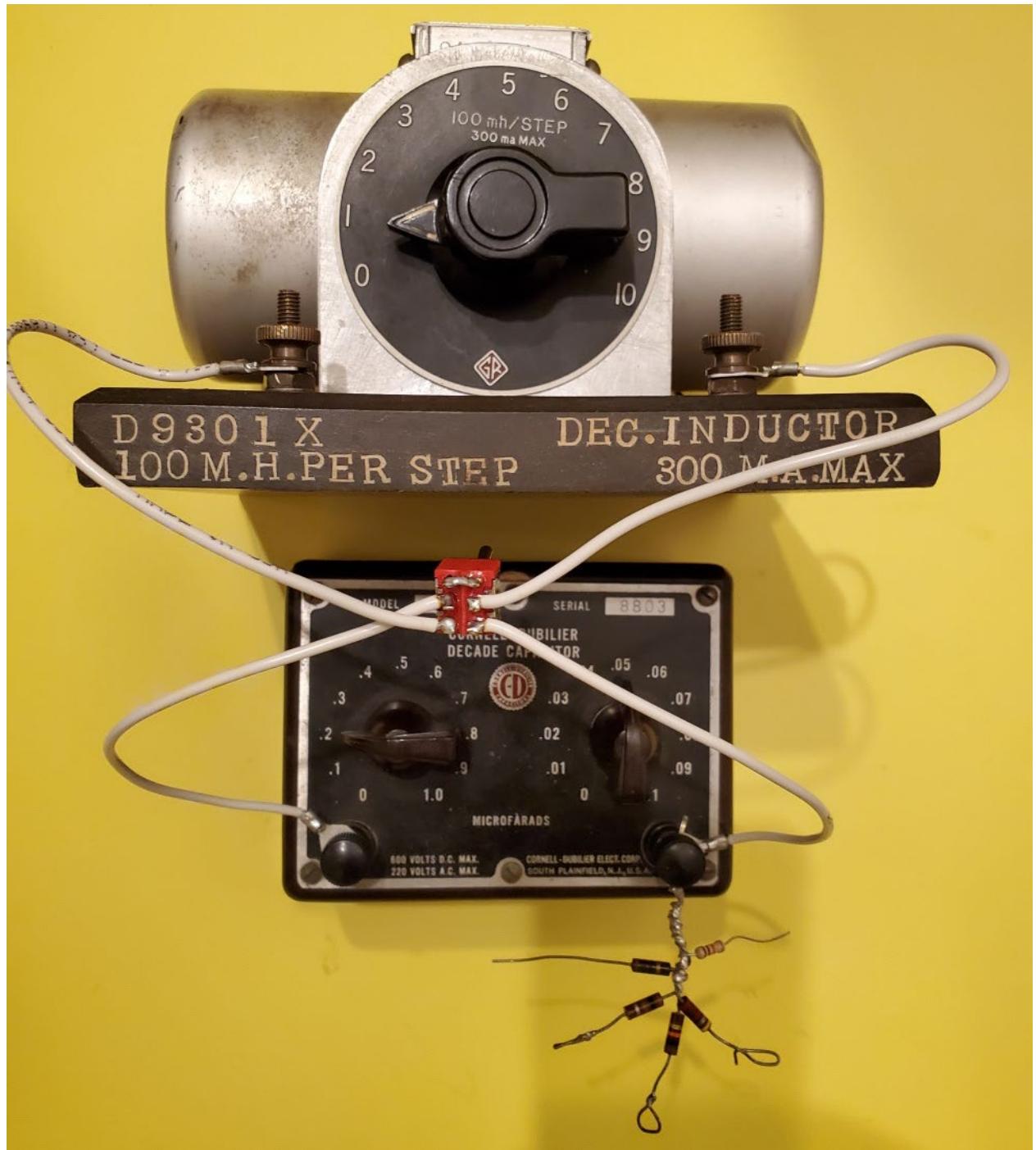


Demo: Series-LC BPF
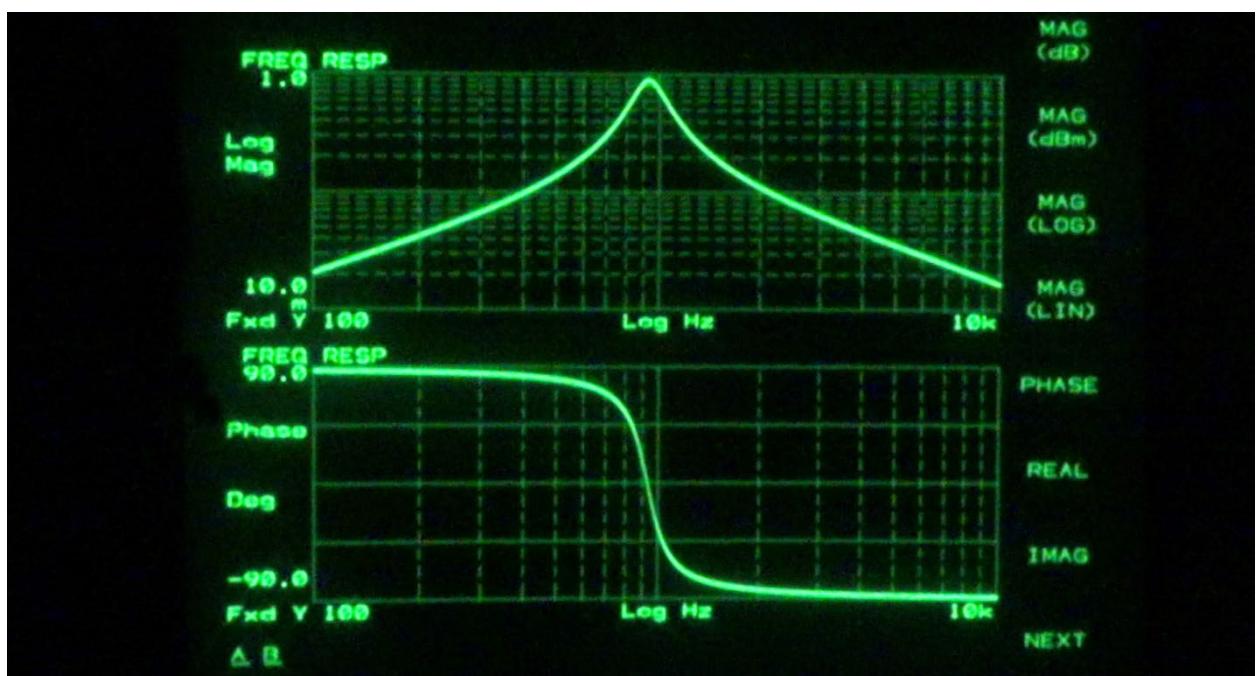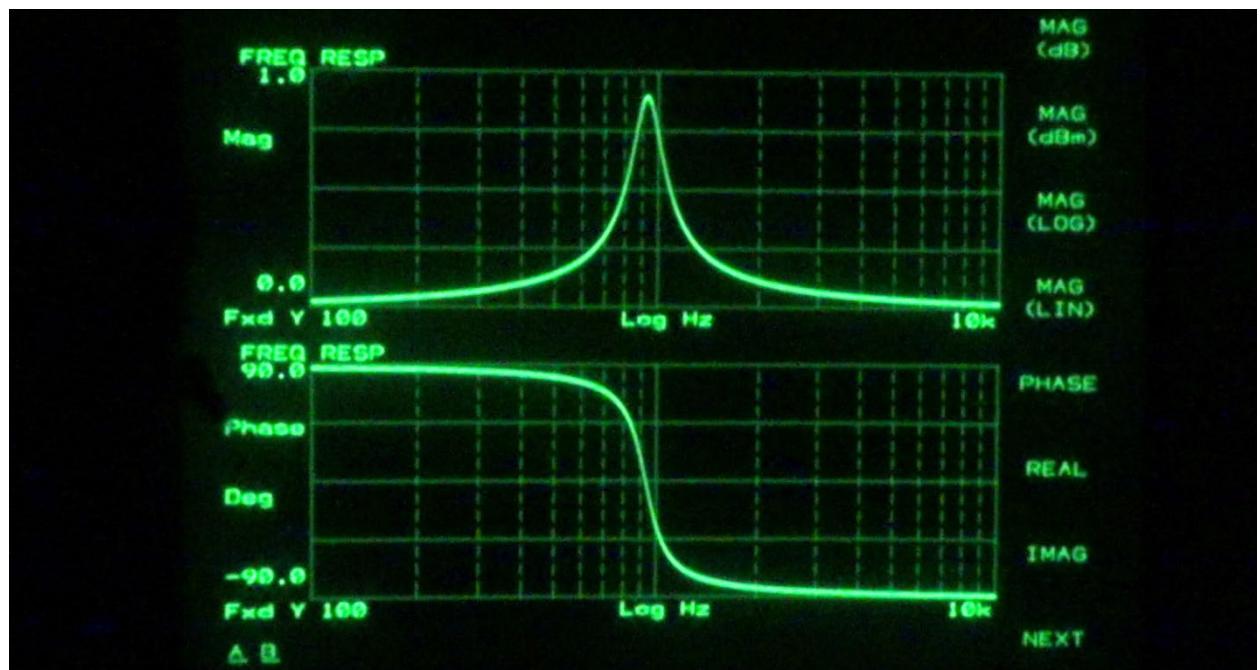
$$L = 0.1 \text{ H} ; C = 0.25 \mu\text{F} ; R = 100 \Omega$$
$$(2\pi\sqrt{LC})^{-1} = 1 \text{ kHz} ; \sqrt{L/C} = 632 \Omega$$




Demo: Series-LC BPF
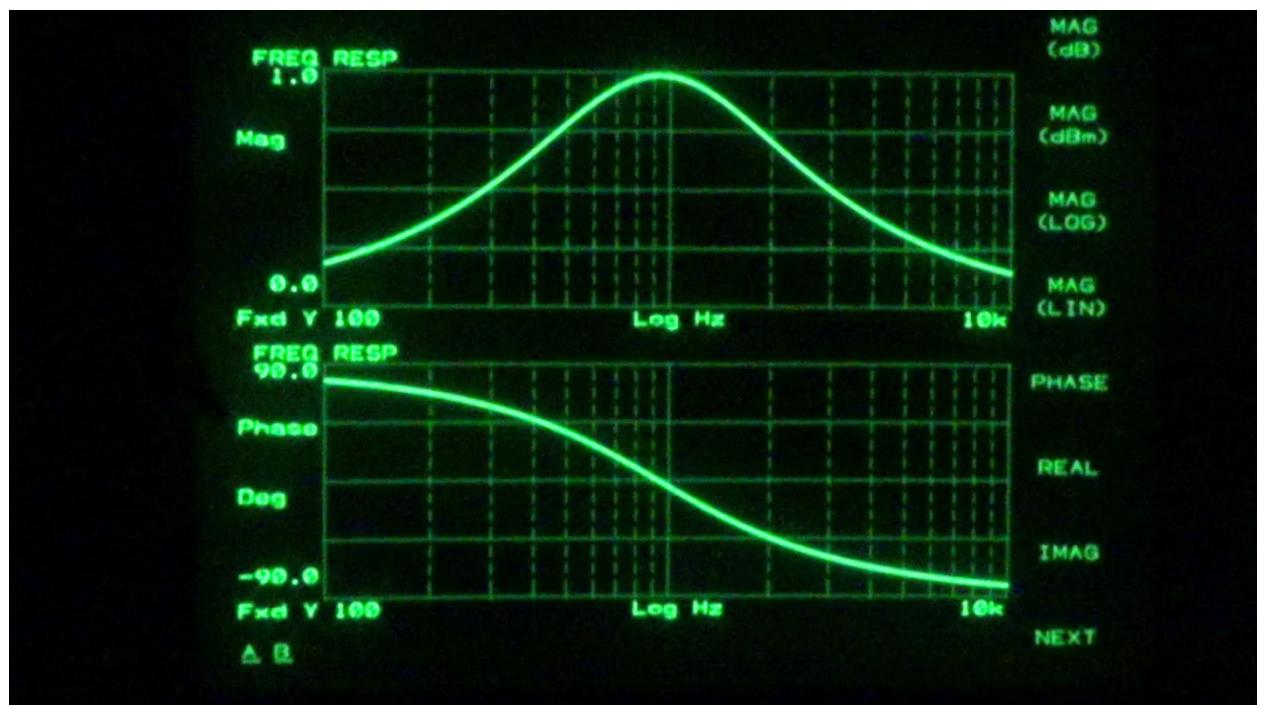
$$L = 0.1 \text{ H} ; C = 0.25 \mu\text{F} ; R = 1 \text{ k}\Omega$$
$$(2\pi\sqrt{LC})^{-1} = 1 \text{ kHz} ; \sqrt{L/C} = 632 \Omega$$




Theory: Parallel-LC BPF

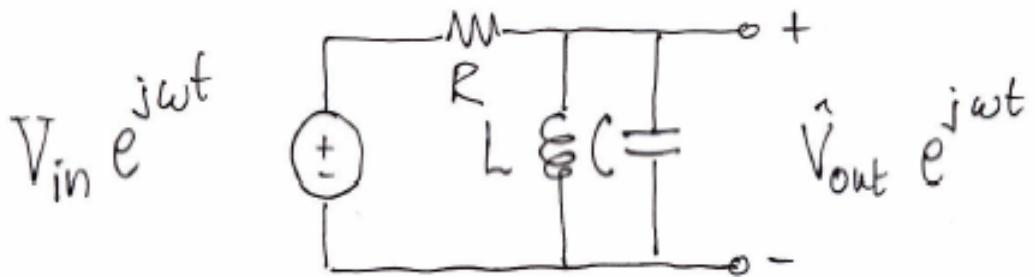

$$\frac{\hat{V}_{out}}{\hat{V}_{in}} = \frac{1/R}{1/R + 1/j\omega L + j\omega C} = \frac{j\omega L/R}{1 - \omega^2 LC + j\omega L/R}$$

$$\left| \frac{\hat{V}_{out}}{\hat{V}_{in}} \right| = \frac{(\omega L/R)}{\sqrt{(1 - \omega^2 LC)^2 + (\omega L/R)^2}}$$

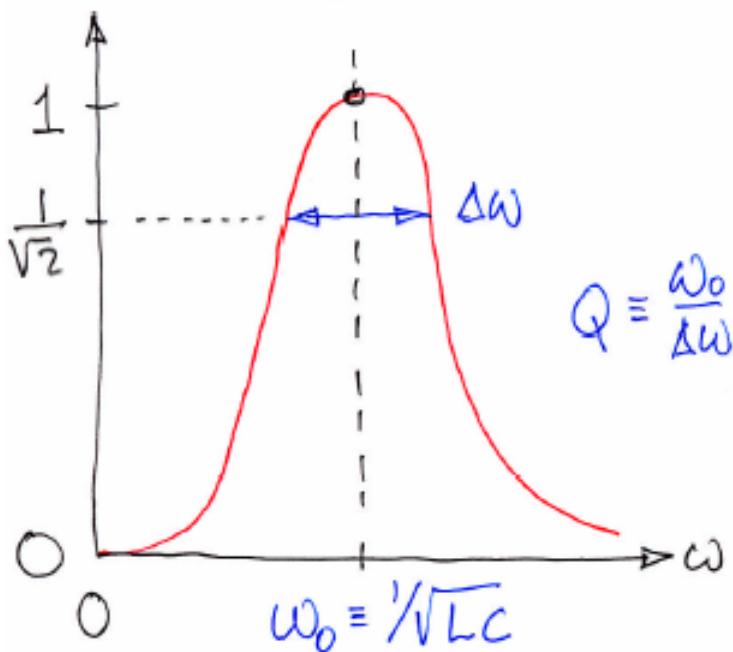

$$Q \equiv \frac{\omega_0}{\Delta\omega} = \frac{R}{\sqrt{LC}}$$

Numbers:

$$L = 0.1 \text{ H}$$

$$C = 0.25 \mu\text{F}$$

$$R = 10 \text{ k}\Omega$$

$$\frac{1}{2\pi\sqrt{LC}} = 1 \text{ kHz}$$


$$\sqrt{LC} = 632 \Omega$$

$$Q = 16$$

Theory: Parallel-LC BPF



$$\left. \begin{array}{l} \text{Low } \omega : \quad \left| \frac{\hat{V}_{\text{out}}}{V_{\text{in}}} \right| \approx \frac{\omega L}{R} = \frac{\omega \sqrt{LC}}{Q} \\ \text{High } \omega : \quad \left| \frac{\hat{V}_{\text{out}}}{V_{\text{in}}} \right| \approx \frac{1}{\omega RC} = \frac{1}{\omega \sqrt{LC} Q} \end{array} \right\} \text{Asymptotes}$$

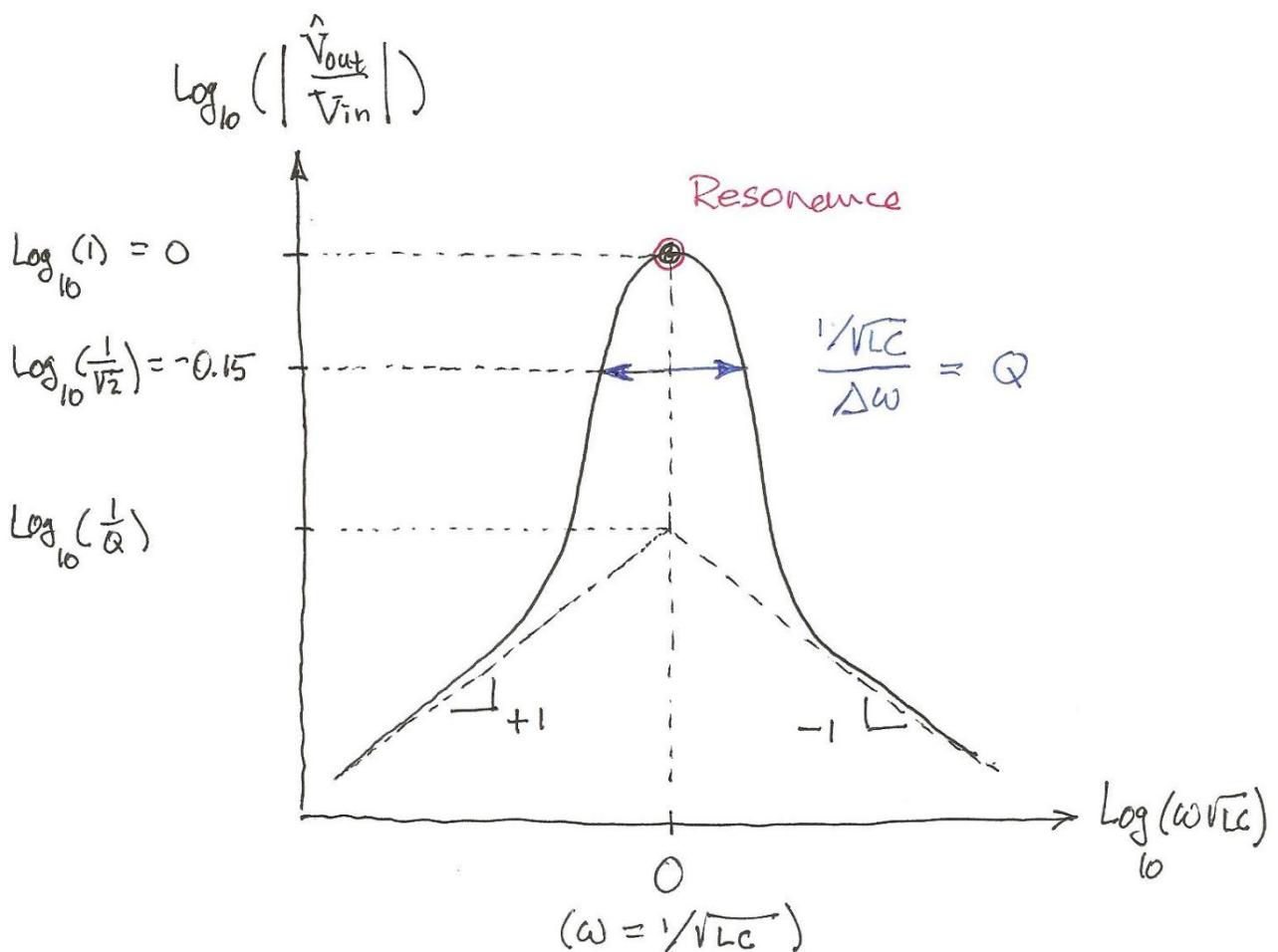Asymptotes cross at $\omega \sqrt{LC} = 1$ with value $\frac{1}{Q}$.




Theory: Parallel-LC BPF
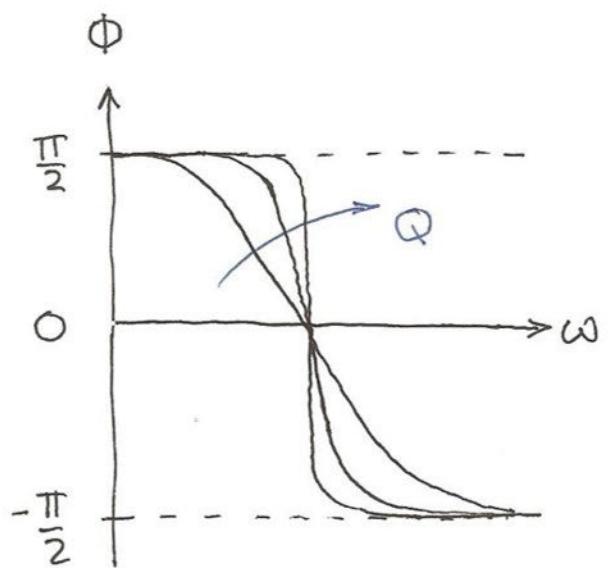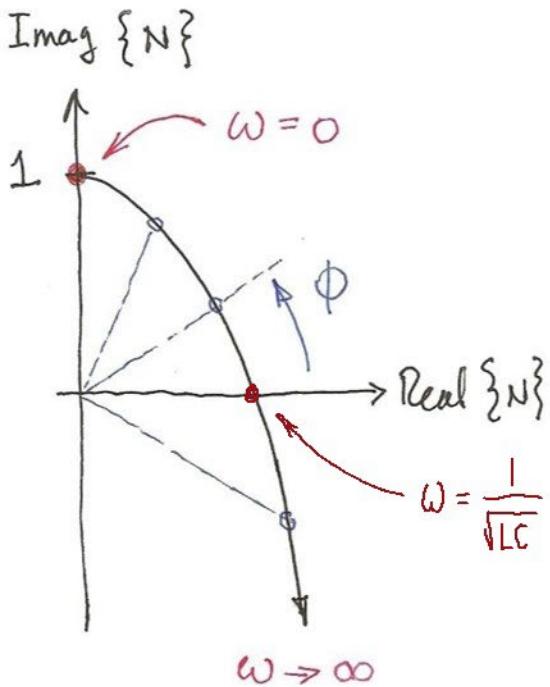
$$\begin{aligned}
 \frac{\hat{V}_{\text{out}}}{V_{\text{in}}} &= \phi = \frac{j\omega L/R}{1 - \omega^2 LC + j\omega L/R} \\
 &= \frac{j\omega L/R (1 - \omega^2 LC - j\omega L/R)}{(1 - \omega^2 LC)^2 + (\omega L/R)^2} \\
 &= j(1 - \omega^2 LC) + \omega L/R \\
 &\equiv N
 \end{aligned}$$






Demo: Parallel-LC BPF

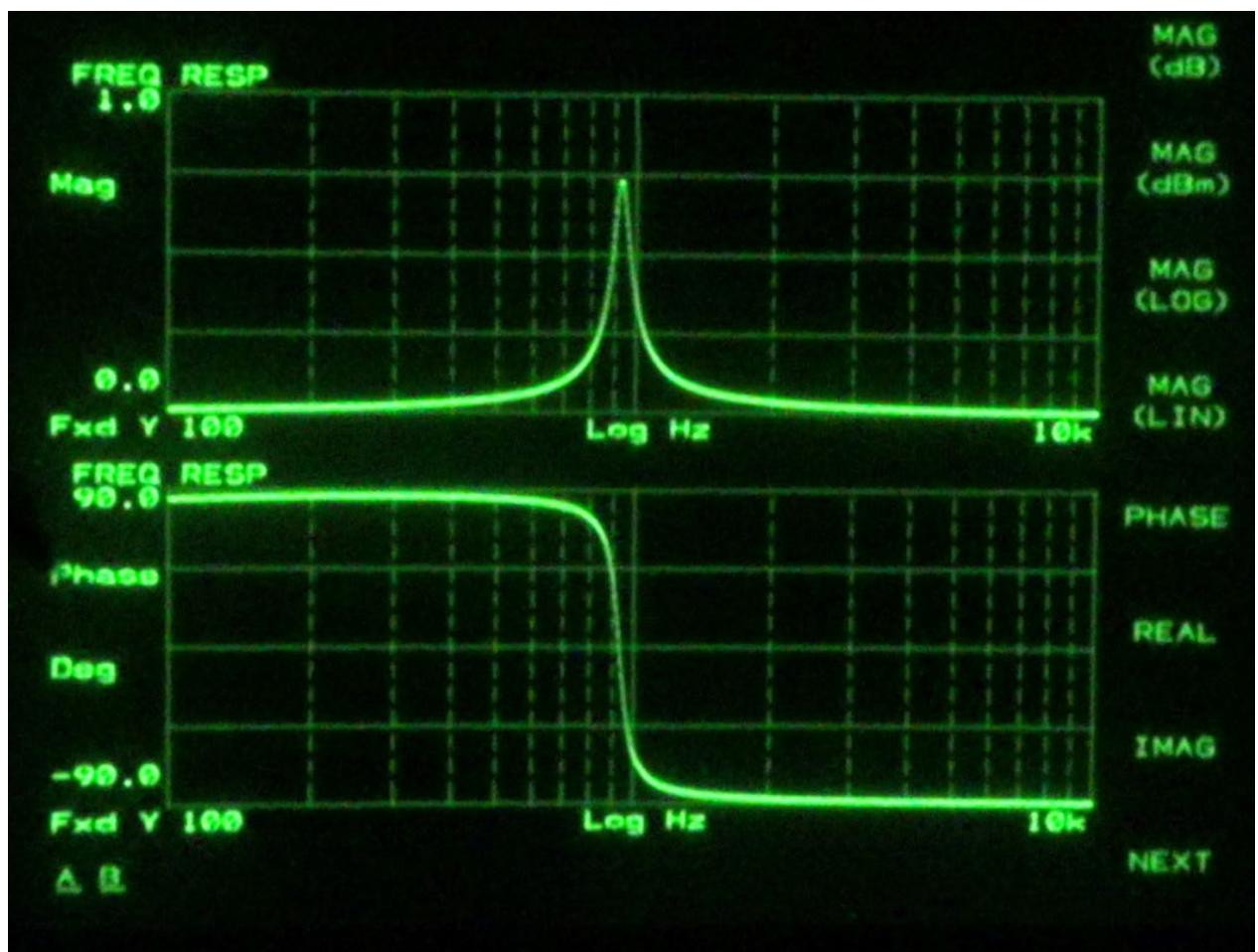
$$L = 0.1 \text{ H} ; C = 0.25 \mu\text{F} ; R = 10 \text{ k}\Omega$$
$$(2\pi\sqrt{LC})^{-1} = 1 \text{ kHz} ; R/\sqrt{L/C} = 16$$



Numerical: Parallel-LC BPF

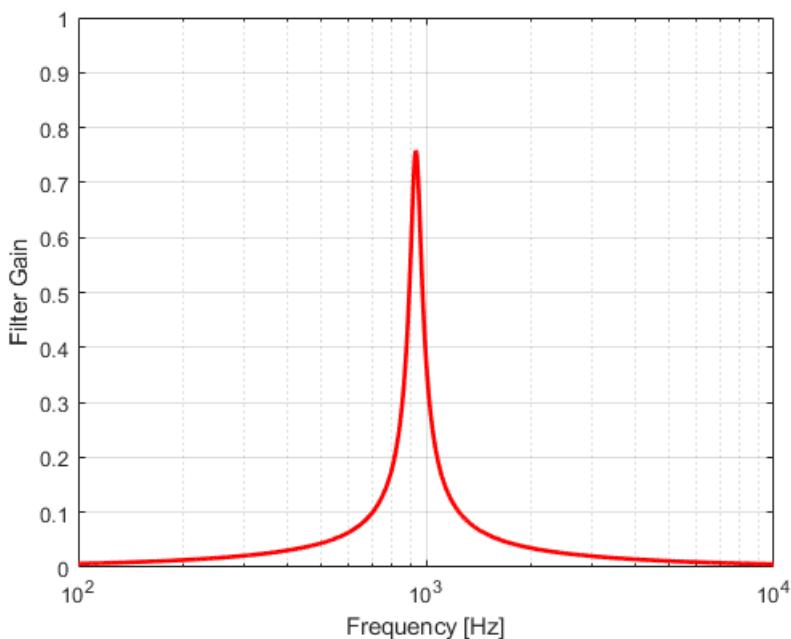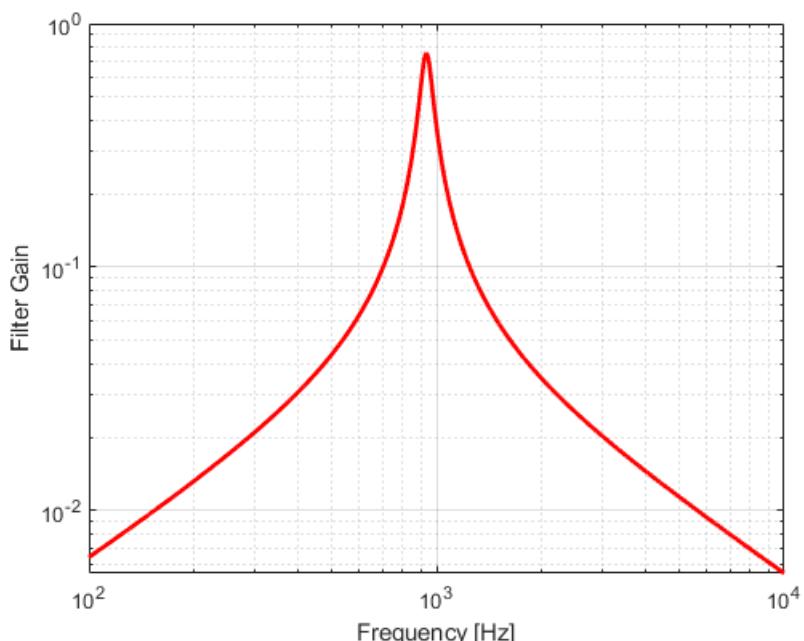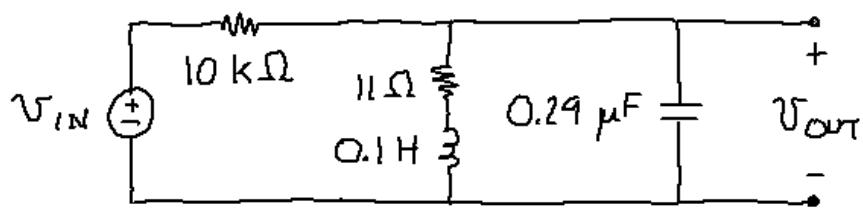

LC Comb Filter

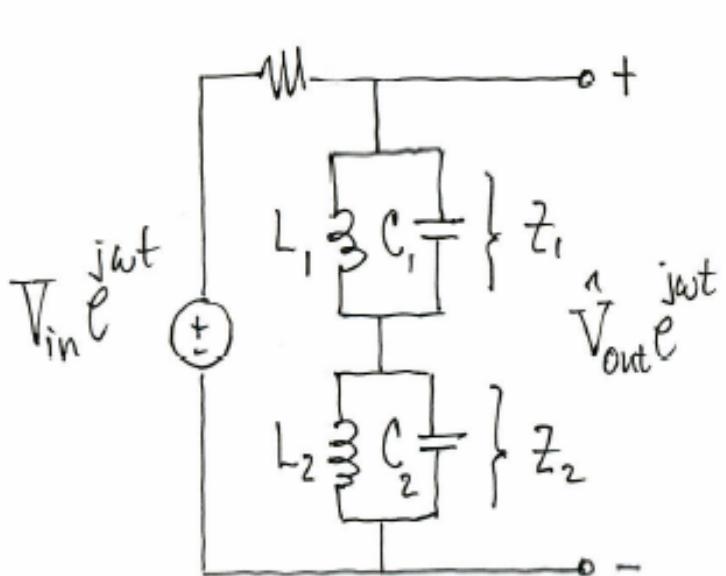


$Z_1 = \text{Open}$ at $\omega = \frac{1}{\sqrt{L_1 C_1}}$

$Z_2 = \text{Open}$ at $\omega = \frac{1}{\sqrt{L_2 C_2}}$


$Z_1 + Z_2 = \text{Short}$ at $\omega = 0, 00$
and between the
two opens

$$|\hat{V}_{out}/V_{in}|$$

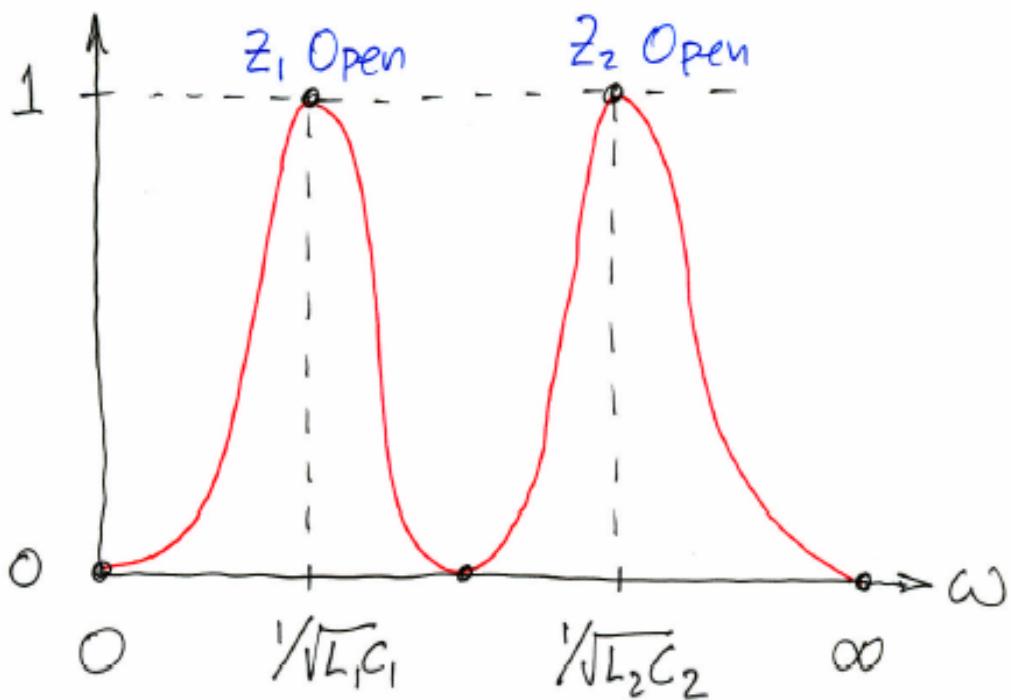


Demo: LC Comb Filter

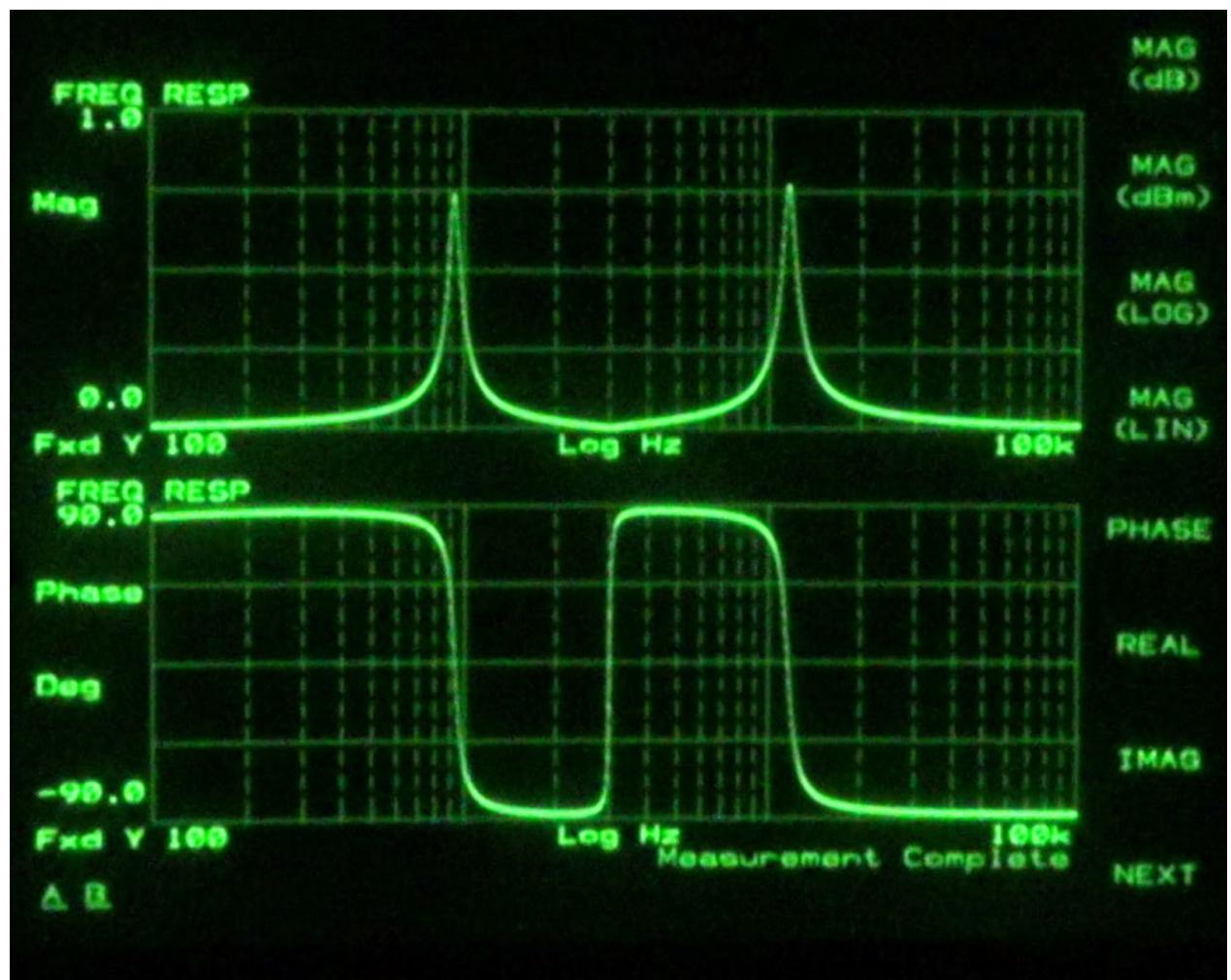$L_1 = 0.1 \text{ H}$; $C_1 = 0.25 \mu\text{F}$; $f_1 = 1 \text{ kHz}$
 $L_2 = 0.01 \text{ H}$; $C_2 = 0.022 \mu\text{F}$; $f_2 = 10 \text{ kHz}$
 $R = 10 \text{ k}\Omega$; $Q1 = Q2 = 16$




Theory: Series-LC BSF

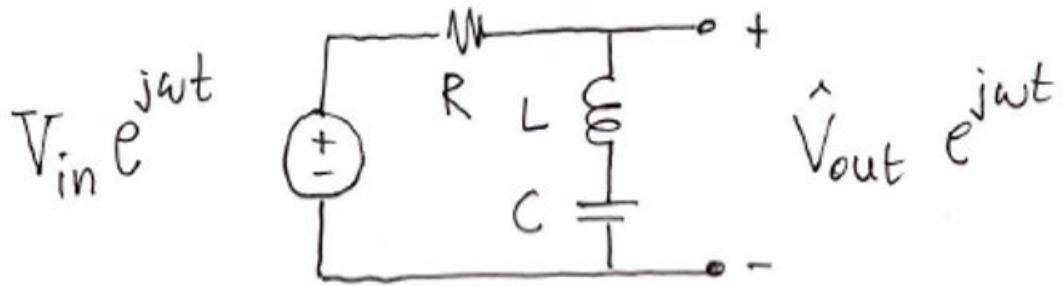

$$\frac{\hat{V}_{\text{out}}}{\hat{V}_{\text{in}}} = \frac{j\omega L + 1/j\omega C}{R + j\omega L + 1/j\omega C} = \frac{1 - \omega^2 LC}{1 - \omega^2 LC + j\omega RC}$$

$$\left| \frac{\hat{V}_{\text{out}}}{\hat{V}_{\text{in}}} \right| = \frac{1 - \omega^2 LC}{\sqrt{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

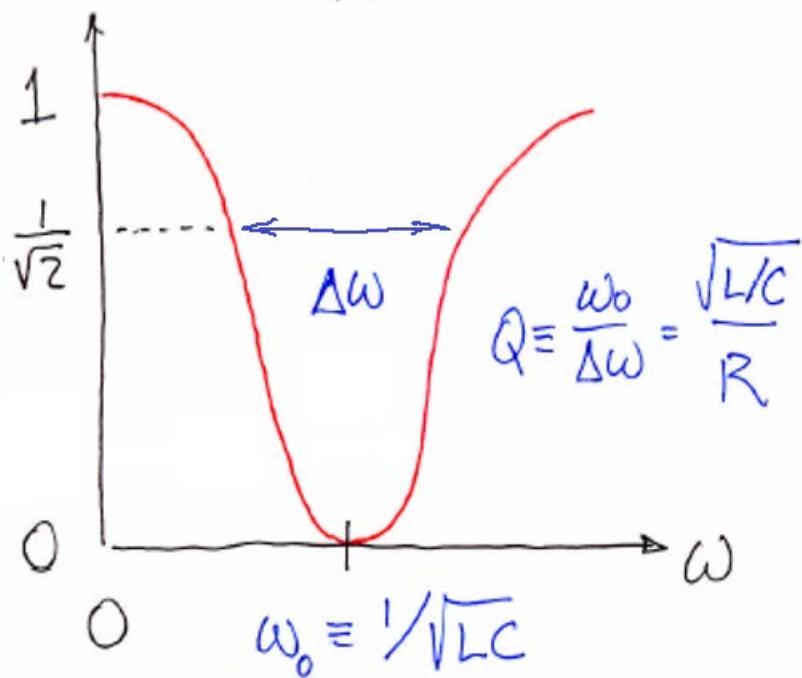

Numbers :

$$L = 0.1 \text{ H}$$

$$C = 0.25 \mu\text{F}$$

$$R = 100 \Omega$$


$$\frac{1}{2\pi\sqrt{LC}} = 1 \text{ kHz}$$

$$\sqrt{L/C} = 632 \Omega$$

$$Q = 6.3$$



Demo: Series-LC BSF
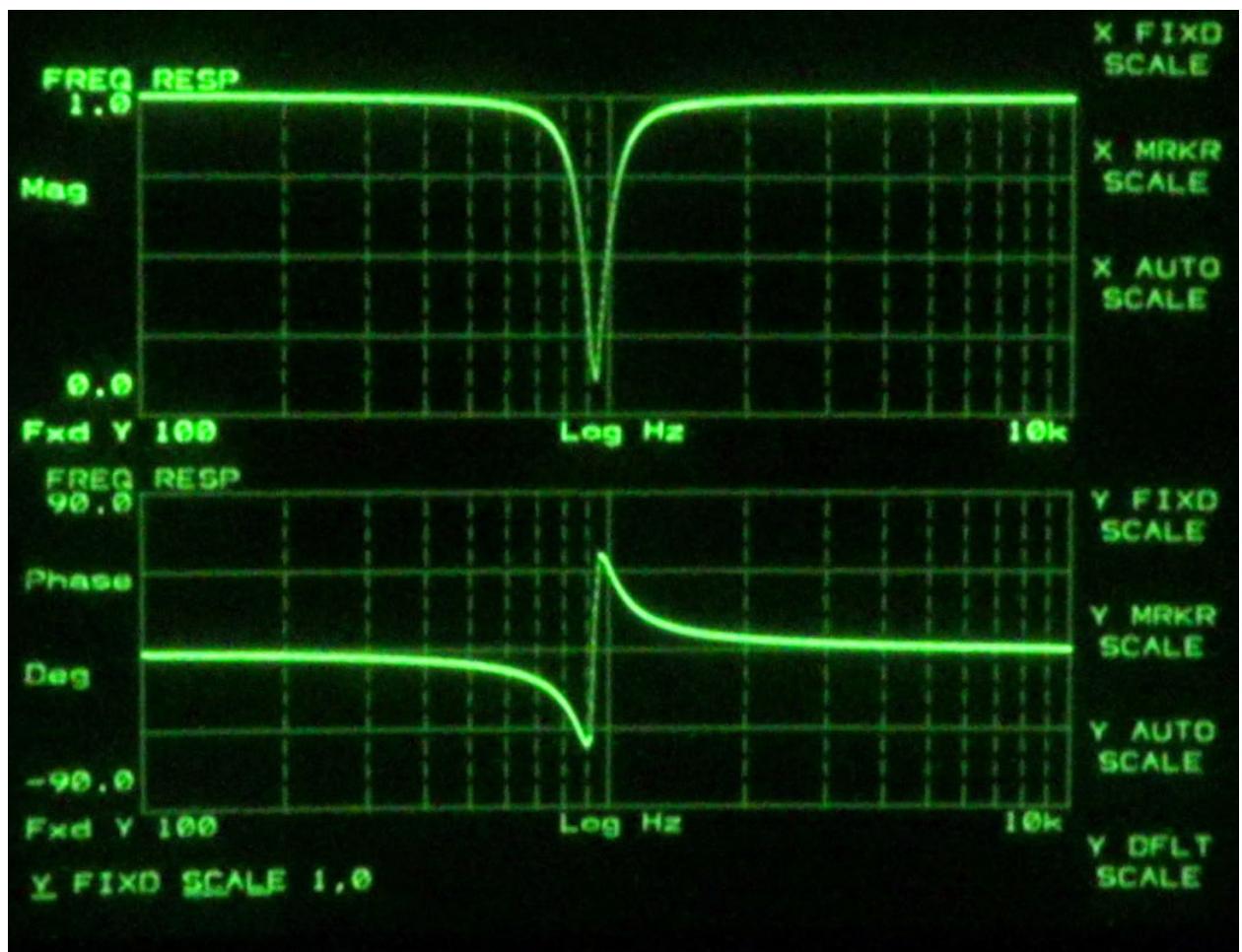
$$L = 0.1 \text{ H} ; C = 0.25 \mu\text{F} ; R = 100 \Omega$$
$$(2\pi\sqrt{LC})^{-1} = 1 \text{ kHz} ; \sqrt{L/C} / R = 6.3$$




Note that the notch does not go to zero due to the parasitic series resistance of the inductor.


Numerical: Series-LC BSF

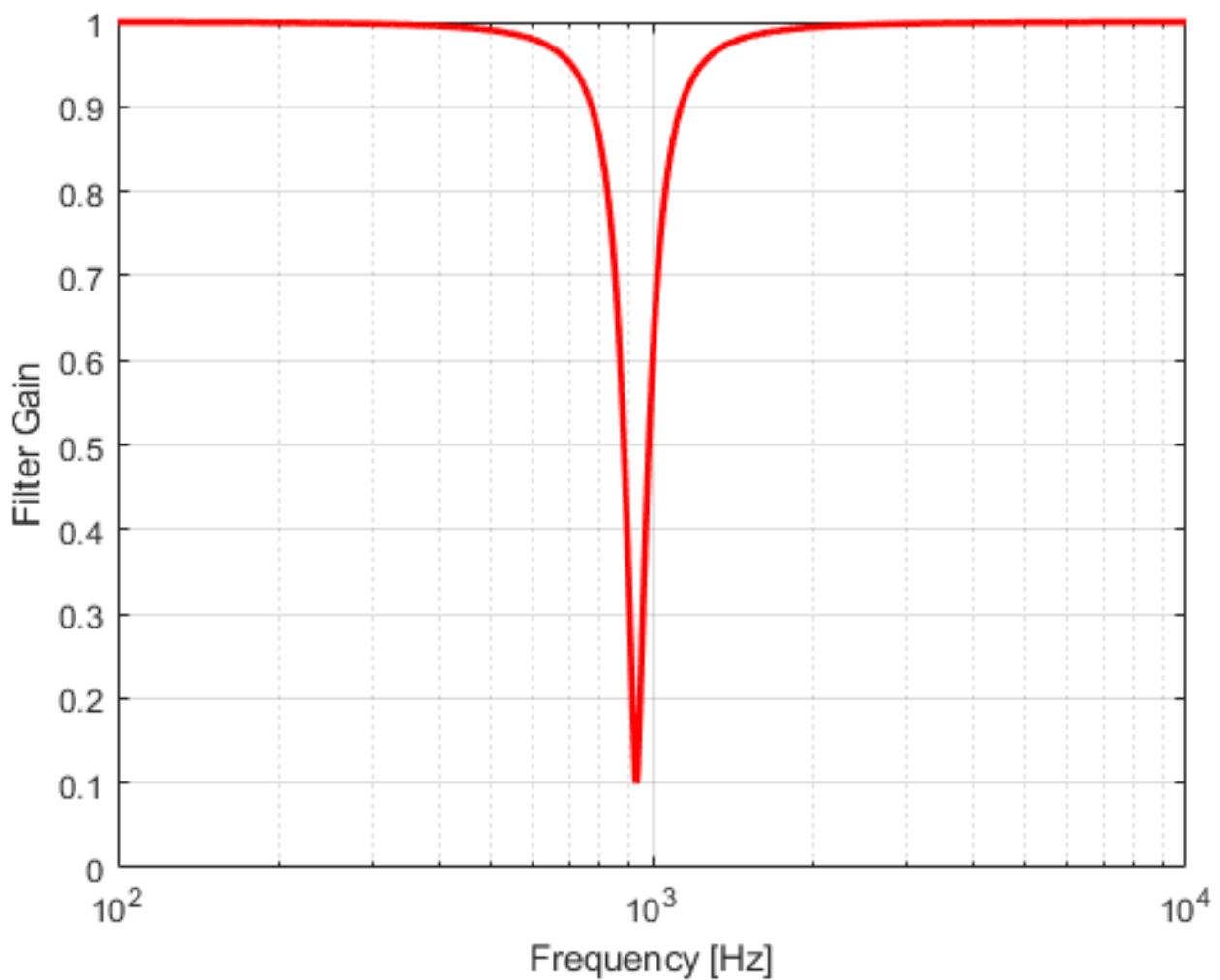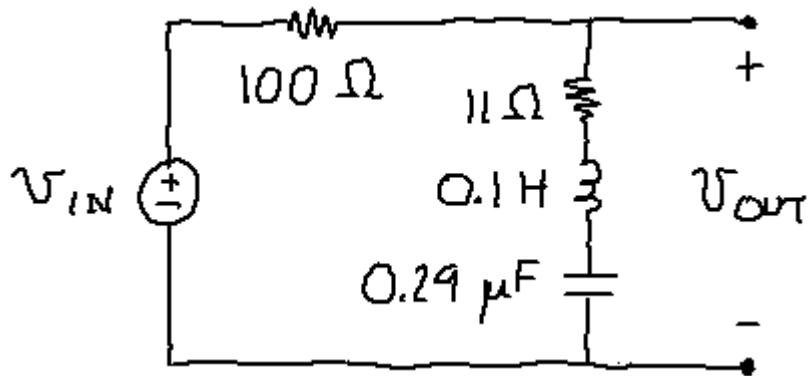

Resonators

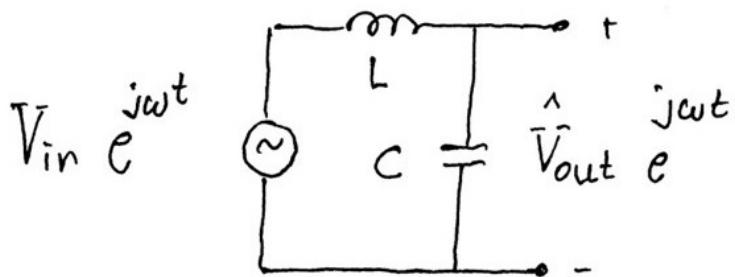
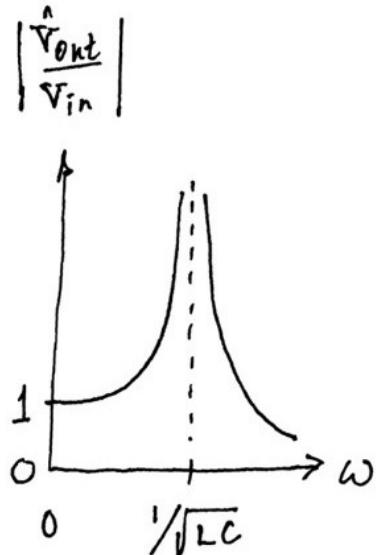
$$\frac{\hat{V}_{out}}{\hat{V}_{in}} = \frac{1/j\omega C}{j\omega L + 1/j\omega C} = \frac{1}{1 - \omega^2 LC}$$



Peak voltage limited by parasitic resistances.


Applications include:

- capacitive shunts along inductive power-grid transmission lines;
- Tesla coil (dual tuned resonator).



Demo: Tesla Coil

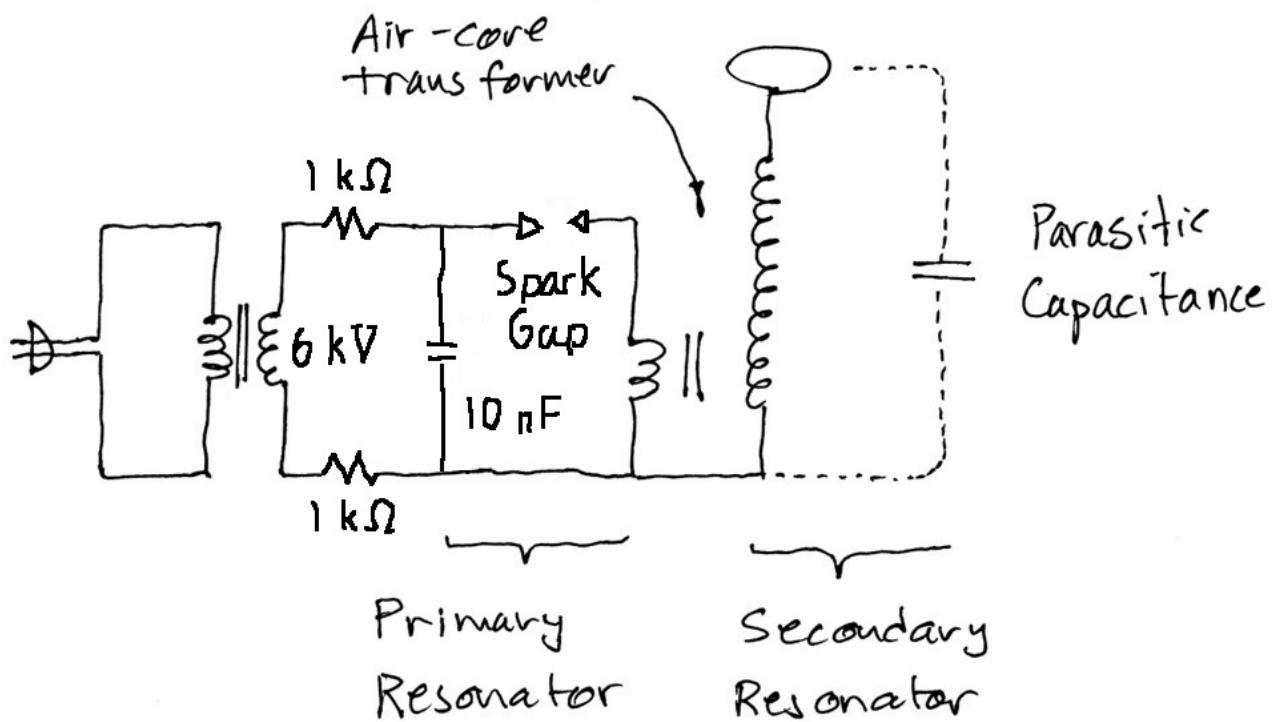The Tesla Coil employs two coupled resonators, with both resonators tuned to the same frequency.



The resistors protect the transformer. At 60 Hz, the transformer fills up the capacitor. When the capacitor voltage gets high enough, the spark gap sparks, and becomes a short allowing the LC resonator to oscillate, driving the rest of the Tesla coil.

Demo: Tesla Coil

