
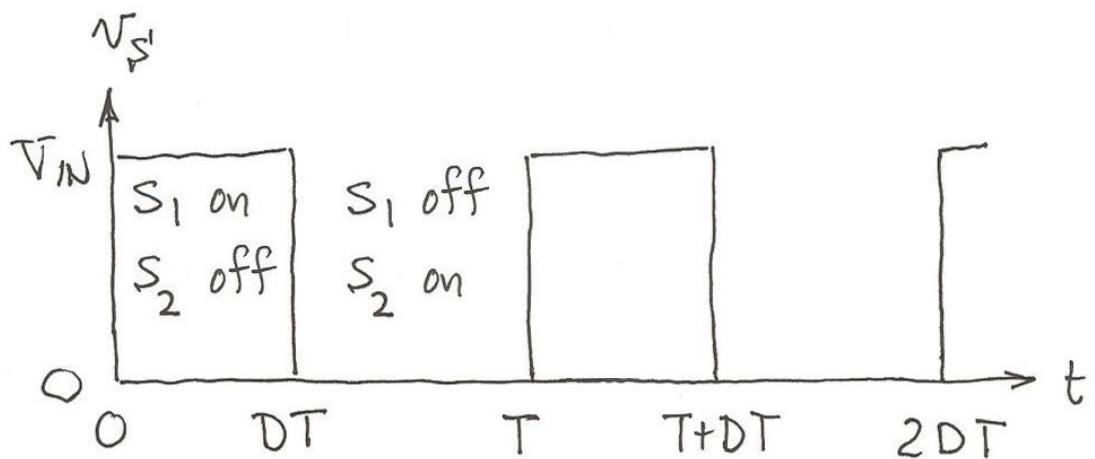


6.200 - Lecture 12A

Buck Converter


- Principles of operation
- Performance improvement
- Analysis via averaging
- Analysis via filtering
- Natural response

Buck Converter

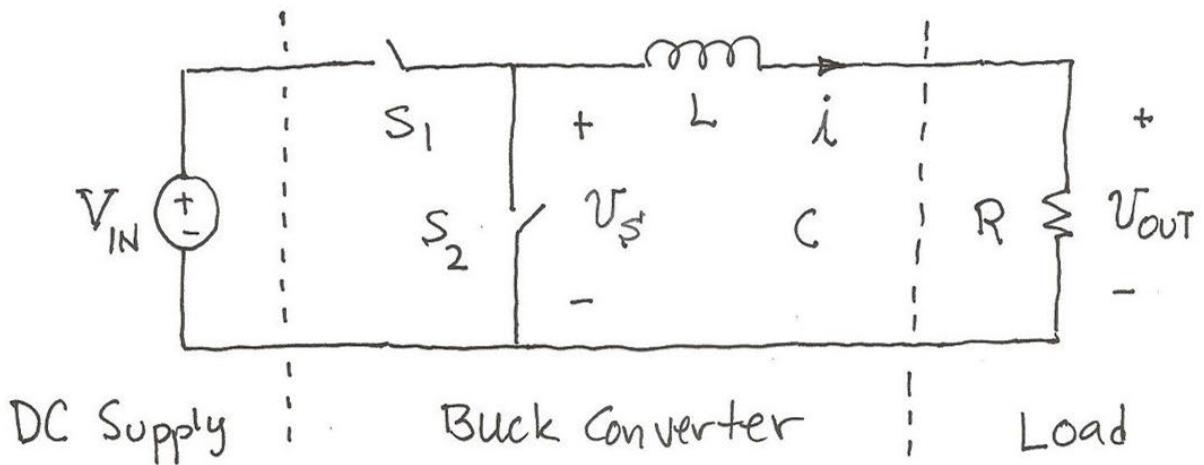

- * Digital electronics wish to operate at low voltage (V_{OUT}) to reduce losses and heat.
- * Power is cheaper to deliver at high voltages due to wiring costs at high current.
- * Buck converters bridge the high \rightarrow low voltage gap.

Improved Buck Converter

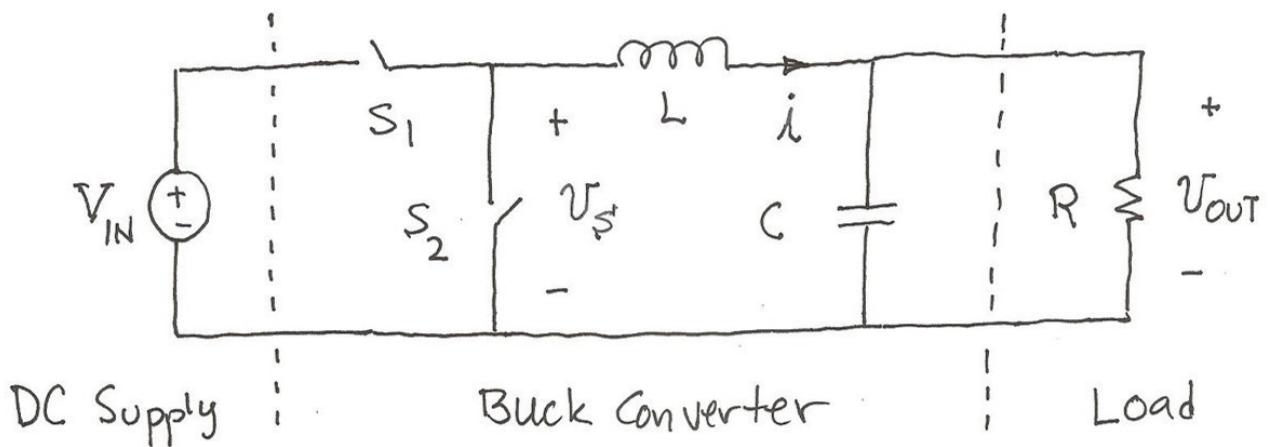

- * The original buck converter exhibited a significant ripple current through, and hence a significant ripple voltage across, the load.
- * The added capacitor offers a low-impedance path for the ripple current and hence filters out the load ripple current and voltage.
- * But, the converter natural response may now be oscillatory.

Average Analysis

- * Assume cyclic continuous ($i > 0$) operation.
- * Define an average: $\langle x(t) \rangle = \frac{1}{T} \int_0^T x(s) ds$.

$$\text{Inductor} \Rightarrow V_s(t) - V_{\text{OUT}}(t) = L \frac{di}{dt}$$

$$\langle V_s(t) \rangle - \langle V_{\text{OUT}}(t) \rangle = \frac{L}{T} (i(T) - i(0)) = 0$$

$$\langle V_{\text{OUT}}(t) \rangle = D V_{\text{IN}}$$

$$\text{Capacitor} \Rightarrow i(t) - \frac{V_{\text{OUT}}(t)}{R} = C \frac{dV_{\text{OUT}}}{dt}$$


$$\langle i(t) \rangle - \frac{\langle V_{\text{OUT}}(t) \rangle}{R} = \frac{C}{T} (V_{\text{OUT}}(T) - V_{\text{OUT}}(0)) = 0$$

$$\langle i(t) \rangle = \frac{\langle V_{\text{OUT}}(t) \rangle}{R} = \frac{D V_{\text{IN}}}{R}$$

Duty cycle D is used to control V_{OUT} .

Ripple Analysis

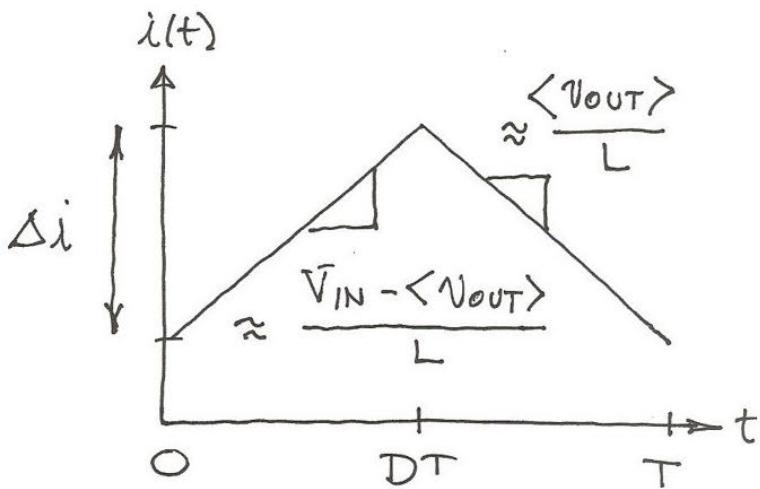
Ideal inductor \Rightarrow inductor current is approximately piecewise linear.



$$\Delta i \approx \frac{\langle V_{out} \rangle}{L} (1-D)$$

$$= \frac{D(1-D) T \bar{V}_{IN}}{L}$$

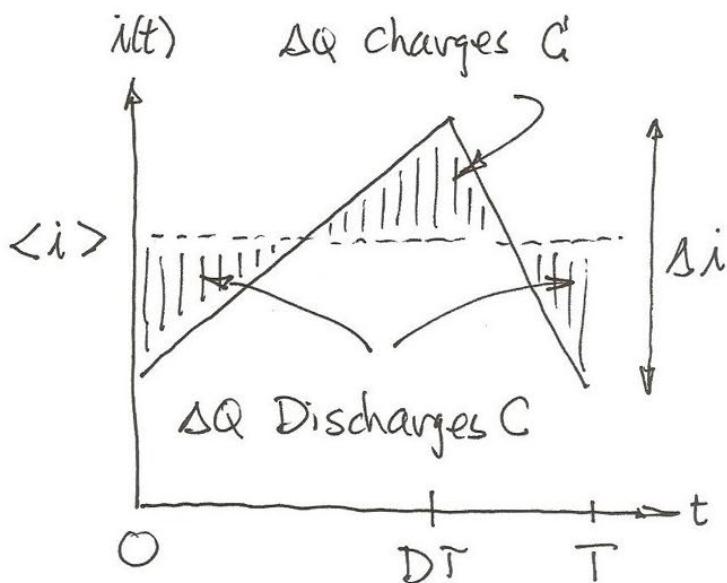High-frequency inductor current passes largely through capacitor because $\frac{1}{\omega C} \ll R$.




$$\Delta Q \approx \frac{1}{2} \frac{\Delta i}{2} \frac{T}{2}$$

$$= \frac{D(1-D) T^2 \bar{V}_{IN}}{8L}$$

$$\Delta V_{out} = \frac{\Delta Q}{C}$$

$$= \frac{D(1-D) T^2 \bar{V}_{IN}}{8LC}$$

Natural Response

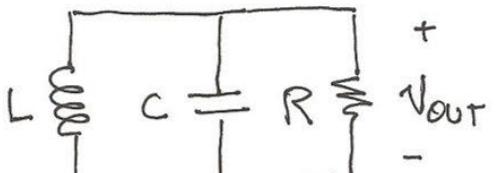

$$V_{\text{out}}$$

$$C \frac{dV_{\text{out}}}{dt} + \frac{V_{\text{out}}}{R} + \frac{1}{L} \int_{-\infty}^t V_{\text{out}} dt = 0$$

$$\underbrace{\frac{d^2 V_{\text{out}}}{dt^2} + \frac{1}{RC} \frac{dV_{\text{out}}}{dt} + \frac{1}{LC} V_{\text{out}}}_{z\alpha} = 0$$

$$\underbrace{\omega_0^2}$$


$$e^{st} \Rightarrow s = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2} \approx -\alpha + j\omega_0$$

Lightly
Damped

Natural response will appear for :

- * change in input voltage V_{IN} ;
- * change in duty cycle D;
- * change in load resistance R.

Demo :

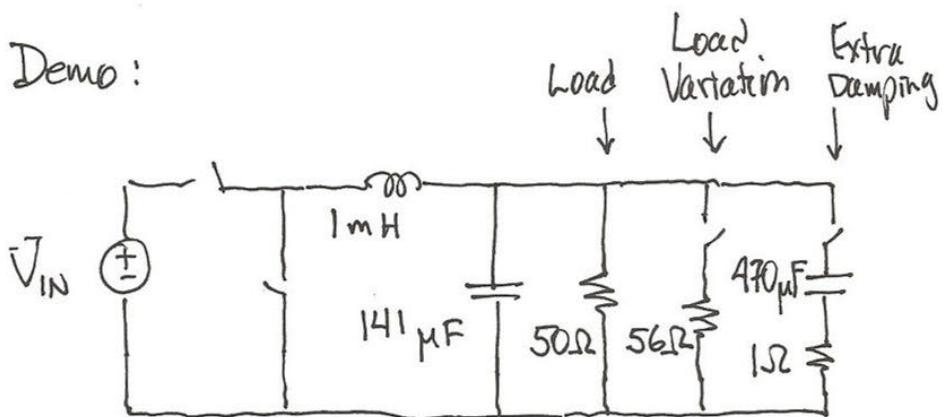

Demo - Ripple Analysis

$$L = 1 \text{ mH}$$

$$D = 0.5$$


$$V_{IN} = 12 \text{ V}$$

$$C = 141 \mu\text{F}$$

$$T = 25 \mu\text{s}$$

$$\Delta i = \frac{D(1-D) T V_{IN}}{L} = 75 \text{ mA}$$
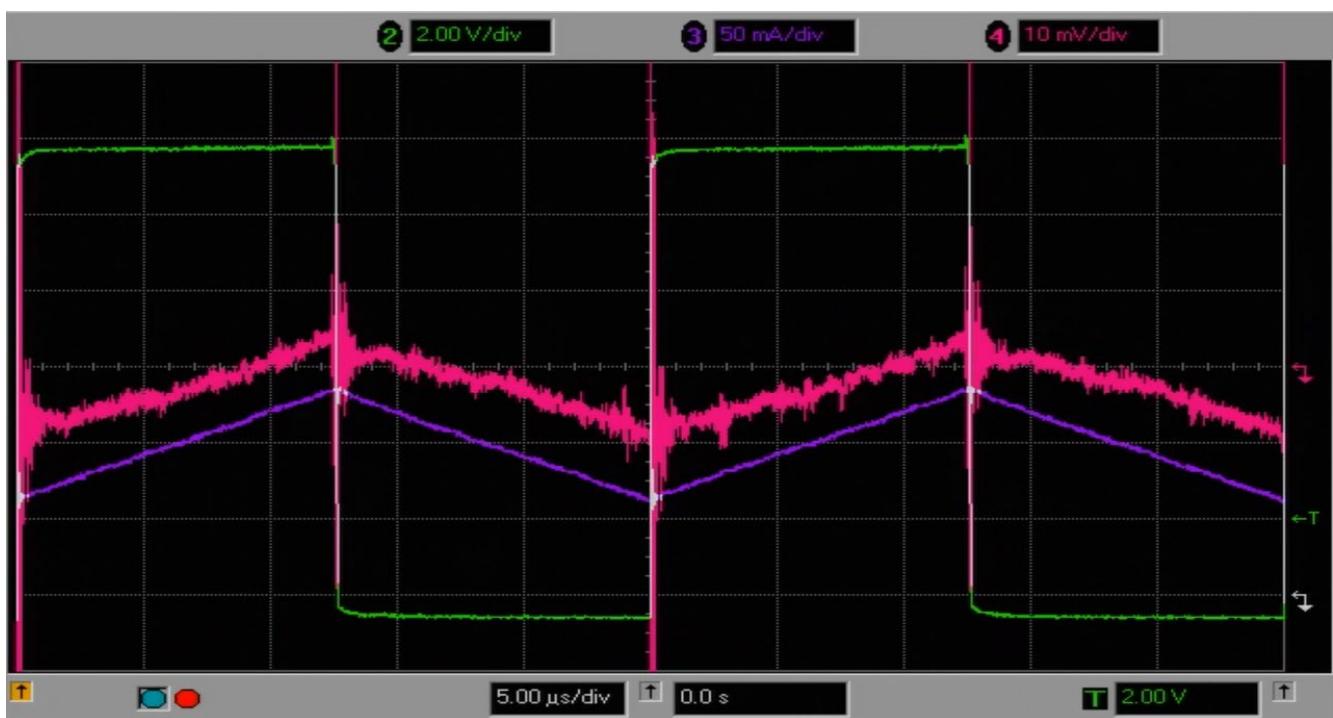
$$\Delta V_{OUT} = \frac{\Delta i T}{C} = 13 \text{ mV}$$



Demo - Natural Response

$$L = 1 \text{ mH}$$

$$D = 0.5$$

$$V_{IN} = 12 \text{ V}$$


$$C = 141 \mu\text{F}$$

$$T = 25 \mu\text{s}$$

$$R = 50 \Omega$$

$$\text{Period} = 2\pi\sqrt{LC} = 2.4 \text{ ms} \leftrightarrow 424 \text{ Hz}$$

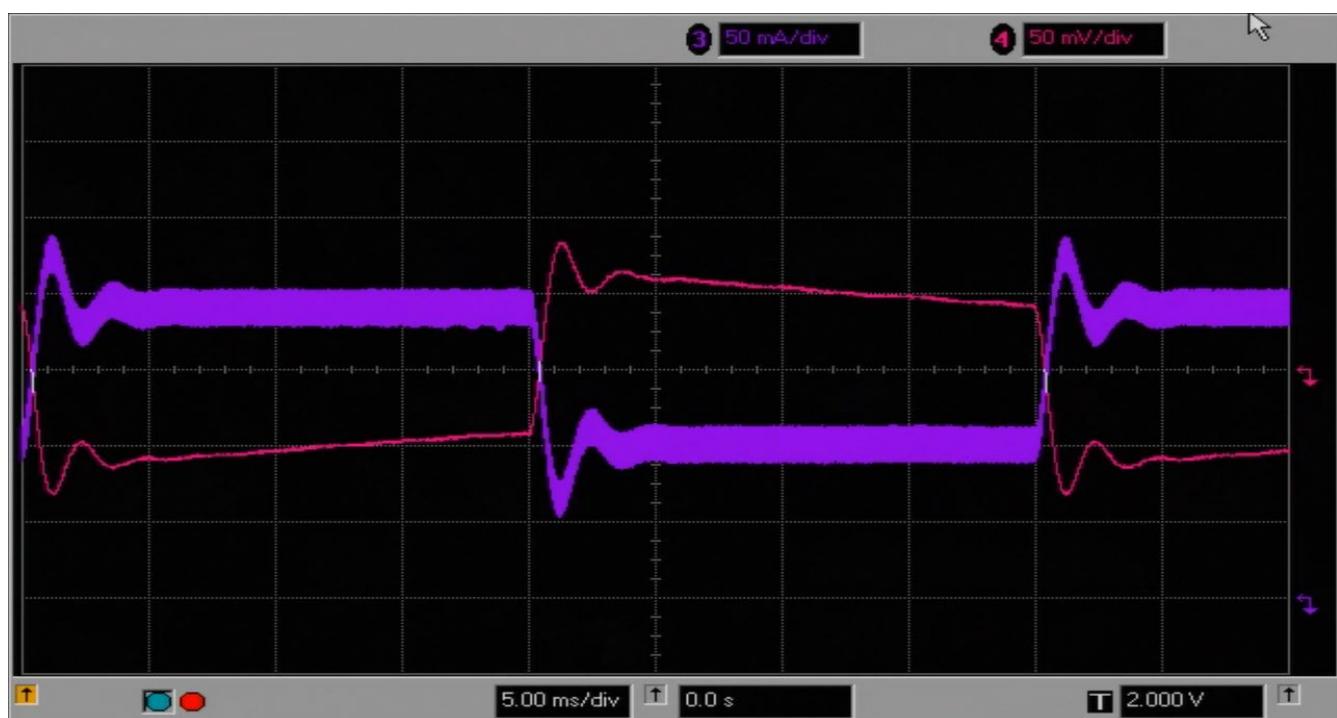
$$Q = \frac{R}{\sqrt{L/C}} = 19 \text{ Without Inductor Loss}$$



Q

$$Q = 2\pi \frac{\text{Stored Energy}}{\text{Energy Lost Per Cycle}}$$
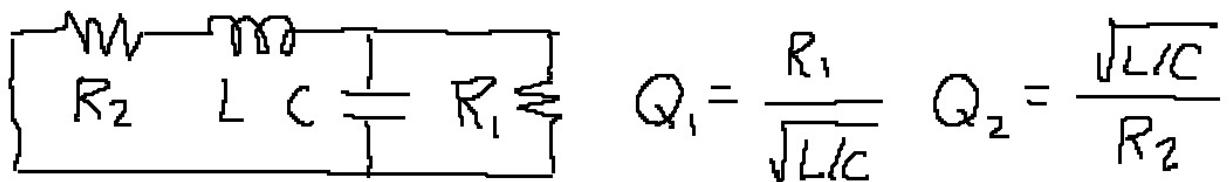
$$\frac{1}{Q} = \frac{1}{2\pi} \frac{1}{\text{Stored Energy}} \sum_i \text{Cycle Loss}_i$$




$$L = 1 \text{ mH} \quad C = 141 \mu\text{H} \quad R_1 = 50 \Omega \quad R_2 = 0.5 \Omega$$

$$Q_1 = 19 \quad Q_2 = 5.3 \quad Q = 4.2$$

Damping

Demo:

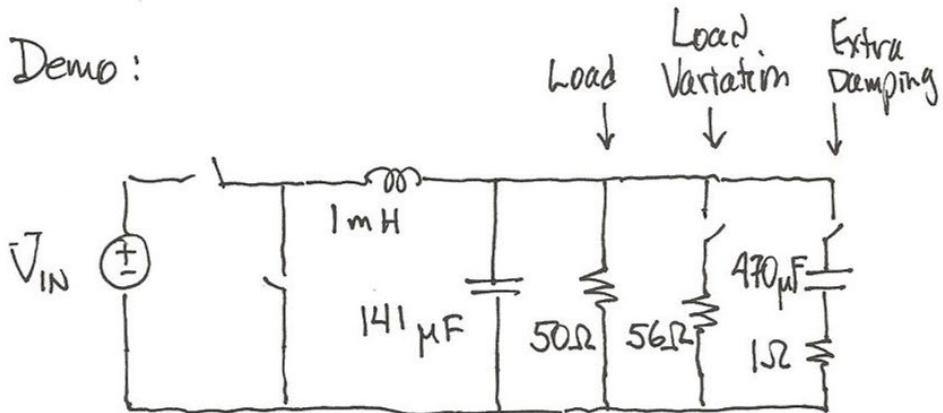

Objective is to reduce the oscillatory load - step response.


- * Does not affect average (DC) behavior because of series capacitor.
- * Does not carry much ripple current (get hot) because $1\Omega \gg 1/(\omega_5 \cdot 141\text{ }\mu\text{F})$.
- * Provides significant damping because 1Ω and $1/(\omega_N \cdot 470\text{ }\mu\text{F}) \ll 50\Omega$.

Damping



Damping network $\Rightarrow R = 1 \Omega ; C = 470 \mu F$

* $1/\omega_N C = 0.8 \Omega$ at $\omega_N = 424 \text{ Hz} \Rightarrow$ small but not strictly negligible. I ignore anyway.

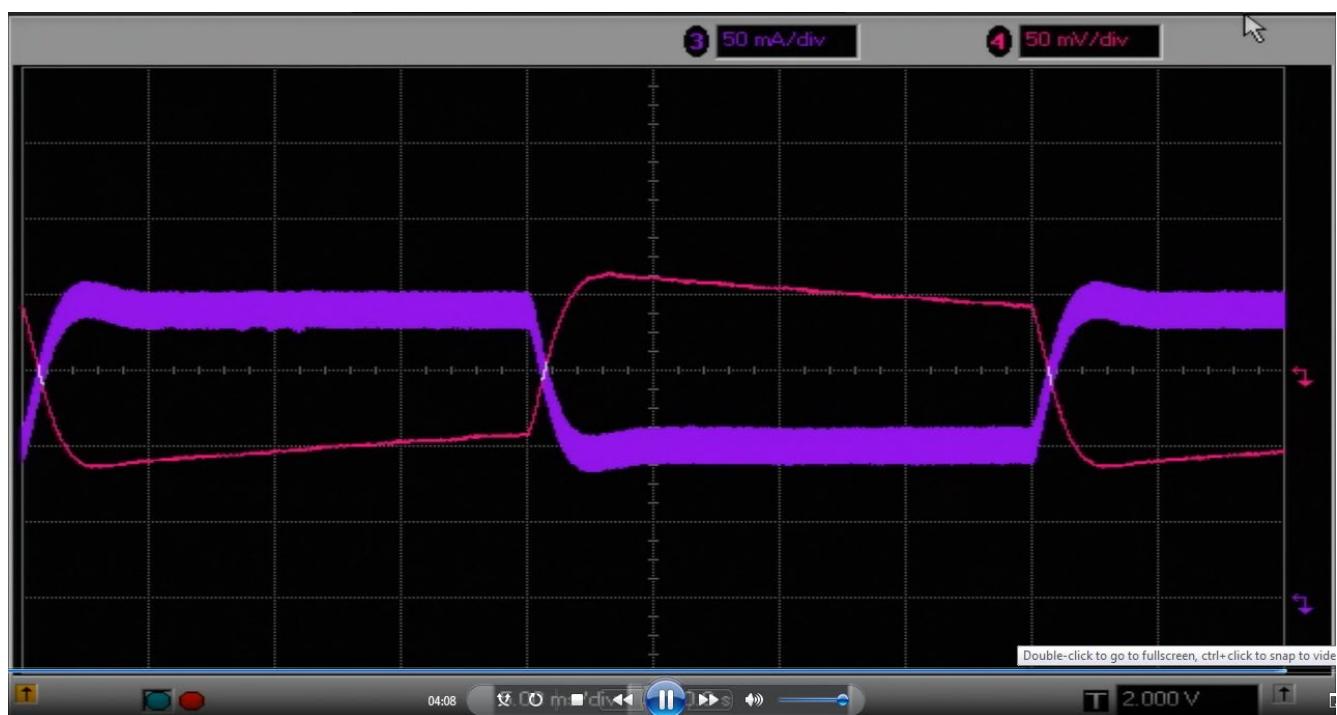* $Q = \frac{R}{Z_0} = 0.4 \Rightarrow$ Overdamped



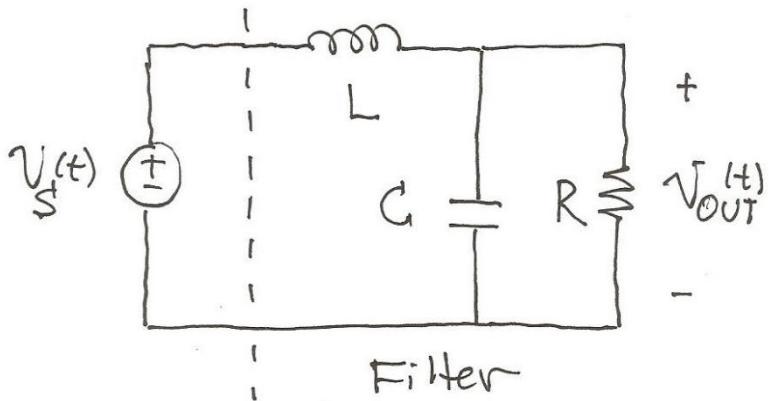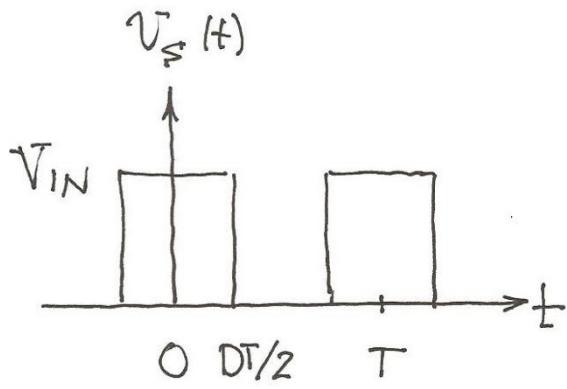Buck Converter \Rightarrow Low-Pass Filter



Fourier decomposition of $V_S(t)$:


$$V_S(t) = D \bar{V}_{IN} + \sum_{n=1}^{\infty} \frac{2 \bar{V}_{IN} \sin(n\pi D)}{n\pi} \cos(n\omega_s t)$$

$$\omega_s T \equiv 2\pi$$

Filter each Fourier component separately and then recombine results to get complete response.


Can do this for all signals: $V_{OUT}(t)$, $i(t)$, ...

Filter Analysis (Driven Response)

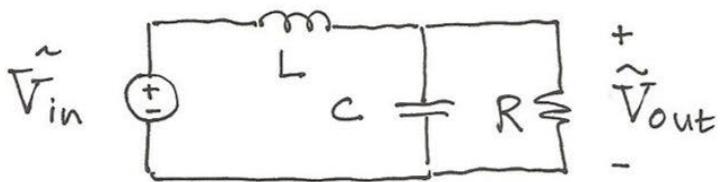

$$\tilde{V}_{\text{out}} = \frac{(R \parallel \frac{1}{j\omega C}) \tilde{V}_{\text{in}}}{j\omega L + (R \parallel \frac{1}{j\omega C})} = \frac{\tilde{V}_{\text{in}}}{1 - \omega^2 LC + \frac{j\omega L}{R}} \equiv H(j\omega) \tilde{V}_{\text{in}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{(1 - \omega^2 LC)^2 + (\frac{\omega L}{R})^2}} \quad \Rightarrow H(j\omega) = \tan^{-1} \left(\frac{-\omega L / R}{1 - \omega^2 LC} \right)$$

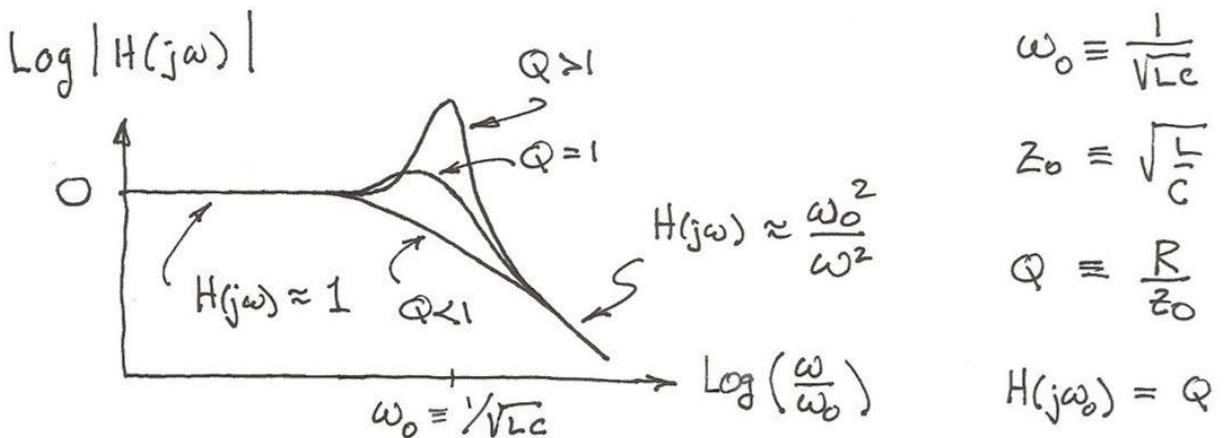

$$\text{Demo} \Rightarrow L = 1 \text{ mH} ; C = 141 \mu\text{F}$$

$$\Rightarrow \omega_0 = 2.6 \frac{\text{k rad}}{\text{s}} (424 \text{ Hz})$$

Filtering Interpretation

- At $\omega = 0$, $H(j\omega) = 1 \Rightarrow \tilde{V}_{\text{out}} = D\bar{V}_{\text{IN}} = \langle v_s(t) \rangle$.
Same result as before!
- $f_s = 40 \text{ kHz} \Rightarrow \omega_s = 80\pi \frac{\text{krad}}{\text{s}} \gg \omega_0 = 2.6 \frac{\text{krad}}{\text{s}}$.
 \Rightarrow All switching harmonics are greatly attenuated
 \Rightarrow Small ripple!

- Ripple fundamental $\Rightarrow \frac{2\bar{V}_{\text{IN}} \sin(\pi D)}{\pi} \frac{\omega_0^2}{\omega_s^2}$ amplitude.

$$\text{For } D = \frac{1}{2}, \text{ amplitude} = \frac{2\bar{V}_{\text{IN}}}{\pi} \frac{T^2}{4\pi^2 LC}$$

$$= \frac{T^2 \bar{V}_{\text{IN}}}{2\pi^3 LC} \approx \frac{T^2 \bar{V}_{\text{IN}}}{62 LC}$$

Compare with $\frac{1}{2} \frac{T^2 \bar{V}_{\text{IN}}}{32 LC} = \frac{T^2 \bar{V}_{\text{IN}}}{64 LC}$ from
ripple analysis!