

# 6.200 - Lecture 12B

## Active “LC” Filters

- Successful LC Filters
- Active Filter Motivation
- Sallen-Key Topologies
- Examples

# Successful LC Filters

## Power System Inductor & Capacitor Banks




[eaton.com](http://eaton.com)




<https://electrical-engineering-portal.com>

## Audio Crossover Networks

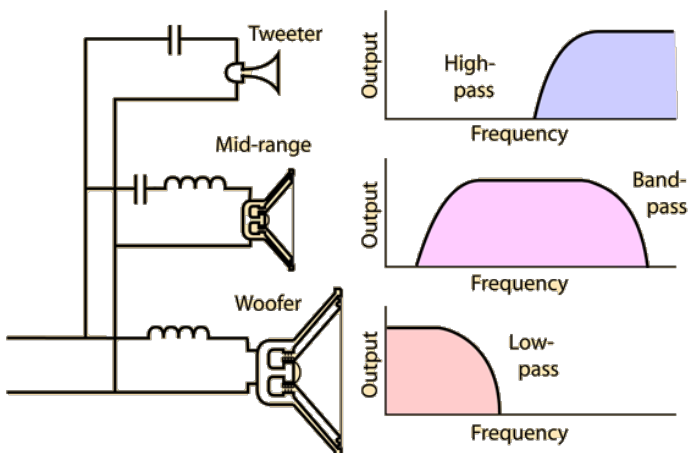


<http://hyperphysics.phy-astr.gsu.edu>

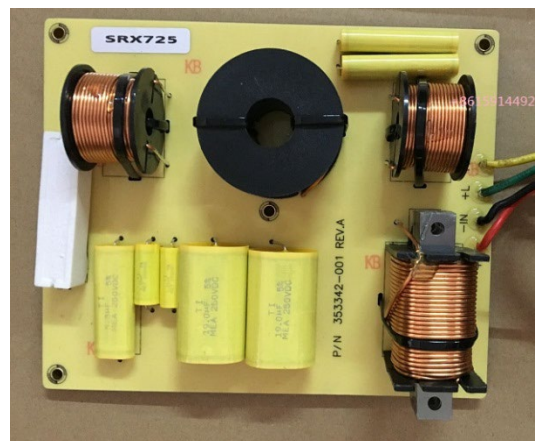

[guangshou shengda audio](http://guangshou-shengda-audio.com)


# Motivating Example

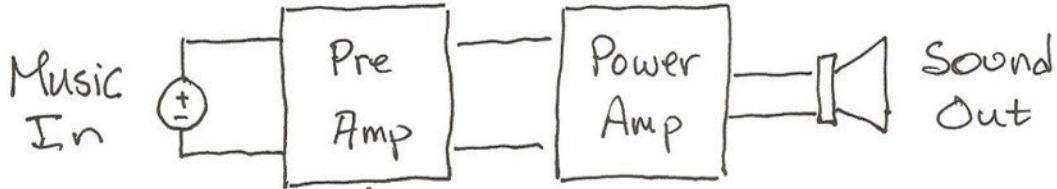

60 Hz  
Noise




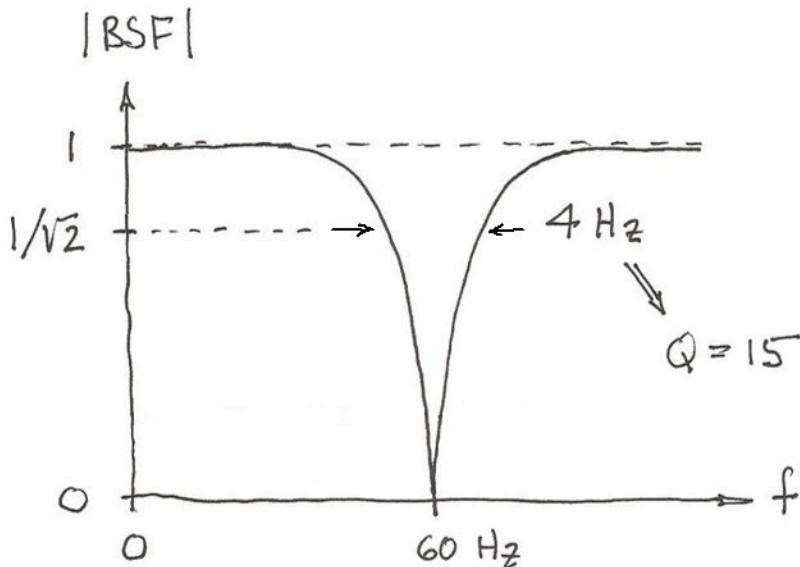(Best is to eliminate the noise itself.  
Next best is to employ a bandstop filter.)



# Passive BSF

Design

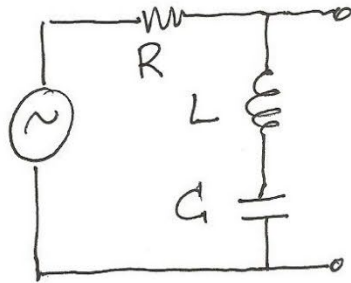

$$\omega_0 = 1/\sqrt{LC}$$

$$Z_0 = \sqrt{L/C}$$

$$Q = Z_0/R$$

$$L = 1 \text{ H}$$

$$C = 7 \mu\text{F}$$


$$R = 25 \Omega$$

$$\omega_0 = 377 \frac{\text{rad}}{\text{s}} = 60 \text{ Hz}$$

$$Z_0 = 377 \Omega$$

$$Q = 15$$

Reality

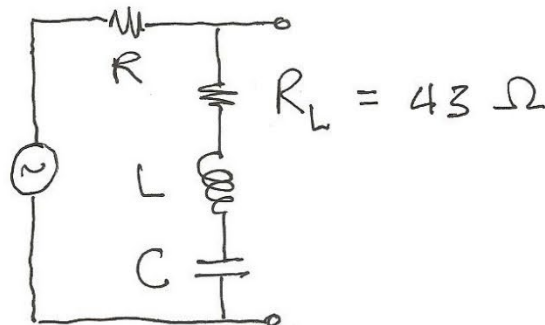


$$\text{Minimum Gain} = \frac{43}{43+25} = 0.63$$

$$Q = Z_0/(R+R_L) = 5.5$$
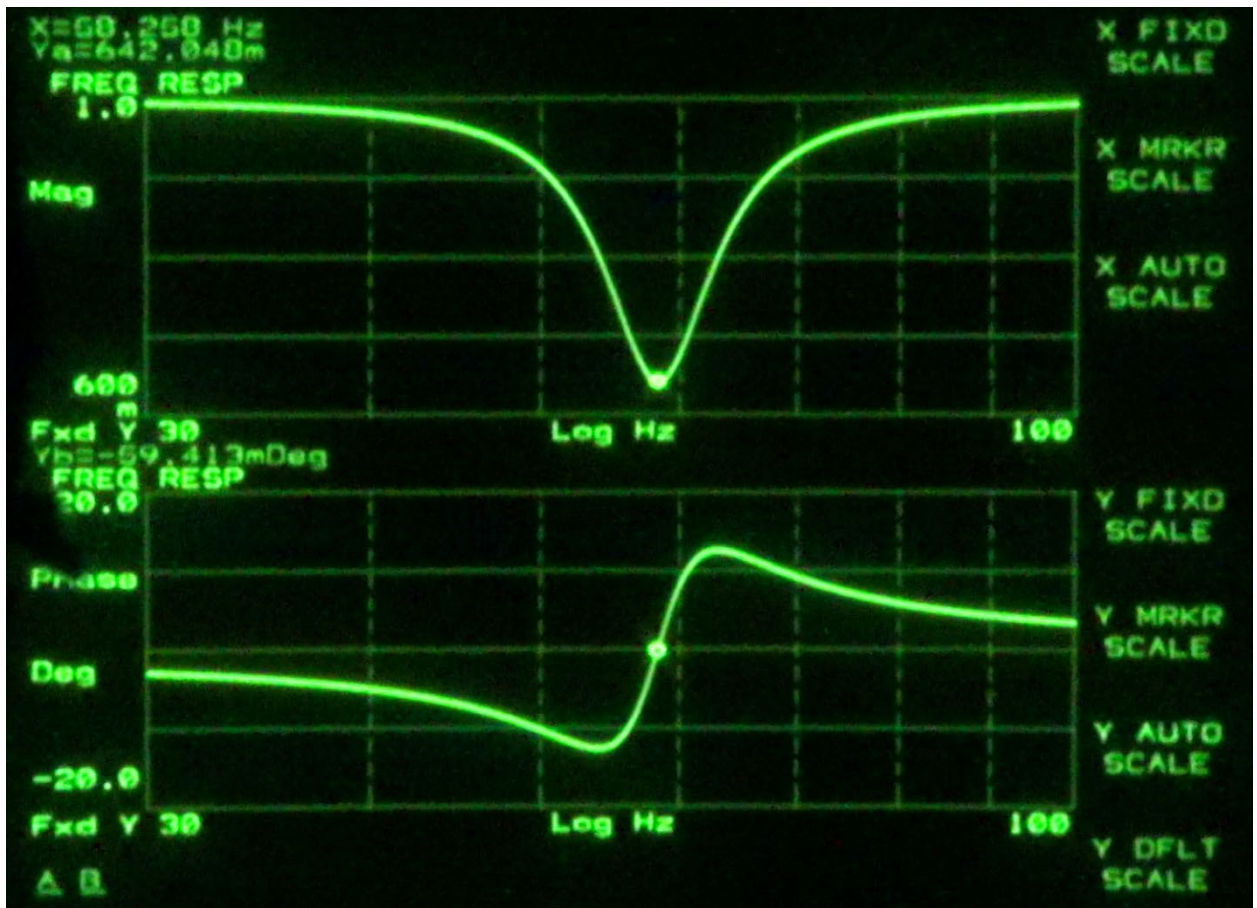
# Demo



$L = 1 \text{ H}$  ;  $C = 7 \mu\text{F}$  ;  $R = 25 \Omega$  (Hopefully)  
 $(2\pi\sqrt{LC})^{-1} = 60 \text{ Hz}$  ;  $\sqrt{L/C} = 377 \Omega$   
 $Q = 15$  (Hopefully)



The DC resistance of the inductor is  $43 \Omega$ ,  
so the stop band will drop only to 0.63!

# Magnetics Scaling

Inductor

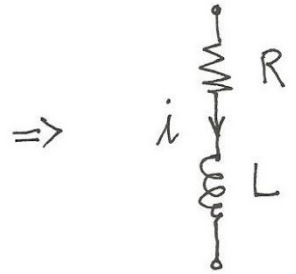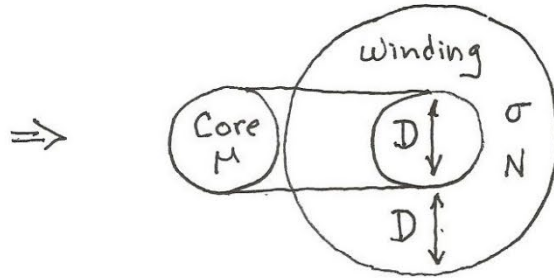

$$L = \frac{N^2 \mu \text{Area}}{\text{Length}} = \frac{N^2 \mu \pi D^2 / 4}{\pi D} = \frac{N^2 \mu D}{4}$$


$$R = \frac{N^2 \text{Length}}{\sigma \text{Area}} = \frac{N^2 \pi D}{\sigma \pi D^2 / 4} = \frac{4N^2}{\sigma \pi D}$$

Sinusoidal Steady State  $\Rightarrow i = I \cos(\omega t)$

$$Q = 2\pi \frac{\text{Peak Stored Energy}}{\text{Energy Lost Per Cycle}} = 2\pi \frac{LI^2/2}{\frac{1}{2} I^2 R \frac{2\pi}{\omega}} = \frac{\omega \mu \sigma D^2}{64}$$

$Q \sim D^2 \Rightarrow \begin{cases} \text{Bigger is better} \\ \text{Smaller is worse} \end{cases}$

# Single - Amplifier Topology

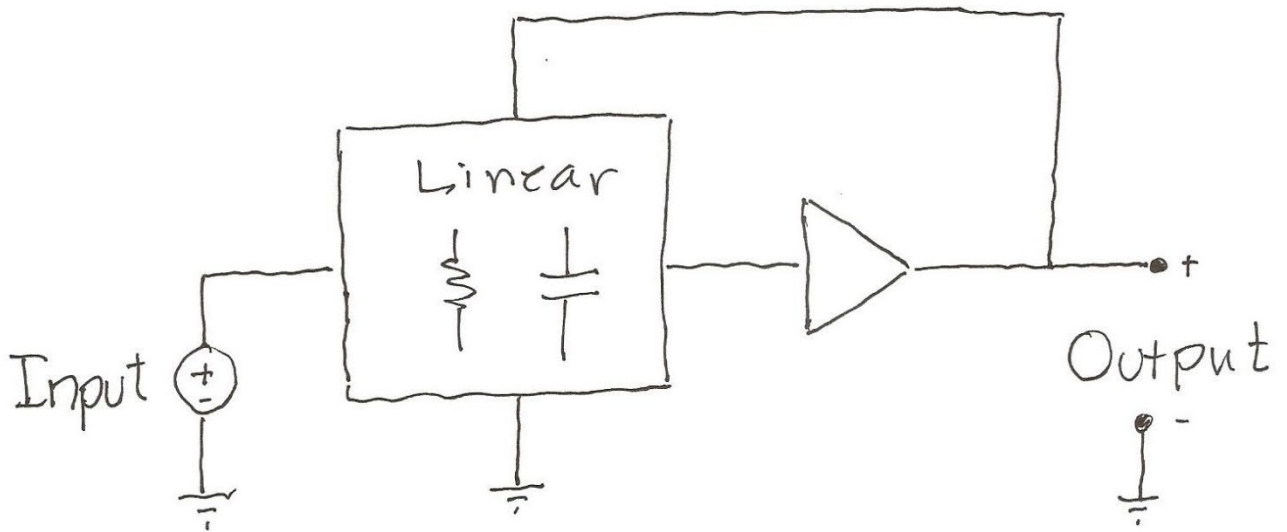

Amplifier :

- Linear
- Finite  $\pm$  Gain gain
- Infinite bandwidth
- Infinite input impedance
- Zero output impedance

# Performance Issues

- Gain versus frequency
- Phase versus frequency
- Sensitivity to component values
- Sensitivity to amplifier behavior
- Simplicity and cost



# Unity - Gain Second - Order Filters

$$s \equiv j\omega \leftrightarrow d/dt$$

$$\text{LPF} \quad \frac{V_{out}}{V_{in}} = \frac{\omega_0^2}{s^2 + s\omega_0/Q + \omega_0^2}$$

$$\text{HPF} \quad \frac{V_{out}}{V_{in}} = \frac{s^2}{s^2 + s\omega_0/Q + \omega_0^2}$$


$$\text{BPF} \quad \frac{V_{out}}{V_{in}} = \frac{s\omega_0/Q}{s^2 + s\omega_0/Q + \omega_0^2}$$

$$\text{BSF} \quad \frac{V_{out}}{V_{in}} = \frac{s^2 + \omega_0^2}{s^2 + s\omega_0/Q + \omega_0^2}$$

$$\ddot{V}_{out} + \frac{\omega_0}{Q} \dot{V}_{out} + \omega_0^2 V_{out} = \underbrace{\ddot{V}_{in} + \frac{\omega_0}{Q} \dot{V}_{in} + \omega_0^2 V_{in}}_{\text{Selected by filtering type}}$$
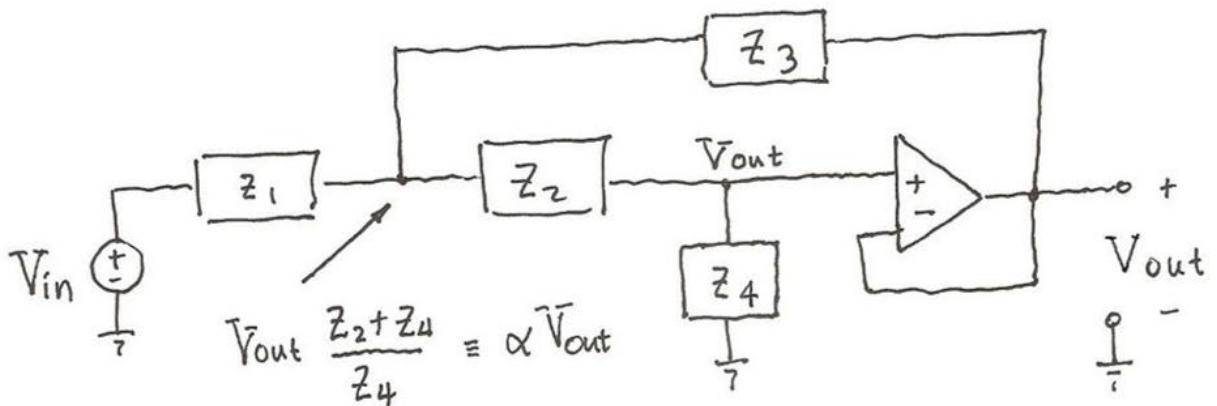
# Simple Sallen - Key Filter

R. P. Sallen and E. L. Key, "A Practical Method of Designing RC Active Filters", IRE Circuit Theory, 2:1, 74-85, March 1955



$$\text{KCL} \Rightarrow \frac{\alpha \bar{V}_{out} - \bar{V}_{in}}{z_1} + \frac{\bar{V}_{out}}{z_4} + \frac{\alpha \bar{V}_{out} - \bar{V}_{out}}{z_3} = 0$$

$$\bar{V}_{in} \left[ \frac{1}{z_1} \right] = \bar{V}_{out} \left[ \frac{\alpha}{z_1} + \frac{1}{z_4} + \frac{z_2}{z_3 z_4} \right]$$

$$\bar{V}_{in} = \bar{V}_{out} \left[ \frac{z_2 + z_4}{z_4} + \frac{z_1}{z_4} + \frac{z_1 z_2}{z_3 z_4} \right]$$

$$\bar{V}_{out} = \frac{z_3 z_4}{z_1 z_2 + z_1 z_3 + z_2 z_3 + z_3 z_4} \bar{V}_{in}$$


$$= \frac{Y_1 Y_2}{Y_1 Y_2 + Y_1 Y_4 + Y_2 Y_4 + Y_3 Y_4} \bar{V}_{in}$$

## Example: LPF Design

Resistor:  $Z = R$  ;  $Y = 1/R$

Capacitor:  $Z = 1/sC$  ;  $Y = sC$


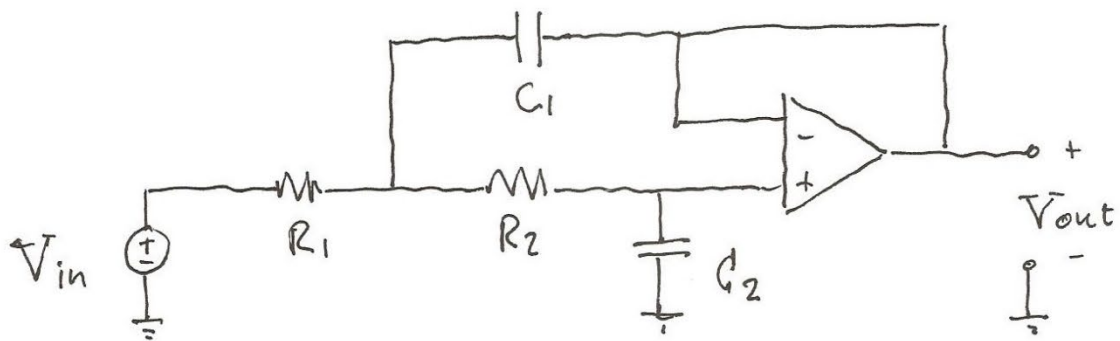
Constant LPF transfer function numerator  
 $\Rightarrow Y_1 = 1/R_1$  and  $Y_2 = 1/R_2$ . Second-order system  
 $\Rightarrow Y_3 = sC_1$  and  $Y_4 = sC_2$ .




$$V_{out} = \frac{1}{R_1 R_2 C_1 C_2} \frac{V_{in}}{s^2 + s \left( \frac{1}{R_1 C_1} + \frac{1}{R_2 C_1} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

$$\omega_0^2 = \frac{1}{R_1 R_2 C_1 C_2} \quad Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{(R_1 + R_2) C_2}$$

# BSF Design

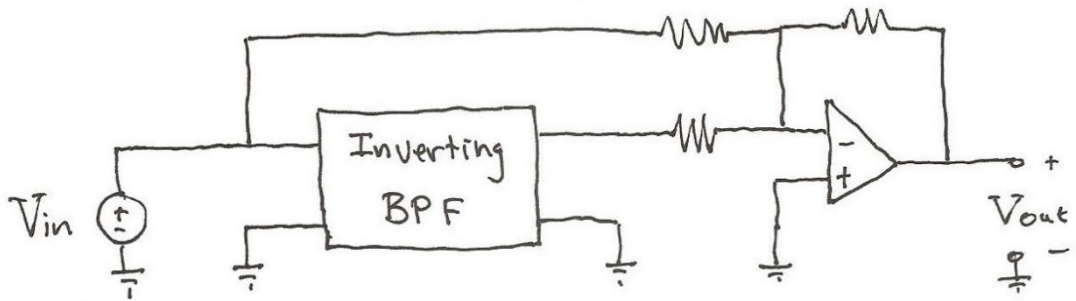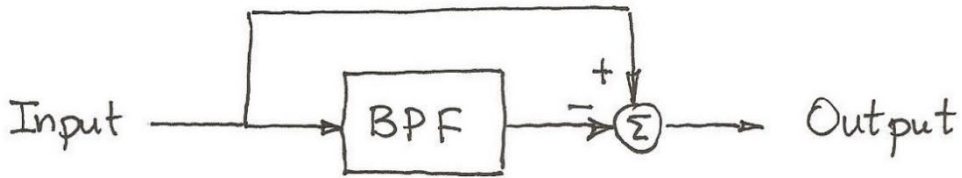

Inverting  
BPF

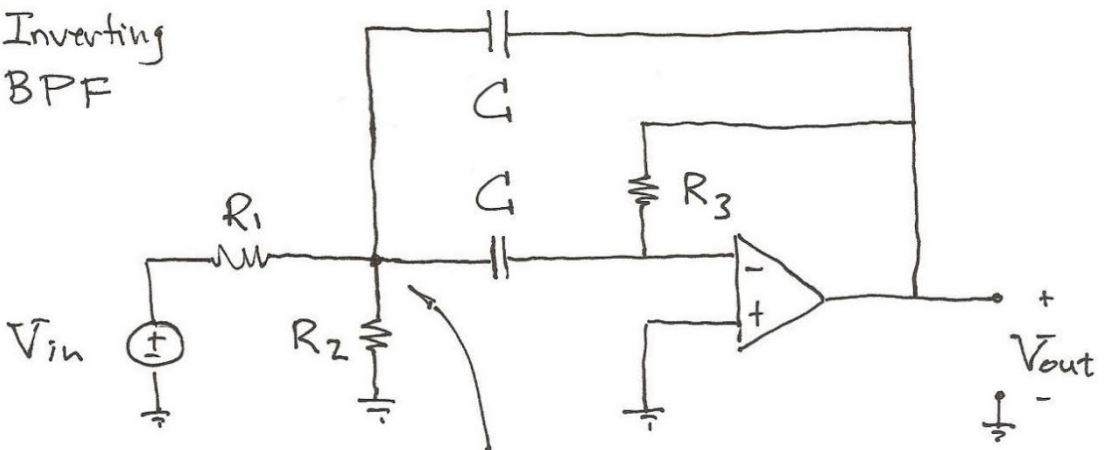

$$-V_{out}/sRC$$

# Analysis

$$\text{KCL} \Rightarrow \frac{\bar{V}_{in} + \frac{\bar{V}_{out}}{sR_3C}}{R_1} + \frac{\frac{\bar{V}_{out}}{sR_3C}}{R_2} + \frac{\bar{V}_{out}}{sR_3C} sG + \left[ \bar{V}_{out} + \frac{\bar{V}_{out}}{sR_3C} \right] sC = 0$$

$$\bar{V}_{in} \left[ \frac{s}{R_1 C} \right] + \bar{V}_{out} \left[ s^2 + \frac{s}{R_3 C} + \frac{s}{R_3 C} + \frac{1}{R_1 R_3 C^2} + \frac{1}{R_2 R_3 C^2} \right] = 0$$

$$\bar{V}_{out} \left[ s^2 + \underbrace{\frac{2}{R_3 C}}_{\omega_0/Q} s + \underbrace{\frac{R_1 + R_2}{R_1 R_2 R_3 C}}_{\omega_0^2} \right] = -\bar{V}_{in} \left[ \underbrace{\frac{1}{R_1 C}}_{G\omega_0/Q} s \right]$$

$$\omega_0^2 = \frac{R_1 + R_2}{R_1 R_2 R_3 C^2}$$

$$R_1 = \frac{Q}{G\omega_0 C}$$

$$Q = \frac{1}{2} \sqrt{\frac{(R_1 + R_2) R_3}{R_1 R_2}}$$

$$R_2 = \frac{Q}{[2Q^2 - Q]\omega_0 C}$$

$$G = \frac{R_3}{2R_1}$$

$$R_3 = \frac{2Q}{\omega_0 C}$$

# Demo Design

$$\omega_0 = 2\pi \times 60 \text{ Hz}$$

$$R1 = 20 \text{ k}\Omega$$


$$Q = 15$$

$$R2 = 90 \Omega$$

$$G = 2$$

$$R3 = 80 \text{ k}\Omega$$

$$C = 1 \mu\text{F}$$

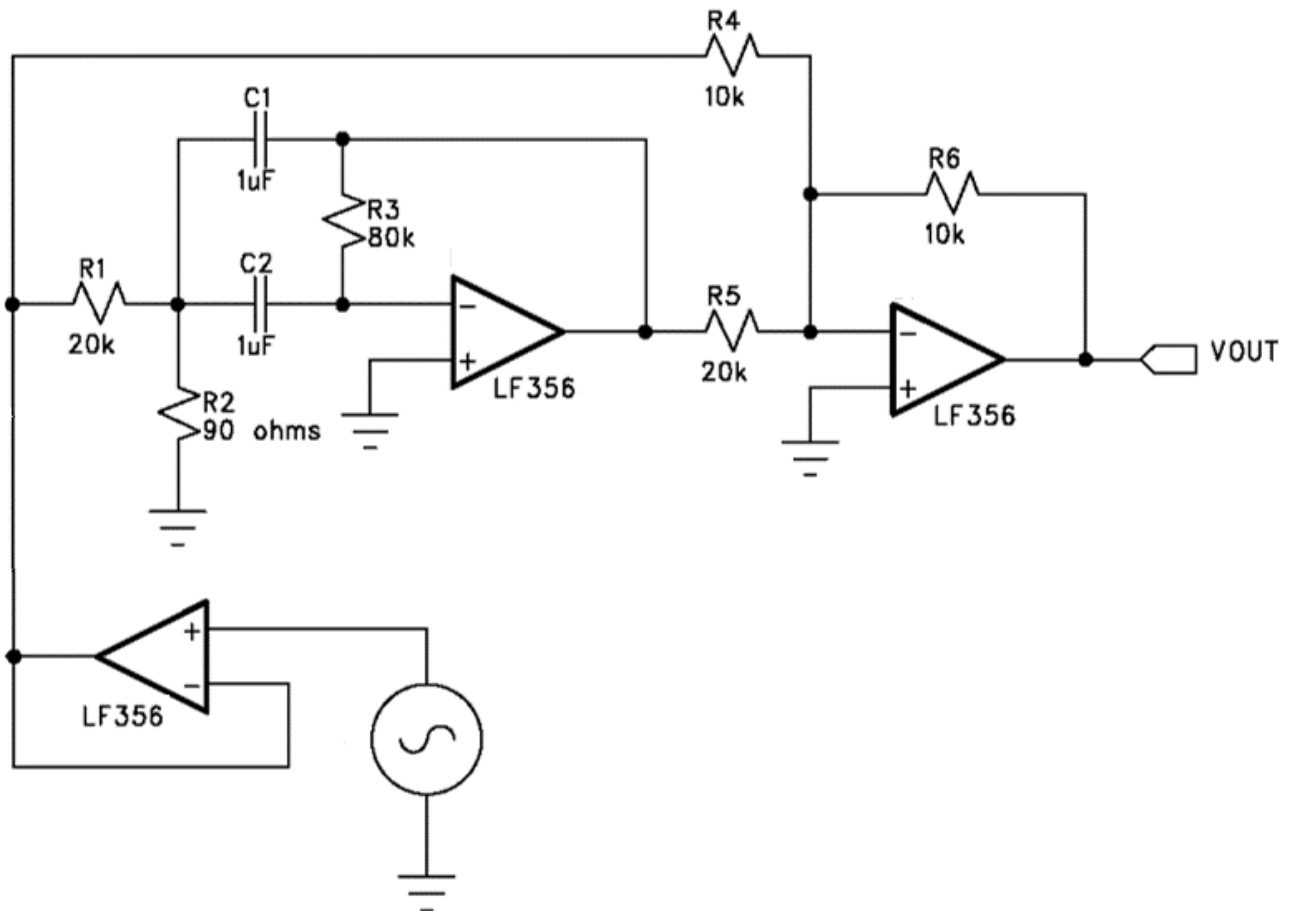

# Demo

