

# 6.002 - Lecture 05



## Circuit Analysis Simplifications

- Linearity Review
- Superposition Review
- Thevenin & Norton Equivalence
- Five-Lecture Summary




# Homogeneity & Superposition

Homogeneity and superposition are properties of linear systems.

Homogeneity:

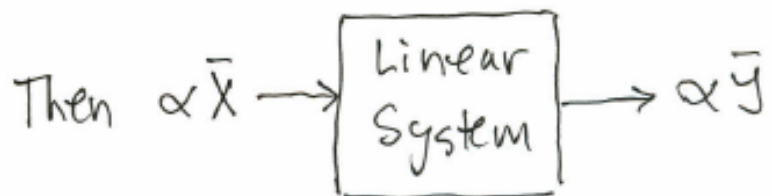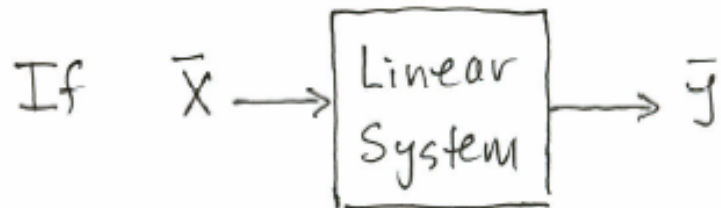


Superposition:

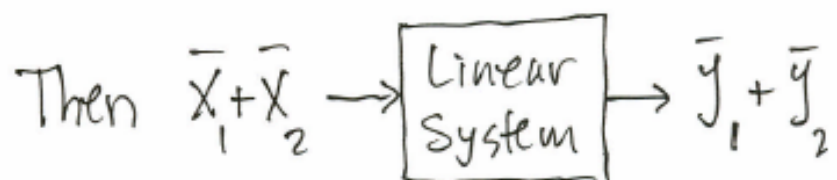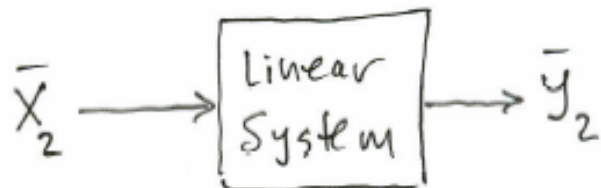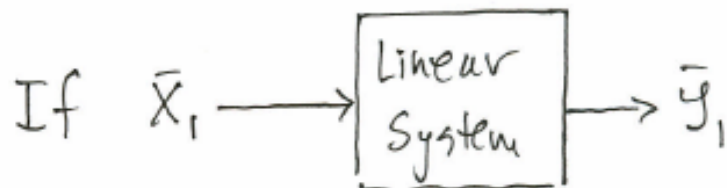
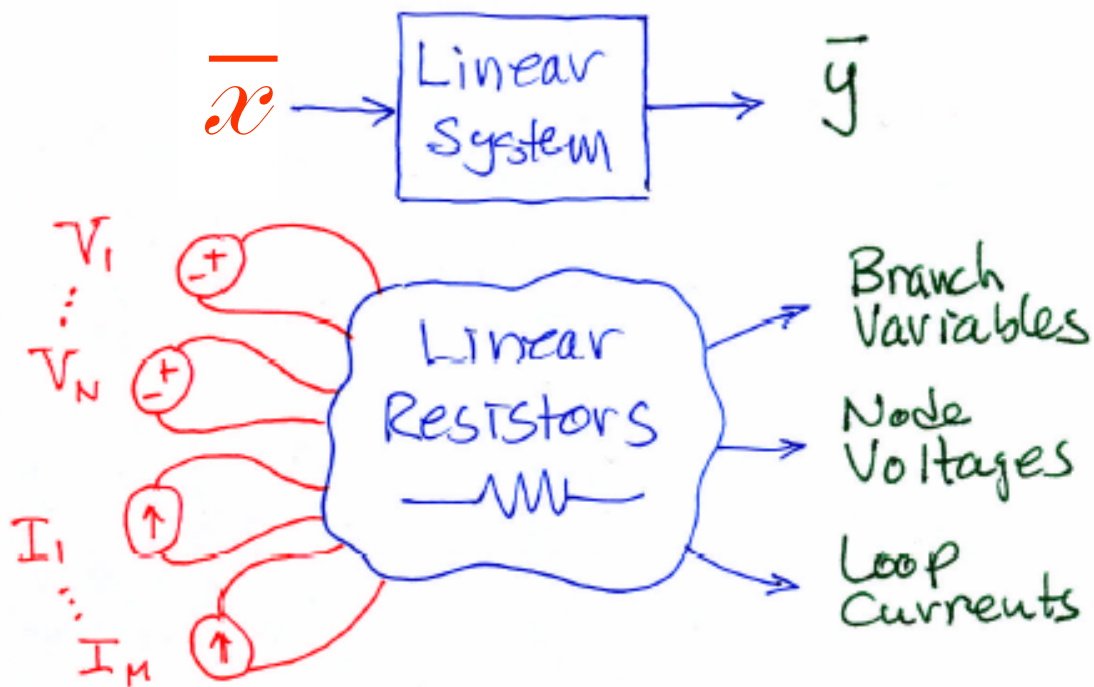
# Linear Networks and Systems

Linear system  $\Rightarrow$  all stimuli are external inputs. For example,  $y = x_1 + x_2$  is linear from  $\bar{x} \rightarrow y$ , but  $y = x_1 + x_2 + 1$  is not.




No source should be left within the network for the purposes of superposition. Superposition is carried out over all sources.


# Divide & Conquer

Use superposition to analyze a linear circuit one source at a time. (All sources except one are set to zero each time.)

How to set a source to zero?

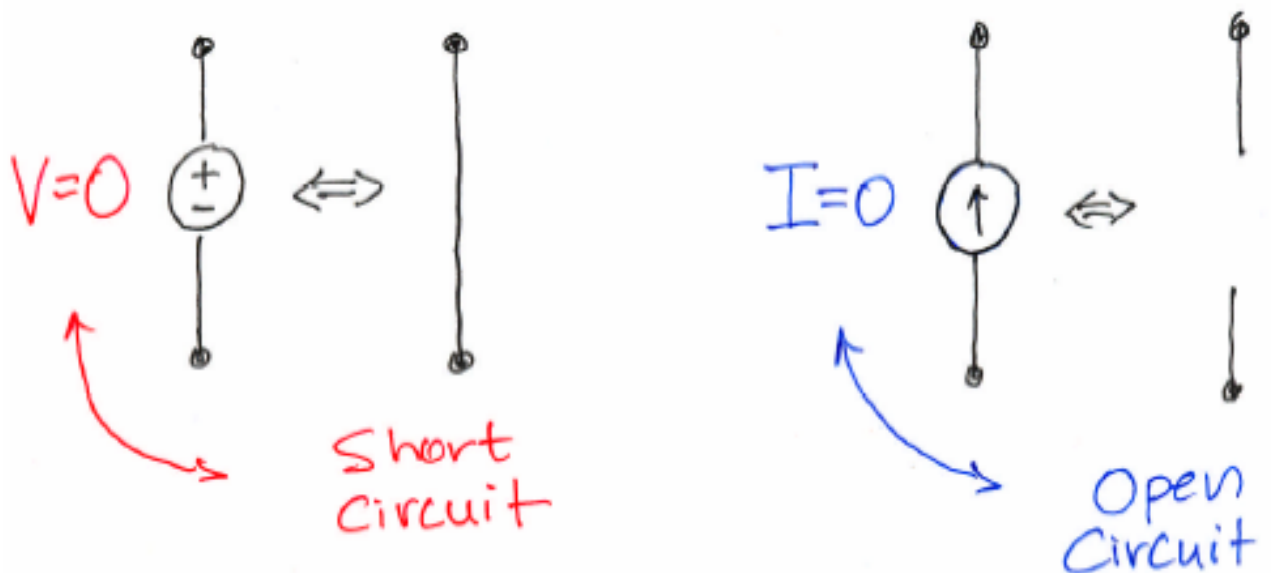


# Thevenin & Norton Equivalence

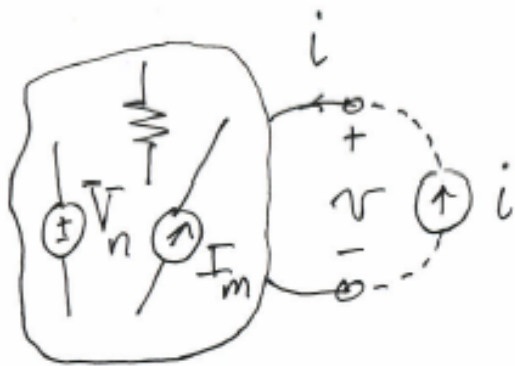

Linear Network

$$v = \sum_n \alpha_n V_n + \sum_m \beta_m I_m + R_{TH} i$$

Superposition


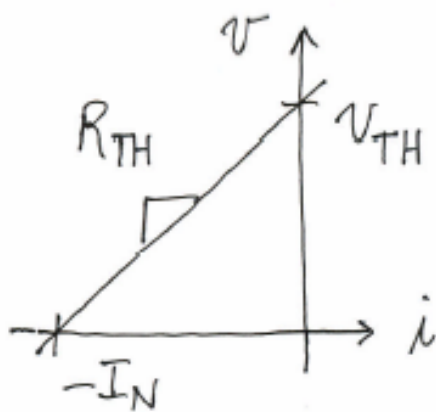


Open Circuit  
( $i=0$ )


$$\Rightarrow V_{TH} = \sum_n \alpha_n V_n + \sum_m \beta_m I_m$$

Short Circuit  
( $v=0$ )
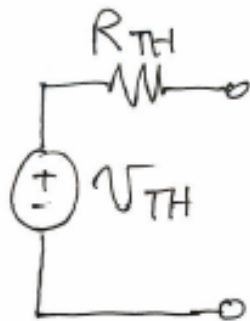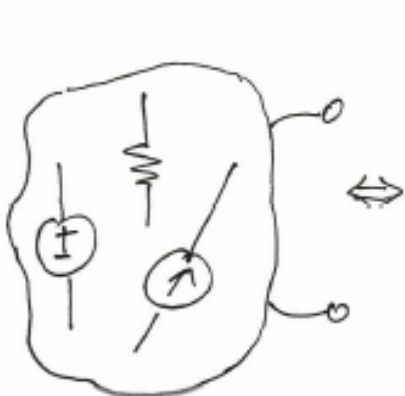
$$\Rightarrow I_N = \frac{V_{TH}}{R_{TH}}$$




Thevenin

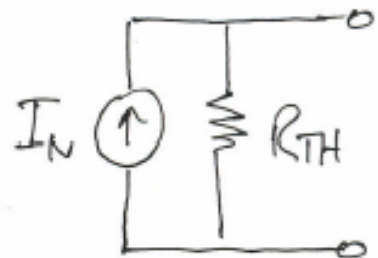


Norton


# Thevenin / Norton Summary

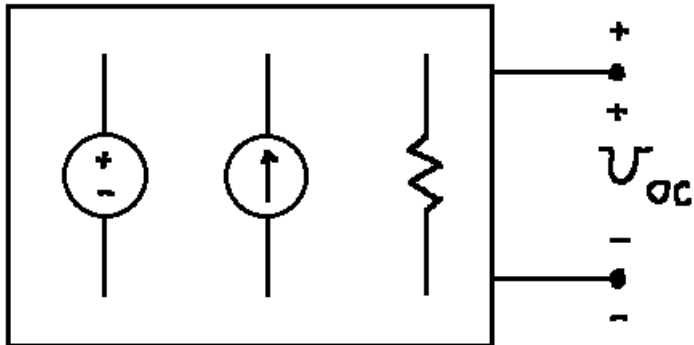

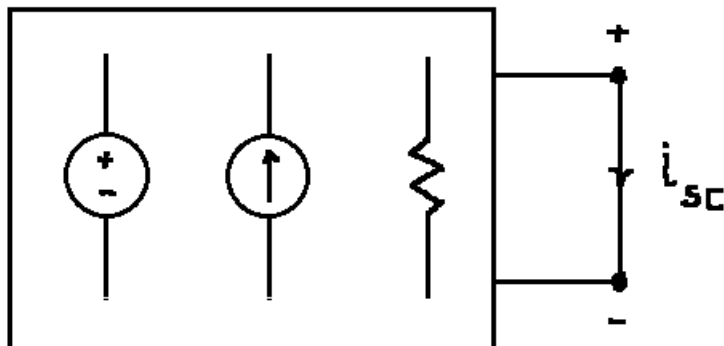The Thevenin voltage  $v_{TH}$  is the open-circuit voltage  $v_{OC}$ .




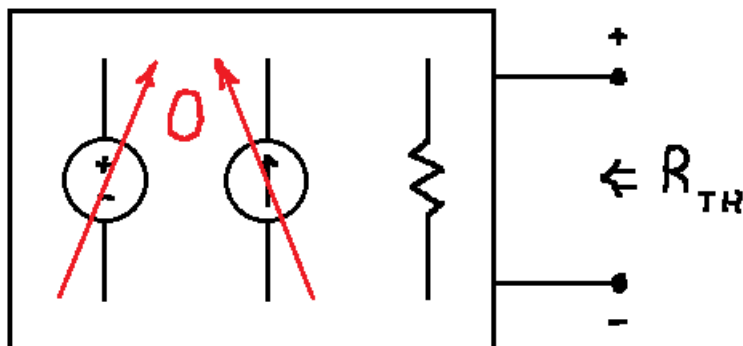The Norton current  $i_N$  is the short-circuit current  $i_{SC}$ .




The Thevenin/  
Norton resistance  $R_{TH}$  is the terminal resistance computed with zeroed sources.



# Thevenin / Norton Example #1

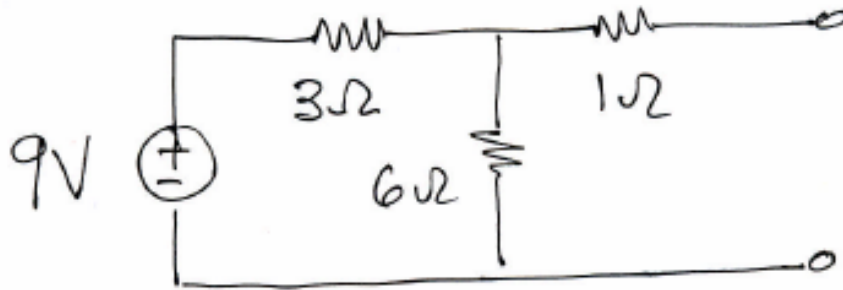

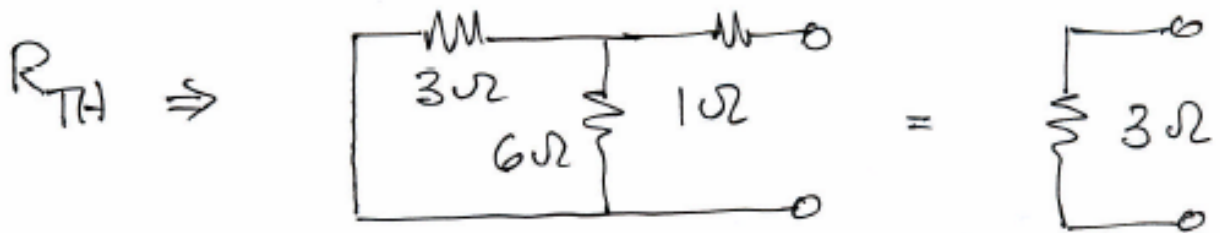
Open-circuit voltage = 6 V via  
voltage divider  $\Rightarrow V_{TH} = 6 V$




$$I_N = V_{TH} / R_{TH} = 2 A$$

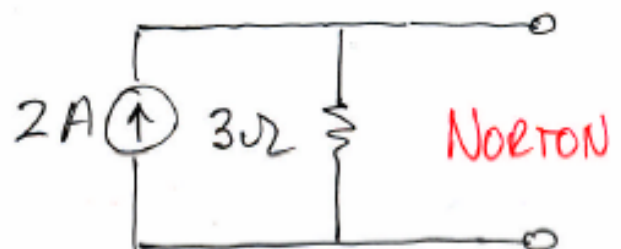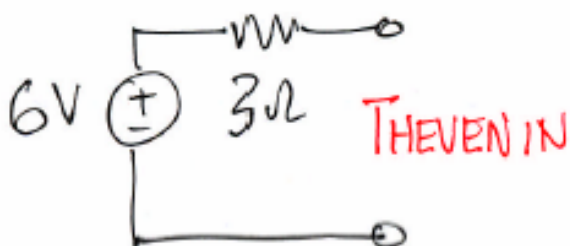


# Confirm Equivalence

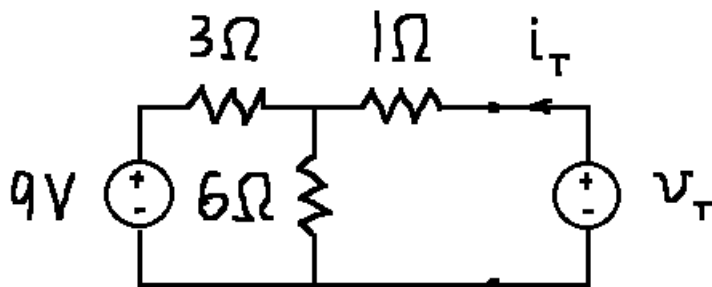
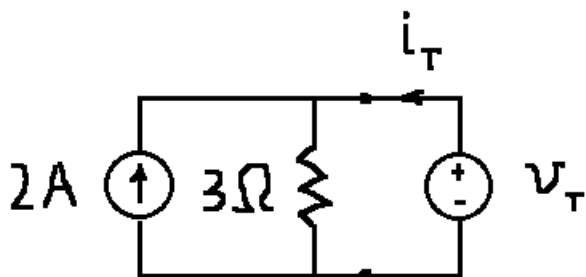
$$\begin{aligned} i_T &= \frac{v_T}{3\Omega} - \frac{6}{7} \frac{9V}{(3+6/7)\Omega} \\ &= v_T / 3\Omega - 2A \\ &= (v_T - 6V) / 3\Omega \end{aligned}$$



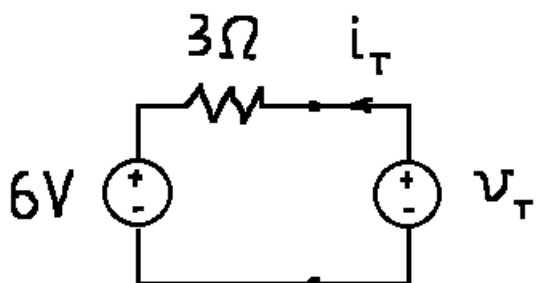
$$\begin{aligned} i_T &= v_T / 3\Omega - 2A \\ &= (v_T - 6V) / 3\Omega \end{aligned}$$



$$i_T = (v_T - 6V) / 3\Omega$$



# DAC Example

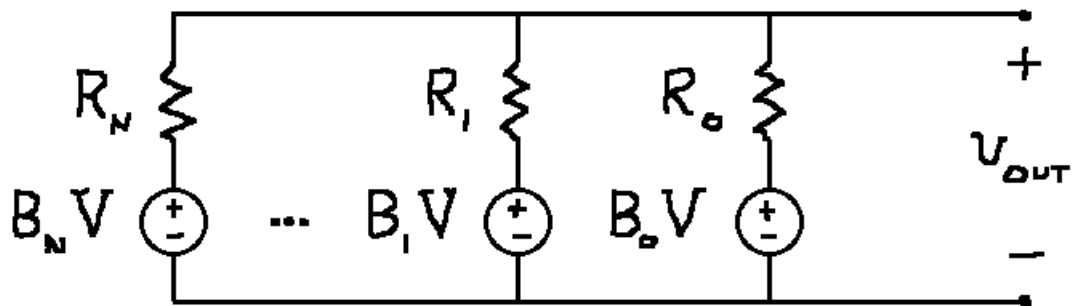

DAC  $\Rightarrow$  Digital Data =  $\boxed{B_N \cdots B_1 B_0}$

$$V_{OUT} = KV \sum_n B_n 2^n ; B_n = \{0, 1\}$$





Use superposition and voltage division:

$$\begin{aligned} V_{OUT,m} &= \frac{(\sum_{n \neq m} G_n)^{-1} B_m V}{R_m + (\sum_{n \neq m} G_n)^{-1}} = \frac{B_m V}{1 + R_m \sum_{n \neq m} G_n} \\ &= \frac{B_m V}{R_m G_m + R_m \sum_{n \neq m} G_n} = \frac{G_m B_m V}{\sum_n G_n} \end{aligned}$$



$$V_{OUT} = V \left( \frac{\sum_n G_n B_n}{\sum_n G_n} \right) \dots \text{by superposition}$$

$$\text{Design} \Rightarrow G_n = G^* 2^n \Rightarrow K = 1 / \left( \sum_m 2^m \right)$$

# Thevenin / Norton Example #2

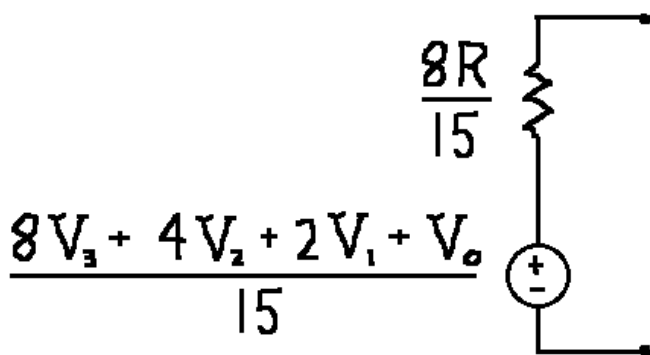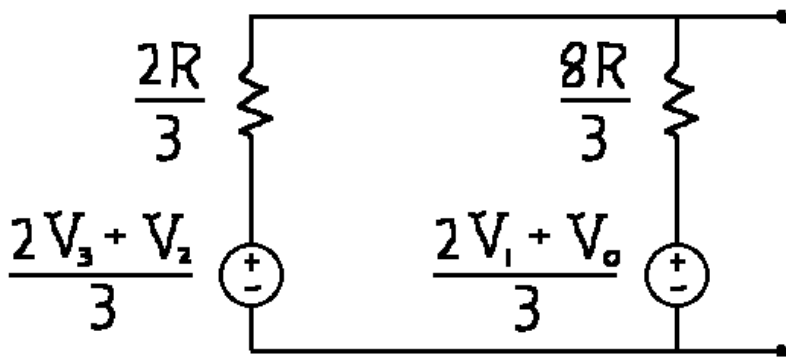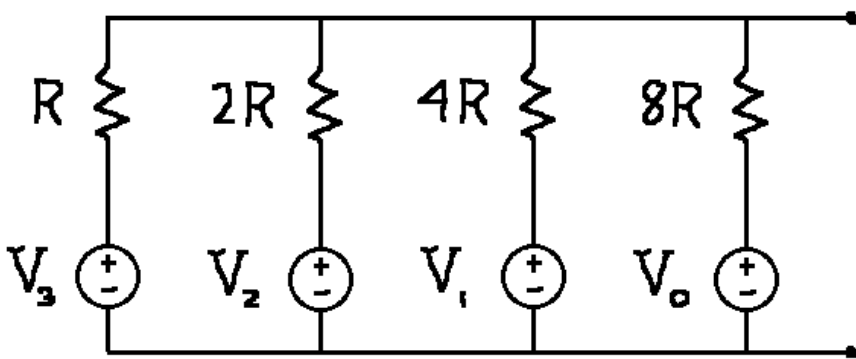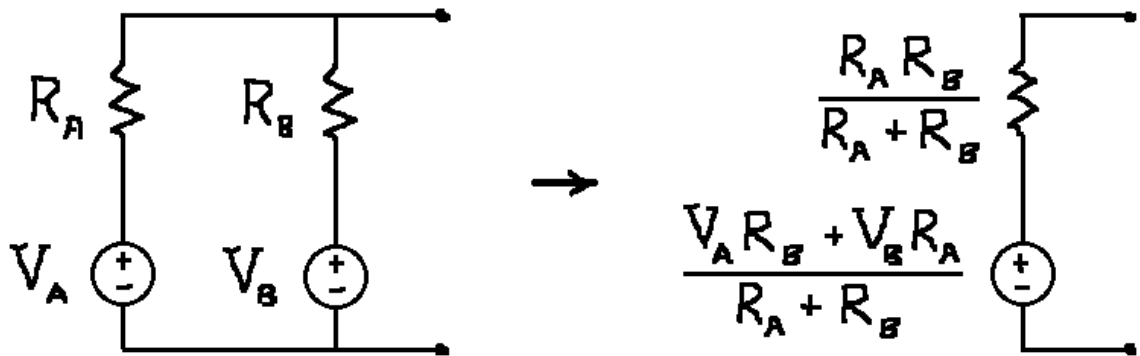


# Thevenin / Norton Example #2

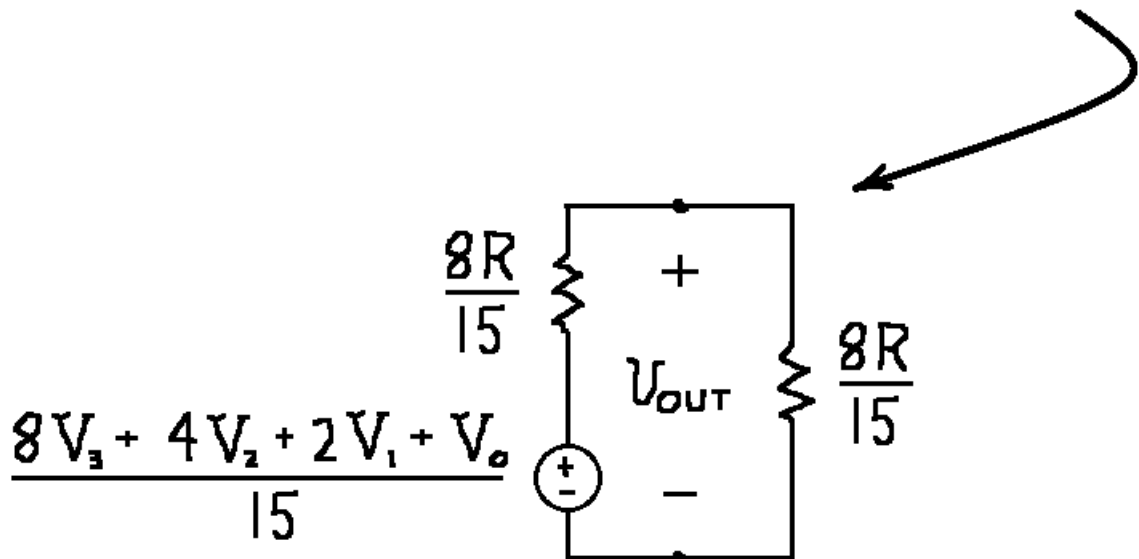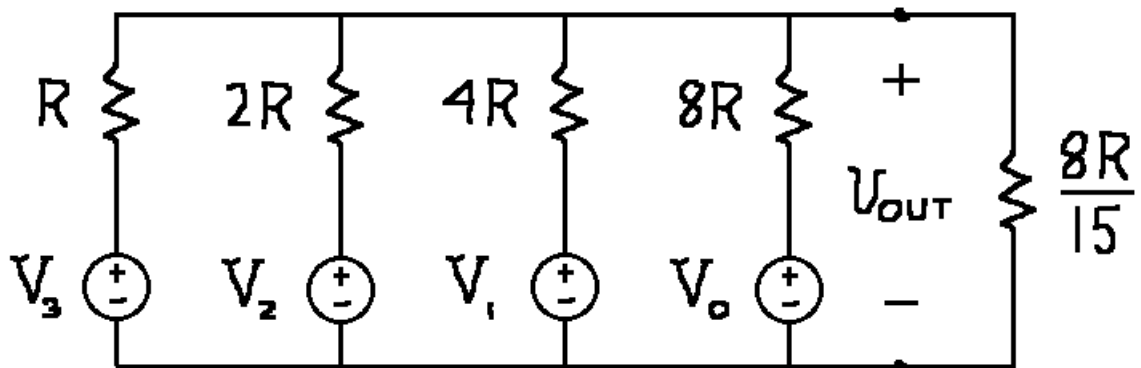


Loading the DAC with  $8R/15$  will reduce its output by 50%.

# Thevenin / Norton Example #3

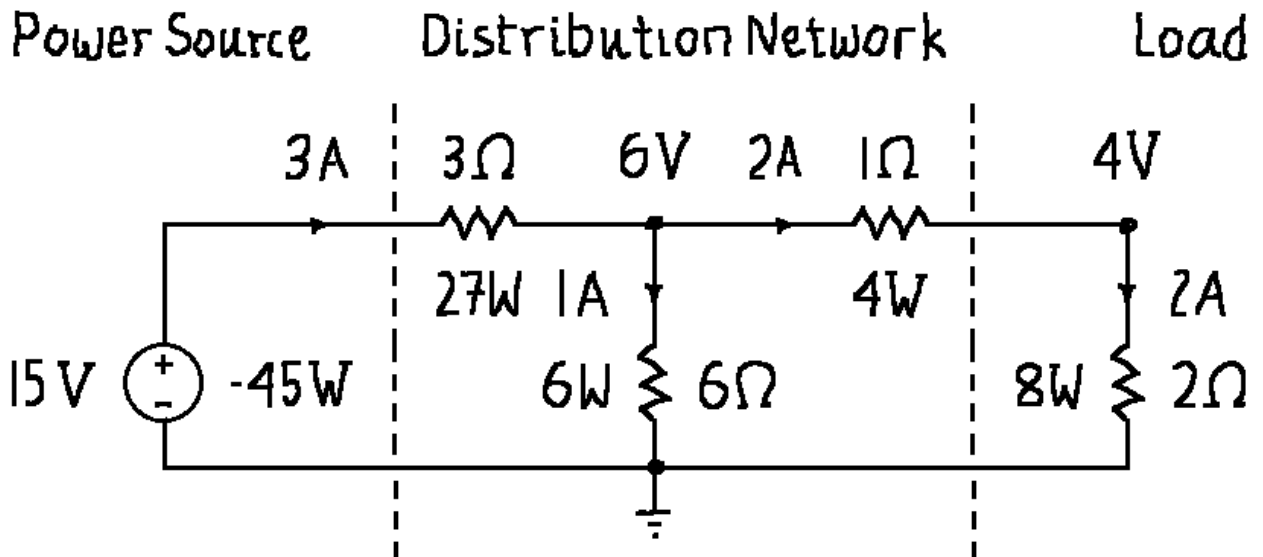


Equivalence

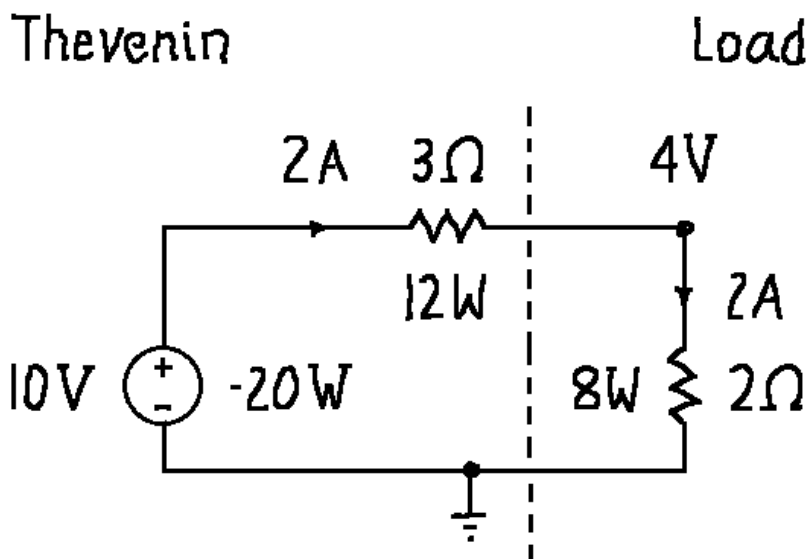


Thevenin and Norton equivalents do not preserve power considerations!

# Experimental Battery Example

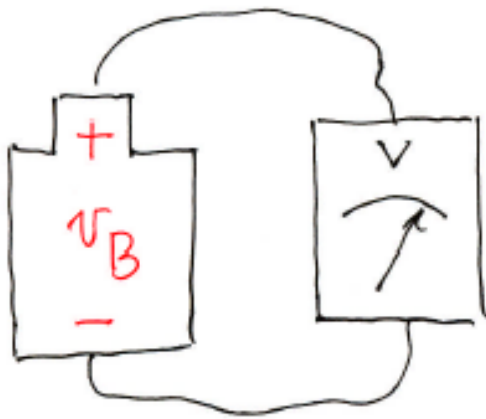


Open-Circuit Voltage

$$v_B = 1.5 \text{ V}$$

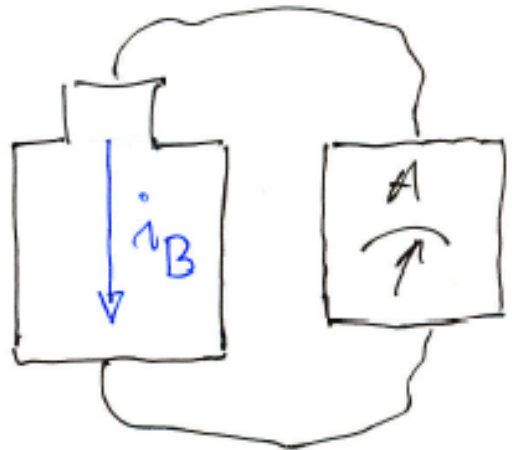


Short-Circuit Current

$$i_B = -1 \text{ A}$$

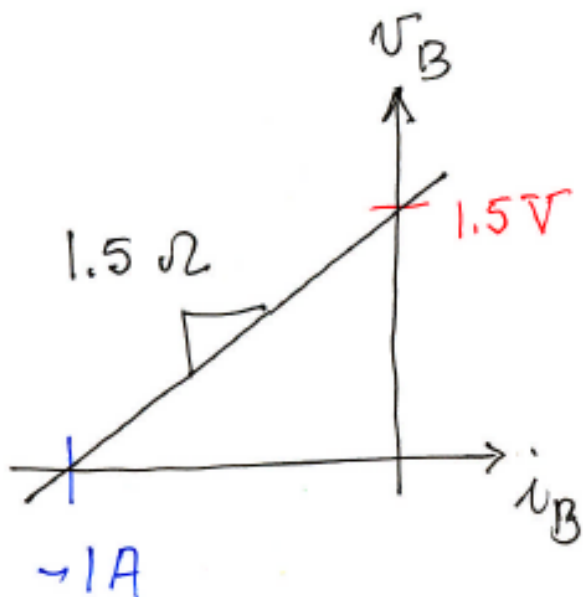

Thevenin Equivalent

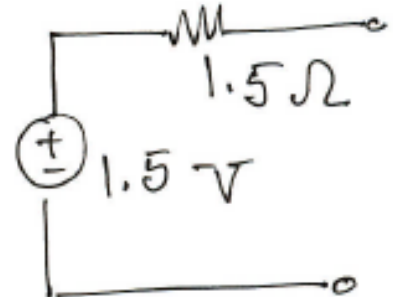

## 5-Lecture Summary

- Two-terminal devices :  $V, I, R$
- KCL and KVL
- Brute-force analysis
- Node analysis
- Parallel and series reductions
- Voltage and current dividers
- Superposition
- Thevenin and Norton equivalence