
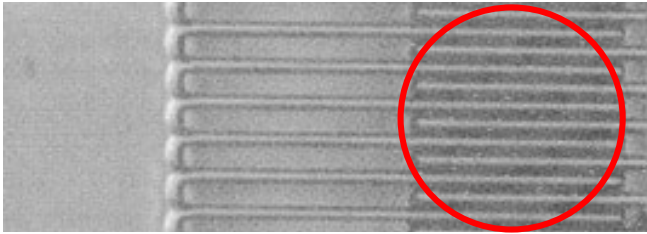
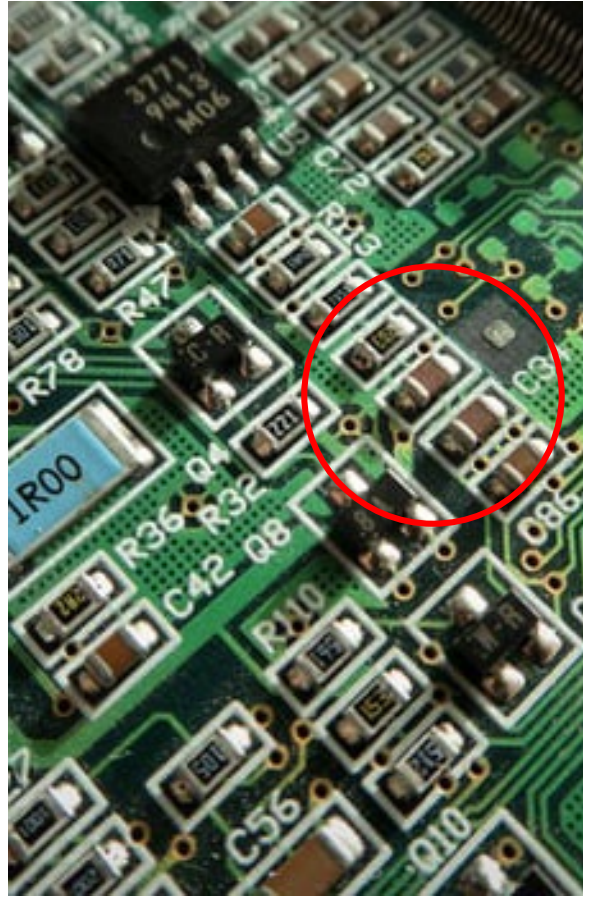


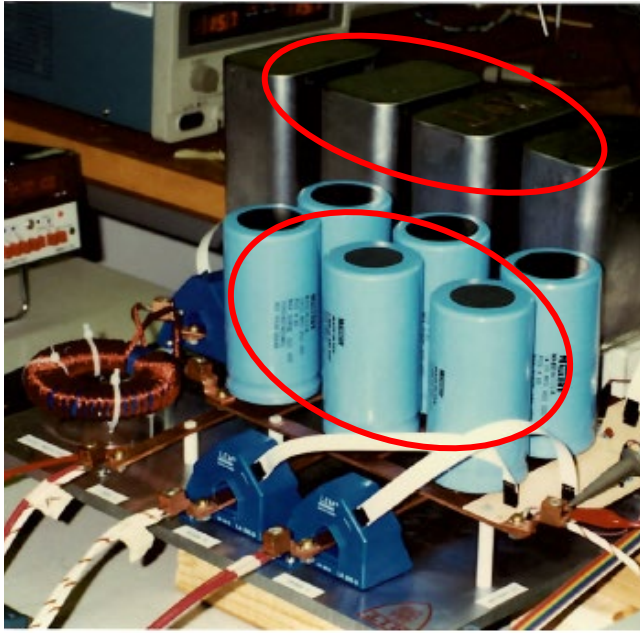6.002 - Lecture 10

Capacitors

- Capacitors are Everywhere
- Uses
- Basic Physics
- First-Order ODEs



Breadboard Capacitance



<https://learn.sparkfun.com/tutorials/how-to-use-a-breadboard>



<https://wiki.analog.com/university/courses/electronics/electronics-lab-breadboard-coupling>

Uses & Memory

Capacitor Uses:

- Energy Storage
- Memory
- Time-Domain Dynamics
- Frequency-Domain Filtering
- Timing
- Resonators
- Sensing & Energy Transduction

Memory Devices

(Excluding Thermal Memory)


- Capacitors
- Inductors

Memoryless Devices:

(Absent Thermal Memory)

- Sources
- Resistors
- Ideal Diodes
- Ideal Transistors
- Ideal Transformers

Ideal Capacitor

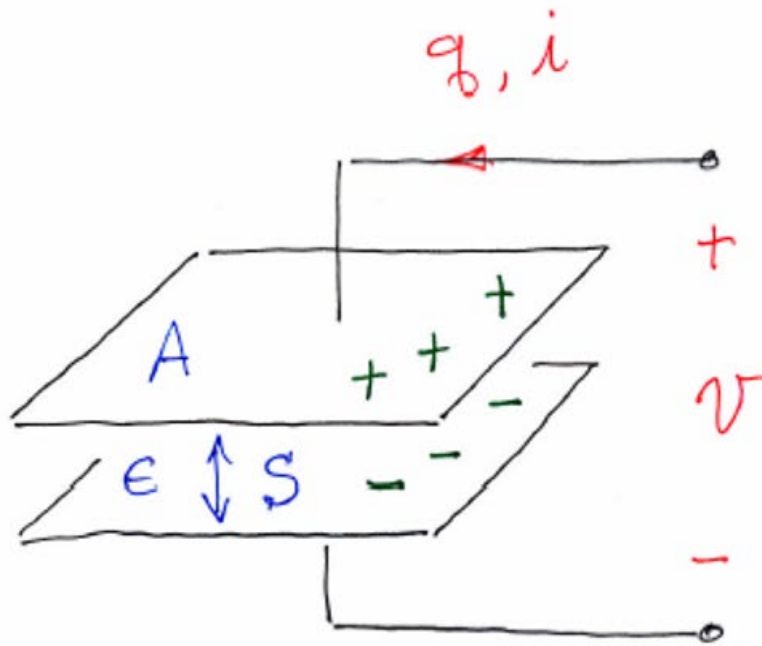

Farads

↓

$$q = C V$$

↑ ↑

Coulombs Volts

$$C = \frac{\epsilon A}{S}$$

$$q = \int_{-\infty}^t i dt \quad i = \frac{dq}{dt} = \frac{d}{dt}(Cv) = C \frac{dv}{dt}$$

Memory ↑ 6.200


$$P = vi = C v \frac{dv}{dt} = \frac{d}{dt} \left(\frac{1}{2} C v^2 \right)$$

Two signs possible ⇒ Reversible stored Energy


Common Nonidealities

- Electrode series resistance
- Electrode series inductance
- Parallel dielectric conductance

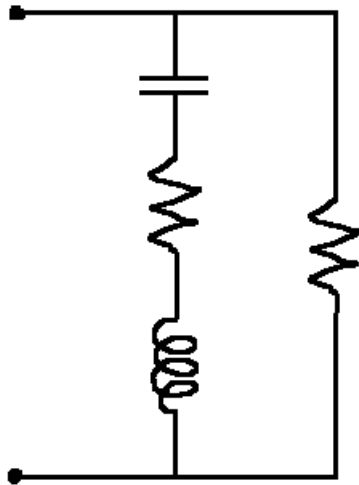A lumped-parameter model can often represent these non ideal behaviors.





Dynamics & Memory

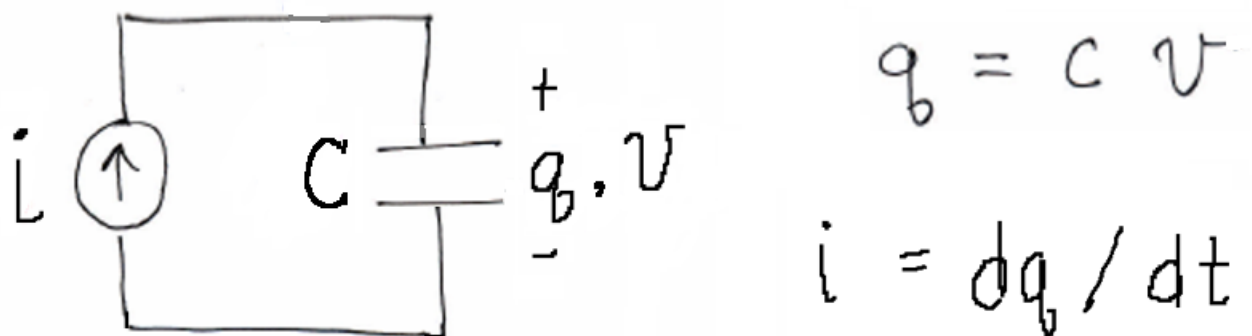

$$q(t) = \int_{-\infty}^t i(t) dt = \int_{-\infty}^{t_0} i(t) dt + \int_{t_0}^t i(t) dt$$
$$= \underbrace{q(t_0)}_{\text{Memory}} + \int_{t_0}^t i(t) dt$$


- Charge (and voltage) depends on the entire current history.
- Charge summarizes (memorizes) the current history relevant to the future.

State Continuity

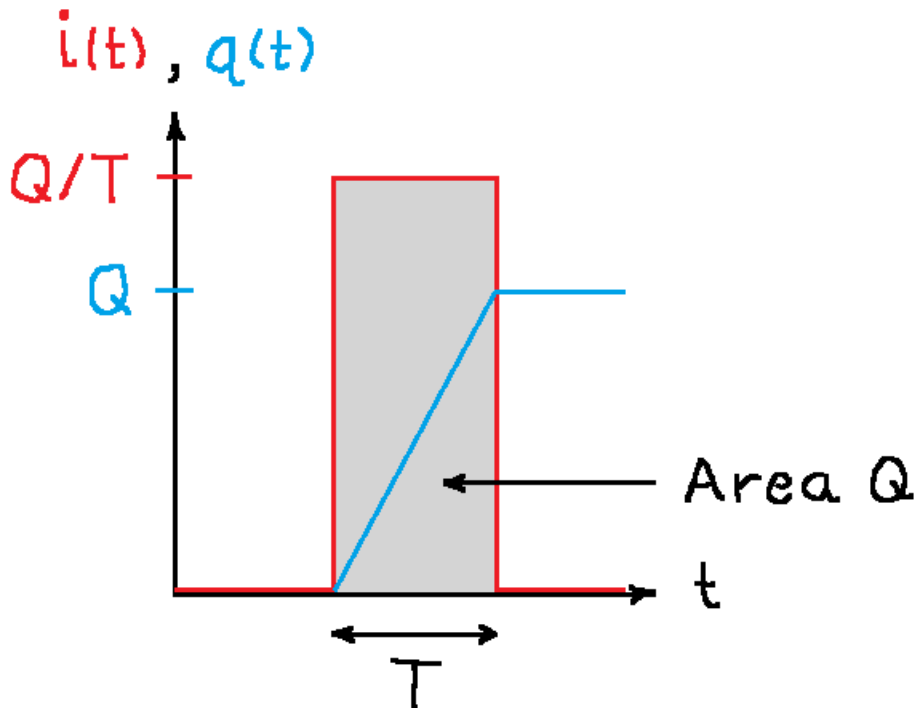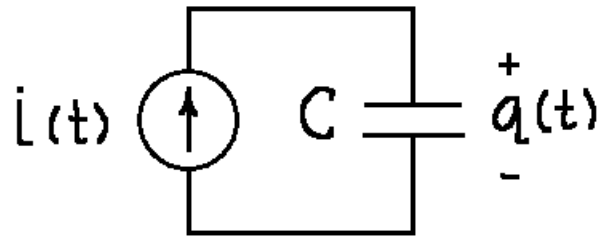

- $\lim T \rightarrow 0 : q(t) \rightarrow \text{step and } i(t) \rightarrow \infty$
- Without infinite current, $q(t)$ cannot step and so is continuous

Power & Energy


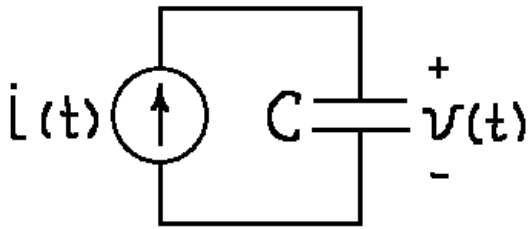


$$v = V \sin(\omega t)$$

$$i = \omega C V \cos(\omega t)$$


$$p = \omega C V^2 \sin(2\omega t) / 2$$

$$w = C V^2 \sin^2(\omega t) / 2$$

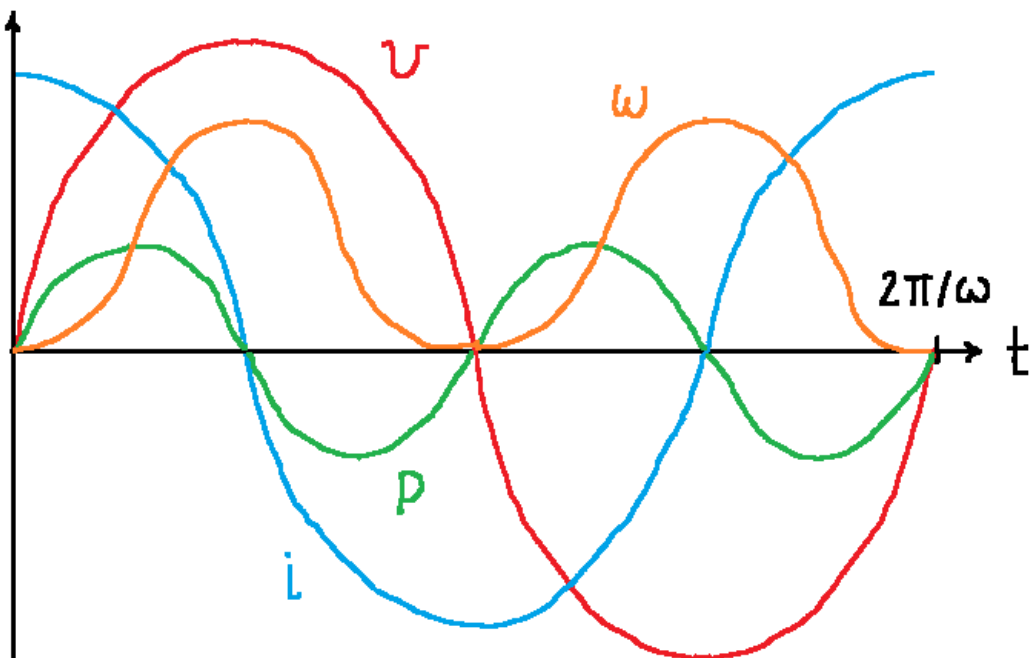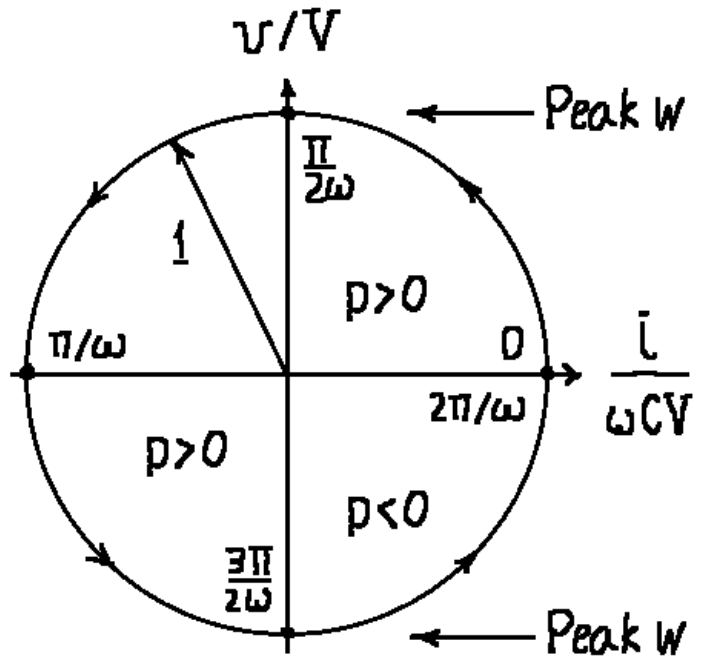

Capacitor Combinations

Parallel

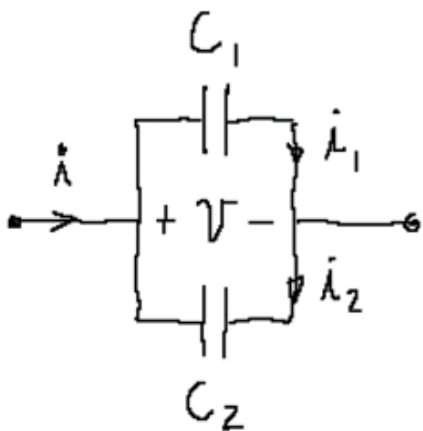


$$\dot{\lambda} = \dot{\lambda}_1 + \dot{\lambda}_2$$

$$= C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt}$$

$$= \underbrace{(C_1 + C_2)} \frac{dV}{dt}$$

Effective capacitance \Rightarrow
parallel capacitances add

Series

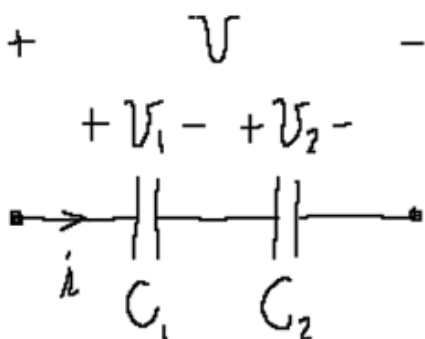

$$\frac{dV}{dt} = \frac{dV_1}{dt} + \frac{dV_2}{dt}$$


$$= \frac{1}{C_1} \dot{\lambda} + \frac{1}{C_2} \dot{\lambda}$$

$$= \underbrace{\left(\frac{1}{C_1} + \frac{1}{C_2} \right)} \dot{\lambda}$$

Effective reciprocal capacitance

\Rightarrow series reciprocal capacitances add

RC Node Analysis

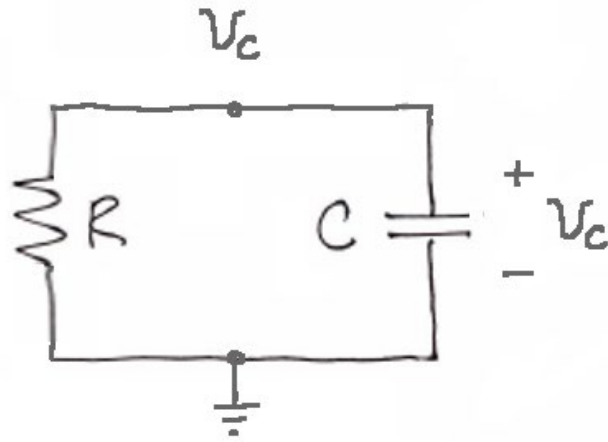

Node Method $\Rightarrow \frac{v_c}{R} + C \frac{dv_c}{dt} = 0$

Time $\left(RC \frac{dv_c}{dt} + v_c = 0 \right)$

Well-Posed Problem $\Rightarrow v_c(0)$ Given

Solution $\Rightarrow v_c(t) = v_c(0) e^{-t/RC}$

ODE Solution

$$RC \frac{dV_c}{dt} + V_c = 0$$

$$\frac{dV_c}{V_c} = -\frac{1}{RC} dt$$

$$\int_{V_c(0)}^{V_c(t)} \frac{dV_c}{V_c} = -\frac{1}{RC} \int_0^t dt$$

$$\ln(V_c(t)) - \ln(V_c(0)) = -\frac{t}{RC}$$

$$\ln\left(\frac{V_c(t)}{V_c(0)}\right) = -\frac{t}{RC}$$

$$V_c(t) = V_c(0) e^{-t/RC}$$

Exponential Decay

$$\frac{d}{dt} e^{-t/T} = \frac{-e^{-t/T}}{T} = \text{Slope} = \frac{\text{Rise}}{\text{Run}}$$

