
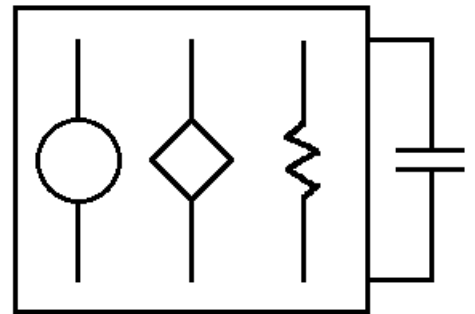
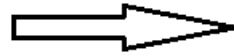


6.002 - Lecture 12

First-Order Driven Response

- RC and RL Step Responses
- Long- and Short-Time Behavior
- Superposition: ZIR and ZSR


RC Network

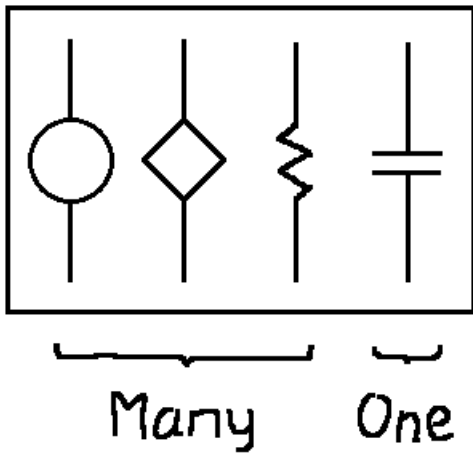

Node Analysis:

$$\frac{V_c}{R} + C \frac{dV_c}{dt} - i = 0$$

$$RC \frac{dV_c}{dt} + V_c = Ri$$

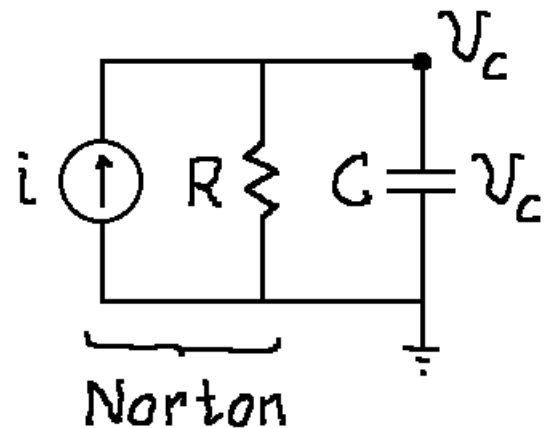


Well-posed problem: $RC \frac{dV_c}{dt} + V_c = Ri$

$V_c(t=0)$ given

$i(t \geq 0)$ given


RL Network

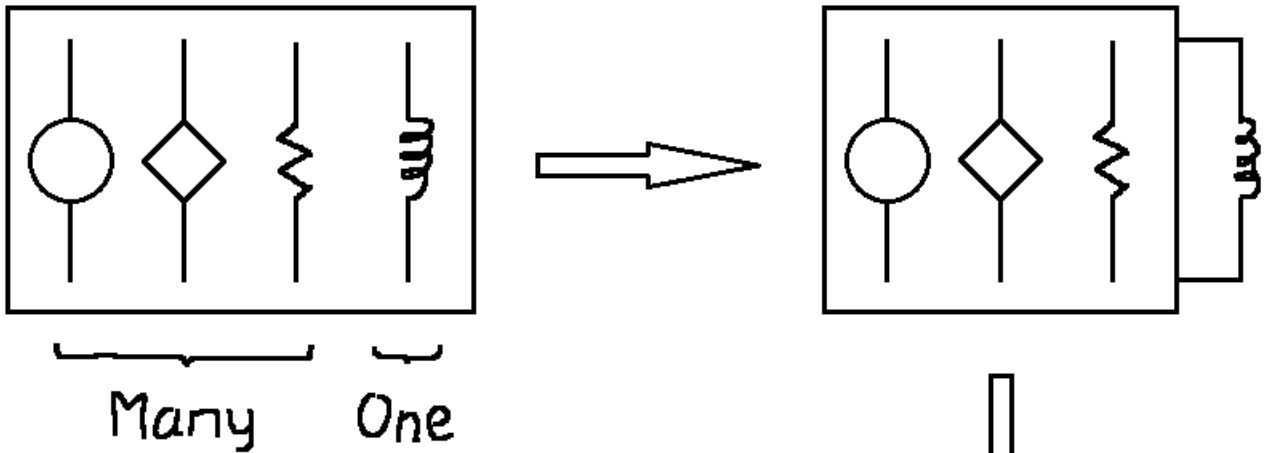

Node Analysis:

$$\frac{V_L - V}{R} + i_L = 0$$
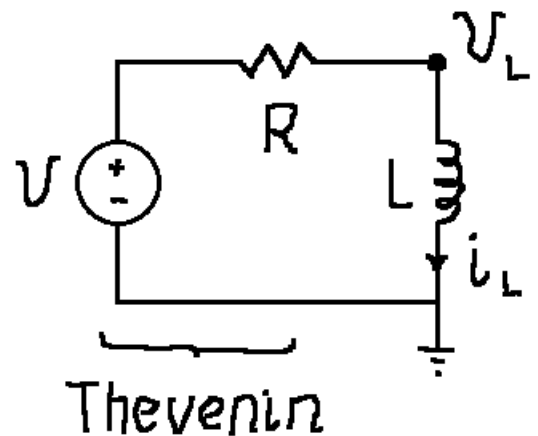
$$\frac{L}{R} \frac{di_L}{dt} + i_L = \frac{V}{R}$$




Well-posed problem: $\frac{L}{R} \frac{di_L}{dt} + i_L = \frac{V}{R}$

$i_L(t=0)$ given

$V(t \geq 0)$ given


General First-Order Dynamics

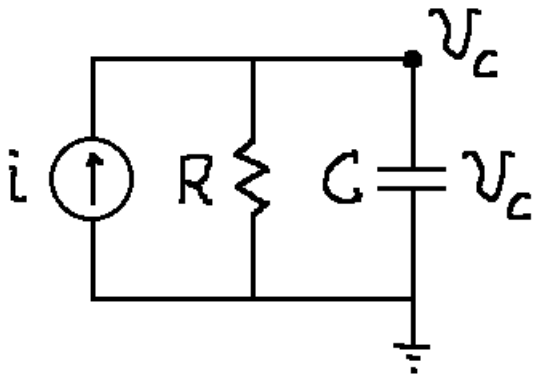

$$RC \frac{dv_c}{dt} + v_c = Ri$$

$$v_c(t=0) \text{ given}$$

$$i(t \geq 0) \text{ given}$$

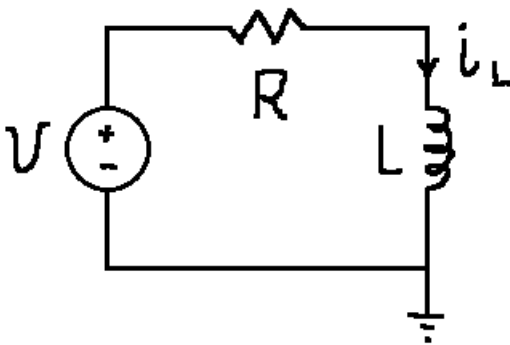

$$\frac{L}{R} \frac{di_L}{dt} + i_L = \frac{v}{R}$$

$$i_L(t=0) \text{ given}$$

$$v(t \geq 0) \text{ given}$$

General problem: $\tau \frac{dx}{dt} + x = y$

$$x(t=0) \text{ given}$$

$$y(t \geq 0) \text{ given}$$

$$\tau = \text{Time constant}$$

First-Order Dynamic Response

$$\tau \frac{dx}{dt} + x = y \quad x(0) \text{ Given} \quad y(t) \text{ Given for } t \geq 0$$

$$x(t) = \begin{array}{l} \text{Particular} \\ \text{Solution} \end{array} + \begin{array}{l} \text{Homogeneous} \\ \text{Solution} \end{array} = x_p(t) + x_H(t)$$

Particular solution satisfies the differential equation, but not necessarily the initial condition

Homogeneous solution adjusts the total solution to satisfy the initial condition

Let \dot{x} denote dx/dt and substitute $x = x_p + x_H$

$$\begin{array}{c} \text{Defined Match} \\ \downarrow \quad \downarrow \quad \downarrow \\ \tau (\dot{x}_p + \dot{x}_H) + (x_p + x_H) = y + 0 \\ \uparrow \quad \uparrow \quad \uparrow \\ \text{Residual Match} \end{array}$$

$$\left. \begin{array}{l} \tau \dot{x}_H + x_H = 0 \\ x_H(0) = x(0) - x_p(0) \end{array} \right\} x_H(t) = (x(0) - x_p(0)) e^{-t/\tau}$$

$$x(t) = x_p(t) + (x(0) - x_p(0)) e^{-t/\tau}$$

First-Order Step Response

$$\tau \frac{dx}{dt} + x = y \quad x(0) \text{ Given} \quad y(t) = Y \text{ for } t \geq 0$$

$$x_p(t) = Y \quad \dots \text{ By inspection}$$


$$x(t) = Y + (x(0) - Y)e^{-t/\tau} \quad [1]$$

$$= Y(1 - e^{-t/\tau}) + x(0)e^{-t/\tau} \quad [2]$$


[1] $\Rightarrow x(t)$ decays exponentially from $x(0)$ to Y

[2] $\Rightarrow x(0)$ disappears exponentially (ZIR) while Y appears exponentially (ZSR)

ZIR/ZSR = zero input/state response

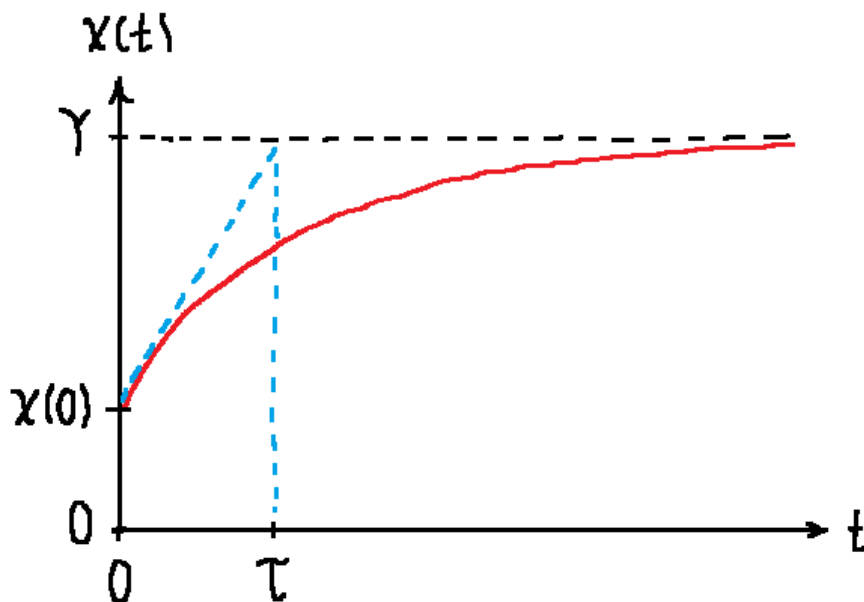

RC Network Step Response

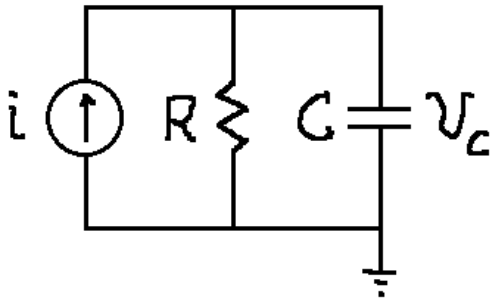


$$RC \frac{dv_c}{dt} + v_c = RI$$

$$v_c(0) \text{ given}$$

$$i(t \geq 0) \equiv I$$


$$v_c(t) = v_c(0)e^{-t/RC} + RI(1 - e^{-t/RC})$$
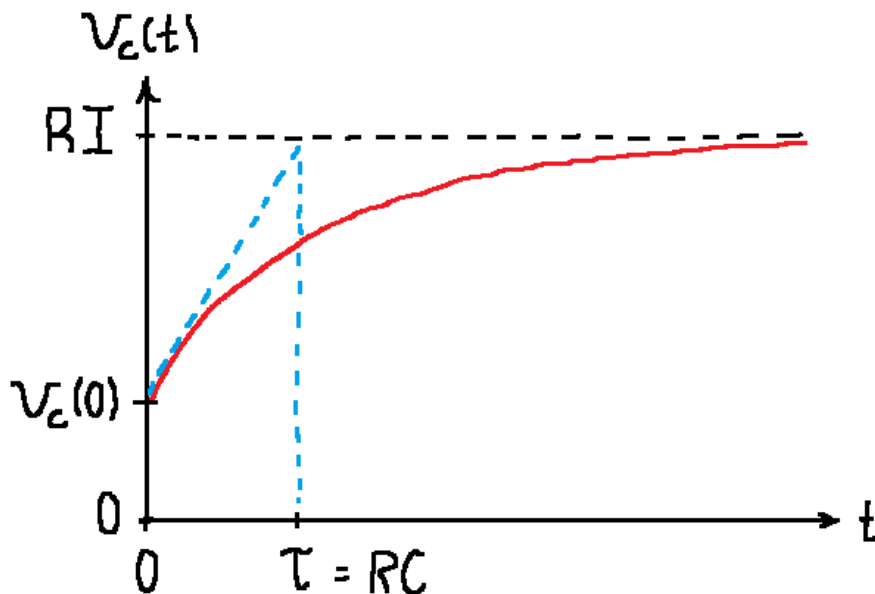
$$i_c = C \frac{dv_c}{dt} = (I - v_c(0)/R)e^{-t/RC}$$



- In the absence of infinite i_c , $v_c(t)$ is continuous. Thus, for $t \ll RC$, $v_c(t) \approx v_c(0)$, rising linearly at first.
- For $t \rightarrow \infty$, the network reaches steady state with $d/dt \rightarrow 0$. Thus, $i_c \rightarrow 0$, the capacitor acts as an open circuit, and v_c settles to $v_c(t) \rightarrow RI$.

RL Network Step Response

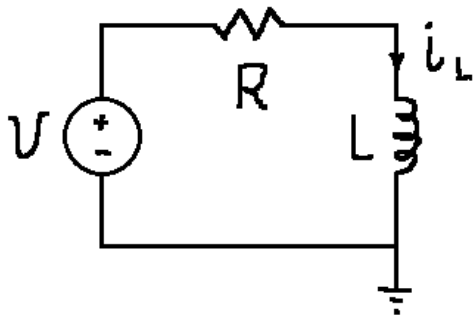


$$(L/R) di_L/dt + i_L = V/R$$

$$i_L(0) \text{ given}$$

$$V(t \geq 0) = V$$

$$i_L(t) = i_L(0) e^{-t/(L/R)} + (V/R)(1 - e^{-t/(L/R)})$$
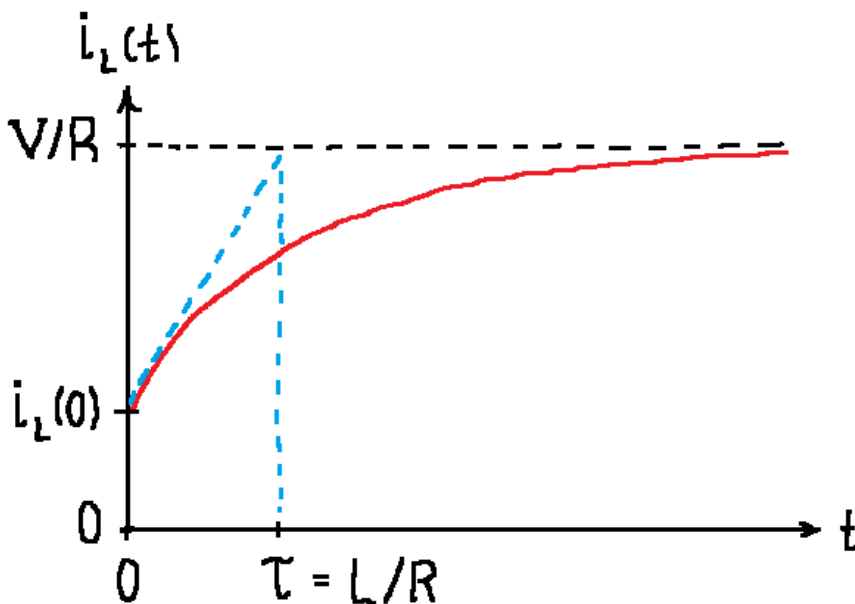
$$v_L = L di_L/dt = (V - Ri_L(0)) e^{-t/(L/R)}$$



- In the absence of infinite v_L , $i_L(t)$ is continuous. Thus, for $t \ll L/R$, $i_L(t) \approx i_L(0)$, rising linearly at first.
- For $t \rightarrow \infty$, the network reaches steady state with $d/dt \rightarrow 0$. Thus, $v_L \rightarrow 0$, the inductor acts as a short circuit (wire), and i_L settles to $i_L(t) \rightarrow V/R$.