

# 6.002 - Lecture 19

## Boost Converter

- Power Electronics
- Energy Processing
- Boost Converter Example
- LC Network Review
- LC Network Application

# Power Electronics

“Power electronics” does not necessarily mean “powerful electronics”. Rather it refers to electronics designed to process power/energy as opposed to electronics that process signals/information.

Power electronics concerns include:



- efficiency and temperature rise;
- power density;
- regulation of output voltage or current; and
- response bandwidth in the presence of source and load variations.

As a consequence of the concern for efficiency, power electronics involve (to first order) only ideally lossless devices:

- capacitors and inductors acting as energy stores;
- transistors and diodes acting as switches to direct energy flow;
- transformers for isolation and voltage and current transformation.

To learn more, consider 6.131 and/or 6.334.

# Boost Converter?

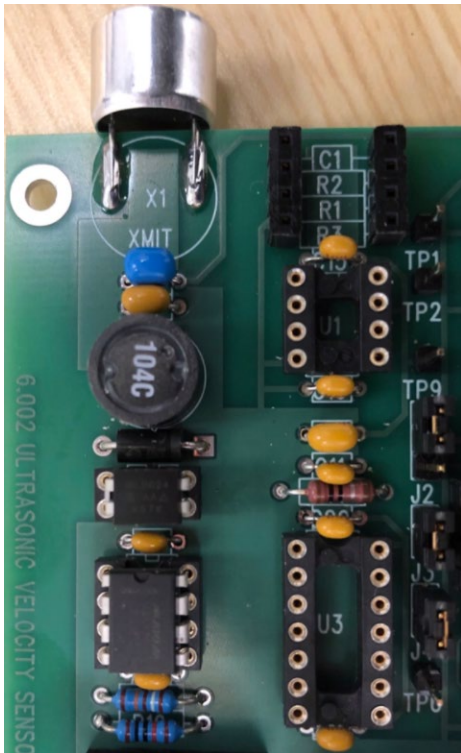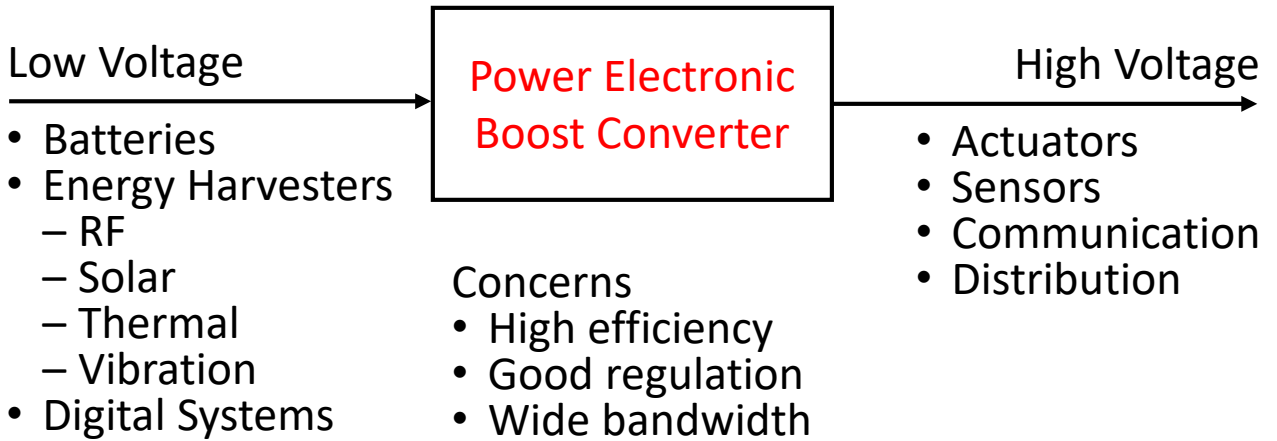

6.002 Ultrasound Boost Converter



Hansen, Martin and Perrault  
DOI:10.1109/TPEL.2019.2900021





Kodak Camera

Ofori-Tenkorang,  
PhD Thesis, MIT, 1997




# Single-Use Camera

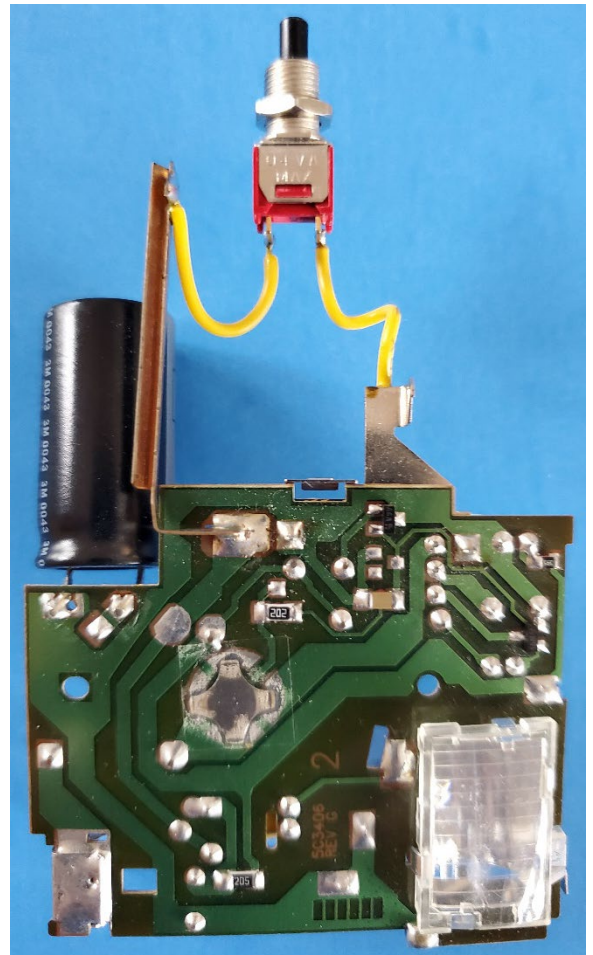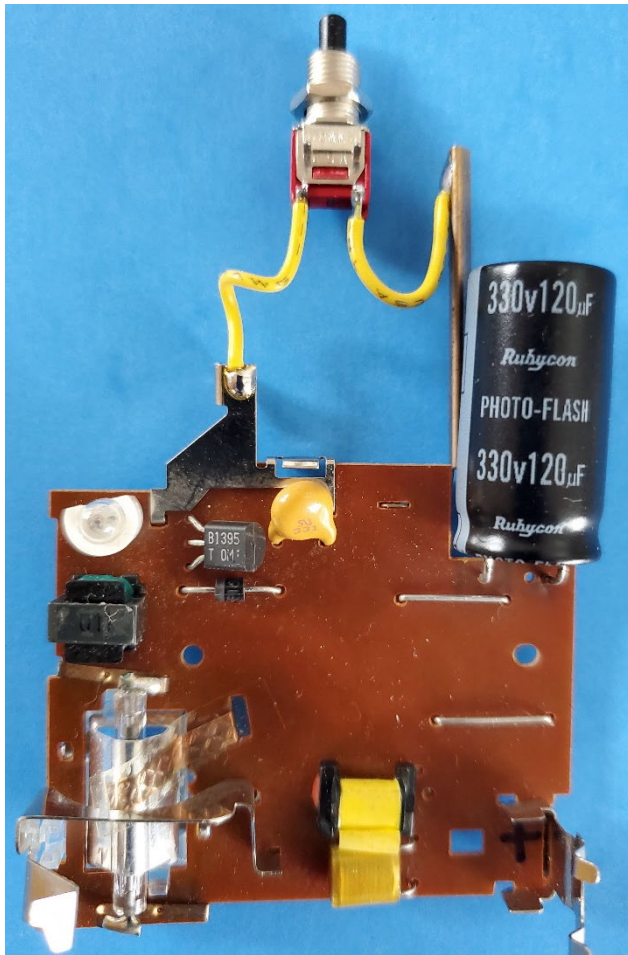

# Simplified Camera Flash Circuit

Flash Trigger

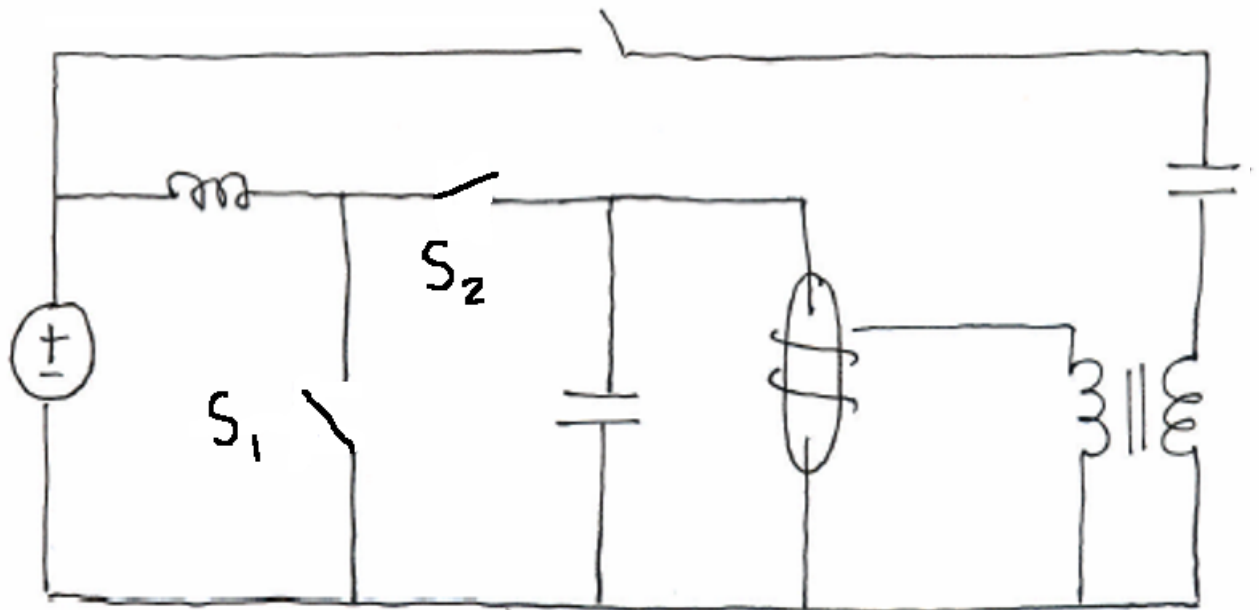

Voltage Pump

Flash

Igniter


Typical Operation:

1.5 V @ Battery

300 V @ Capacitor


10 kV @ Igniter

# Voltage Pump (Boost Converter)

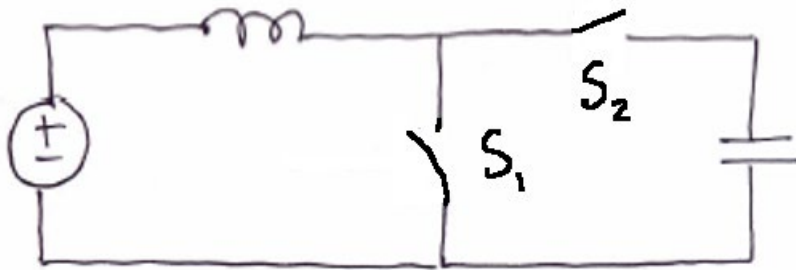


State I

$S_1$  On  
 $S_2$  Off

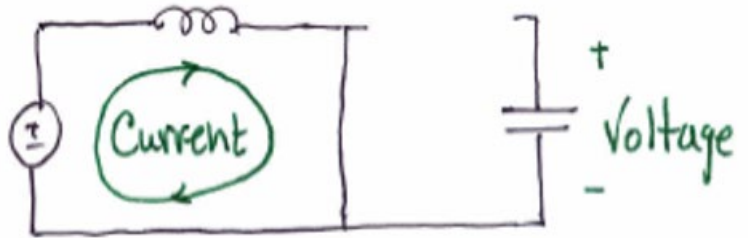


State II

$S_1$  Off  
 $S_2$  On

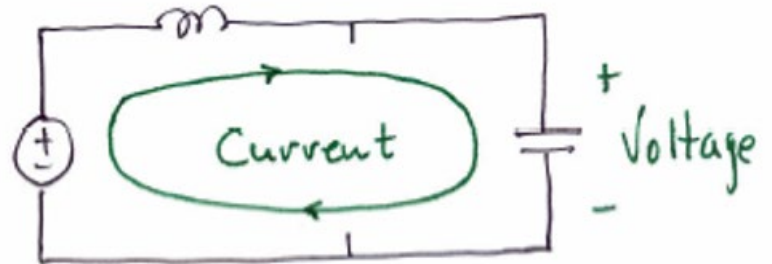


State III

$S_1$  off  
 $S_2$  off

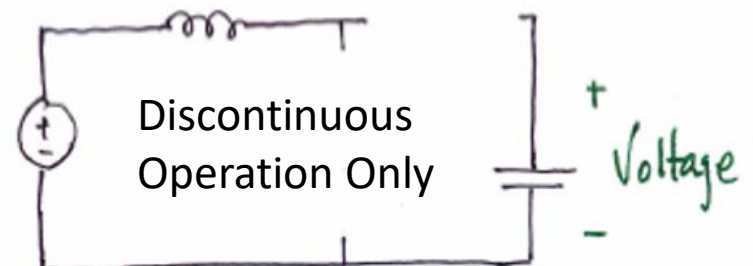

# State I

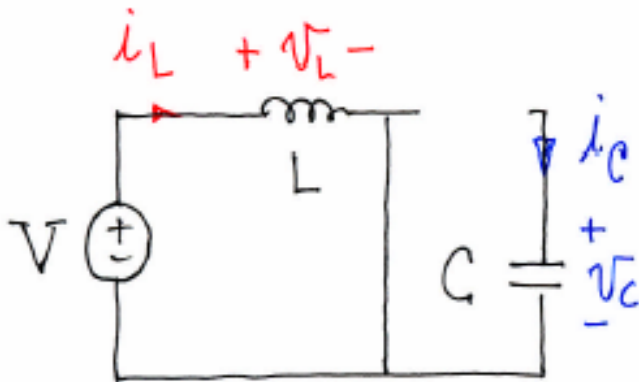


$$-T \leq t \leq 0$$

$$i_L(-T) = 0$$


$$v_C(-T) = \text{Given}$$

$$V = v_L = L \frac{di_L}{dt} \Rightarrow i_L(t) = \frac{V}{L} (t+T)$$
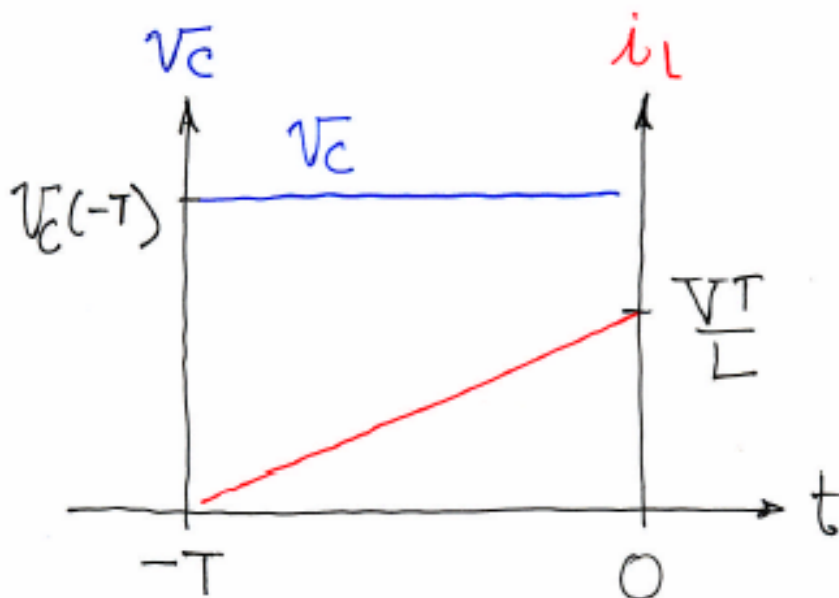
$$0 = i_C = C \frac{dv_C}{dt} \Rightarrow v_C(t) = v_C(-T)$$



## State II

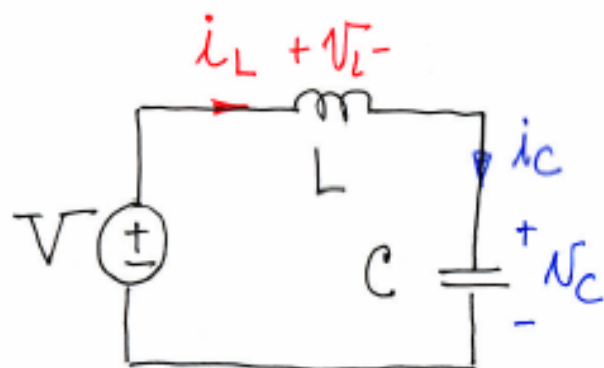

$0 \leq t \leq$  Diode Turn Off

$$i_L(0) = \text{Given}$$

$$V_C(0) = \text{Given}$$

$$\bar{V} = LC \frac{d^2 V_C}{dt^2} + V_C \quad \& \quad i_C = C \frac{dV_C}{dt}$$

$$V_C = \bar{V} + A \sin\left(\frac{t}{\sqrt{LC}}\right) + B \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_L = C \frac{dV_C}{dt} = \sqrt{\frac{C}{L}} A \cos\left(\frac{t}{\sqrt{LC}}\right) - \sqrt{\frac{C}{L}} B \sin\left(\frac{t}{\sqrt{LC}}\right)$$

$$V_C = \bar{V} + \sqrt{\frac{L}{C}} i_L(0) \sin\left(\frac{t}{\sqrt{LC}}\right) + (V_C(0) - \bar{V}) \cos\left(\frac{t}{\sqrt{LC}}\right)$$

$$i_L = i_L(0) \cos\left(\frac{t}{\sqrt{LC}}\right) - \sqrt{\frac{C}{L}} (V_C(0) - \bar{V}) \sin\left(\frac{t}{\sqrt{LC}}\right)$$




# All States Together

State II Review:



$\phi = \text{Positive}$

$$V_C(t) = V + \sqrt{(V_C(0) - V)^2 + \frac{L}{C} i_L(0)^2} \cos\left(\frac{t}{\sqrt{LC}} - \tan^{-1}\left(\sqrt{\frac{L}{C}} \frac{i_L(0)}{V_C(0) - V}\right)\right)$$
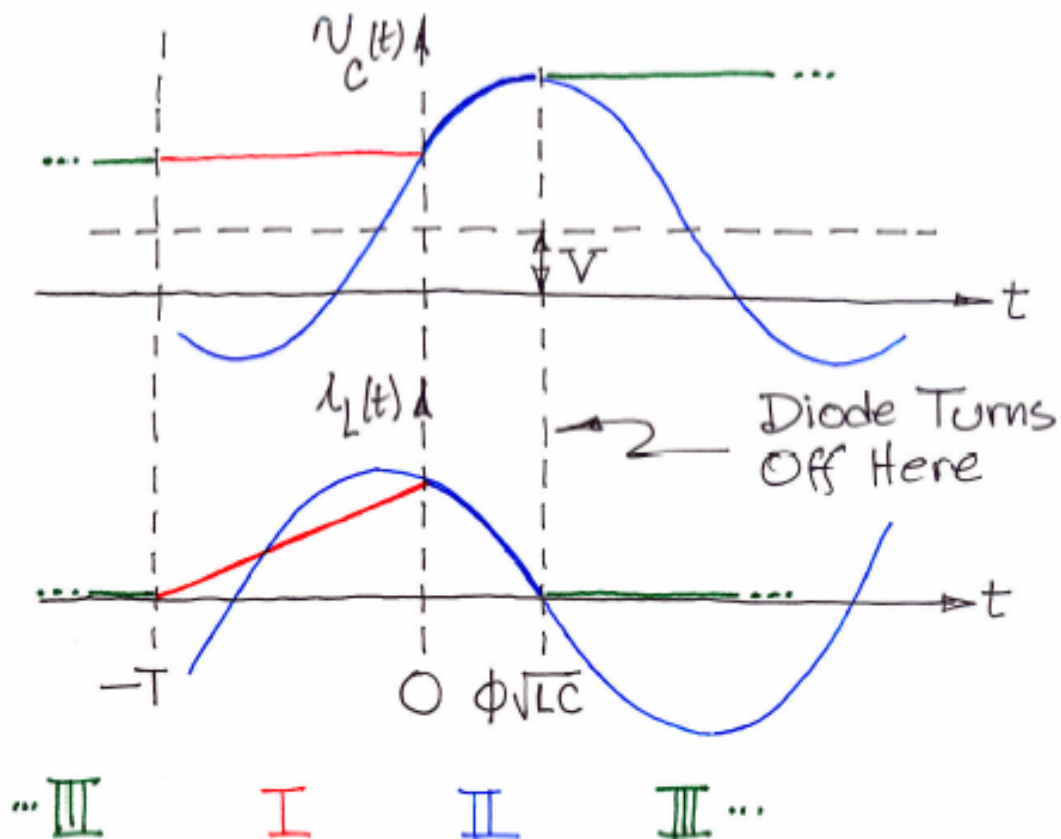
$$i_L(t) = -\sqrt{\frac{C}{L}(V_C(0) - V)^2 + i_L(0)^2} \sin\left(\frac{t}{\sqrt{LC}} - \tan^{-1}\left(\sqrt{\frac{L}{C}} \frac{i_L(0)}{V_C(0) - V}\right)\right)$$



# (Lossless) Cycle Analysis

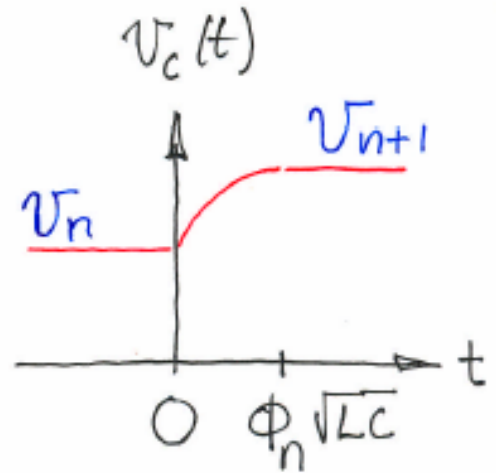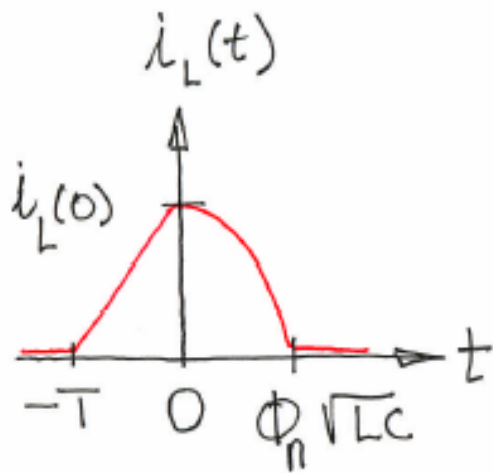

$$\begin{aligned}v_{n+1} &= V + \sqrt{(v_n - V)^2 + \frac{L}{C} i_L^2(0)} \\ &= V + \sqrt{(v_n - V)^2 + \frac{V^2 T^2}{LC}}\end{aligned}$$

$$(v_{n+1} - V)^2 = (v_n - V)^2 + \frac{V^2 T^2}{LC} \quad (v_0 - V)^2 = 0$$

$$v_n = V + V \sqrt{\frac{n T^2}{LC}}$$

# Cycle Analysis Via Energy

Conservation:  $\Delta W_C = -\Delta W_B + W_L$

Capacitor:  $\Delta W_C = \frac{1}{2} C v_{n+1}^2 - \frac{1}{2} C v_n^2$

Inductor:  $W_L = \frac{1}{2} L i_L^2(t)$

Battery:  $-\Delta W_B = V \Delta Q$


Charge:  $\Delta Q = C v_{n+1} - C v_n$

$$\frac{C}{2} v_{n+1}^2 - \frac{C}{2} v_n^2 = C V v_{n+1} - C V v_n + \frac{L}{2} i_L^2(t)$$


$$v_{n+1}^2 - 2V v_{n+1} + V^2 = v_n^2 - 2V v_n + V^2 + \frac{L}{C} i_L^2(t)$$

$$(v_{n+1} - V)^2 = (v_n - V)^2 + \frac{L}{C} i_L^2(t) \quad \dots \text{As Before!}$$

# Demo

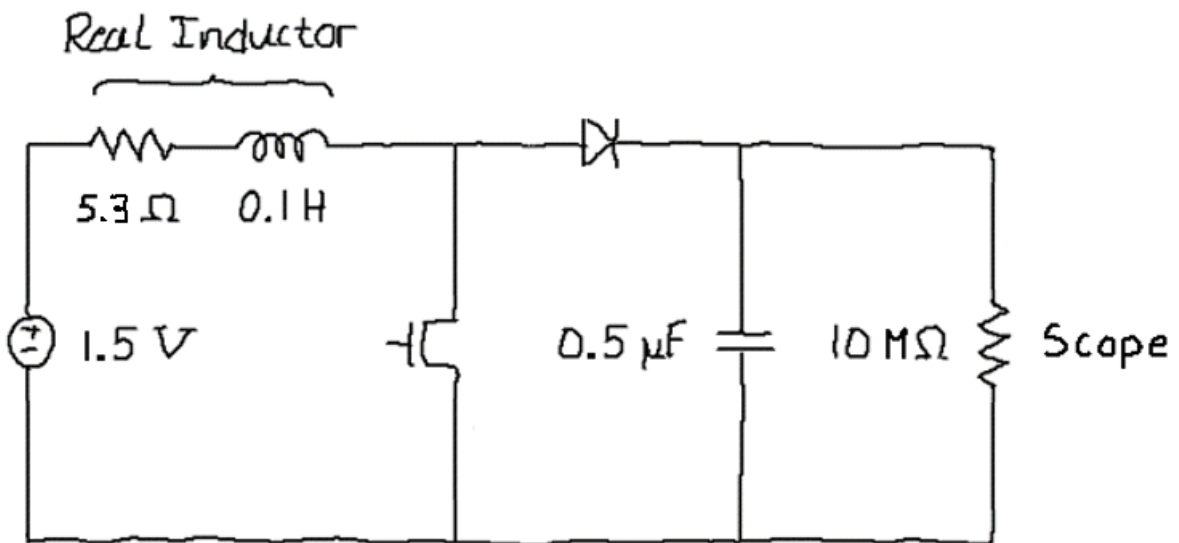


MOSFET Switching

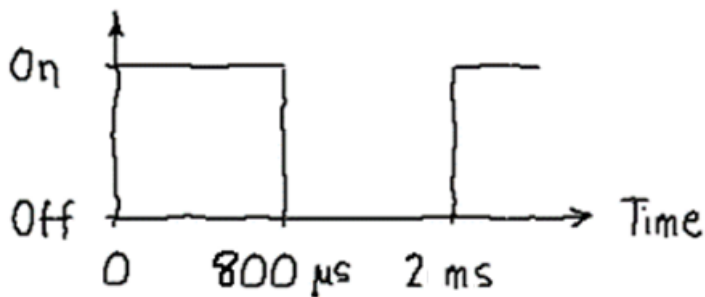

- Transistor Rating = 50V
- Capacitor Rating  $\geq$  100V
- Diode Rating  $\geq$  100V
- Inductor Rating = ?

# Operation

First two switching cycles

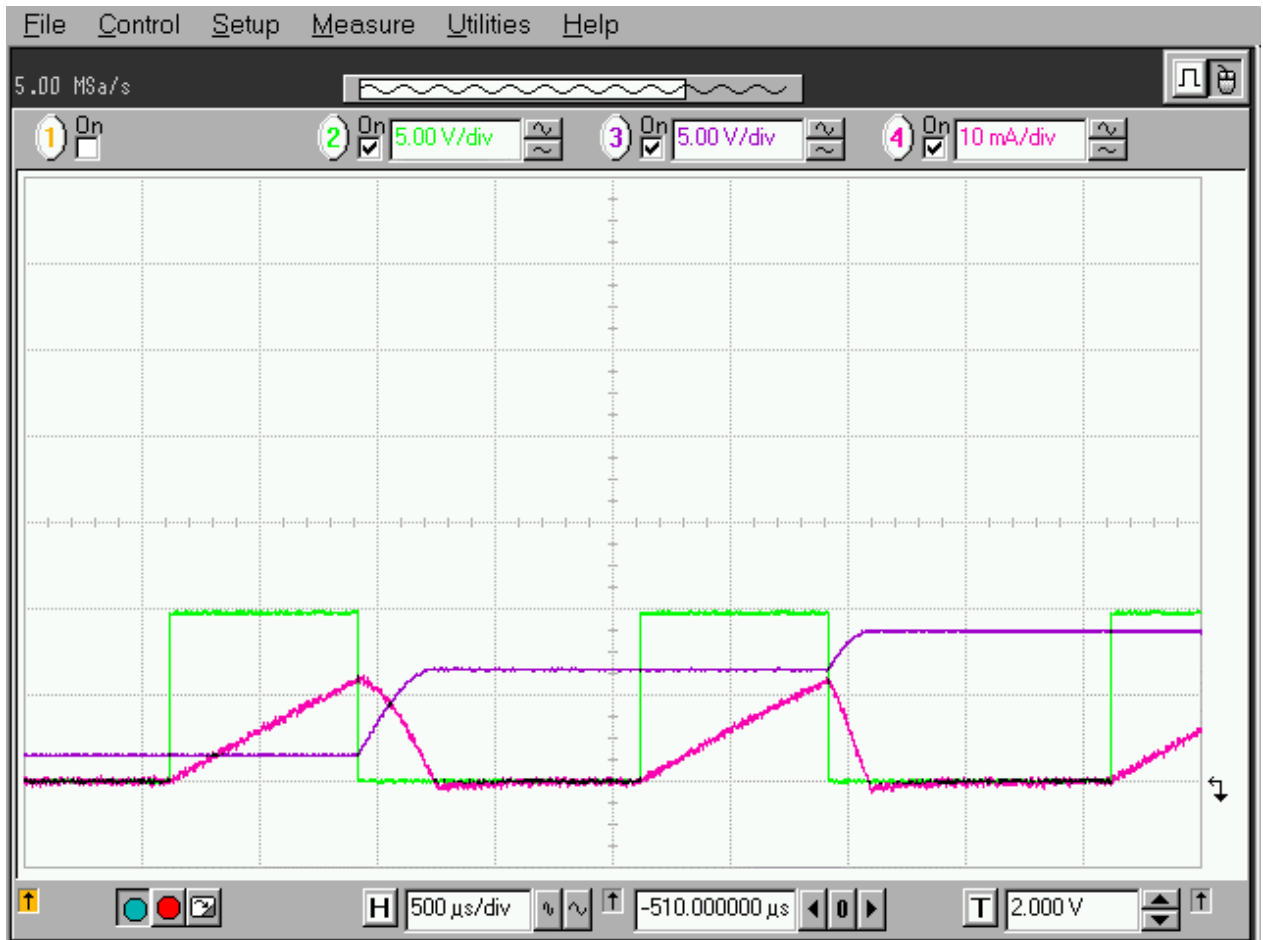


Green: S1 switch state (high = on and low = off)

Red: inductor current (10 mA/division)

Purple: capacitor voltage (5 V/division)

# Operation

First fifty switching cycles

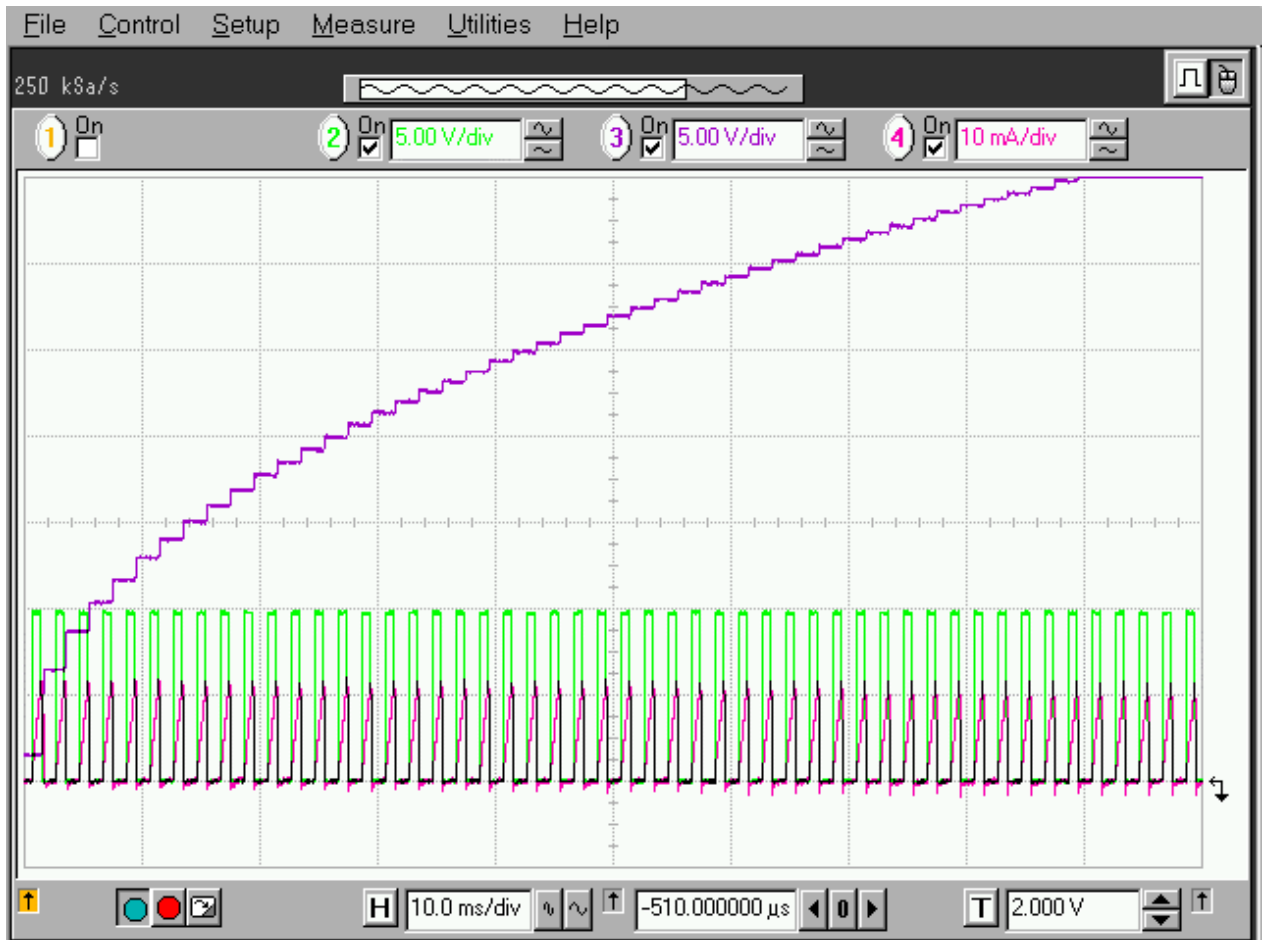

Green: S1 switch state (high = on and low = off)  
Red: inductor current (10 mA/division)  
Purple: capacitor voltage (5 V/division)

# Simulation

This simulation omits all losses:  
inductor, scope, transistor and diode.

