


6.200 - Lecture 26

Coupled Resonators


- Transformers
- Resonators
- Coupled Resonators
- Tesla Coil
- Wireless Power Xfer

Transformer Summary

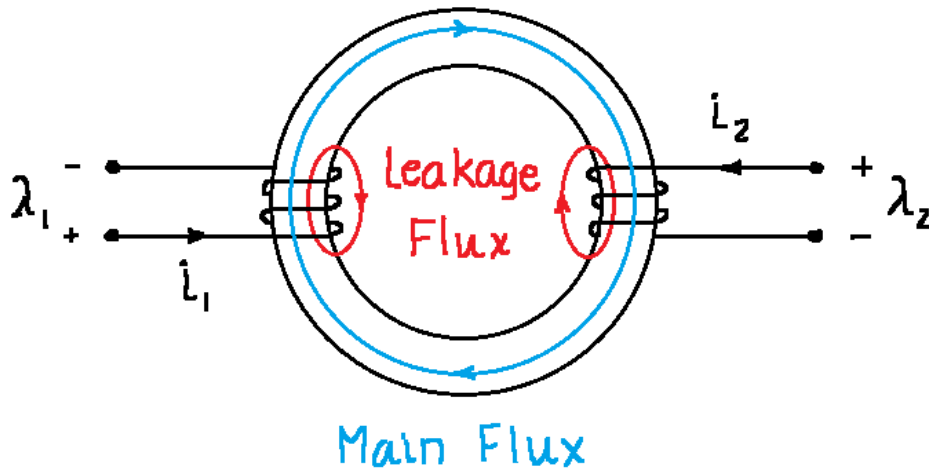A transformer is a pair (or more) of magnetically-coupled inductors.


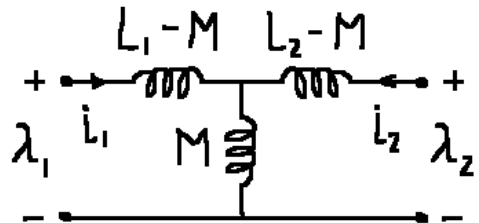
$$\begin{bmatrix} \lambda_1 \\ \lambda_2 \end{bmatrix} = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



L = Self inductance


M = Mutual inductance

$$= k\sqrt{L_1 L_2}$$


k = Fraction of magnetic flux produced by one winding that passes through the other

Simple model omits isolation

Two Poorly-Coupled Transformers

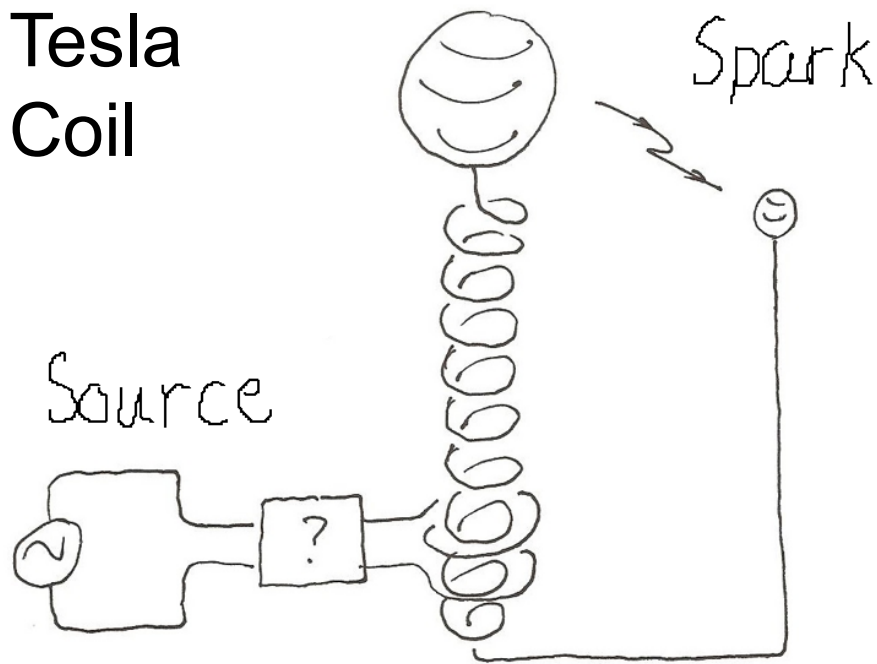


Wireless Power Transfer

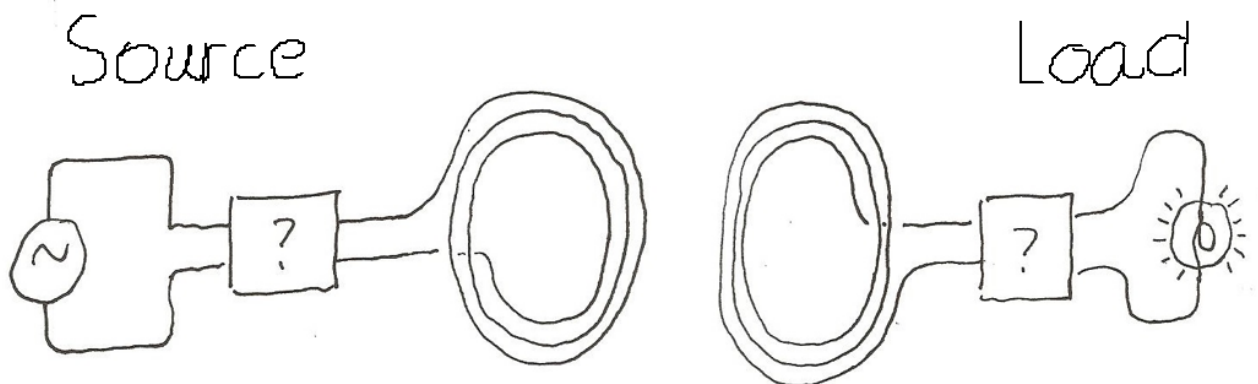



Demo: Tesla Coil

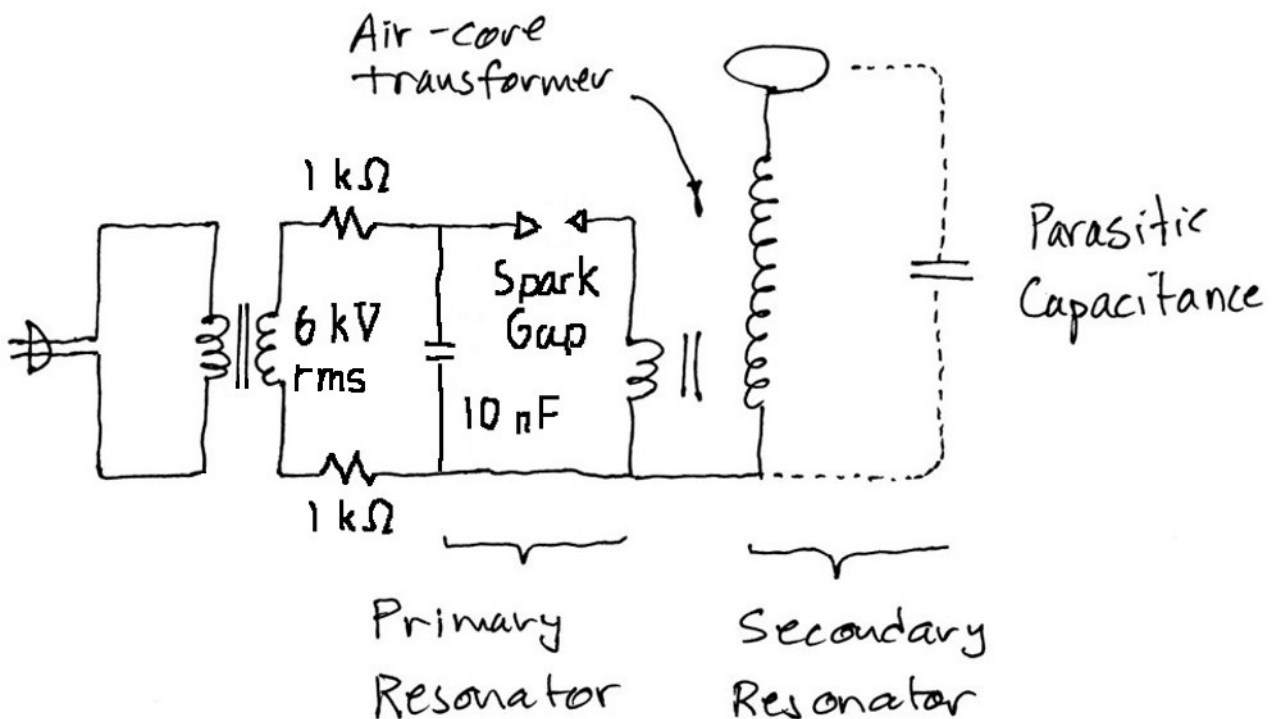The Tesla Coil employs two coupled resonators, with both resonators tuned to the same frequency.



The resistors protect the transformer, which charges the capacitor (+/-) at 120 Hz. When the capacitor voltage gets high enough, the spark gap sparks, and becomes a short allowing the LC resonator to oscillate, driving the rest of the Tesla coil.


Demo: Tesla Coil

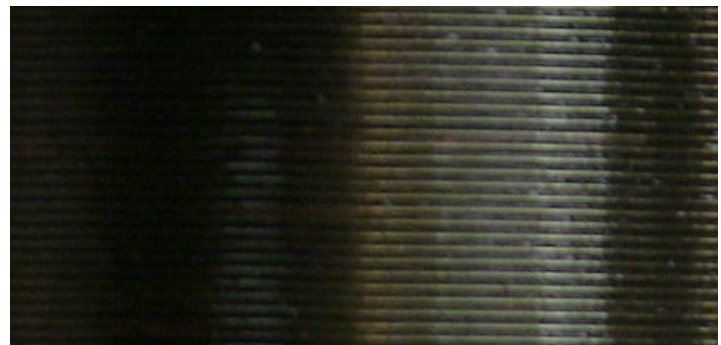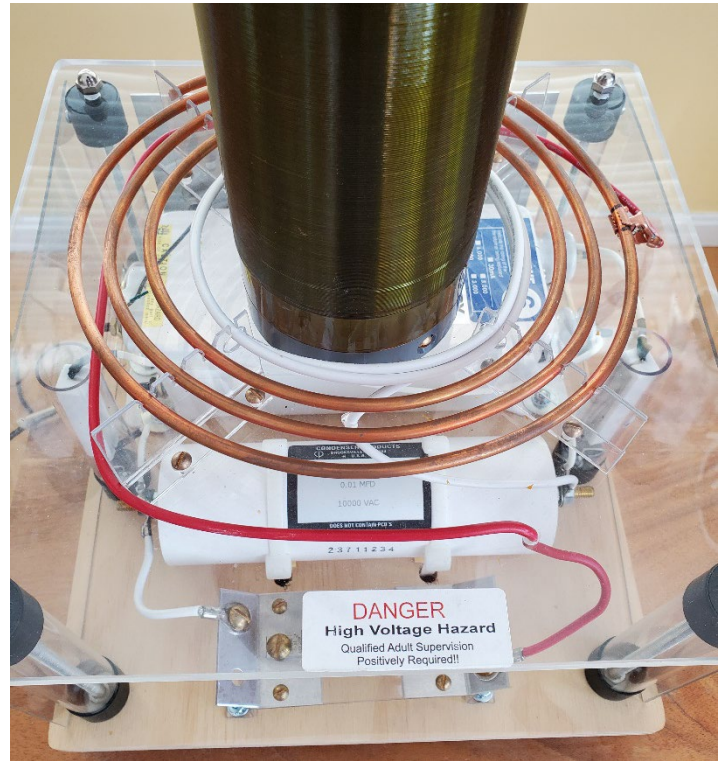

Demo: Key Design Features

- The use of a coreless transformer prevents core loss and arcing to the core, and aids in achieving a low coupling factor
- The dome is smoothed to prevent premature breakdown, and sized for a small secondary capacitance
- The secondary winding geometry results in a high inductance, while using a single layer to prevent turn-to-turn breakdown
- The primary winding geometry results in a low inductance and a low coupling factor
- The primary capacitance is large
- The primary and secondary resonance frequencies are tuned to be equal
- The driving step-up transformer provides 6 kV rms, and recharges the primary capacitor twice per mains cycle.

Tesla Coil Circuit Design

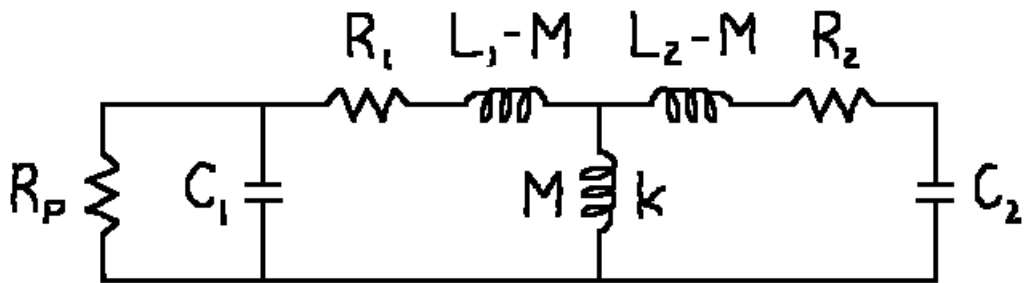

$$L_1 = 7.62 \mu\text{H (Measured)}$$

$$L_2 = 5.24 \text{ mH (Measured)} = L_1 \times 688$$

$$C_1 = 10 \text{ nF (Measured)}$$

$$C_2 = 14 \text{ pF (Estimated)} = C_1 / 688$$

$$1/2\pi\sqrt{L_1 C_1} = 1/2\pi\sqrt{L_2 C_2} = 582 \text{ kHz}$$

$$\sqrt{L_1 / C_1} = 27.6 \Omega$$

$$\sqrt{L_2 / C_2} = 19.3 \text{ k}\Omega$$

$$R_1 = 17 \text{ m}\Omega \text{ (Measured)}$$

$$R_2 = 10.8 \Omega \text{ (Measured)}$$

$$R_p = 2000 \Omega \text{ (Measured)}$$



$$4\pi\epsilon_0 (\text{Dome Diameter}) = 11 \text{ pF}$$

$$k = ? \approx 0.1$$



$$R_p C_1 = 20 \mu\text{s}$$

Coupled Resonator Simulation

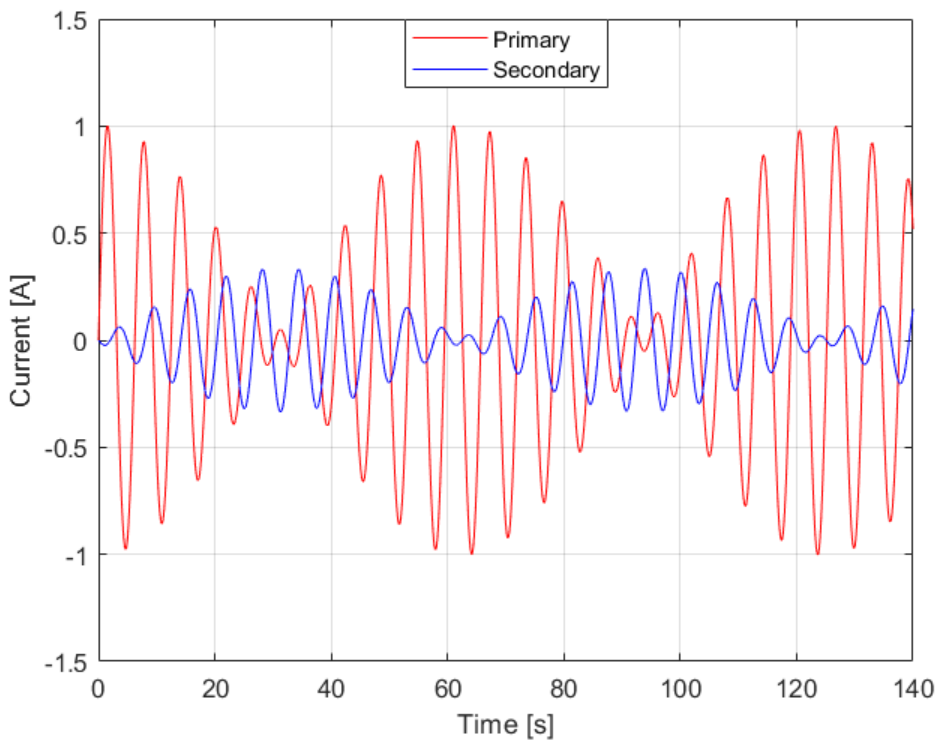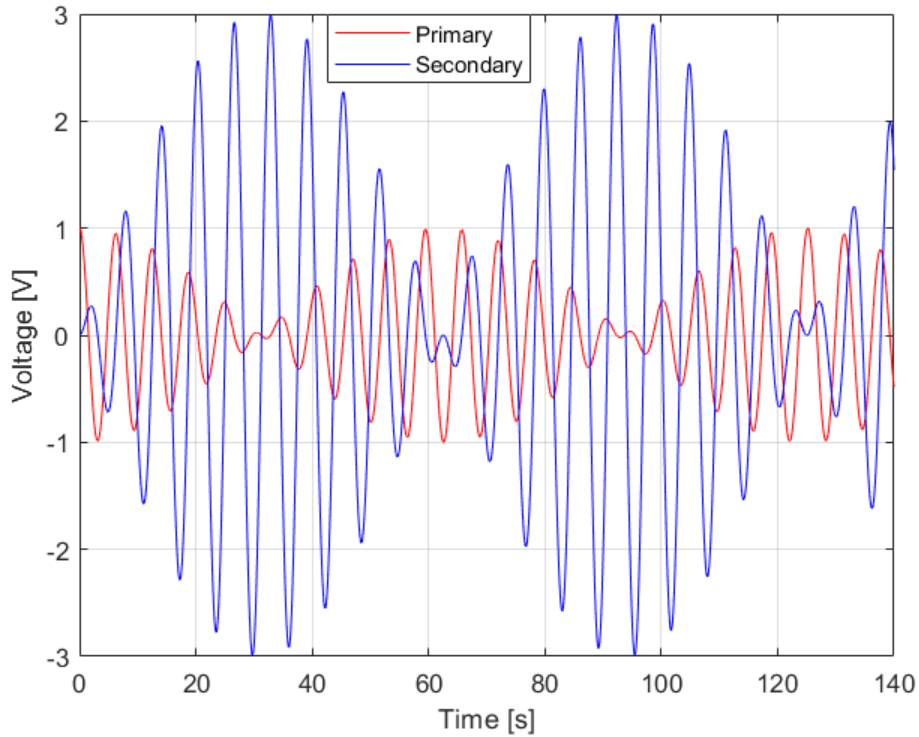$C1 = 1 \text{ F}$; $C2 = 1/9 \text{ F}$; $L1 = 1 \text{ H}$; $L2 = 9 \text{ H}$; $k = 0.1$







Wireless Power Transfer

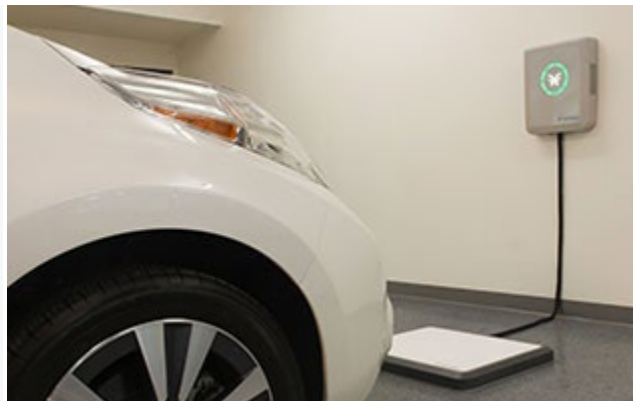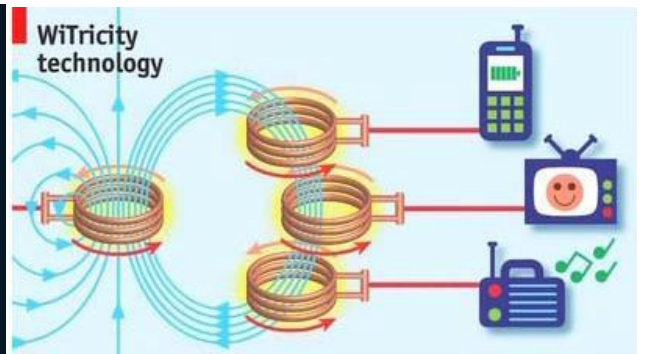


Wireless Power Transfer

Matched
coils

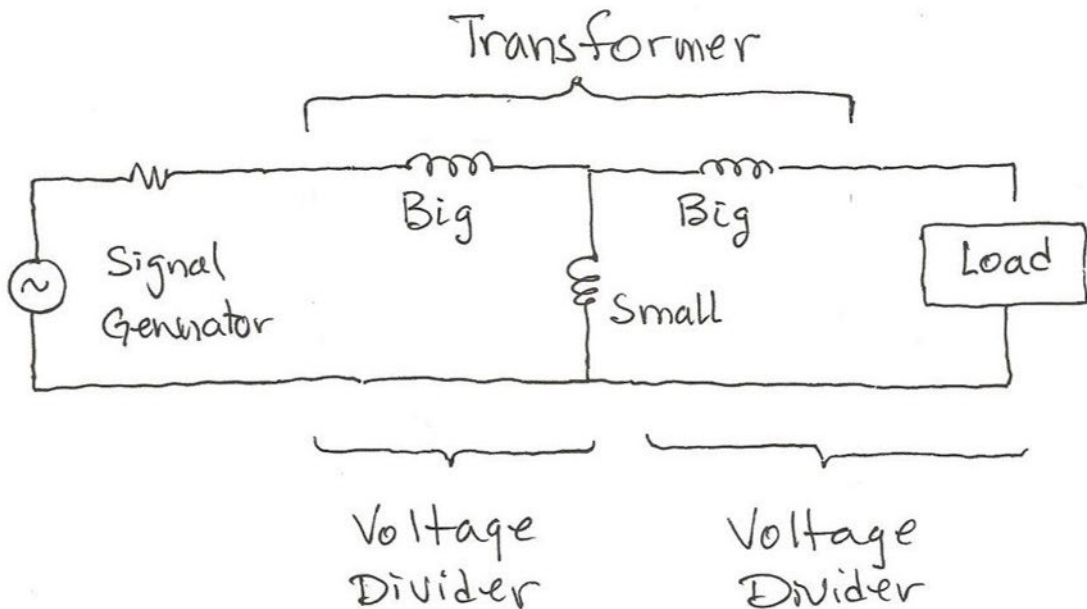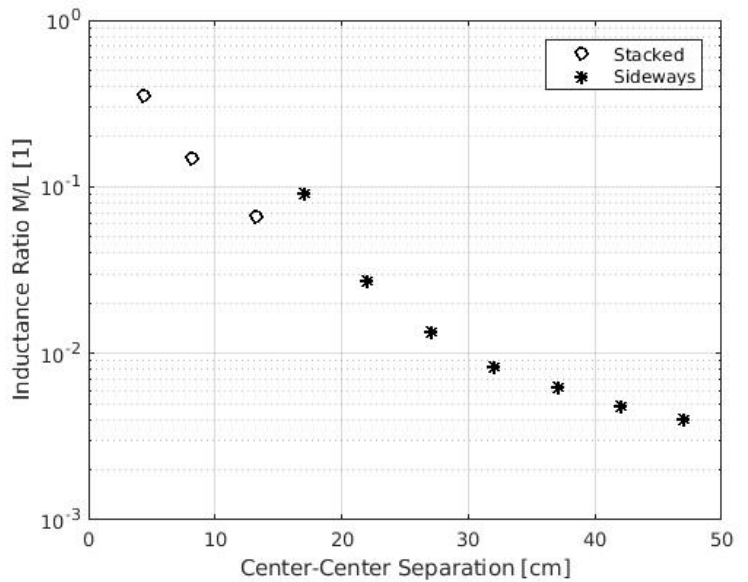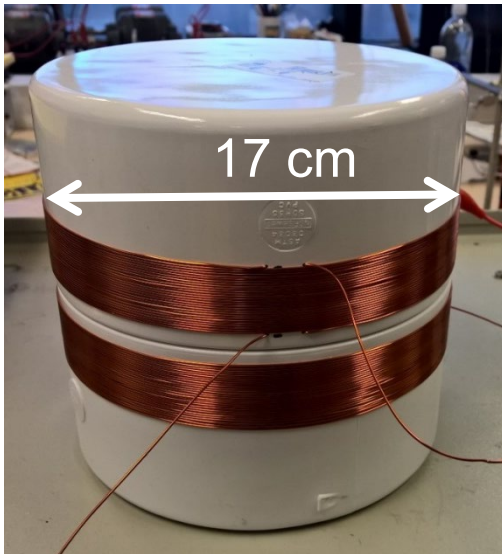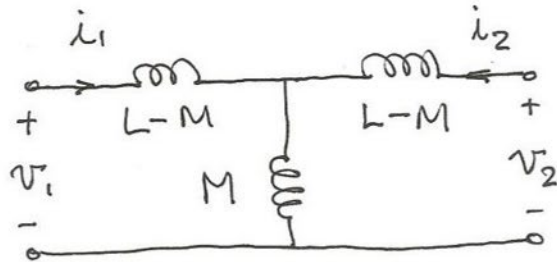


Wireless Power Transfer Approach

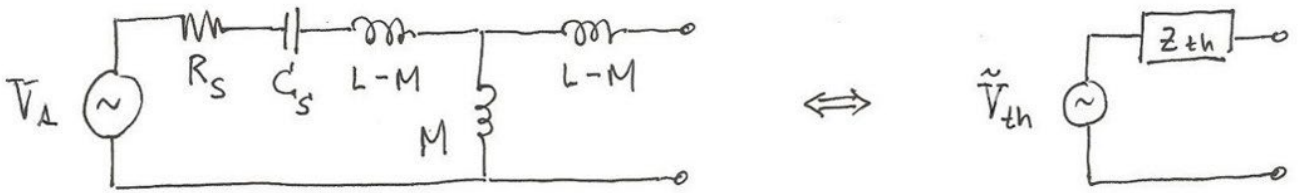

Choose $L-C_S$ resonance $\Rightarrow \omega L = 1/\omega C_S$

$$\tilde{V}_{th} = \frac{j\omega M \tilde{V}_A}{R_S + \frac{1}{j\omega C_S} + j\omega L} = \frac{j\omega M}{R_S} \tilde{V}_A$$

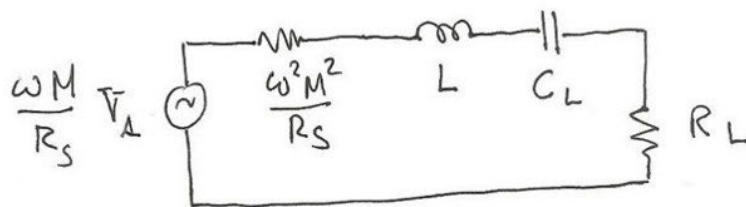
$$Z_{th} = j\omega(L-M) + \frac{j\omega M (R_S + \frac{1}{j\omega C_S} + j\omega L - j\omega M)}{R_S + \frac{1}{j\omega C_S} + j\omega L} = \frac{\omega^2 M^2}{R_S} + j\omega L$$



Choose $L-C_L$ resonance $\Rightarrow \omega L = 1/\omega C_L$, and


$R_L = \frac{\omega^2 M^2}{R_S}$ to achieve maximum power transfer.

Double resonators!

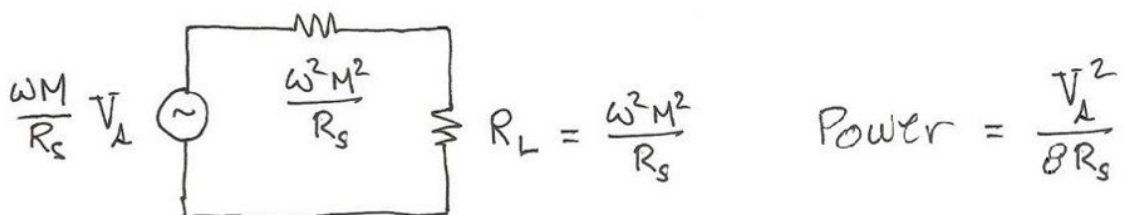

Matching Network

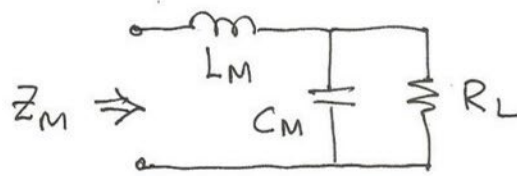What if $R_L \neq \frac{\omega^2 M^2}{R_S}$? Matching network!



$$\begin{aligned} Z_M &= \frac{R_L \frac{1}{j\omega C_M}}{R_L + \frac{1}{j\omega C_M}} + j\omega L_M = \frac{R_L - j\omega R_L^2 C_M}{1 + \omega^2 R_L^2 C_M^2} + j\omega L_M \\ &= \frac{R_L}{1 + \omega^2 R_L^2 C_M^2} - \frac{j\omega R_L^2 C_M}{1 + \omega^2 R_L^2 C_M^2} + j\omega L_M \end{aligned}$$


Choose C_M to reduce R_L , and L_M to obtain zero reactance.

For a substantial reduction of R_L ,

$$\omega^2 R_L^2 C_M^2 \ll 1 \Rightarrow Z_M \approx \frac{R_L}{\omega^2 R_L^2 C_M^2} + \frac{1}{j\omega C_M} + j\omega L_M$$

Demo

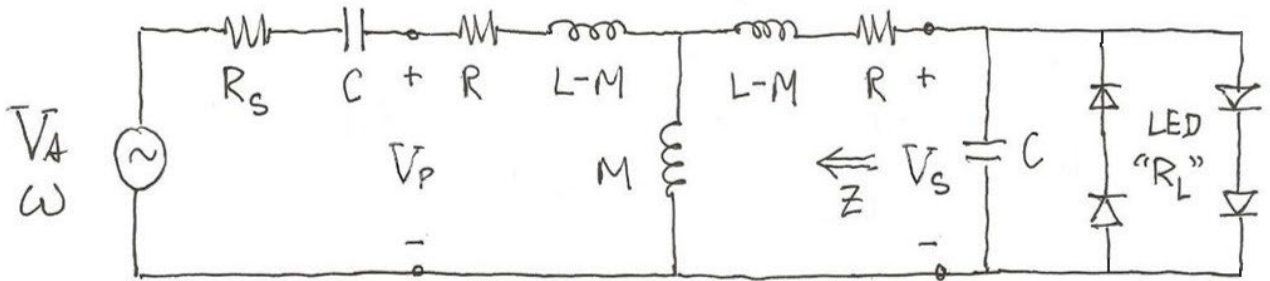For an LED load, voltage is more important than load matching, so choose a resonator output over a load matching output.



$$\tilde{V}_S = 10 V_{Pk}$$

$$L = 230 \mu H$$

$$C = 9.6 nF$$

$$\omega = 2\pi \cdot 107.1 \frac{\text{krad}}{\text{s}}$$

$$M \sim \frac{L}{10} \text{ to } \frac{L}{200}$$

$$R_L \sim 1 k\Omega \text{ to } 5 k\Omega$$

$$R_S = 50 \Omega$$

$$R = 0.5 \Omega$$

$$\bullet \omega \equiv \frac{1}{\sqrt{LC}}$$

$$\bullet \text{Primary } Q = \sqrt{L/C} / R_S = 3 \Rightarrow \tilde{V}_P = 30 \tilde{V}_{Pk}$$

$$\bullet \text{For large separation, } Z \approx R + j\omega L \Rightarrow$$

$$\text{Secondary parallel } Q \approx R_L / \sqrt{L/C} \approx 20$$

$$\text{Secondary series } Q \approx \sqrt{L/C} / R \approx 300$$

$$\bullet \tilde{V}_{th} = \frac{\omega M}{R_S} \tilde{V}_A \approx \frac{M}{L} 30 \tilde{V}_{Pk}$$

What Comes After 6.200?

- Labs:
 - 6.204 [6.101] analog systems
 - 6.205 [6.111] digital systems
 - 6.206 [6.115] microcomputer systems
 - 6.222 [6.131] power electronics
- Classroom:
 - 6.208 analog circuits
 - 6.209 [6.301] advanced analog circuits
 - 6.220 electric energy systems
 - 6.250 [6.012] nanoelectronics and computing
 - 6.600 [6.775] analog and mixed-signal CMOS
 - 6.601 [6.374] digital integrated circuits
 - 6.602 [6.776] high-speed integrated circuits
 - 6.622 [6.334] power electronics
 - 6.650 [6.720] integrated microelectronic devices