

6.200 Circuits and Electronics

Week 3 Lecture A:
Thevenin and Norton







