

Name: SOLUTIONS

Kerberos Username: _____

Sketch $v_c(t) = V_0 e^{-t/RC}$ and label $v_c(t)$:

