

# 6.200 Circuits and Electronics

## Week 6, Lecture A: Operational Amplifiers


Grab participation sheet by the door.

Midterm: Tuesday after the break (info and review materials on web).

No p-set this week.
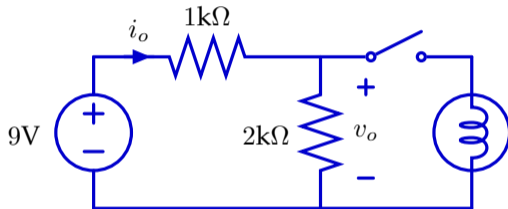
## Loading


Circuit design is complicated by interactions among the elements. Adding an element changes voltages and current *throughout* the circuit. For example, what happens when the switch is closed in the following circuit (effectively adding the light bulb as a new component)?



0.  $v_o$  and  $i_o$  stay the same
1.  $v_o$  decreases,  $i_o$  decreases
2.  $v_o$  decreases,  $i_o$  increases
3.  $v_o$  increases,  $i_o$  decreases
4.  $v_o$  increases,  $i_o$  increases
5. depends on the bulb's resistance
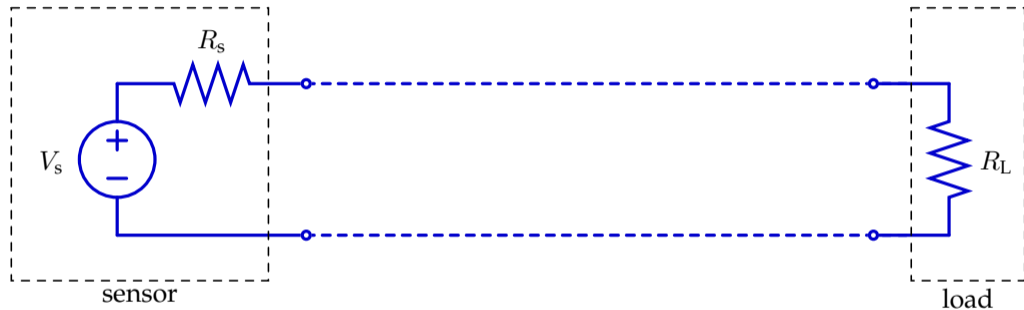
## Memories...


Consider an arbitrary sensor with a small output voltage, driving a load of some kind:



What is the problem here?
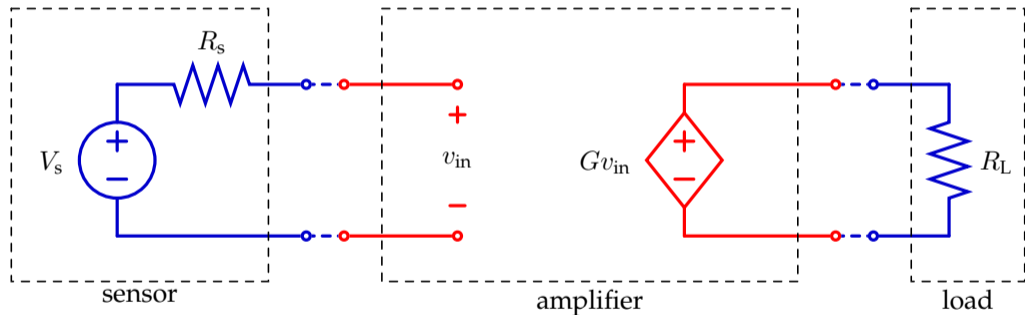
# Amplifiers



We could resolve this issue by building a circuit that behaves like the following, to isolate the sensor and the load (and also scale up the sensor's voltage):



Goals:  $v_{load} = G \times V_s$ , where  $G$  is adjustable and reliable
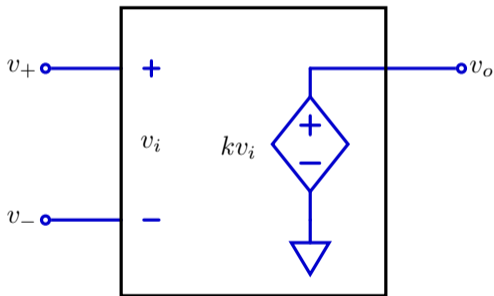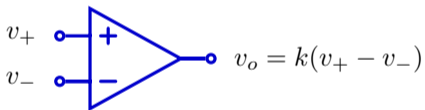
# Operational Amplifiers


An operational amplifier (“op-amp”) can be modeled\* as a voltage-controlled voltage source, where  $k$  is intentionally large (typically  $\sim 10^5 - 10^7$ ):



\* sometimes


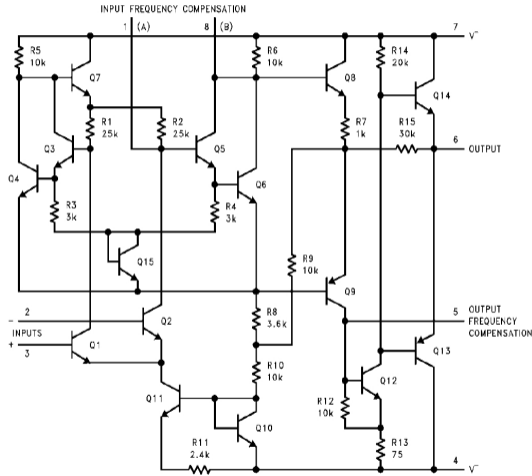
# Operational Amplifiers

What's *actually* in an op-amp? Here is a more accurate circuit model of a  $\mu A709$  op-amp:



But that's a pain...

# Characterizing an Op-amp (VCVS Model)

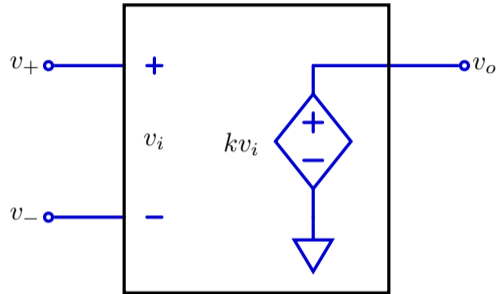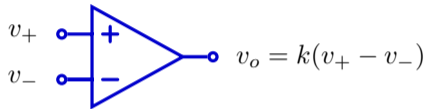

$$v_o = k(v_+ - v_-)$$


$$i_+ = i_- = 0$$

Sketch a graph of  $v_o$  versus  $(v_+ - v_-)$

## Supply Rails

Op-amps derive power from connections to a power supply, and the output voltage is typically constrained by that power supply:


$$V_{S-} < v_o < V_{S+}$$

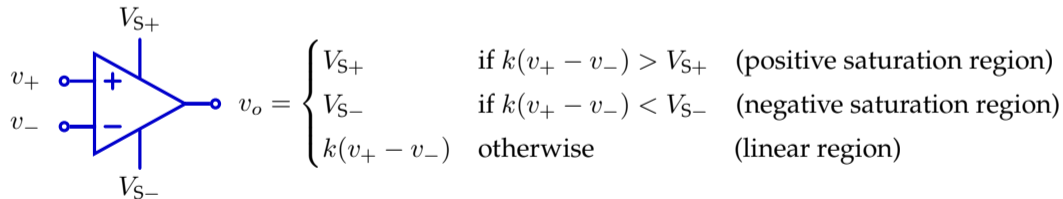


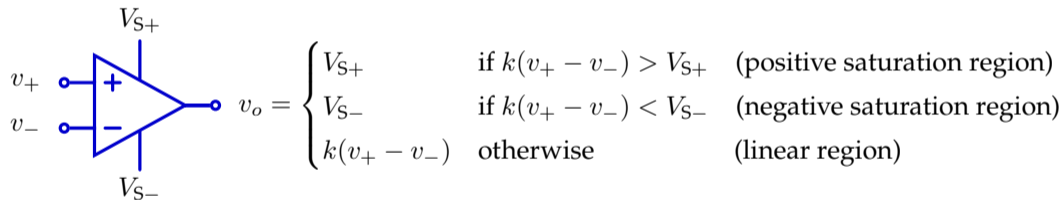
## Op-Amps as Comparators


Other than the (tiny) range of  $v_+ - v_-$  values where we're operating in the linear region, the op-amp's output voltage will be forced to one or the other of the supply rails, so the op-amp naturally behaves as a comparator:




Under (approximately) what conditions is the output equal to  $V_{CC}$ ?

Under (approximately) what conditions is the output equal to  $V_{EE}$ ?

## Check Yourself

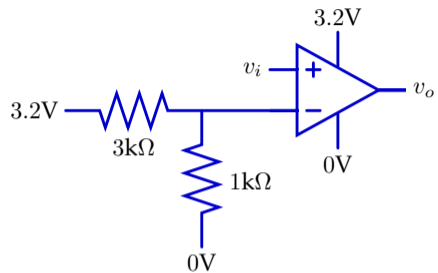

## Check Yourself

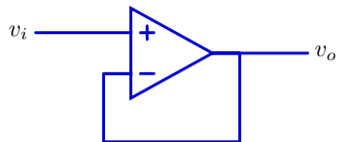

## Check Yourself

