

Massachusetts Institute of Technology
Department of Electrical Engineering and Computer Science

6.200 – Circuits & Electronics
Spring 2026

Final Exam

20 May 2026


Name: Solutions

MIT EMail: _____@MIT.EDU



- There are 19 pages in this quiz, including this cover page.
- Please put your name and MIT EMail ID in the spaces provided above.
- Please do not remove any pages from this quiz.
- Do your work for each question within the boundaries of that question, or on the back of the preceding page.
- *This exam cannot be re-graded. Therefore, do your work in a neat and organized manner so that it can be easily understood. When finished with each part, clearly write your answer for that part into the corresponding answer box or graph.*
- *All numerical answers require proper units.*
- *In order to guarantee receipt of full credit, all answers should be justified by supporting math and/or explanations.*
- This is a closed-book closed-electronics quiz but a single two-sided page of notes is allowed.
- Good luck!

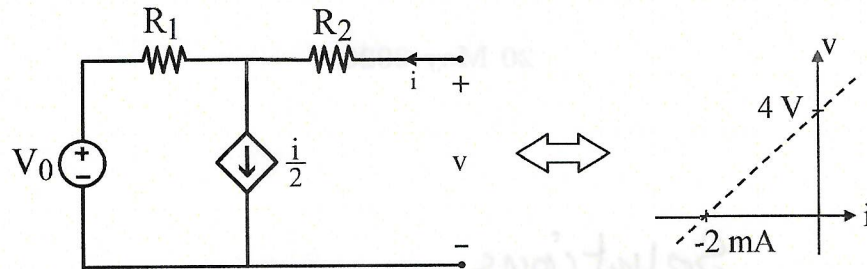Problem 1: Unknown Parameters - 10%

The network shown below comprises an independent voltage source, a dependent current source, and two resistors. All devices but the dependent current source have unknown values. The network also has a port at which the $i-v$ relation is as shown below. Finally, it is known that R_1 dissipates 2 mW when $v = 0$. Using the information given, determine the unknown values V , R_1 and R_2 .



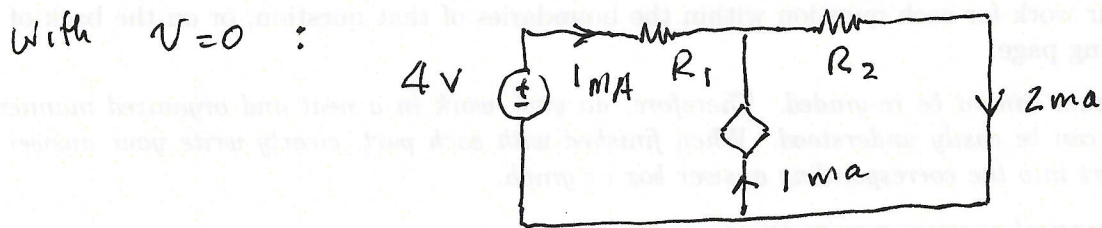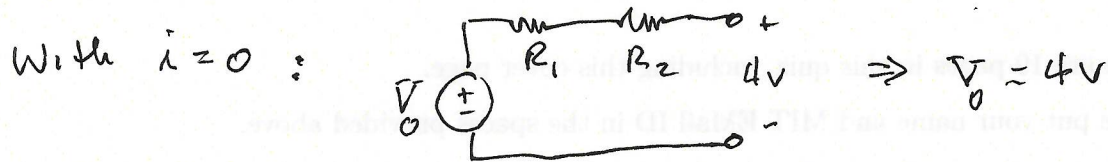$V_0 = 4 \text{ V}$ $R_1 = 2 \text{ k}\Omega$ $R_2 = 1 \text{ k}\Omega$




$R_1 \text{ power} = (1 \text{ mA})^2 R_1 = 2 \text{ mW} = R_1 = 2 \text{ k}\Omega$

and the R_1 voltage drop is 2 V, So

$R_2 = 2 \text{ V} / 2 \text{ mA} = 1 \text{ k}\Omega$

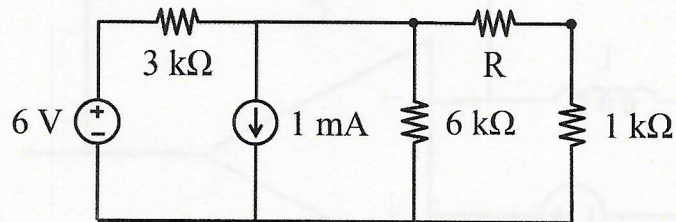Problem 2: Maximum Power Transfer - 10%


The network shown below contains a resistor having an unknown resistance R . Determine the numerical value of R that maximizes the power dissipated in that resistor. Additionally, determine the maximized power.



$$R = 3 \text{ k}\Omega$$

$$\text{Power} = \frac{1}{3} \text{ mW}$$

Thevenin equivalence \Rightarrow

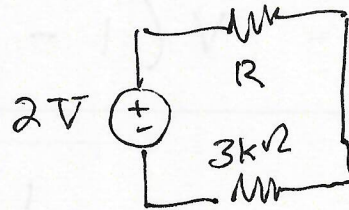


So, for maximum power, $R = 3 \text{ k}\Omega$ and

$$\text{the power is } \left(\frac{2\text{V}}{2}\right)^2 / 3 \text{ k}\Omega = \frac{1}{3} \text{ mW}.$$

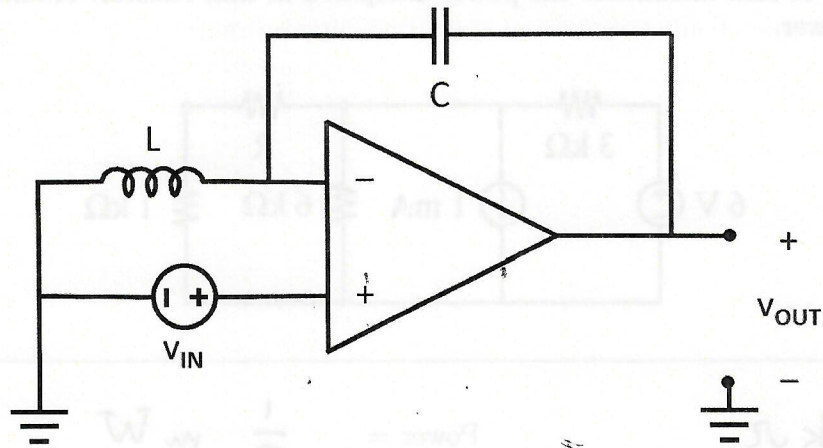Problem 3: Op Amp With LC Twice - 15%

Both parts of this problem concern the circuit shown below in which the op amp is ideal.



- (3A) Let $v_{IN} = V \cos(\omega t)$. Further, assume that v_{OUT} has a zero-valued time average. Determine v_{OUT} in the sinusoidal steady state.


$$v_{OUT} = V \left(1 - \frac{1}{\omega^2 LC} \right) \cos(\omega t)$$

$$\tilde{v}_{out} = \frac{j\omega L + \frac{1}{j\omega C}}{j\omega L} \tilde{v}_{in} = \left(1 - \frac{1}{\omega^2 LC} \right) \tilde{v}_{in}$$

$$\Rightarrow v_{out} = V \left(1 - \frac{1}{\omega^2 LC} \right) \cos(\omega t)$$

- (3B) Assume that for $t < 0$, $V_{IN} = 0$ so that the capacitor voltage and inductor current are both zero. Then, at $t = 0$, V_{IN} steps up to $V_{IN} = V$ where V is constant. Determine v_{OUT} for $t \geq 0$.
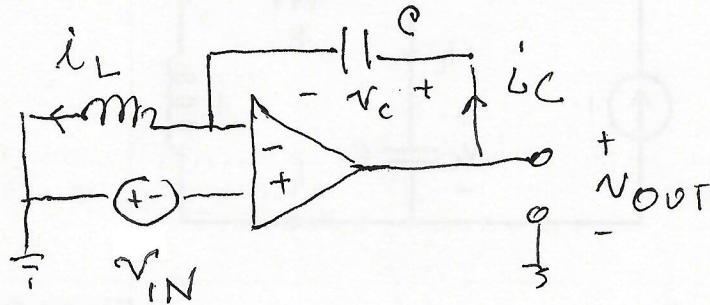
$$v_{OUT} = V \left(1 + \frac{t^2}{2LC} \right)$$



$$V = v_{IN} = v_+ = v_- = L \frac{di_L}{dt} \Rightarrow i_L = i_C = \frac{Vt}{L}$$

$$= C \frac{dv_C}{dt} \Rightarrow v_C = \frac{1}{2} \frac{Vt^2}{LC}$$

$$\text{Finally, } v_{OUT} = v_{IN} + v_C = V \left(1 + \frac{t^2}{2LC} \right)$$

$$\uparrow$$

$$\dots = v_+ = v_- \equiv V$$

Problem 4: RLC Transient - 25%

The circuit shown below is initially at rest such that $v_C = 0$ and $i_L = 0$ for $t < 0$. At $t = 0$, the current source steps up to $I = 1$ A. The figures shown below plot four waveforms within the circuit following the current step. Their horizontal axes all show time measured in seconds [s]. Their vertical axes show either voltage measured in Volts [V] or current measured in Amperes [A], as appropriate. *Note that the initial slopes of the waveforms in Figures 1 and 3 are positive, while the initial slopes of the waveforms in Figures 2 and 4 are zero.*

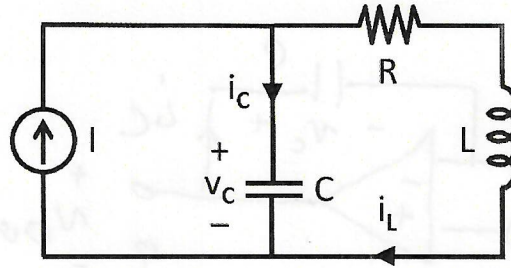


Figure 1

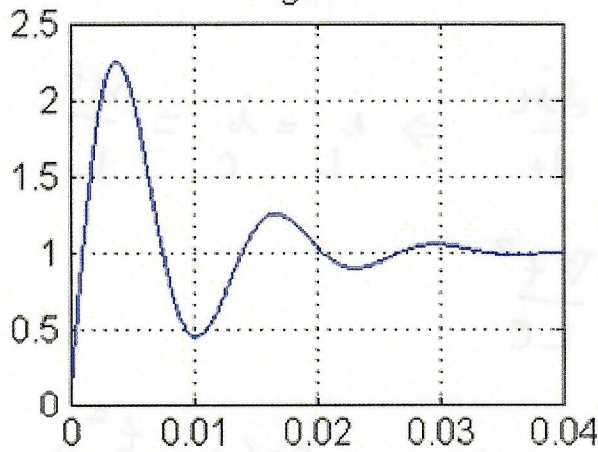


Figure 2

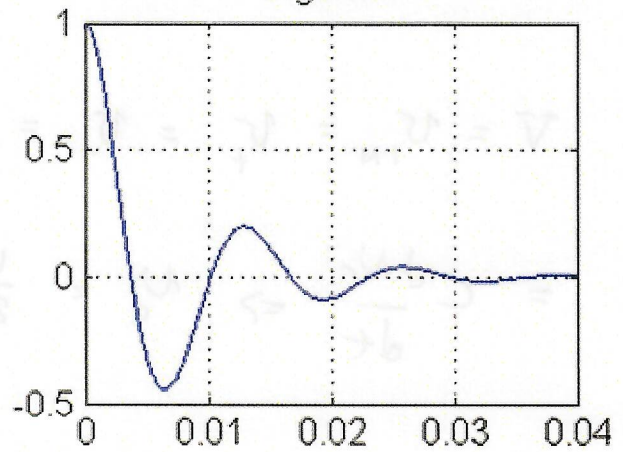


Figure 3


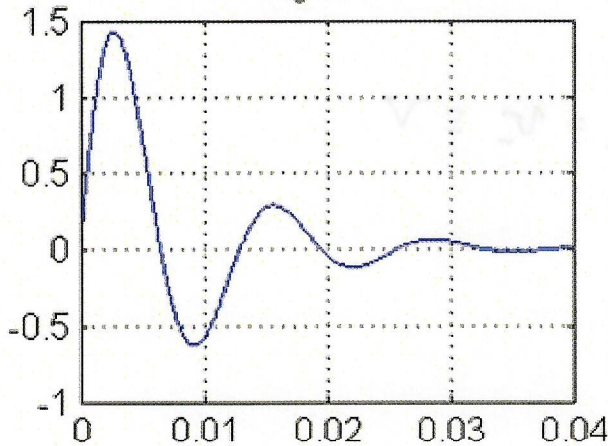


Figure 4

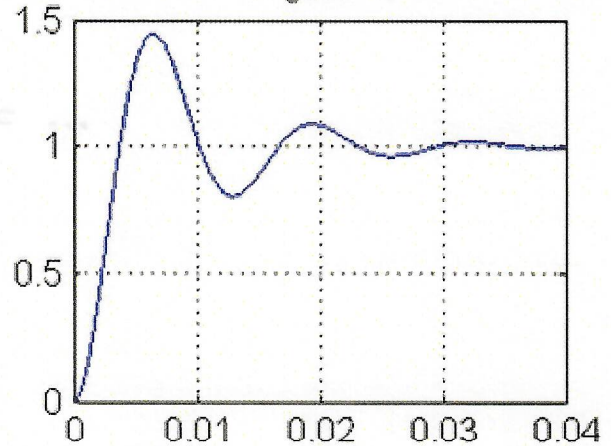

(4A) For each variable listed below, identify the corresponding figure by circling the figure number. Briefly explain your reasoning in the space below.

$v_C \rightarrow$ Figure	<u>1</u>	2	3	4
$i_C \rightarrow$ Figure	1	<u>2</u>	3	4
$i_L \rightarrow$ Figure	1	2	3	<u>4</u>

At $t=0$, the source current goes entirely through the capacitor. Only Figure 2 shows this behavior. At $t=0$, therefore, the capacitor voltage increases linearly. As $t \rightarrow \infty$ it settles to $R \cdot I_A$. Only Figure 1 shows this behavior. At $t=0$, the inductor current is proportional to the integral of the capacitor

Explain: voltage, and hence grows quadratically.

It settles to $2A$ as $t \rightarrow \infty$. Only Figure 4 shows this behavior. Figure 3 is the inductor voltage.

(4B) Estimate the value of R .

$$R = 1 \Omega$$

$$U_c(\infty) = R \cdot I_A. \text{ From Figure 1, } R = 1 \Omega$$

(4C) Estimate the value of C .

$$C = 0.001 \text{ F}$$

The figures show that about 1.5 cycles of oscillation take approximately 20 ms. Therefore

$$2\pi\sqrt{LC} \times 1.5 \approx 20 \text{ ms or } \sqrt{LC} \approx 2 \text{ ms.}$$

Combining 4B and 4E, $\sqrt{\frac{L}{C}} \approx 2 \Omega$. Thus,

$$C \approx \frac{2 \text{ ms}}{2 \Omega} = 0.001 \text{ F}$$

(4D) Estimate the value of L .

$$L = 0,004 \text{ H}$$

Following 4C, $L \approx 2 \text{ ms} \cdot 2 \Omega \approx 0,004 \text{ H}$

(4E) Estimate the quality factor Q of the circuit.

$$Q = 2$$

It takes approximately Q cycles of oscillation for a signal to drop to 4% of its original amplitude. Thus, it takes about $Q/2$ cycles to drop to 20%. From the figures all signals drop to about 20% of their original amplitude in just one cycle. Therefore, $Q \approx 2$. Note that $Q = \sqrt{L/C} / R$ for a series resonator.

(4F) For each statement below, circle the correct completion. Briefly explain your reasoning in the space below.

- If the resistance R is increased, the quality factor Q will ...

... increase. ... decrease. ... remain unchanged.

- If the capacitance C is increased, the quality factor Q will ...

... increase. ... decrease. ... remain unchanged.

- If the inductance L is increased, the quality factor Q will ...

... increase. ... decrease. ... remain unchanged.

Explain:

$$Q = \frac{\sqrt{LC}}{R}$$

(4G) For each statement below, circle the correct completion. Briefly explain your reasoning in the space below.

- If the resistance R is increased, the period of oscillation will ...

... increase. ... decrease. ... remain unchanged.

- If the capacitance C is increased, the period of oscillation will ...

... increase. ... decrease. ... remain unchanged.

- If the inductance L is increased, the period of oscillation will ...

... increase. ... decrease. ... remain unchanged.

The oscillations come from the natural (homogeneous) response of the network.

Explain:

$$\text{KVL} \Rightarrow 0 = v_c + R\left(C\frac{dv_c}{dt}\right) + L\frac{d}{dt}\left(C\frac{dv_c}{dt}\right)$$

$$\Rightarrow \ddot{v}_c + \frac{R}{L}\dot{v}_c + \frac{1}{LC}v_c = 0$$

$$v_c \sim e^{st} \Rightarrow s = -\frac{R}{2L} \pm j \underbrace{\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}}_{\omega_D}$$

$$\text{Period} = \frac{2\pi}{\omega_D}$$

(4H) After a long time T , the current source steps down to turn off. For each statement below concerning the subsequent decay of stored energy, circle the correct completion. *Briefly explain your reasoning in the space below.*

- If the resistance R is increased, the time at which the stored energy falls to half its value at time T will ...

... increase. ... decrease. ... remain unchanged.

- If the capacitance C is increased, the time at which the stored energy falls to half its value at time T will ...

... increase. ... decrease. ... remain unchanged.

- If the inductance L is increased, the time at which the stored energy falls to half its value at time T will ...

... increase. ... decrease. ... remain unchanged.

From $4G$, $S = -\frac{R}{2L} \pm j \sqrt{\frac{1}{Lc} - \left(\frac{R}{2L}\right)^2}$



↑
Decay rate

Decay time $\sim \frac{L}{R}$

Explain:

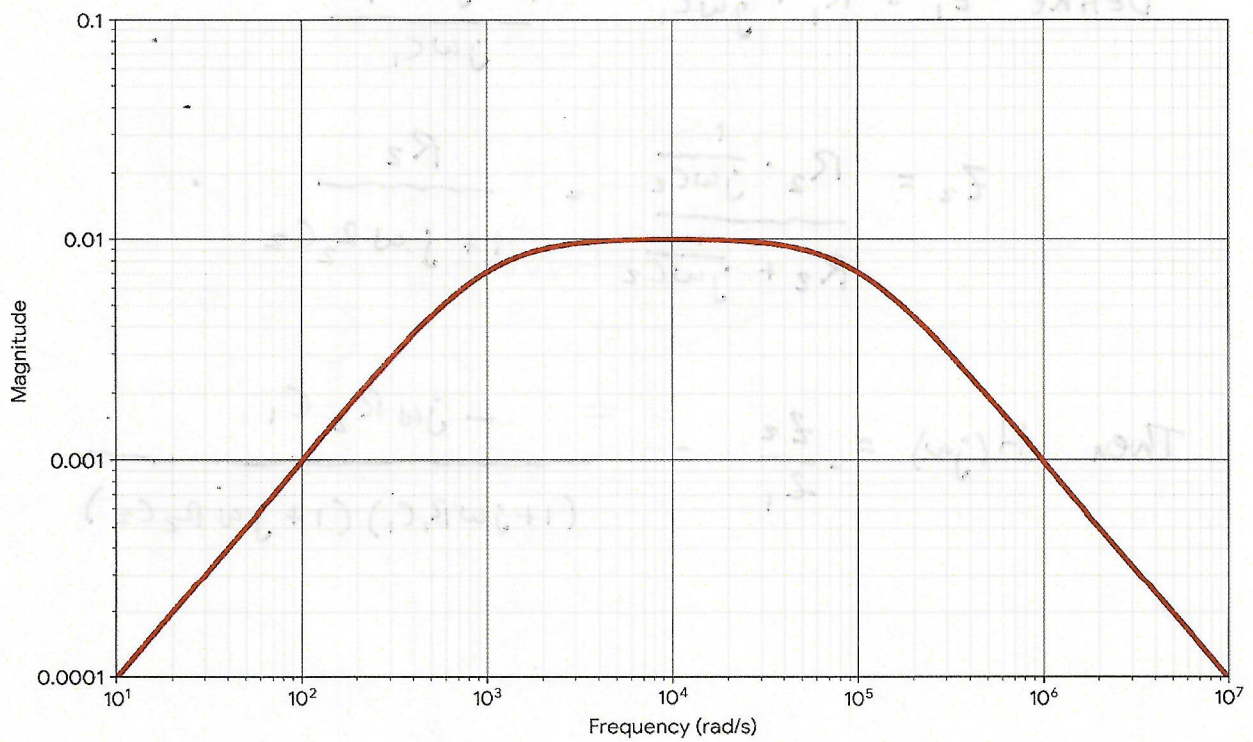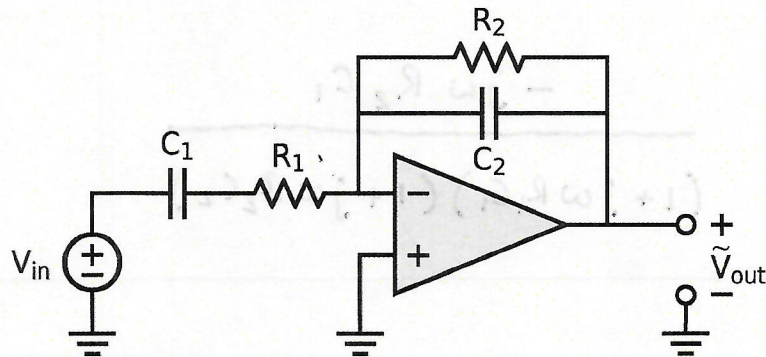Problem 5: RC Filter - 20%

This problem concerns the filter shown below together with a measurement of its transfer function.



- (5A) Determine the symbolic transfer function $H(j\omega) \equiv \tilde{V}_{\text{out}}/\tilde{V}_{\text{in}}$ in terms of R_1 , R_2 , C_1 , and C_2 where \tilde{V}_{in} and \tilde{V}_{out} are the complex amplitudes of $v_{\text{IN}}(t)$ and $v_{\text{OUT}}(t)$, respectively, when operating in the sinusoidal steady state.

$$H(j\omega) = \frac{-j\omega R_2 C_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$

$$\text{Define } Z_1 = R_1 + \frac{1}{j\omega C_1} = \frac{1 + j\omega R_1 C_1}{j\omega C_1}$$

$$Z_2 = \frac{R_2 \cdot \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{R_2}{1 + j\omega R_2 C_2}$$

$$\text{Then } H(j\omega) = -\frac{Z_2}{Z_1} = \frac{-j\omega R_2 C_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$

- (5B) Assume that $C_1 = C_2 = 1\mu\text{F}$. Determine numerical values for R_1 and R_2 from the measured transfer function.

$$R_1 = 1\text{ k}\Omega \qquad R_2 = 10\ \Omega$$

$$\text{Low frequencies} \Rightarrow |H| = 10^{-5} \frac{\text{s}}{\text{rad}} \cdot \omega = \omega R_2 C_1.$$

$$\text{With } C_1 = 10^{-6} \text{ F}, R_2 = 10\ \Omega.$$

$$\text{High frequencies} \Rightarrow |H| = 10^3 \frac{\text{rad}}{\text{s}} / \omega = \frac{1}{R_1 C_2 \omega}.$$

$$\text{With } C_2 = 10^{-6} \text{ F}, R_1 = 1000\ \Omega$$

- (5C) Suppose the filter is excited with the input $v_{\text{IN}}(t) = \tilde{V}_{\text{in}} \cos(\omega t + \phi)$, where $\tilde{V}_{\text{in}} = 5 \text{ V}$, $\omega = 10^4 \text{ rad/s}$, and $\phi = \pi/4 \text{ rad}$. Determine a numerical expression for $v_{\text{OUT}}(t)$.

$$V_{\text{out}} = -\frac{5 \text{ V}}{101} \cos\left(10^4 \frac{\text{rad}}{\text{s}} t + \frac{\pi}{4}\right)$$

$$\text{At } \omega = 10^4 \frac{\text{rad}}{\text{s}}, \quad H(j\omega) = \frac{-j 10^4 \cdot 10 \cdot 10^{-6}}{(1 + j 10^4 \cdot 10^3 \cdot 10^{-6})(1 + j 10^4 \cdot 10 \cdot 10^{-6})}$$

$$= \frac{-0.1j}{(1 + j)(1 + j10)} = -\frac{1}{101}$$

Problem 6: Filter Design - 20%

This objective of this problem is to design an op-amp-based band-pass filter that implements the transfer function $H(j\omega)$ given by


$$H(j\omega) = \frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \frac{\pm G(j\omega)\omega_0/Q}{(j\omega)^2 + (j\omega)\omega_0/Q + \omega_0^2}$$

where \tilde{V}_{in} and \tilde{V}_{out} are the complex amplitudes of the sinusoidal-steady-state input and output voltages, respectively, and G , ω_0 , and Q are pre-specified constants. The “ \pm ” in the transfer function indicates that both signs are acceptable.

The implementation of the transfer function should also observe the following constraints.

- The filter should be implemented with no more than two op amps, and no more than four capacitors, inductors and resistors in total.
- The op-amp(s) may be considered ideal, but any inductor should be considered imperfect due to a series resistance R given by $R = L/\tau$ where L is the inductance and τ is a known constant.
- Assume that the filter will be driven by a Thevenin equivalent. The operation of the filter should be independent of the resistance of that equivalent.
- The operation of the filter should be independent of any load attached to its output.

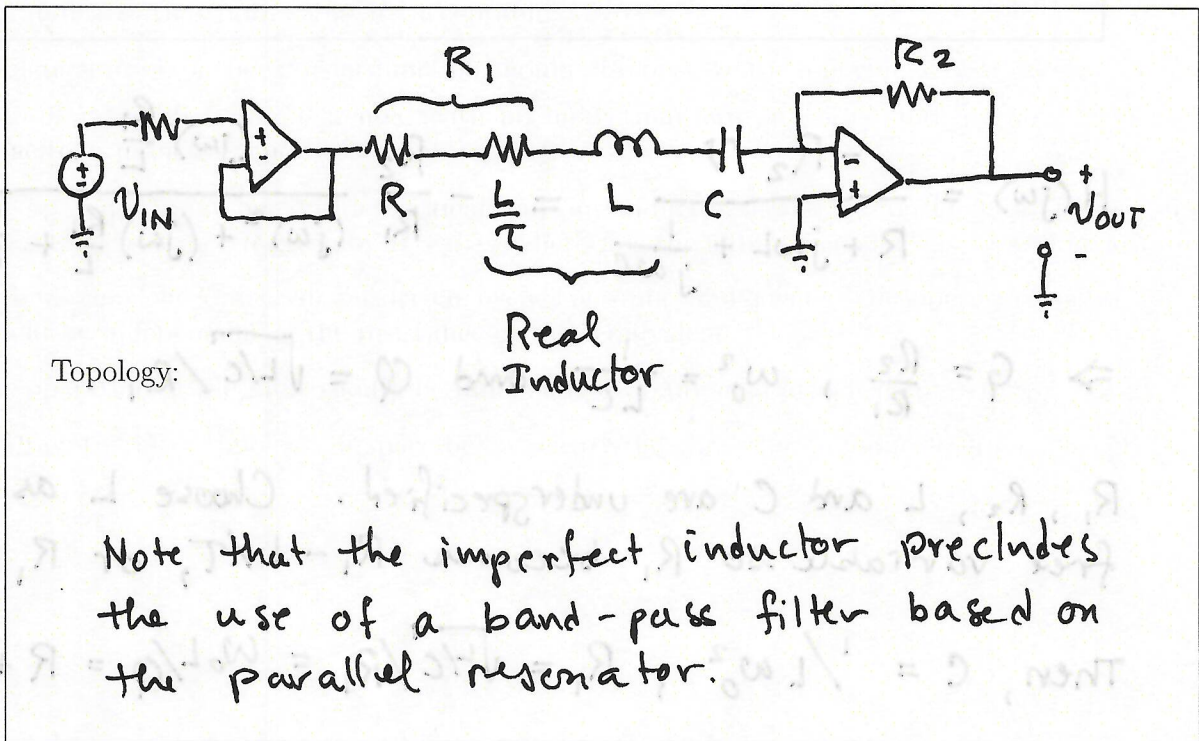(6A) Draw the filter topology in space below, clearly labeling the symbolic component values.



- (6B) Derive expressions for the component (capacitor, inductor, resistor) values in terms of G , ω_0 , Q and τ . If the component values are under-specified, then pick one (or more) as being pre-specified until the remaining component values are uniquely specified. Be clear which component value is being specified below.

Component #1:	C	Value = $1/L\omega_0^2$
Component #2:	R	Value = $L\left(\frac{\omega_0}{Q} - \frac{1}{\tau}\right)$
Component #3:	R_2	Value = $G\omega_0 L/Q$
Component #4:		Value =
Under-specified component(s):	L	

$$H(j\omega) = \frac{-R_2}{R + j\omega L + \frac{1}{j\omega C}} = -\frac{R_2}{R_1} \frac{(j\omega) \frac{R_1}{L}}{(j\omega)^2 + (j\omega) \frac{R_1}{L} + \frac{1}{LC}}$$

$$\Rightarrow G = \frac{R_2}{R_1}, \quad \omega_0^2 = \frac{1}{LC} \quad \text{and} \quad Q = \sqrt{LC}/R_1.$$

R_1 , R_2 , L and C are underspecified. Choose L as the free variable so R becomes $R_1 - L/\tau$, or $R_1 = R + L/\tau$.

$$\text{Then, } C = 1/L\omega_0^2, \quad R_1 = \sqrt{LC}/Q = \omega_0 L/Q = R + L/\tau$$

$$\Rightarrow R = L\left(\frac{\omega_0}{Q} - \frac{1}{\tau}\right), \quad \text{and} \quad R_2 = G R_1 = G\left(R + \frac{L}{\tau}\right)$$

$$\Rightarrow R_2 = \frac{G\omega_0 L}{Q}$$

- (6C) Is the achievable Q limited given practical engineering constraints? If so, to what range? Circle the appropriate answer and provide a range if "Yes".

Yes

No

Range:

$$Q < \omega_0 \tau$$

$R = L \left(\frac{\omega_0}{Q} - \frac{1}{\tau} \right)$ must be positive to be a

practical resistance. So, $\frac{\omega_0}{Q} - \frac{1}{\tau} > 0$

$$\text{or } Q < \omega_0 \tau$$