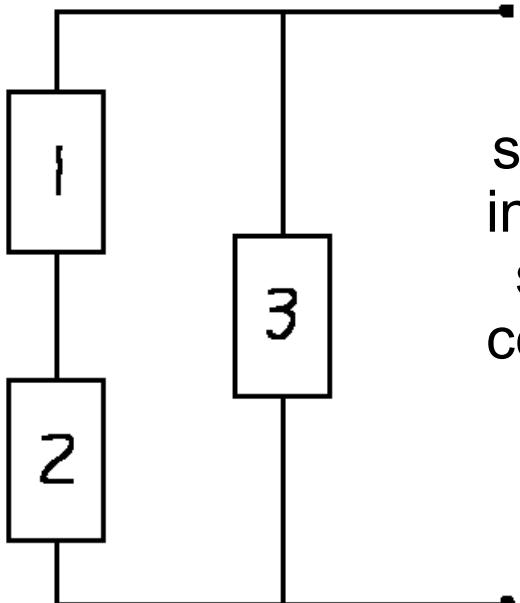


# 6.200 - Lecture 03


## Circuit Analysis Simplifications

- Parallel & Series Reductions
- Dividers
- Node Analysis
- Super Nodes
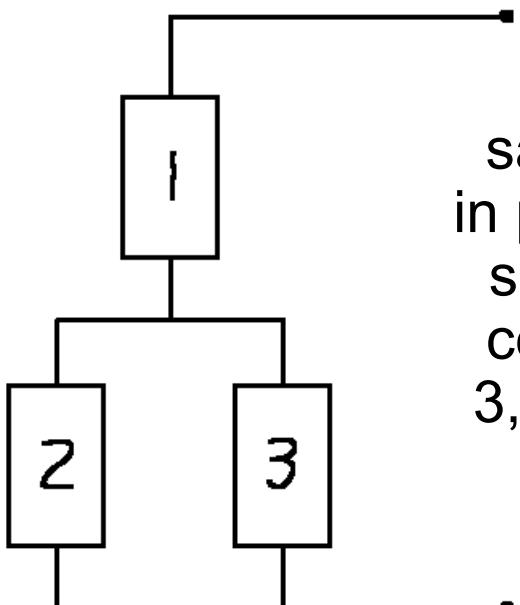
# Series? Parallel?




Devices 1 and 2 share the same current, hence they are in series. Device 3 shares the same voltage with the series combination of Devices 1 and 2, hence it is in parallel with the series combination of Devices 1 and 2.



Devices 2 and 3 share the same voltage, hence they are in parallel. Device 1 shares the same current with the parallel combination of Devices 2 and 3, hence it is in series with the parallel combination of Devices 2 and 3.


# Series Resistors (Common i)

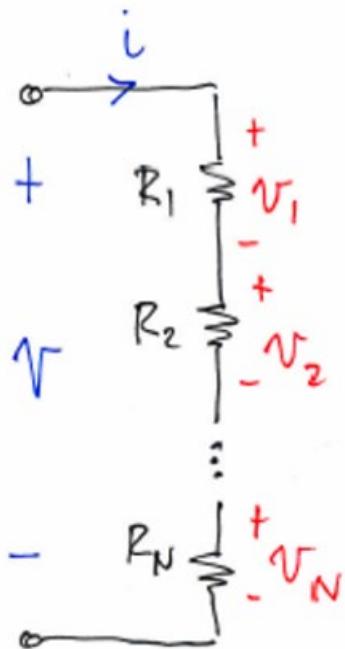

$$\begin{aligned}V &= V_1 + V_2 + \dots + V_N \\&= R_1 i + R_2 i + \dots + R_N i \\&= (R_1 + R_2 + \dots + R_N) i \\&\equiv R i\end{aligned}$$

$$\begin{aligned}R &= R_1 + R_2 + \dots + R_N \\V_n &= R_n / (R_1 + R_2 + \dots + R_N)\end{aligned}$$

# Parallel Resistors (Common v)

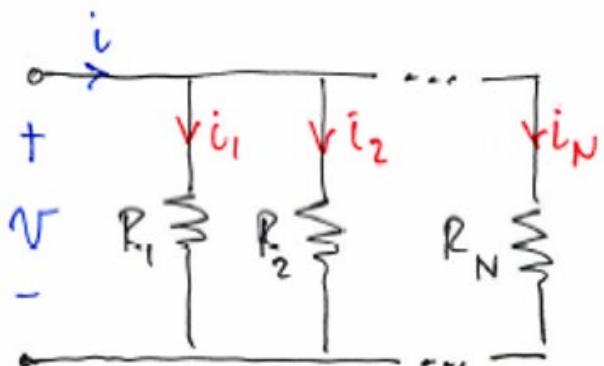


$$\begin{aligned}i &= i_1 + i_2 + \dots + i_N \\&= G_1 V + G_2 V + \dots + G_N V \\&= (G_1 + G_2 + \dots + G_N) V \\&\equiv G V\end{aligned}$$

$$\begin{aligned}G &= G_1 + G_2 + \dots + G_N \\1/G &= 1/R_1 + 1/R_2 + \dots + 1/R_N\end{aligned}$$

# Simplification Process

$$i = ?$$

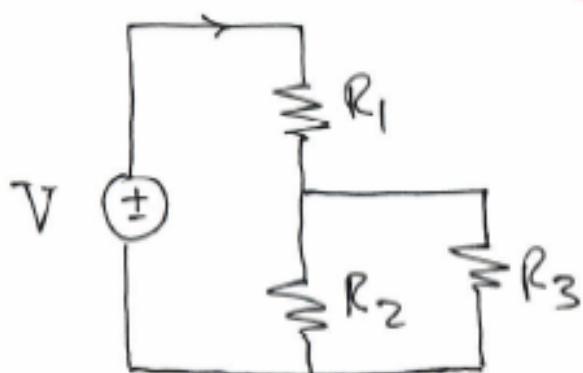

Parallel Reduction


$$i = ?$$



$$R_1$$

$$\frac{R_2 R_3}{R_2 + R_3}$$

$$i = V/R$$

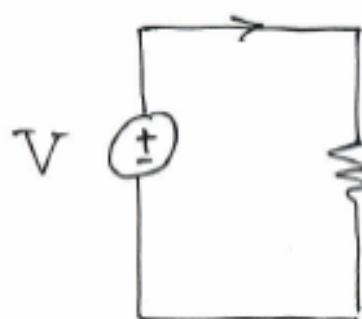


$$R_1 + \frac{R_2 R_3}{R_2 + R_3} \equiv R$$

Series Reduction

Use voltage and current dividers, and device laws to determine remaining branch variables.

# Node Voltages

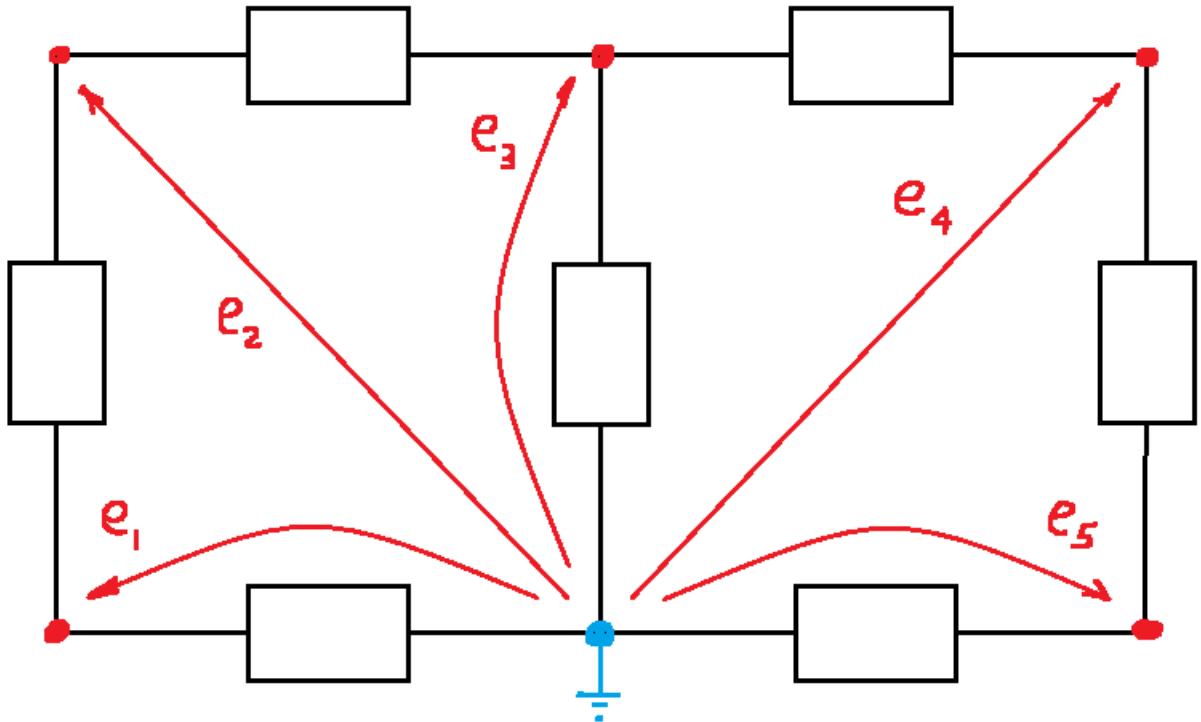

Ground:  $e_a = 0$


A node voltage  $e$  is defined as the potential difference between the corresponding node (+) and the ground (-). The ground is assigned an absolute potential of zero. Therefore the node voltage is also the absolute potential of the corresponding node.

# (Simplified) Node Analysis

The following assumes an absence of floating voltage sources.

- 1) Draw the circuit neatly.
- 2) Select a reference node from which all other node voltages are measured. Define its voltage to be zero. This node is the “ground” node.
- 3) Label all voltage-sourced node voltages with their sourced voltage.
- 4) Label all remaining un-sourced nodes with their unknown node voltages. These are the primary analytic unknowns.
- 5) Write KCL for each node with an unknown node voltage, and immediately back substitute the device laws and KVL. The resulting equations are now in terms of the node voltages.
- 6) Solve the KCL equations for the unknown node voltages.
- 7) Back solve for all branch voltages and then branch currents as desired.

# Node Analysis Example

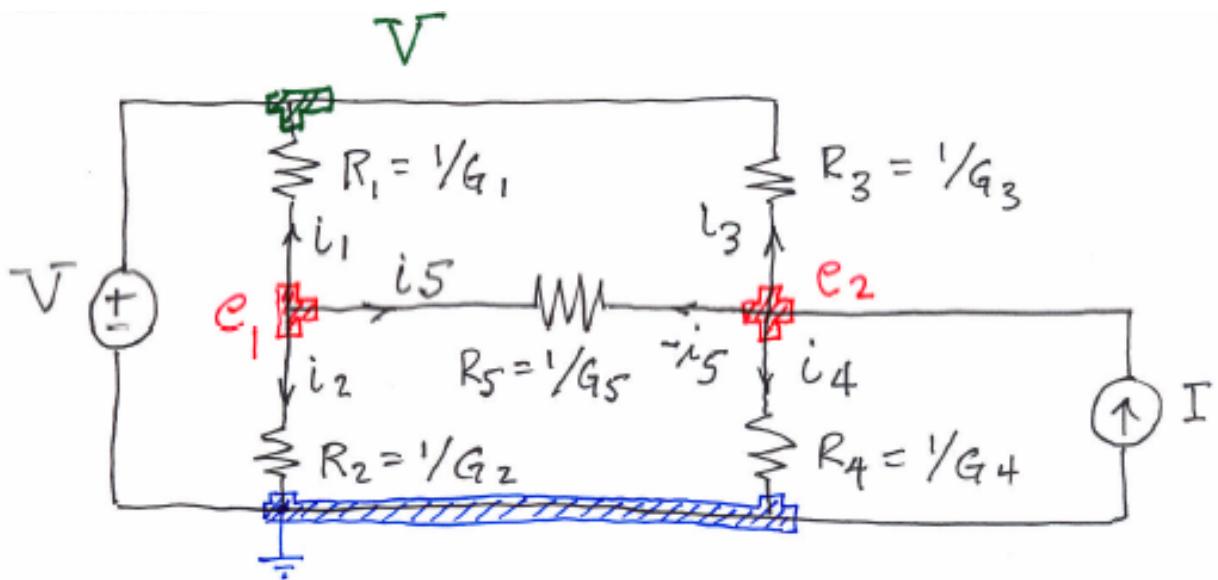

$$e_1 \text{ Node: } i_1 + i_2 + i_5 = 0$$


$$G_1(e_1 - V) + G_2(e_1 - 0) + G_5(e_1 - e_2) = 0$$

$$e_1(G_1 + G_2 + G_5) + e_2(-G_5) = V(G_1)$$

$$e_2 \text{ Node: } i_3 + i_4 + (-i_5) - I = 0$$

$$G_3(e_2 - V) + G_4(e_2 - 0) + G_5(e_2 - e_1) - I = 0$$
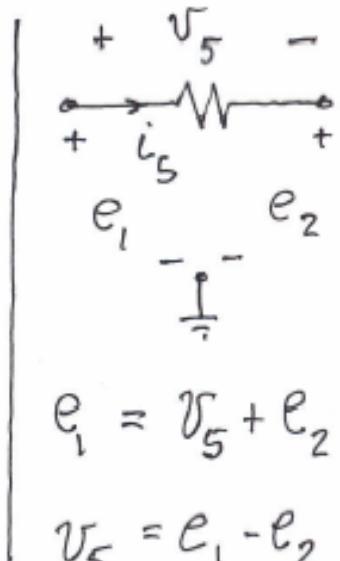
$$e_1(-G_5) + e_2(G_3 + G_4 + G_5) = V(G_3) + I$$



$$e_1 = V_5 + e_2$$

$$V_5 = e_1 - e_2$$

# Solution

$$\begin{bmatrix} G_1 + G_2 + G_5 & -G_5 \\ -G_5 & G_3 + G_4 + G_5 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} G_1 V \\ G_3 V + I \end{bmatrix}$$

$$\begin{bmatrix} G_3 + G_4 + G_5 & G_5 \\ G_5 & G_1 + G_2 + G_5 \end{bmatrix} \begin{bmatrix} G_1 V \\ G_3 V + I \end{bmatrix} = \begin{bmatrix} e_1 \\ e_2 \end{bmatrix}$$

$$(G_1 + G_2 + G_5)(G_3 + G_4 + G_5) - G_5^2$$


$$e_1 = \frac{(G_3 + G_4 + G_5) G_1 V + G_5 (G_3 V + I)}{G_1 G_3 + G_1 G_4 + G_1 G_5 + G_3 G_5 + G_2 G_3 + G_2 G_4 + G_2 G_5 + G_5 G_3 + G_5 G_4}$$

$$e_2 = \frac{G_5 G_1 V + (G_1 + G_2 + G_5) (G_3 V + I)}{(\text{Same Denominator})}$$

## Demo

$$\left. \begin{array}{l} R_1 = R_4 = 8.2 \text{ k}\Omega \\ R_2 = R_3 = 3.9 \text{ k}\Omega \\ R_5 = 1.5 \text{ k}\Omega \\ V = 3 \text{ V} \\ I = 0 \text{ A} \end{array} \right\} \quad \begin{array}{l} e_1 = 1.382 \text{ V} \\ e_2 = 1.618 \text{ V} \end{array}$$

# Node Analysis Structure

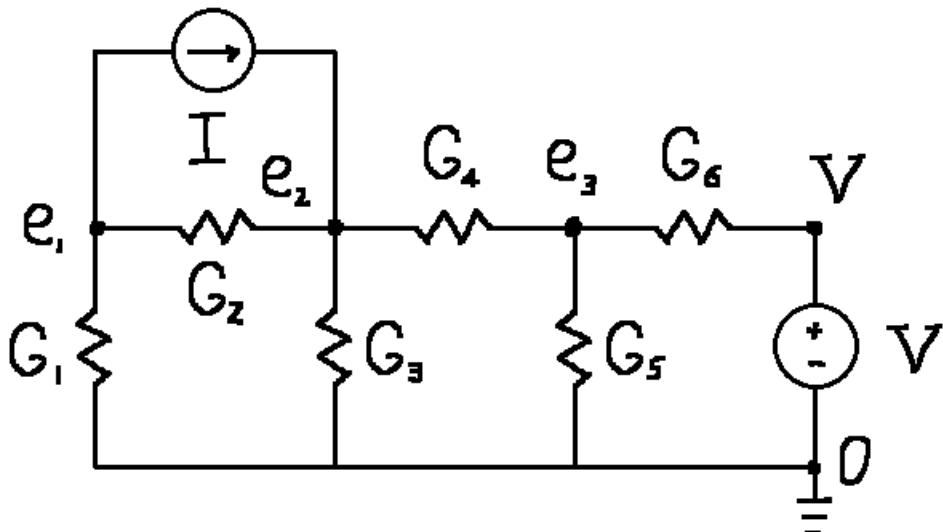

Omit ground node potential (known to be zero) and ground-node KCL (redundant). The patterns can be used to check work.

$$e_1 \text{ KCL: } G_1(e_1 - 0) + G_2(e_1 - e_2) + I = 0$$


$$e_2 \text{ KCL: } G_2(e_2 - 0) + G_1(e_2 - e_1) + G_4(e_2 - e_3) - I = 0$$

$$e_3 \text{ KCL: } G_5(e_3 - 0) + G_4(e_3 - e_2) + G_6(e_3 - V) = 0$$

$$\begin{bmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_1 + G_3 \end{bmatrix} \begin{bmatrix} 0 \\ -G_4 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \end{bmatrix} = \begin{bmatrix} -I \\ +I \end{bmatrix} I + \begin{bmatrix} 0 \\ 0 \end{bmatrix} V$$
$$\begin{bmatrix} 0 & G_5 + G_6 \end{bmatrix} \begin{bmatrix} e_3 \end{bmatrix} = \begin{bmatrix} 0 \\ G_6 \end{bmatrix}$$
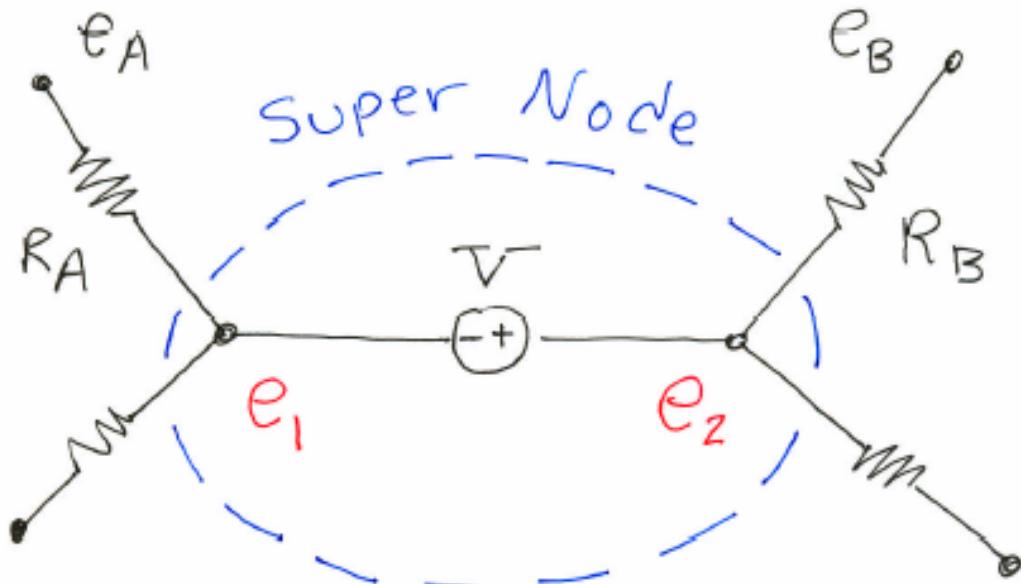
# Super Nodes

Super nodes treat floating voltage sources.



Write only one KCL for each super node.

$$\frac{e_1 - e_A}{R_A} + \frac{\overbrace{e_1 + V - e_B}^{e_2}}{R_B} + \dots = 0$$