

6.200 - Lecture 05

Circuit Analysis Simplifications

- Linearity Review
- Superposition Review
- Thevenin & Norton Equivalence
- Five-Lecture Summary

Homogeneity & Superposition

Homogeneity and superposition are properties of linear systems.

Homogeneity: If $\bar{x} \rightarrow \boxed{\text{Linear System}} \rightarrow \bar{y}$

Then $\alpha \bar{x} \rightarrow \boxed{\text{Linear System}} \rightarrow \alpha \bar{y}$


Superposition: If $\bar{x}_1 \rightarrow \boxed{\text{Linear System}} \rightarrow \bar{y}_1$

$\bar{x}_2 \rightarrow \boxed{\text{Linear System}} \rightarrow \bar{y}_2$

Then $\bar{x}_1 + \bar{x}_2 \rightarrow \boxed{\text{Linear System}} \rightarrow \bar{y}_1 + \bar{y}_2$

Linear Networks and Systems

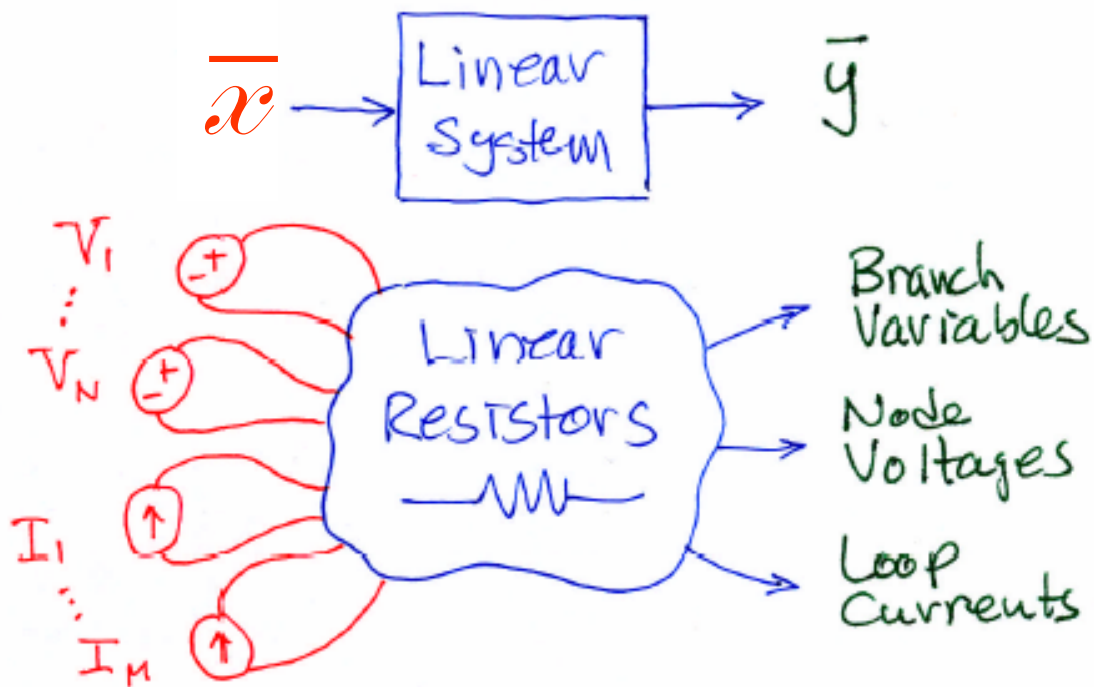Linear system $\Rightarrow$ all stimuli are external inputs. For example, $y = x_1 + x_2$ is linear from $\bar{x} \rightarrow y$, but $y = x_1 + x_2 + 1$ is not.




No source should be left within the network for the purposes of superposition. Superposition is carried out over all sources.


Divide & Conquer

Use superposition to analyze a linear circuit one source at a time. (All sources except one are set to zero each time.)

How to set a source to zero?

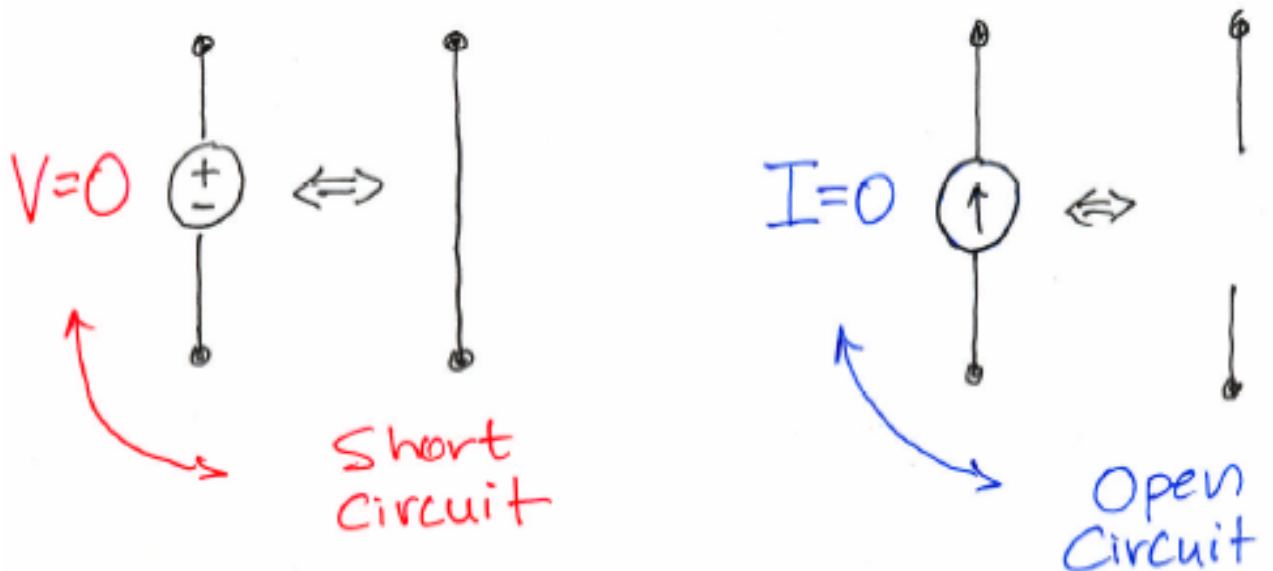


Thevenin & Norton Equivalence

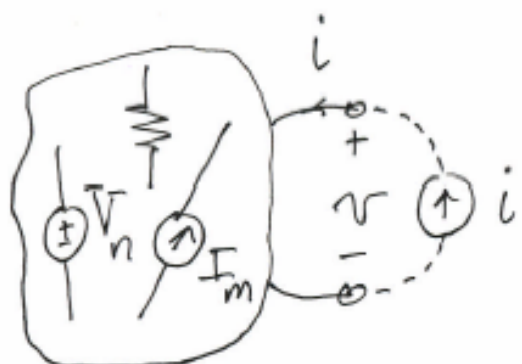

Linear
Network

$$v = \sum_n \alpha_n V_n + \sum_m \beta_m I_m + R_{TH} i$$

Superposition


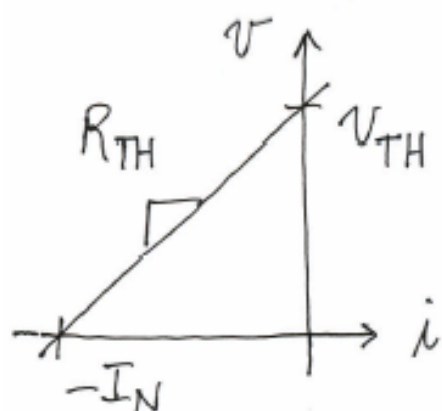


Open
Circuit
($i=0$)


$$\Rightarrow V_{TH} = \sum_n \alpha_n V_n + \sum_m \beta_m I_m$$

Short
Circuit
($v=0$)
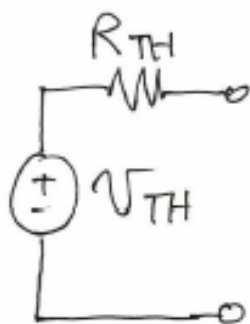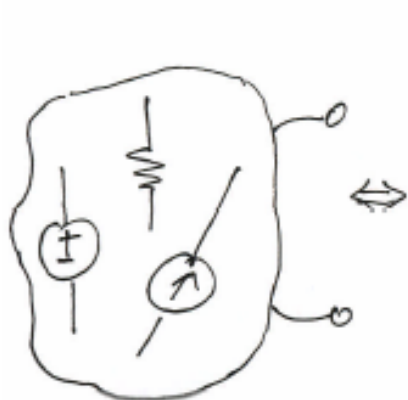
$$\Rightarrow I_N = \frac{V_{TH}}{R_{TH}}$$




Thevenin

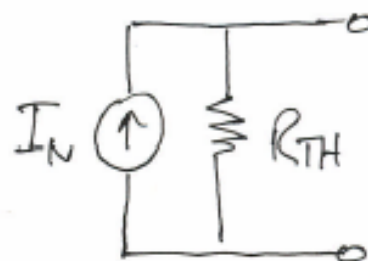


Norton


Thevenin / Norton Summary

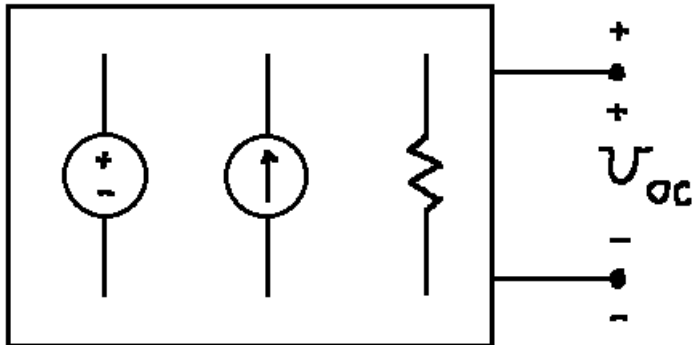

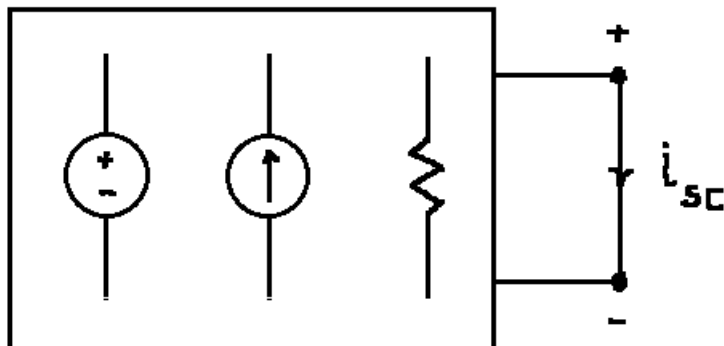The Thevenin voltage v_{TH} is the open-circuit voltage v_{oc} .




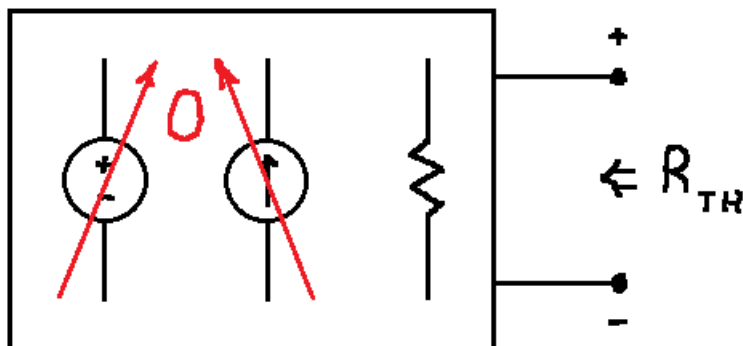The Norton current i_N is the short-circuit current i_{sc} .




The Thevenin/
Norton resistance R_{TH} is the terminal resistance computed with zeroed sources.



Thevenin / Norton Example #1

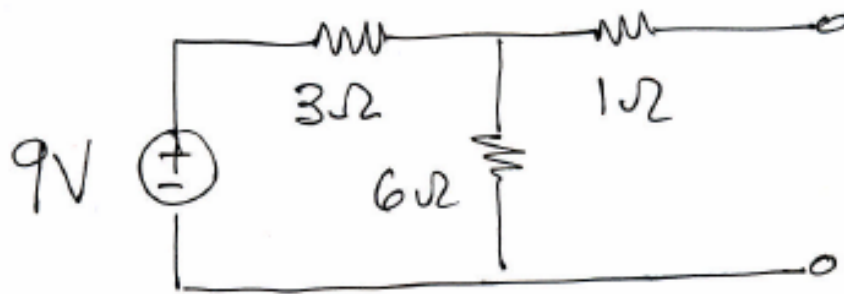

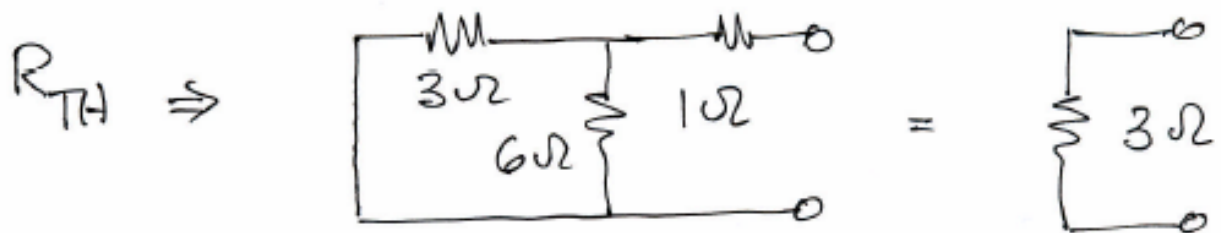
Open-circuit voltage = 6 V via
voltage divider $\Rightarrow V_{TH} = 6 \text{ V}$




$$I_N = V_{TH} / R_{TH} = 2 \text{ A}$$

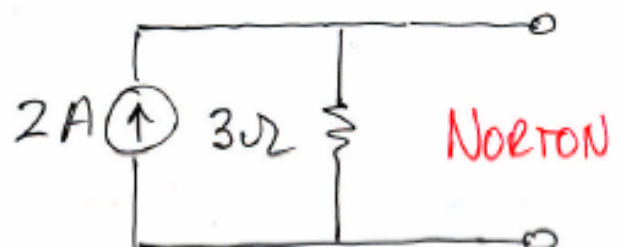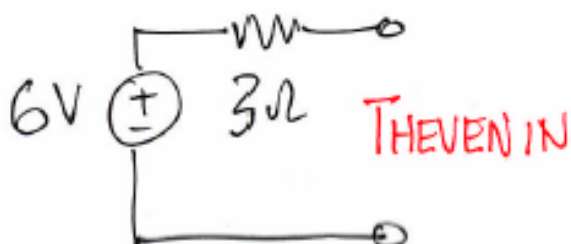


Confirm Equivalence

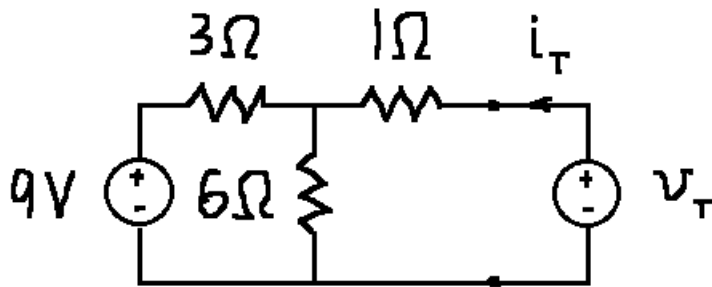
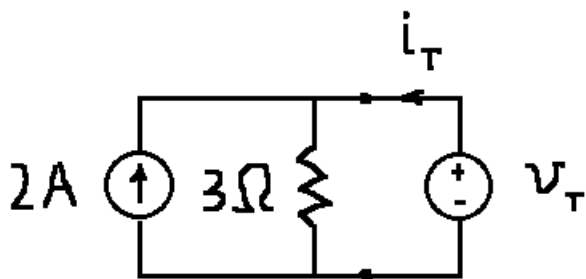
$$\begin{aligned} i_T &= \frac{v_T}{3\Omega} - \frac{6}{7} \frac{9V}{(3+6/7)\Omega} \\ &= v_T / 3\Omega - 2A \\ &= (v_T - 6V) / 3\Omega \end{aligned}$$



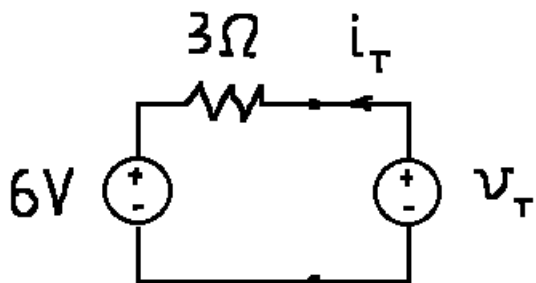
$$\begin{aligned} i_T &= v_T / 3\Omega - 2A \\ &= (v_T - 6V) / 3\Omega \end{aligned}$$




$$i_T = (v_T - 6V) / 3\Omega$$

Use Case I


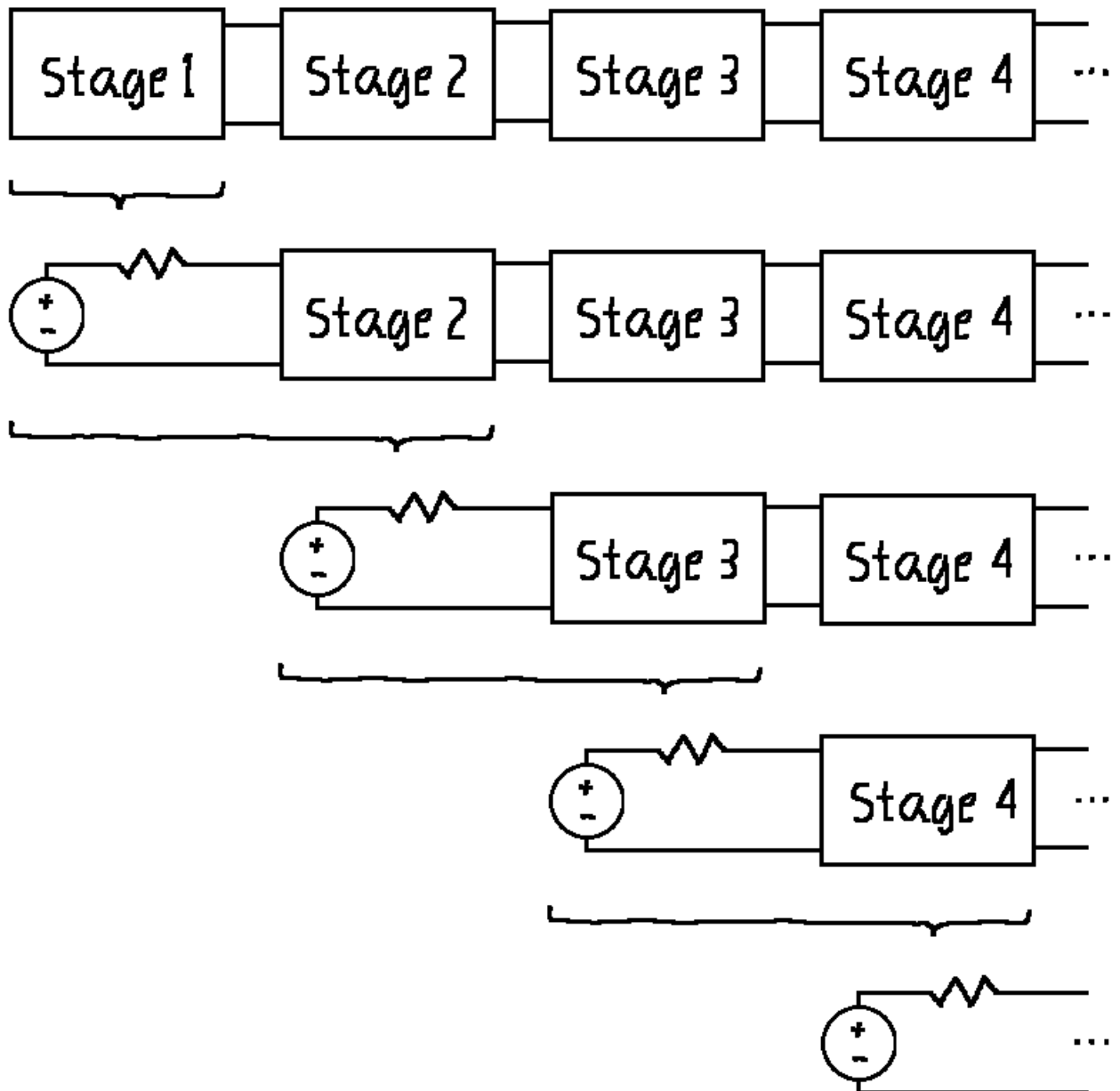
The successive use of Thevenin equivalence allows a complex circuit to be analyzed in steps as a cascade of simpler circuits.





Use Case II

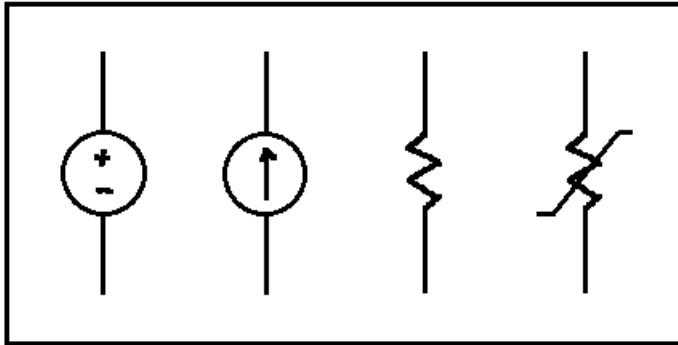

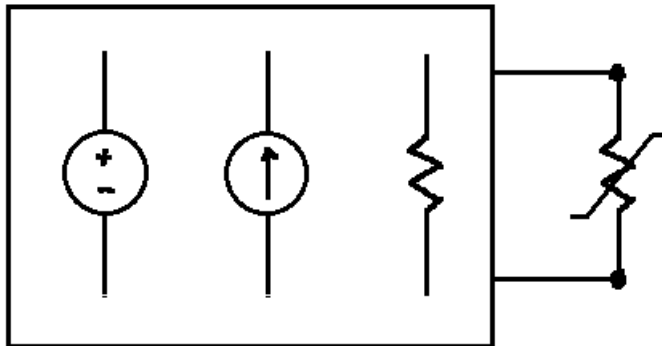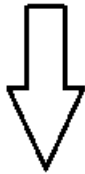Arbitrary linear circuit plus one nonlinear resistor.




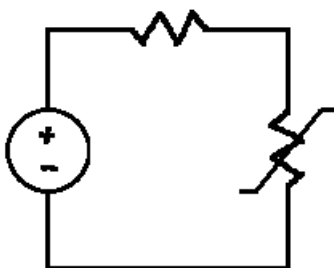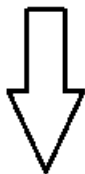Pull the nonlinear resistor out from the arbitrary linear circuit.



Replace the arbitrary linear circuit with a Thevenin (or Norton) equivalent circuit.


DAC Example

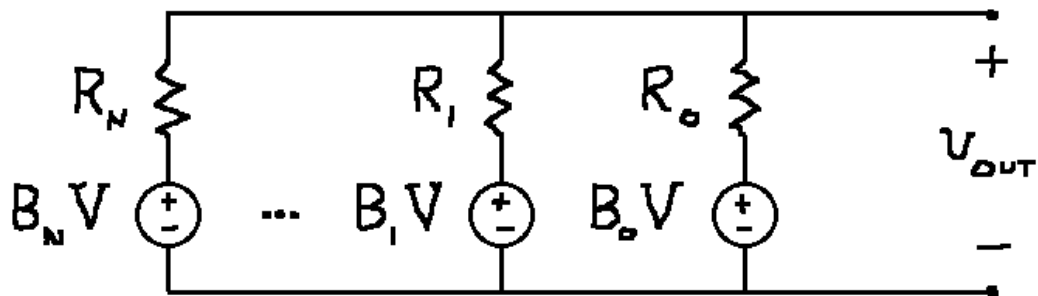

DAC $\Rightarrow$ Digital Data = $\boxed{B_N} \cdots \boxed{B_1} \boxed{B_o}$

$$V_{OUT} = KV \sum_n B_n 2^n ; B_n = \{0, 1\}$$

Use superposition and voltage division:




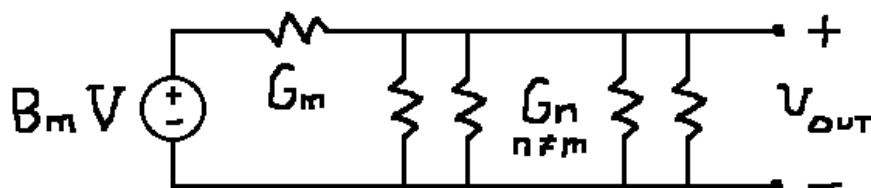


$$V_{OUT, m} = \frac{G_m B_m V}{\sum_{n \neq m} G_n + G_m} = \frac{G_m B_m V}{\sum_n G_n}$$



$$V_{OUT} = V(\sum_n G_n B_n) / (\sum_m G_m) \dots \text{by superposition}$$

$$\text{Design} \Rightarrow G_n = G^* 2^n \Rightarrow K = 1 / (\sum_m 2^m)$$

Thevenin / Norton Example #2

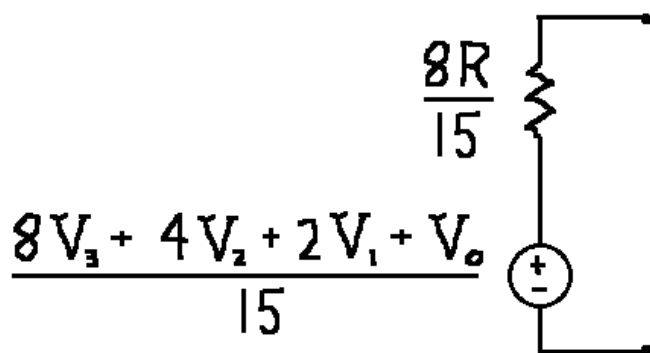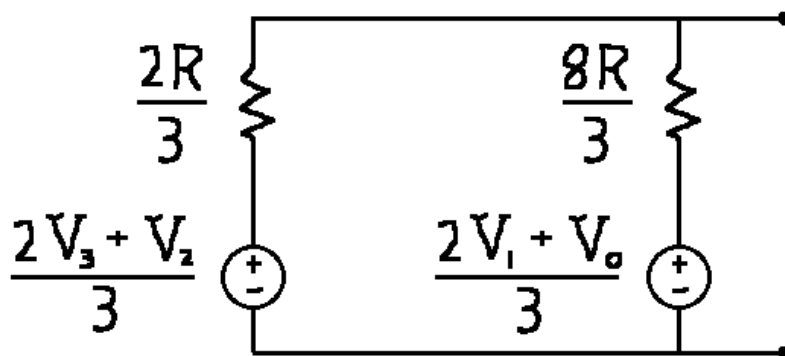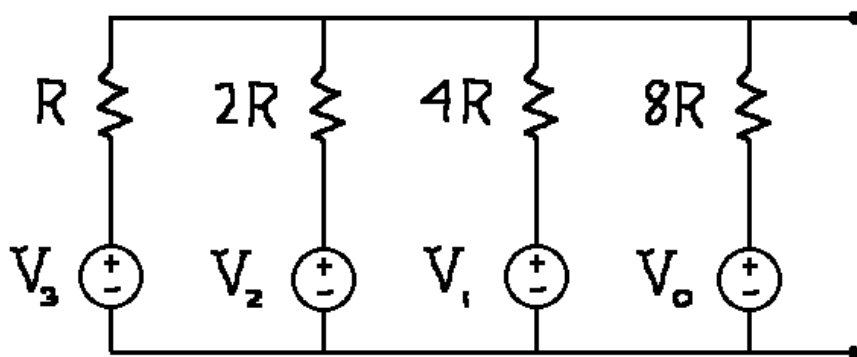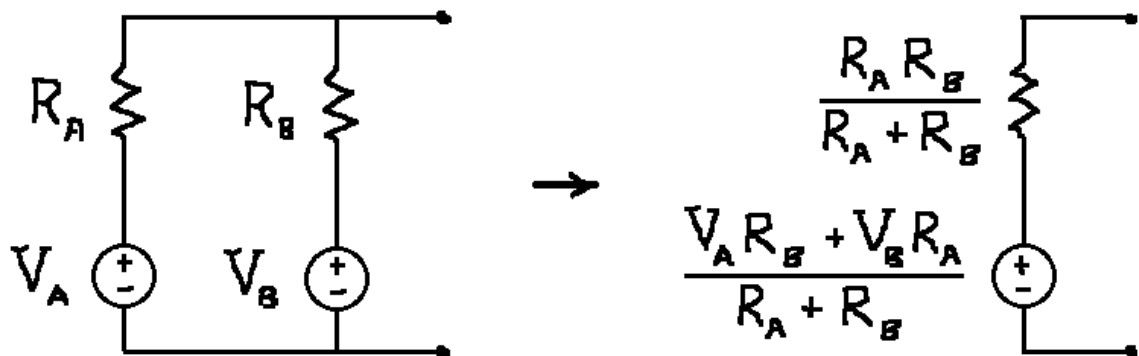


Thevenin / Norton Example #2

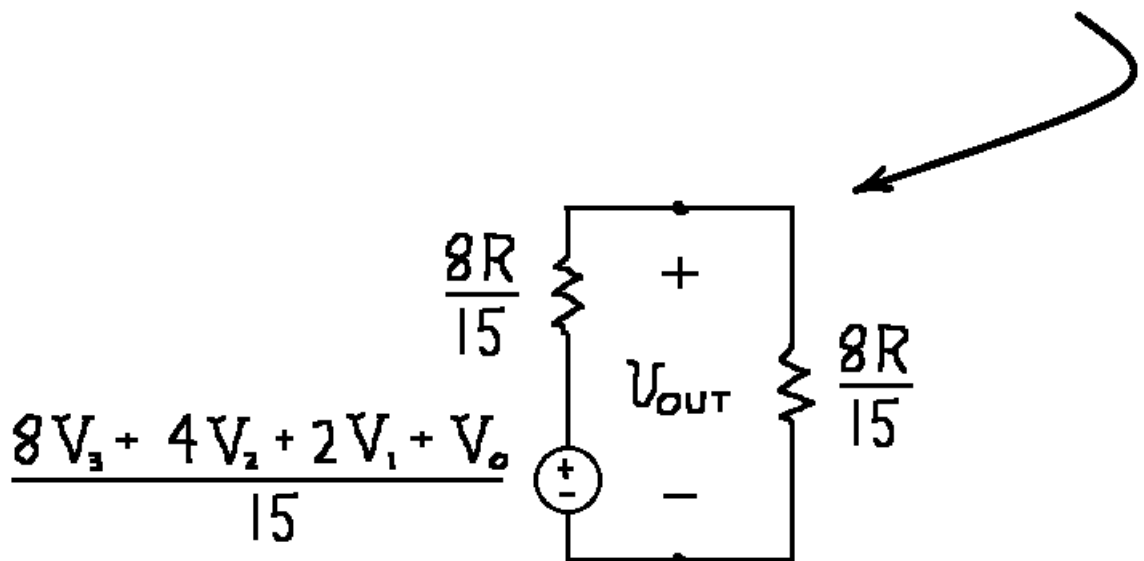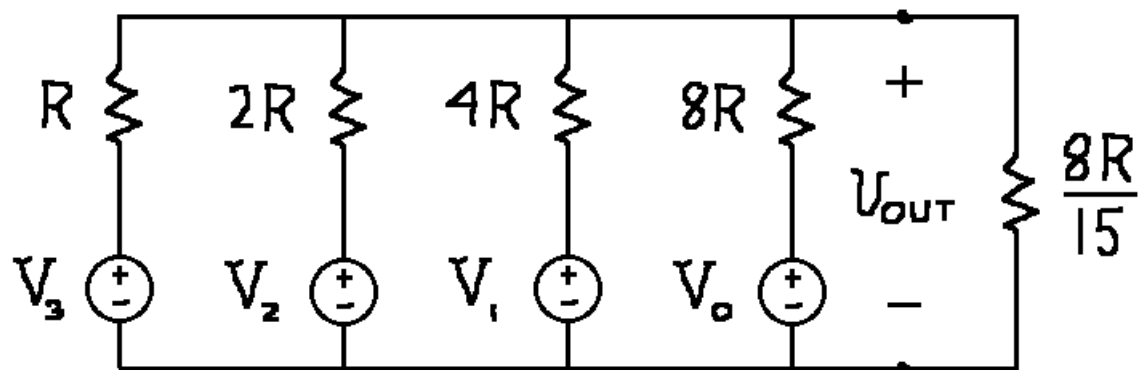


Loading the DAC with $8R/15$ will reduce its output by 50%.

Thevenin / Norton Example #3

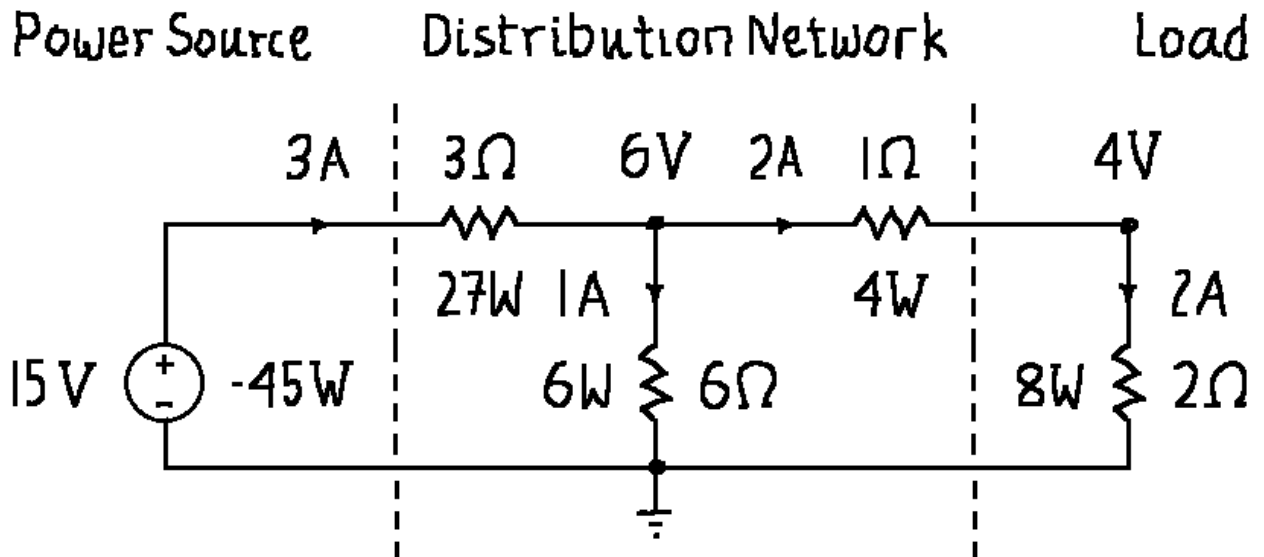


↓ Equivalence

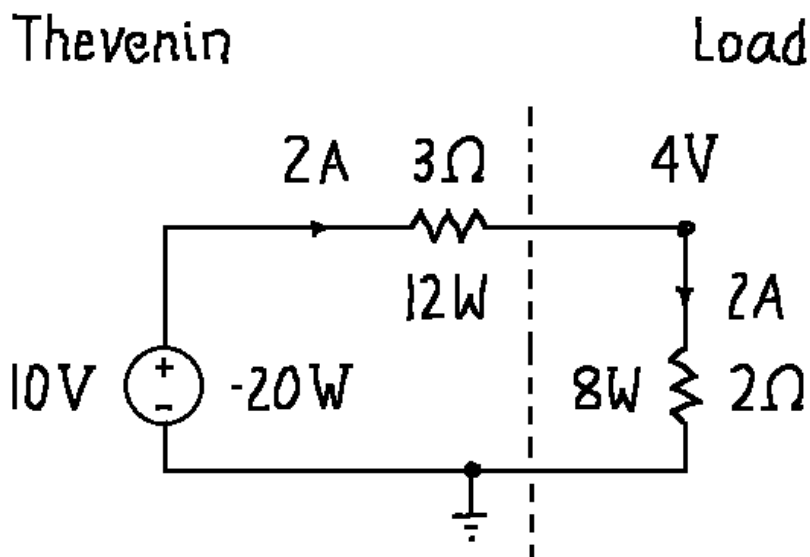


Thevenin and Norton equivalents do not preserve power considerations!

Experimental Battery Example

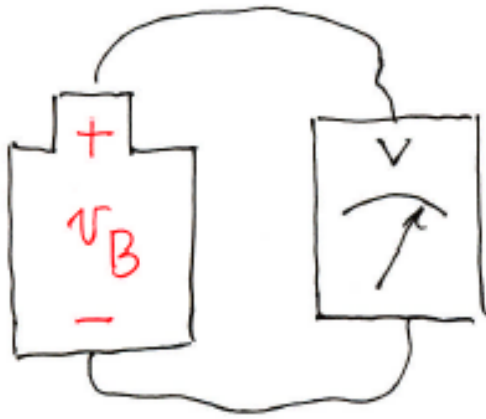


Open-Circuit Voltage

$$v_B = 1.5 \text{ V}$$

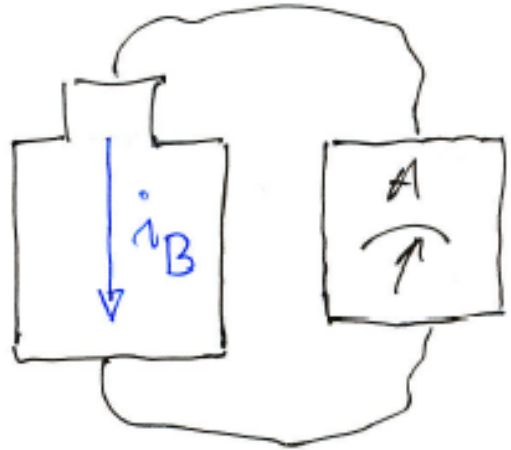


Short-Circuit Current

$$i_B = -1 \text{ A}$$

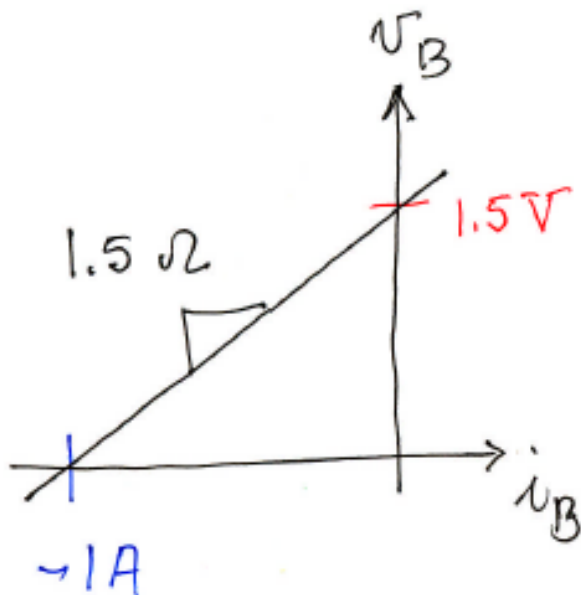

Thevenin Equivalent

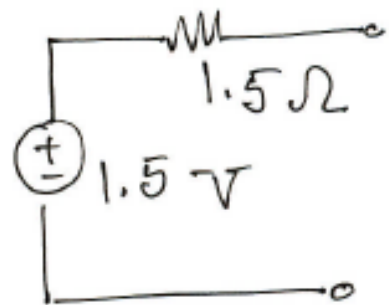

5-Lecture Summary

- Two-terminal devices : V, I, R
- KCL and KVL
- Brute-force analysis
- Node analysis
- Parallel and series reductions
- Voltage and current dividers
- Superposition
- Thevenin and Norton equivalence