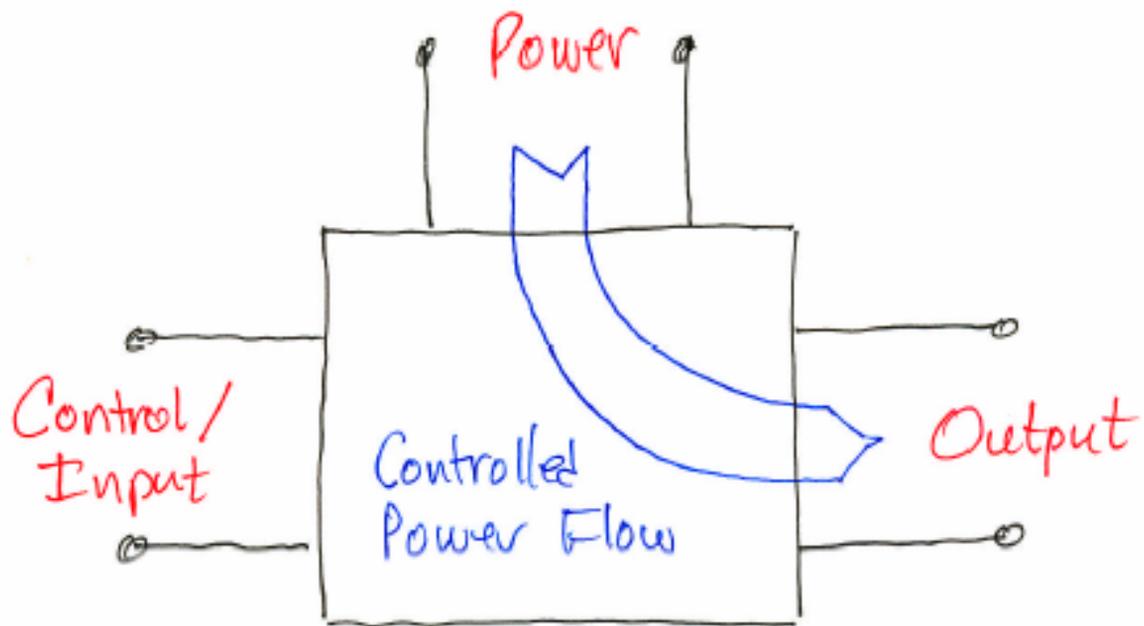


6.200 - Lecture 06

Amplifiers




- Amplifiers
- Amplifier Modeling and Dependent Sources
- Amplifying Devices
- Amplifier Implementation

Amplifiers



- An amplifier is a three-port device.
- Ubiquitous use to improve signal strength, improve signal-to-noise ratio, and provide power gain.
- Examples found in electronics, mechanics, pneumatics, hydraulics, economics, society ...

Amplifier

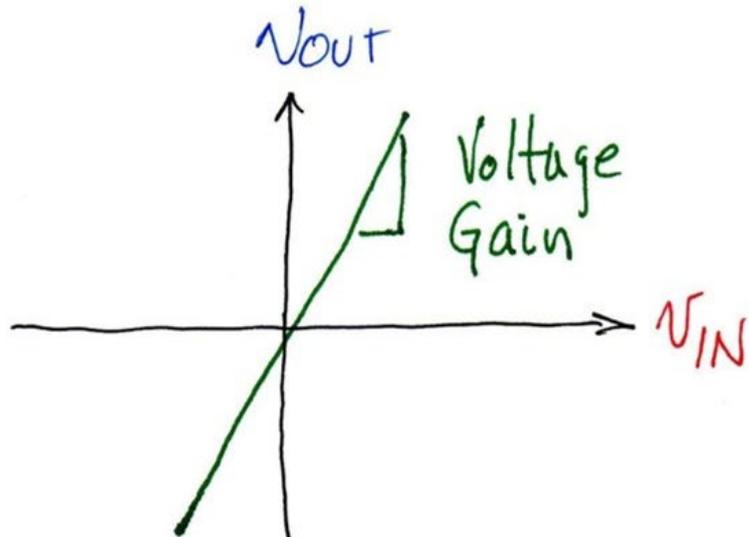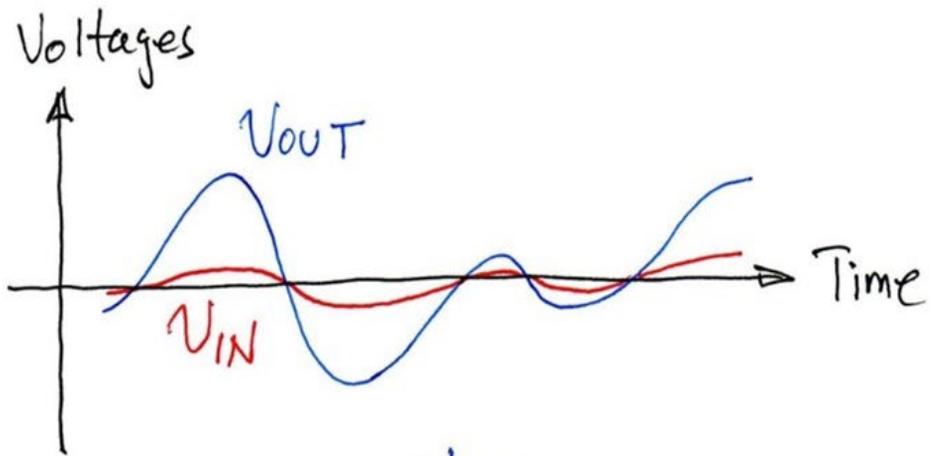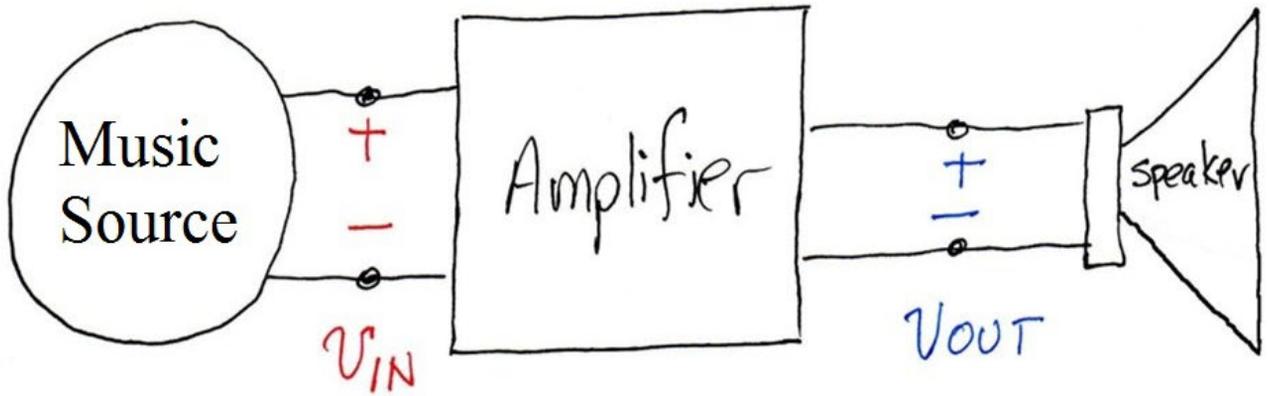



Some Amplifier Properties

- Gain: voltage, current and power

To be an amplifier, a device should provide power gain.

- Linearity
- Equivalence: input and output
- Bandwidth
- Dissipation
- Stability
- Noise
- Size
- Cost


Amplifiers In Other Domains

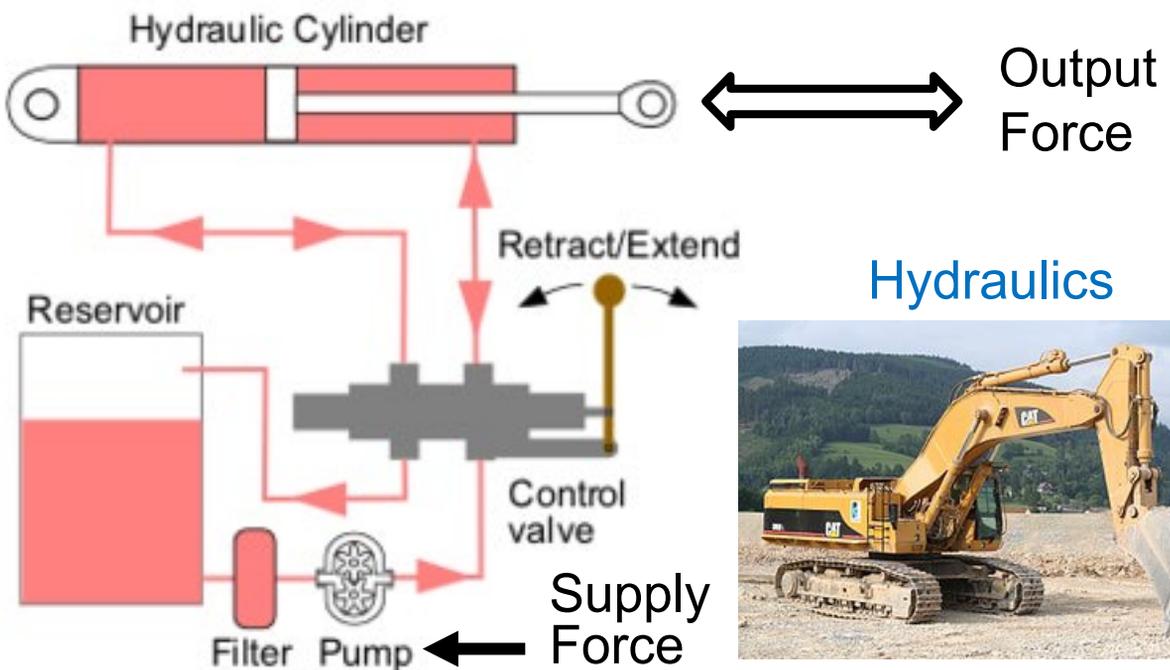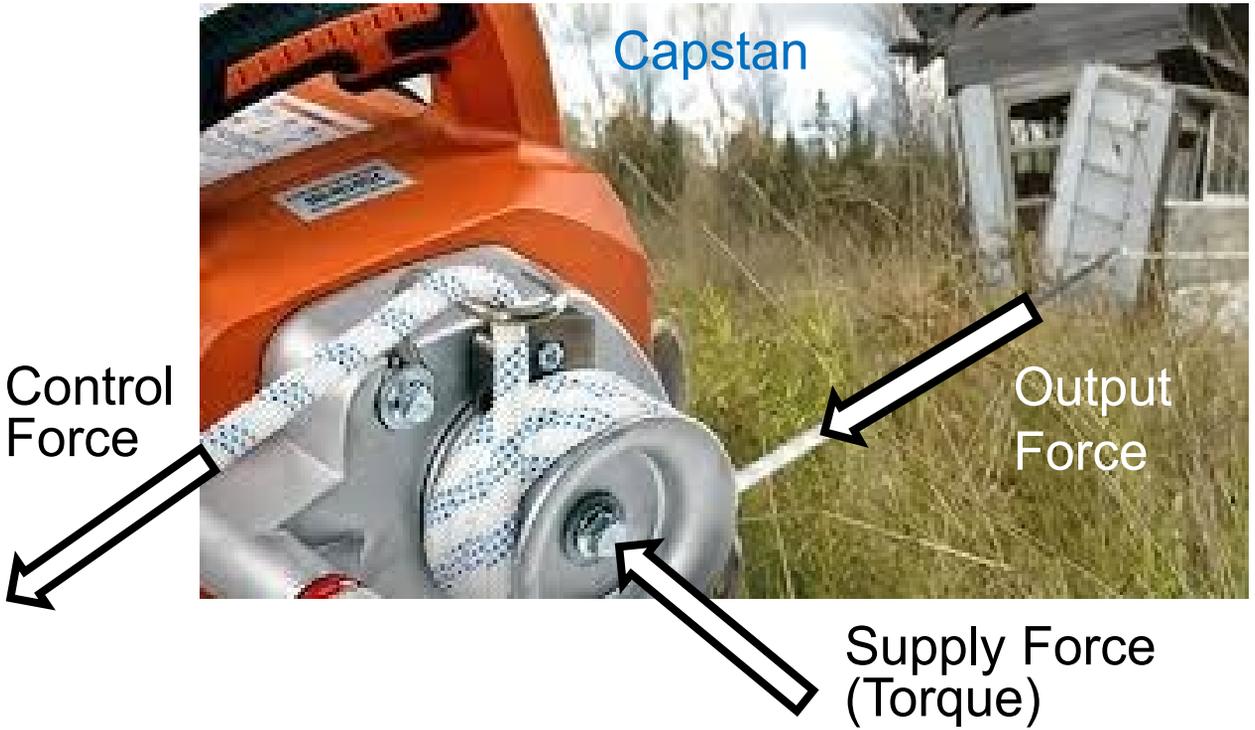

Amplifier Representation

How does one represent a multi-port circuit that can provide power gain?

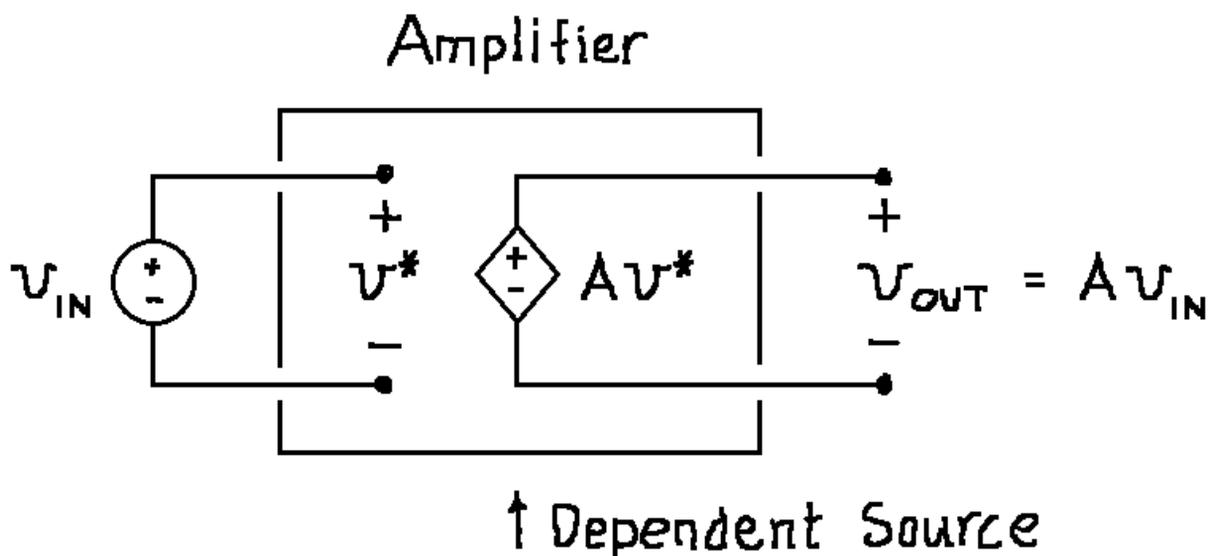- With a detailed circuit diagram drawn at the device level
- Using a high-level summary device, namely a dependent source with an implied power supply for power gain




Independent & Dependent Sources


Independent Sources (ϕ) are external inputs and are independent of all other signals.

Dependent Sources (\diamond) are internal sources having values that depend on other internal branch variables.


Dependent
Voltage Source

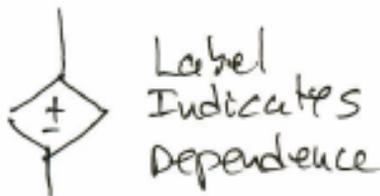


Dependent
Current Source

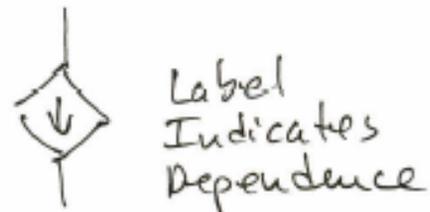

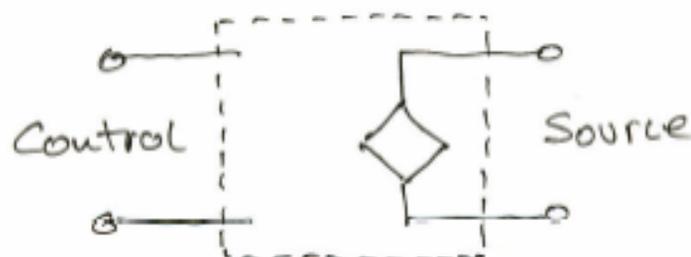Dependent sources are at least two-port devices, and are three-port devices if they can source power.



Some Dependent Sources

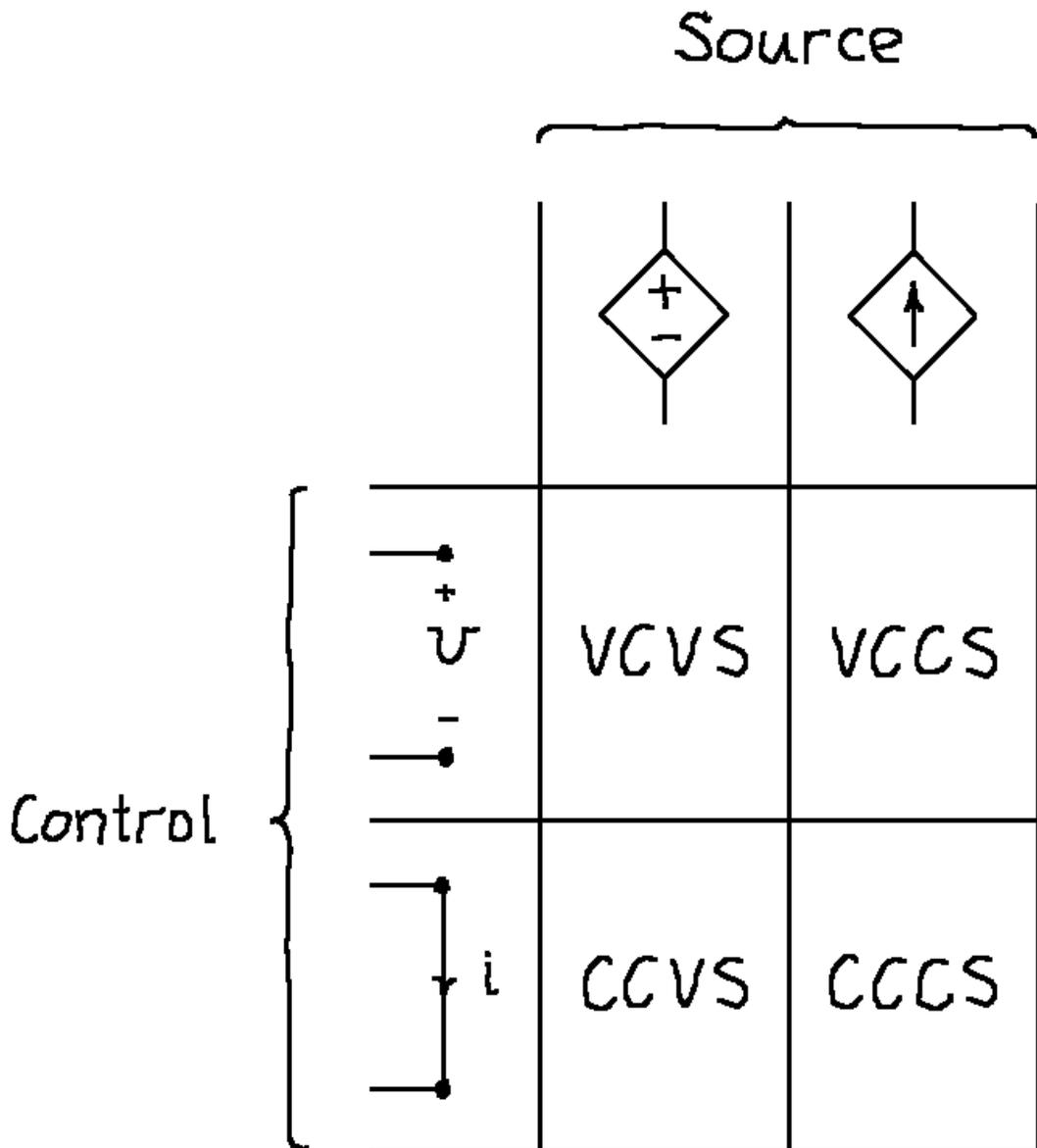

Dependent Source Uses


Dependent sources are used to model amplifying devices and amplifier systems.



Transistors



Vacuum Tubes

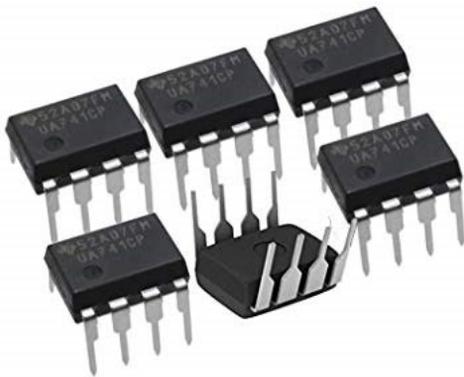

Operational Amplifiers




Amplifier Systems

Device Modeling

Dependent sources are used to model devices that sometimes connect different physical domains


Transformer

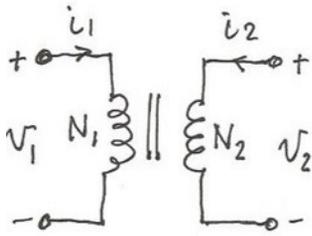


Ideal

$$\frac{v_1}{N_1} = \frac{v_2}{N_2}$$

$$N_1 i_1 + N_2 i_2 = 0$$

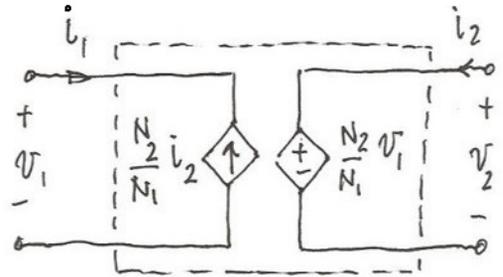


Motor

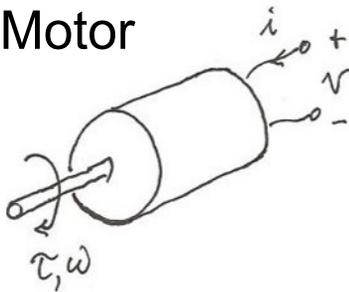

Ideal

$$v = G\omega$$





$$\tau = G_i i$$

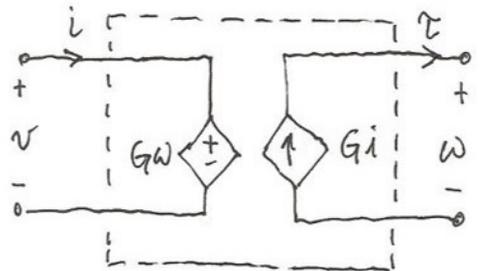

MOSFET Transistor


Idealized

$$i_G = 0$$

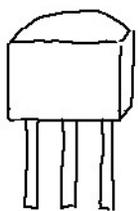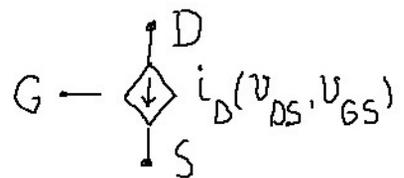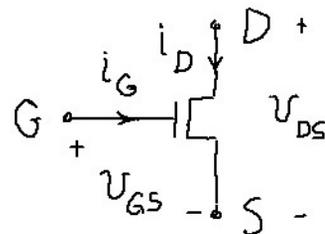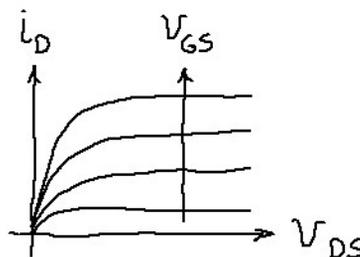

S: Source
D: Drain
SGD G: Gate

Analysis Example: Node Method

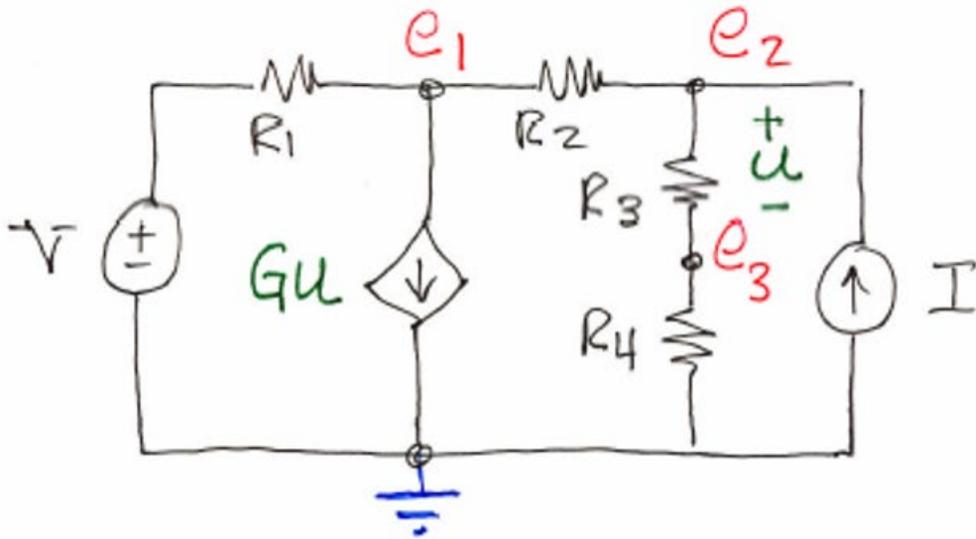

$$\text{Node 1: } G_1(e_1 - \bar{V}) + G(e_2 - e_3) + G_2(e_1 - e_2) = 0$$

$$\text{Node 2: } G_2(e_2 - e_1) + G_3(e_2 - e_3) - I = 0$$



$$\text{Node 3: } G_3(e_3 - e_2) + G_4(e_3) = 0$$

$$\begin{bmatrix} G_1 + G_2 & G - G_2 & -G \\ -G_2 & G_2 + G_3 & -G_3 \\ 0 & -G_3 & G_3 + G_4 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix} = \begin{bmatrix} G_1 & 0 \\ 0 & 1 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} \bar{V} \\ I \end{bmatrix}$$


- Dependent source properties appear in coefficient matrices.
- The network remains linear if the dependent sources are linear.

Superposition

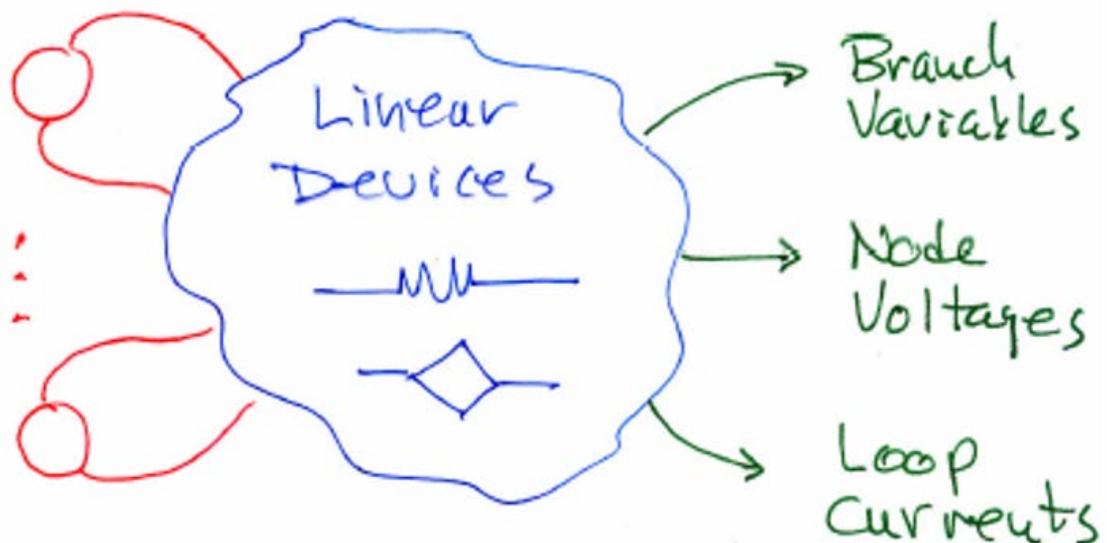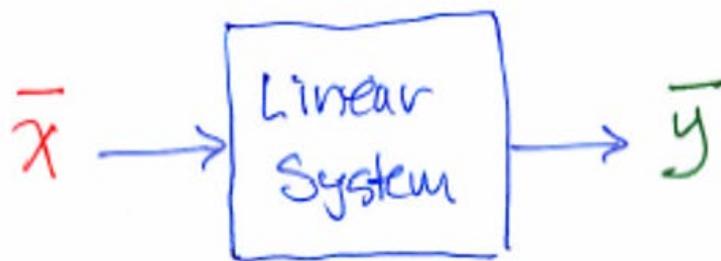Dependent sources are part of the network/system, not part of the independent inputs. It is generally best to carry out superposition only over the independent sources.




Thevenin & Norton Equivalence

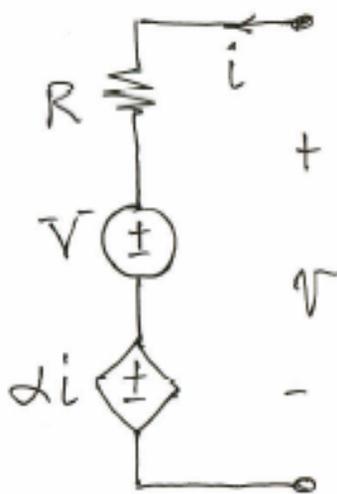

$$v = \alpha i + V + Ri$$

$$= V + (\alpha + R)i$$

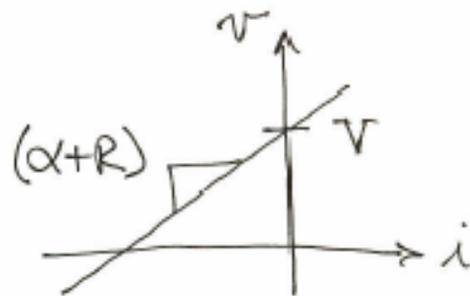


The dependent source is acting like a

resistor \Leftrightarrow


A diagram showing a dependent current source αi in parallel with a resistor α . The current i flows into the current source. The resistor α is shown as a zigzag line.

- Independent sources can only bias the i - v relation at a port.
- Dependent sources can also change the slope of the i - v relation.
- Dependent sources are part of the network, and so must be part of a Thevenin resistance calculation.

BJT Amplifier Implementation

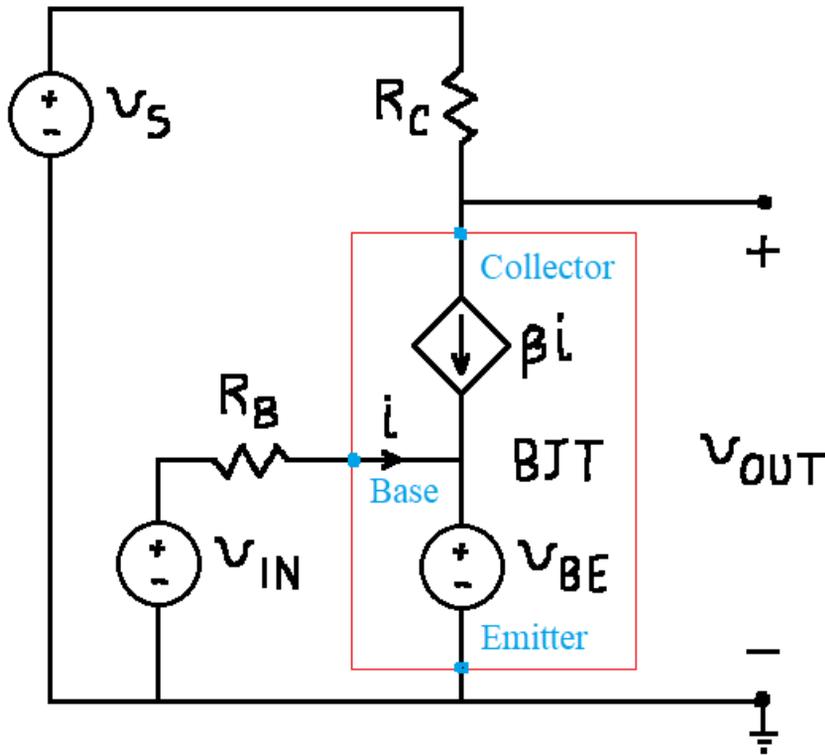

Bipolar Junction Transistor (BJT)

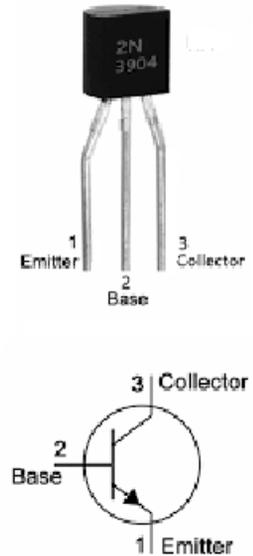

Approximate BJT model valid only for $i > 0$ and $v_{OUT} > v_{BE}$.

Node analysis at v_{OUT} :


$$\frac{v_{OUT} - v_S}{R_C} + \beta \frac{v_{IN} - v_{BE}}{R_B} = 0$$

$$v_{OUT} = v_S - \frac{R_C \beta}{R_B} (v_{IN} - v_{BE})$$

BJT Amplifier Implementation

Input-Output Characteristic
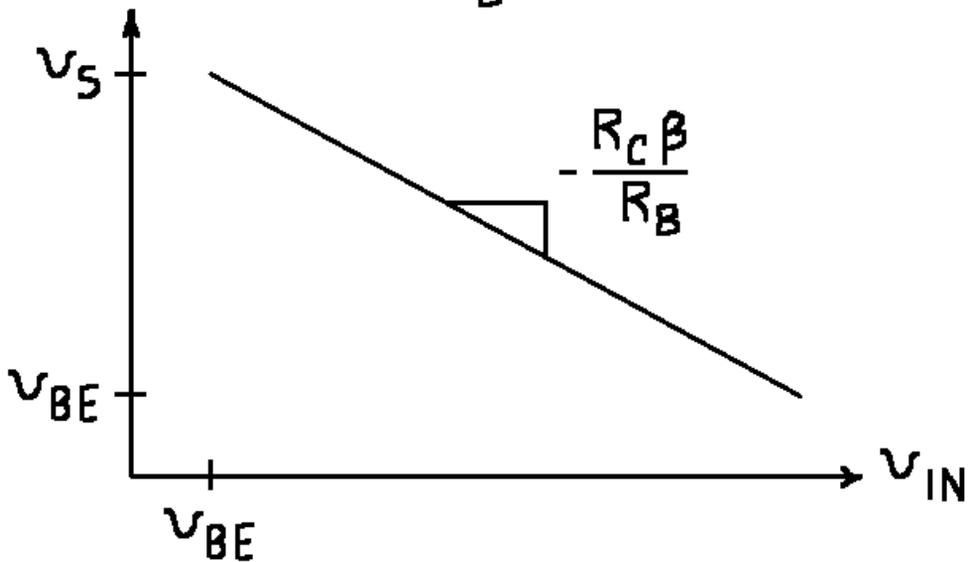
$$v_{OUT} = v_S - \frac{R_C \beta}{R_B} (v_{IN} - v_{BE})$$



Thevenin Equivalent ($v_{BE} \leq v_{OUT} \leq v_S$)

- $v_{TH} = v_{OC} = v_{OUT}$
- $v_S = v_{BE} = v_{IN} = 0 \Rightarrow i = 0$ so $R_{TH} = R_C$

