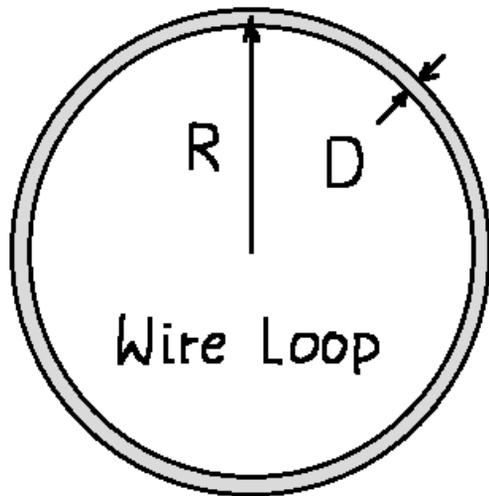


6.200 - Lecture 10


Inductors

- Inductors are Everywhere
- Uses
- Basic Physics
- First-Order ODEs

Wiring Inductance


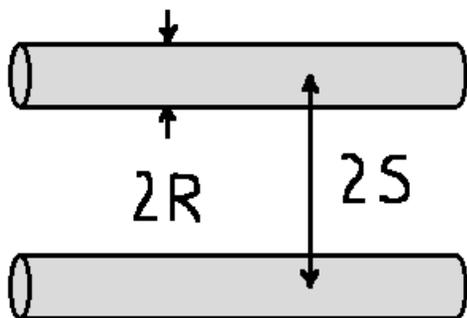
$$L \approx \mu_0 R \left[\ln \left(\frac{16R}{D} \right) - 2 \right]$$



$$L = \frac{\mu_0}{\pi} \ln \left[\frac{S}{R} + \sqrt{\left(\frac{S}{R} \right)^2 - 1} \right]$$


↑ Per Length

Uses

Inductor Uses:

- Energy Storage
- Energy Transduction (Transformers)
- Position and Motion Sensing
- Actuation (Motors)
- Generation (Generators)
- Memory (Original Core Memory!)
- Frequency-Domain Filtering
- Time-Domain Dynamics
- Resonators
- Timing

Ideal Inductor

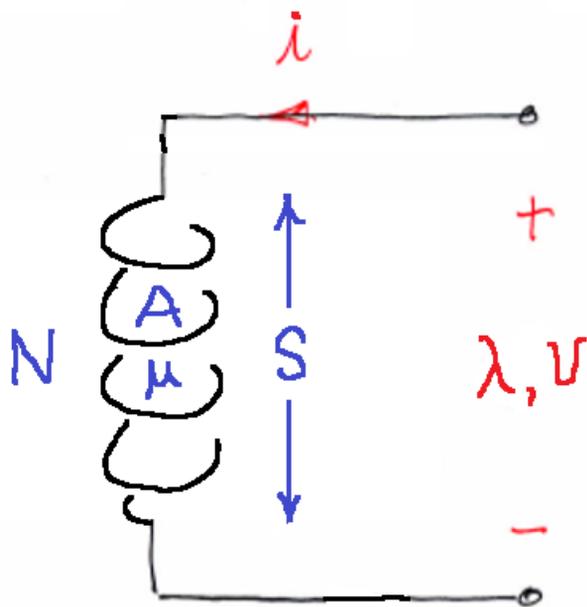

Henries

$$\lambda = L i$$

Webers Amps

$$L = \frac{\mu N^2 A}{S}$$

$$\lambda = \int_{-\infty}^t v dt \quad v = \frac{d\lambda}{dt} = \frac{d}{dt}(Li) = L \frac{di}{dt}$$

Memory

6.200

$$P = v i = \underbrace{Li}_{\text{Stored Energy}} \frac{di}{dt} = \frac{d}{dt} \left(\frac{1}{2} Li^2 \right)$$


Two signs possible
 \Rightarrow Reversible

Stored Energy


Common Nonidealities

- Winding series resistance
- Core loss and saturation
- Winding capacitance

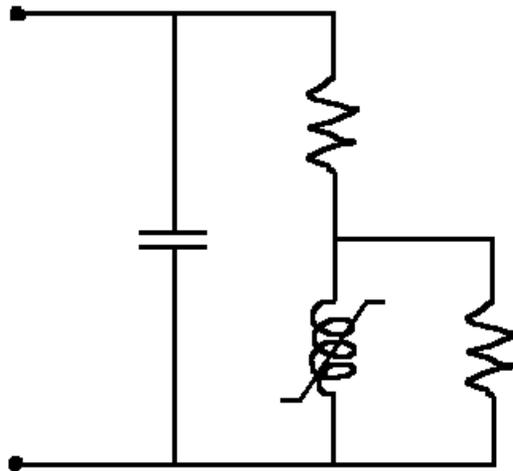A lumped-parameter model can often represent these non ideal behaviors.



Dynamics & Memory

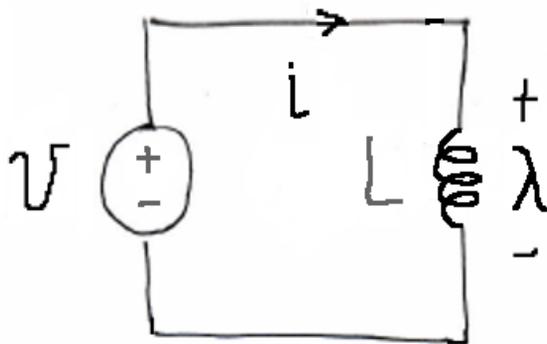



$$\lambda = Li$$

$$v = d\lambda / dt$$

$$\begin{aligned}\lambda(t) &= \int_{-\infty}^t v(t) dt = \int_{-\infty}^{t_0} v(t) dt + \int_{t_0}^t v(t) dt \\ &= \underbrace{\lambda(t_0)}_{\text{Memory}} + \int_{t_0}^t v(t) dt\end{aligned}$$


- Flux linkage (and current) depends on the entire voltage history.
- Flux linkage summarizes (memorizes) the voltage history relevant to the future.

State Continuity

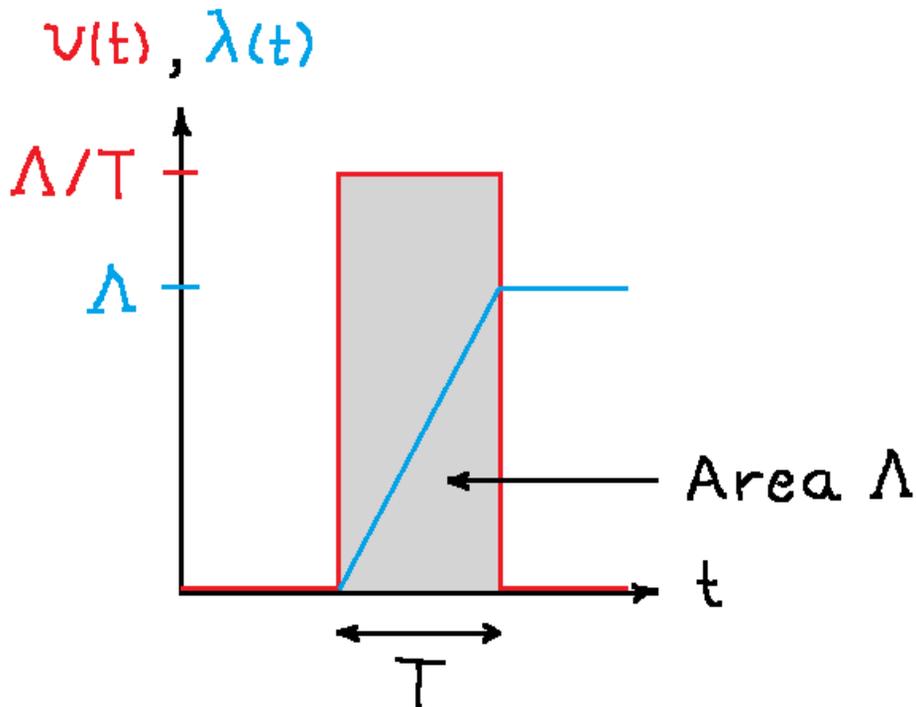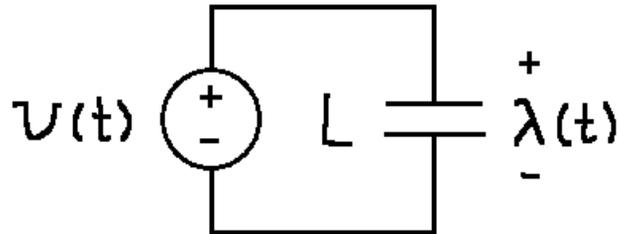

- $\lim T \rightarrow 0 : \lambda(t) \rightarrow \text{step and } v(t) \rightarrow \infty$
- Without infinite voltage, $\lambda(t)$ cannot step and so is continuous

Power & Energy


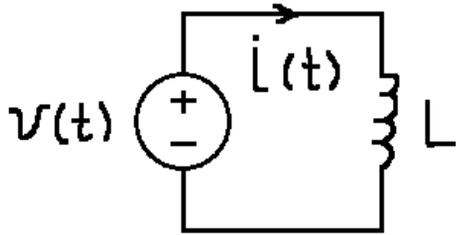


$$i = I \sin(\omega t)$$

$$v = \omega L I \cos(\omega t)$$


$$p = \omega L I^2 \sin(2\omega t) / 2$$

$$w = L I^2 \sin^2(\omega t) / 2$$

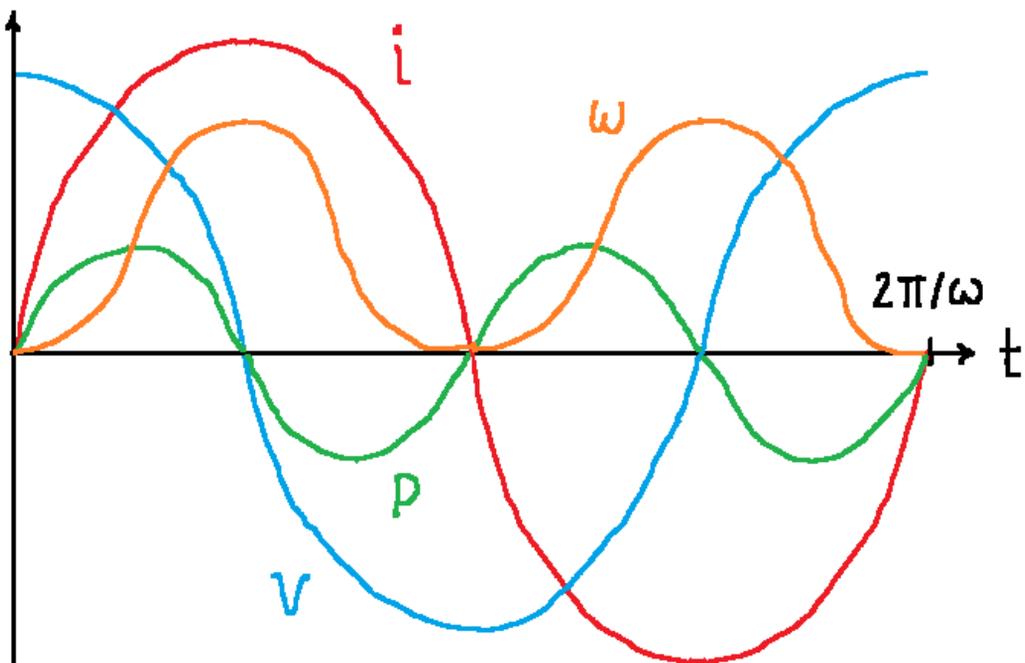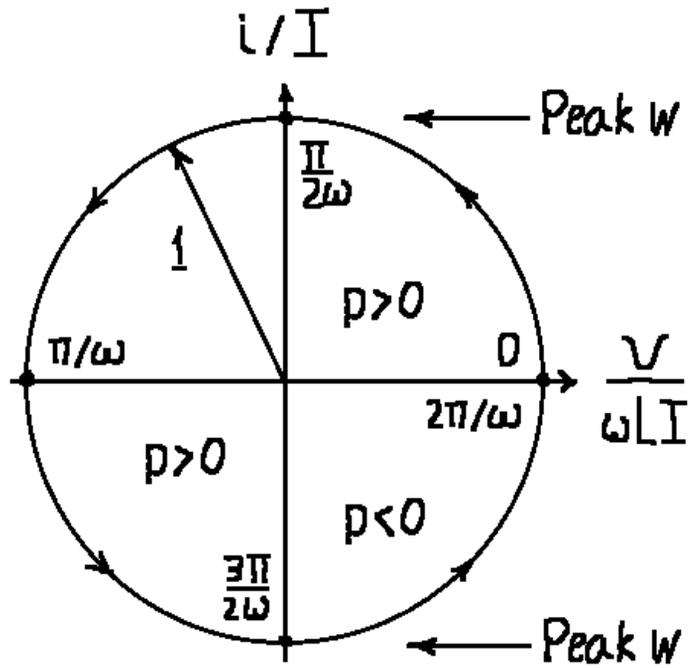

Inductor Combinations

Parallel

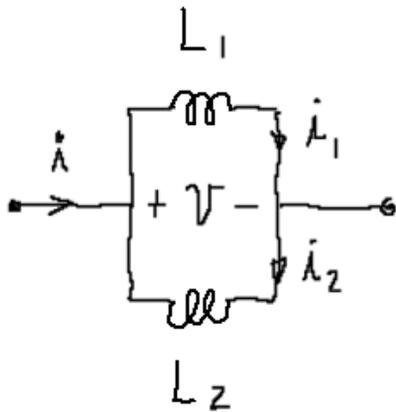


$$\begin{aligned} \frac{di}{dt} &= \frac{di_1}{dt} + \frac{di_2}{dt} \\ &= \frac{1}{L_1} V + \frac{1}{L_2} V \\ &= \underbrace{\left(\frac{1}{L_1} + \frac{1}{L_2} \right)} V \end{aligned}$$

Effective reciprocal inductance

⇒ reciprocal parallel inductances add

Series

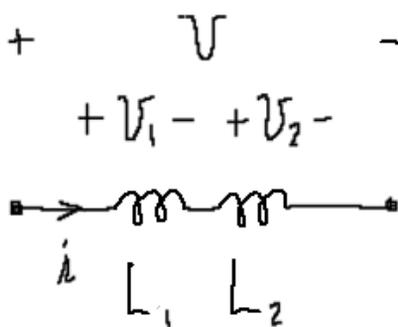


$$\begin{aligned} V &= V_1 + V_2 \\ &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} \\ &= \underbrace{(L_1 + L_2)} \frac{di}{dt} \end{aligned}$$

Effective inductance ⇒

Series inductances add

RL Node Analysis

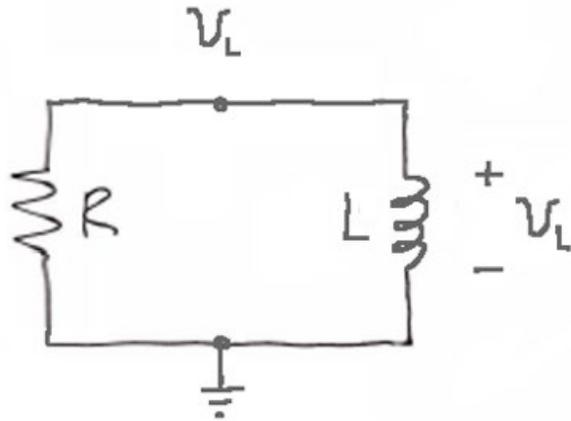

Node Method $\Rightarrow \frac{v_L}{R} + \frac{1}{L} \int_{-\infty}^t v_L(t) dt = 0$

Time $\left(\frac{L}{R} \frac{dv_L}{dt} + v_L = 0 \right)$

Well-Posed Problem $\Rightarrow v_L(0) = -Ri_L(0)$ Given

Solution $\Rightarrow v_L(t) = v_L(0) e^{-t/(L/R)}$

Exponential Decay

$$\frac{d}{dt} e^{-t/T} = \frac{-e^{-t/T}}{T} = \text{Slope} = \frac{\text{Rise}}{\text{Run}}$$

