

Massachusetts Institute of Technology  
Department of Electrical Engineering and Computer Science

6.200 – Circuits & Electronics  
Spring 2026

Quiz #1

11 March 2026

Name: \_\_\_\_\_ *Solutions*


MIT Kerberos ID: \_\_\_\_\_

Recitation Time:    12    1    2

- There are 13 pages in this quiz, including this cover page.
- Please put your name and Kerberos ID in the spaces provided above, and circle the time of your recitation.
- Please do not remove any pages from this quiz.
- Do your work for each question within the boundaries of that question, or on the back of the preceding page. *When finished with each part, clearly write your answer for that part into the corresponding answer box or graph.*
- *All numerical answers require proper units.*
- *In order to guarantee receipt of full credit, all answers should be justified by supporting math and/or explanations.*
- This is a closed-book closed-electronics quiz but a single two-sided page of notes is allowed.
- Good luck!

### Problem 1: Oscilloscope Reading - 4%

Shown below is a voltage waveform measured with the 6.200 oscilloscope. Determine the maximum and minimum voltages, and the period and frequency of the waveform.

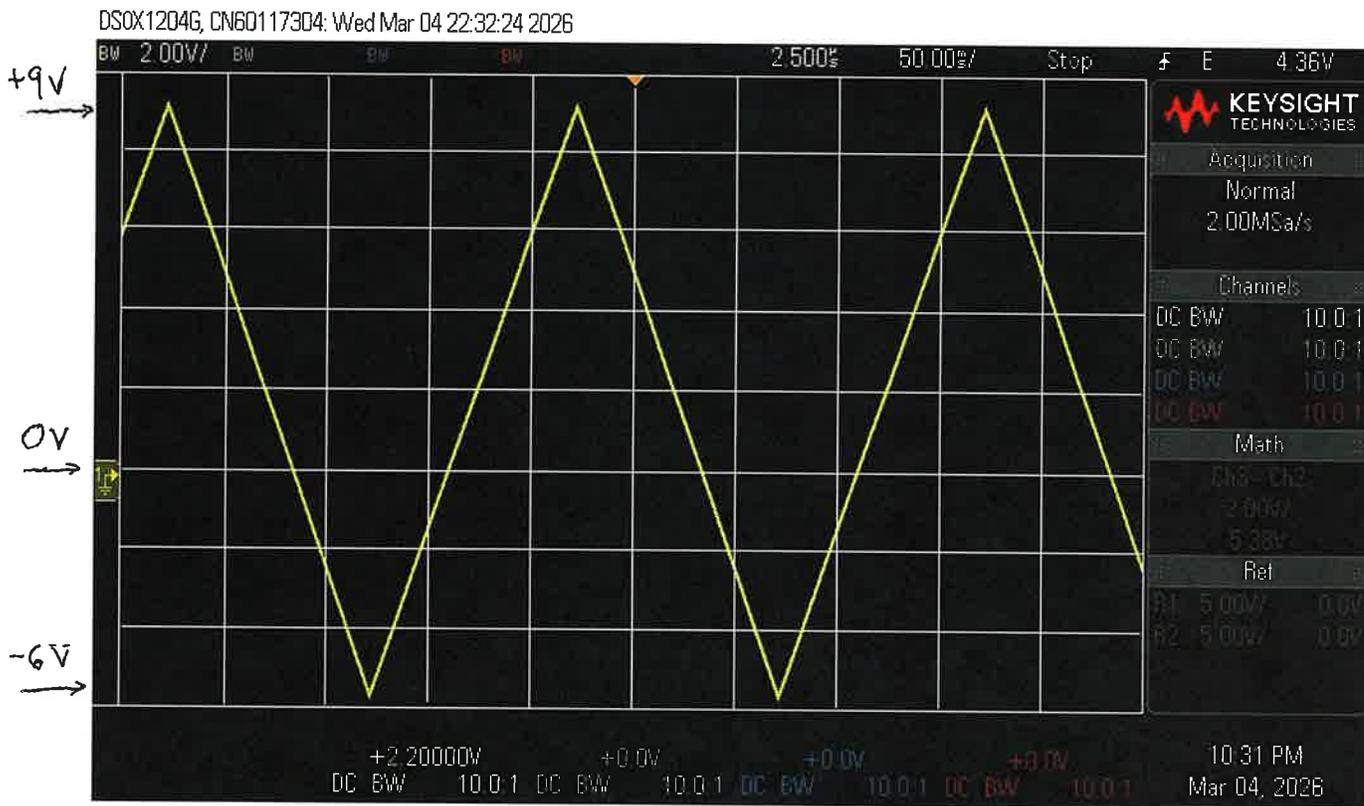


Maximum V: +9 Volts	Minimum V: -6 Volts
Period: 200 ms	Frequency: 5 Hz

$$\text{Period} = 4 \text{ Divisions} \times \frac{50 \text{ ms}}{\text{Division}} = 200 \text{ ms}$$

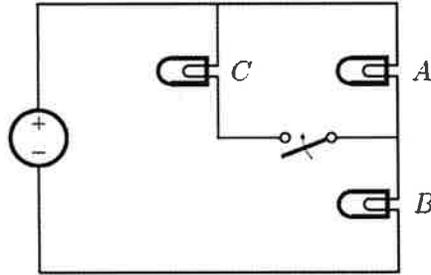**Problem 2: Lights & Power - 4%**

Consider the circuit shown below comprising a constant voltage source, three identical light bulbs, and a switch. Initially the switch is open, and then it closes so that Bulb C turns on. Assume that the light bulbs are resistive in nature with a temperature-independent resistance, and that their brightness increases with their power dissipation.

*Note that correct answers will receive positive credit, incorrect answer will receive negative credit, and empty answers will receive zero credit.*



(2A) After the switch closes, does Bulb A become brighter or darker, or is its brightness unchanged? Does Bulb B become brighter or darker, or is its brightness unchanged? Circle the appropriate answers.

Bulb A:	Brighter	<u>Darker</u>	Unchanged
Bulb B:	<u>Brighter</u>	Darker	Unchanged

(2B) Now let the source in the light bulb circuit be a constant current source. After the switch closes, does Bulb A become brighter or darker, or is its brightness unchanged? Does Bulb B become brighter or darker, or is its brightness unchanged? Circle the appropriate answers.


Bulb A:	Brighter	<u>Darker</u>	Unchanged
Bulb B:	Brighter	Darker	<u>Unchanged</u>

(2A) Closing the switch reduces the voltage across bulb (A) and increases the voltage across bulb (B).

(2B) Closing the switch diverts current from bulb (A) while the current through bulb (B) remains the same.

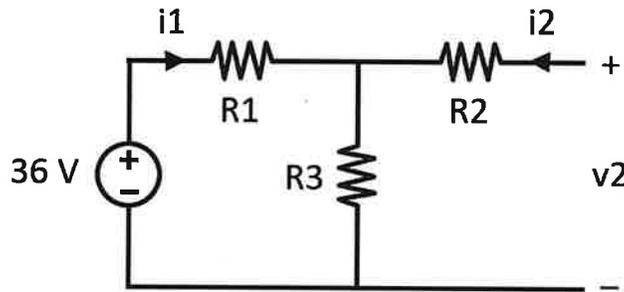
**Problem 3: Mystery Circuit – 16%**

The circuit shown below contains a known voltage source and three resistors with unknown resistances. When  $i_2 = 0$  (open circuit),  $v_2$  is observed to be 27 V. When  $v_2 = 0$  (short circuit),  $i_1$  is observed to be 9 mA and  $i_2$  is observed to be -6 mA. With this information, determine the three unknown resistances  $R_1$ ,  $R_2$  and  $R_3$ .




$R_1 = 2 \text{ k}\Omega \quad R_2 = 36 \Omega \quad R_3 = 6 \text{ k}\Omega$

Experiment #1

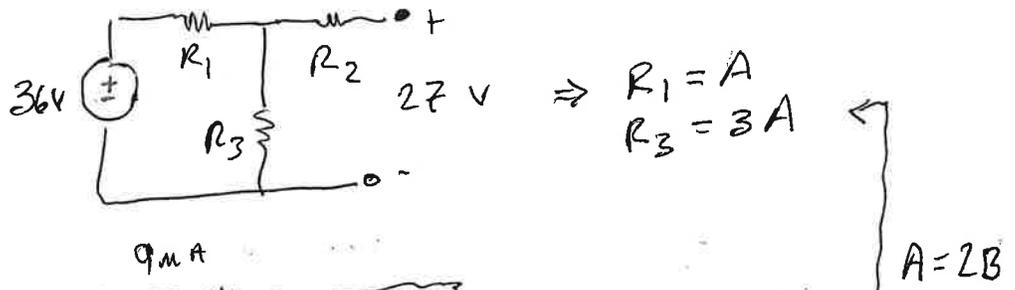

Experiment #2

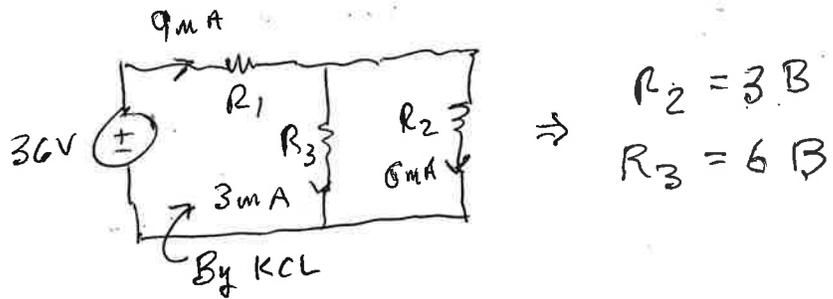


So  $R_1 = 2B$ ,  $R_2 = 3B$ ,  $R_3 = 6B$

Experiment #2  $\Rightarrow \frac{36V}{9mA} = R_1 + R_2 \parallel R_3 = 2B + 2B = 4 \cdot k\Omega$


$\Rightarrow B = 1 \text{ k}\Omega$

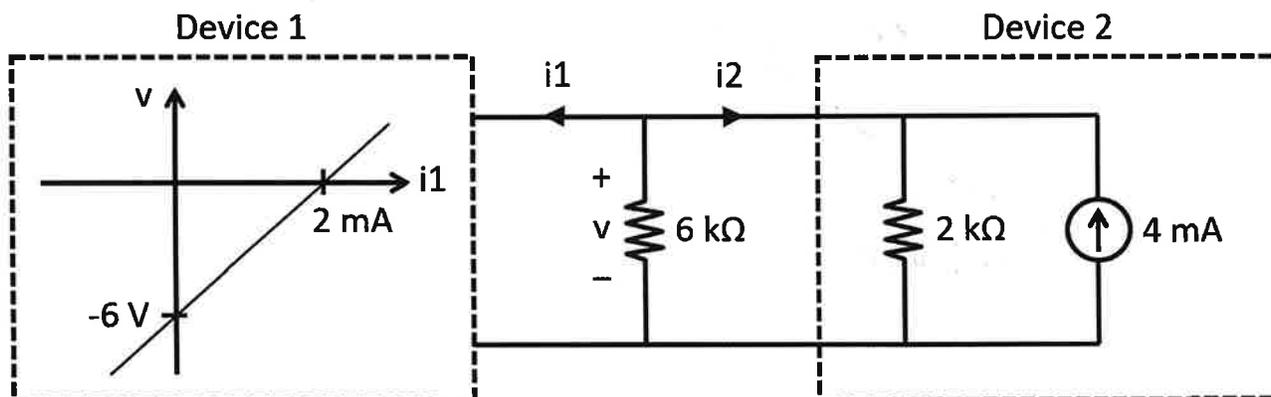**Problem 4: Graphs & Equivalences – 16%**

Two devices, Device 1 and Device 2, are both connected in parallel with a  $2\text{-k}\Omega$  resistor as shown below. The relation between the terminal voltage  $v$  and current  $i_1$  of Device 1 is described graphically. The relation between the terminal voltage  $v$  and current  $i_2$  of Device 2 is described by a Norton equivalent.




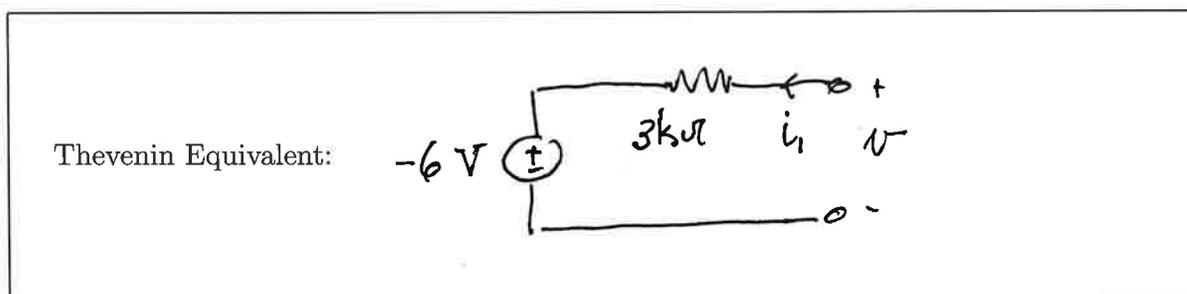- (4A) Draw the Thevenin equivalent of Device 1 in the answer box provided below. Make sure to provide values for all components and label the terminal variables  $i_1$  and  $v$ .



$$\frac{6V}{2mA} = 3k\Omega$$

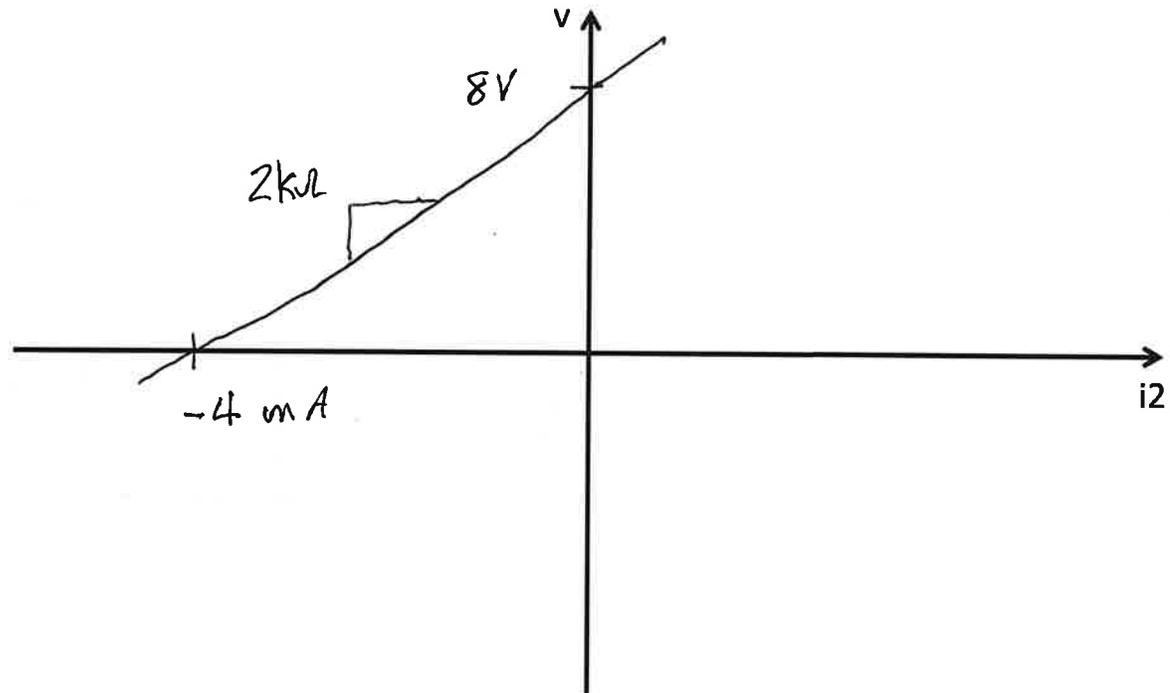
(4B) Graphically sketch the relation between  $i_2$  and  $v$  for Device 2 on the axes provided below. Make sure to label all intercepts and slopes.



(4C) Determine  $v$ .


$v = 2V$

Use Norton equivalences

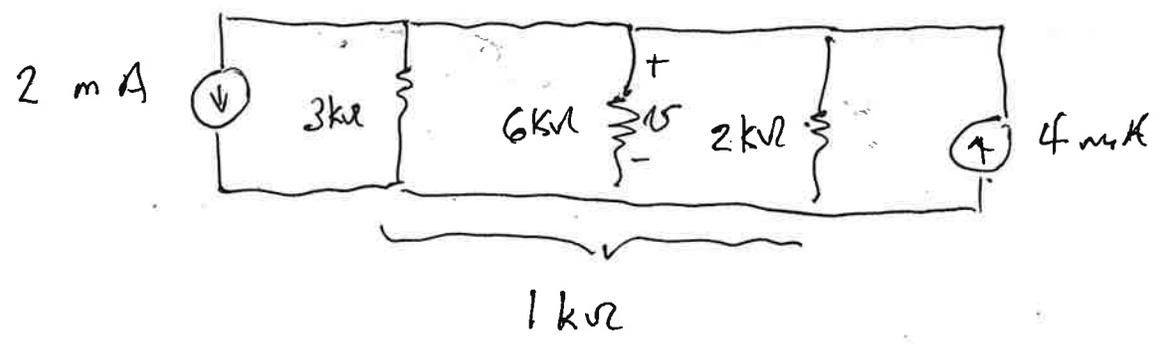

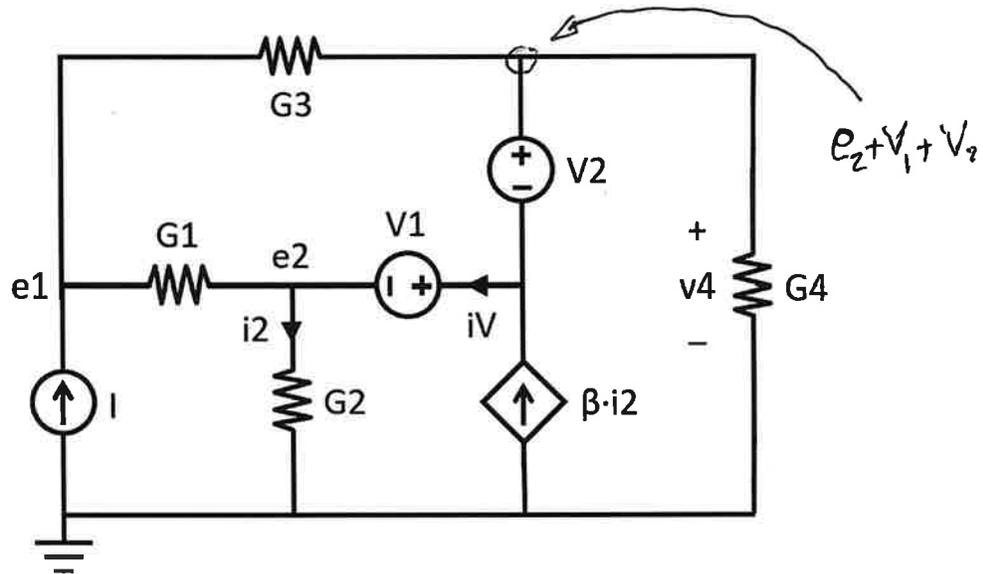**Problem 5: Node Analysis – 12%**

Consider the circuit shown below in which all resistors are labeled with their conductances. The first objective of this problem is to establish a node analysis that can be used to determine the unknown node voltages  $e_1$  and  $e_2$ . The second objective of this problem is to use the results of the node analysis to determine several select branch variables.



- (5A) Provide two node equations that can be solved for the unknown node voltages  $e_1$  and  $e_2$ . The equations should be written in terms of  $e_1$ ,  $e_2$  and the circuit parameters.

Equation 1:  $G_1(e_2 - e_1) + G_3(e_2 + v_1 + v_2 - e_1) + I = 0$

Equation 2:  $G_1(e_1 - e_2) + G_2(0 - e_2) + \beta e_2 G_2 + G_4(0 - e_2 - v_1 - v_2) + G_3(e_1 - e_2 - v_1 - v_2) = 0$

- (5B) Assume that  $e_1$  and  $e_2$  are known from the node-voltage analysis. Express  $v_4$  in terms of the known  $e_1$  and  $e_2$ , and the circuit parameters.

$$v_4 = e_2 + V_1 + V_2$$

- (5C) Assume that  $e_1$  and  $e_2$  are known from the node-voltage analysis. Express  $i_V$  in terms of the known  $e_1$  and  $e_2$ , and the circuit parameters.


$$i_V = G_1(e_2 - e_1) + G_2 e_2$$

**Problem 6: Miscellany – 12% Each Part**


All parts of this problem are independent of the others.

*Use Superposition*

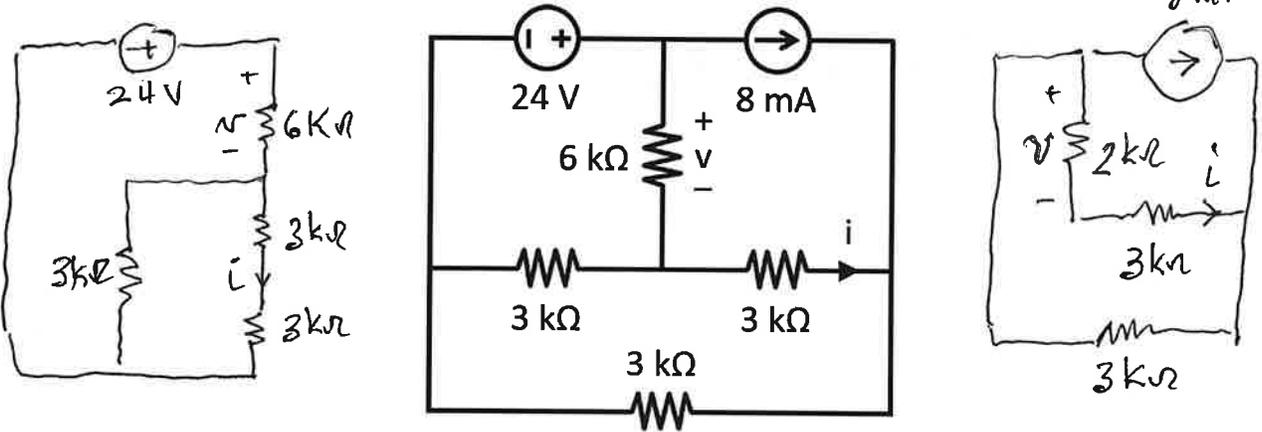(6A) Determine  $i$  and  $v$  in the following circuit.



$i = -2 \text{ mA}$	$v = 12 \text{ V}$
---------------------	--------------------

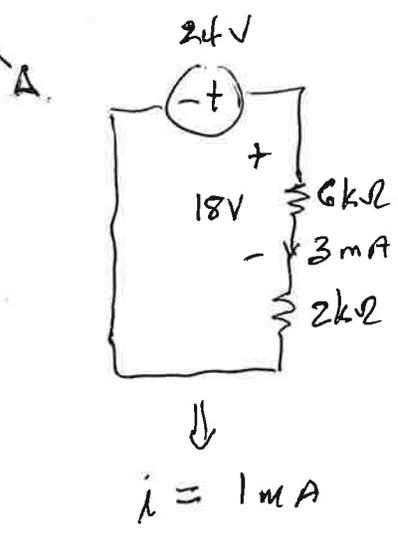






$i = -3 \text{ mA}$

$v = -6 \text{ V}$

$v = 18 \text{ V} - 6 \text{ V} = 12 \text{ V}$

$i = 1 \text{ mA} - 3 \text{ mA} = -2 \text{ mA}$

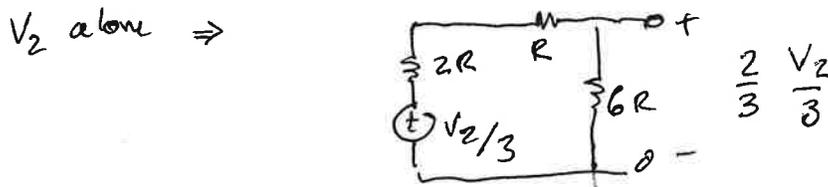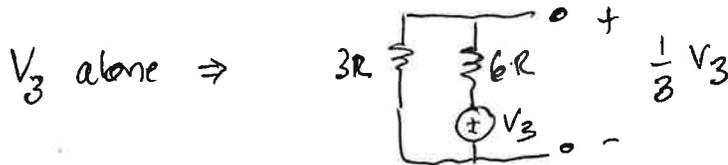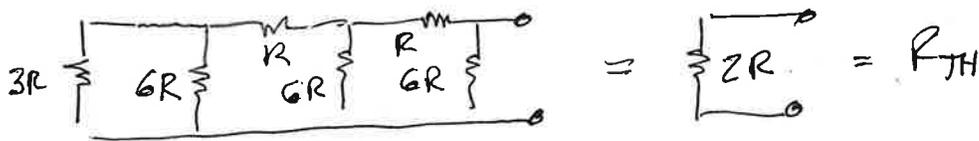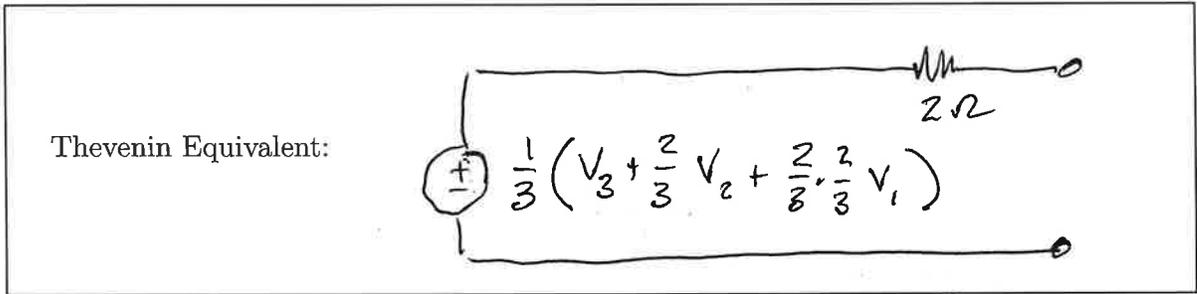
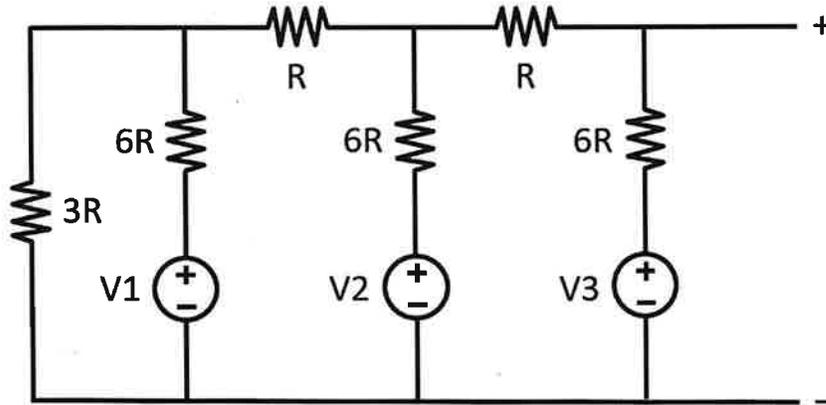
(6B) Draw the Thevenin equivalent of the following circuit in the answer box provided below. Make sure to provide values for all components and label the terminal polarity.



$V_1$  alone  $\Rightarrow \frac{2}{3} \cdot \frac{2}{3} \cdot \frac{V_1}{3}$

Use  
Superposition

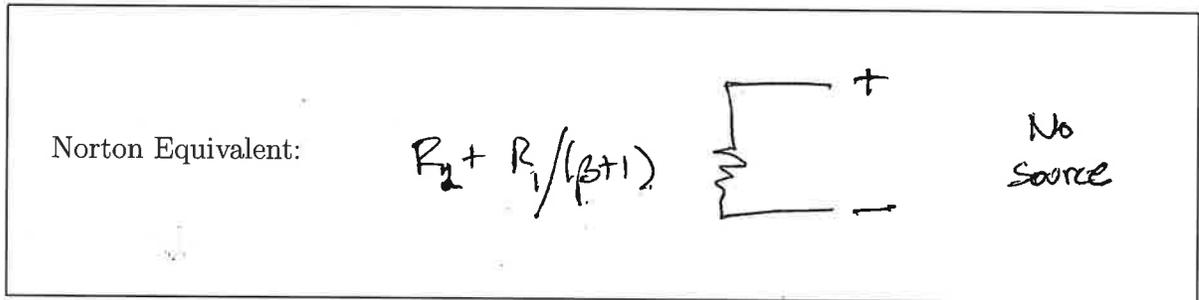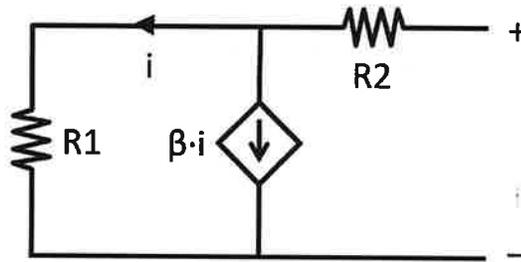- (6C) Draw the Norton equivalent of the following circuit in the answer box provided below. Make sure to provide values for all components and label the terminal polarity.





$(\beta+1)i \equiv i_T$

$$V_T = R_1 i + R_2 (\beta+1)i = (R_1 + R_2(\beta+1)) i$$


$$R_N = \frac{V_T}{i_T} = R_2 + \frac{R_1}{\beta+1}$$

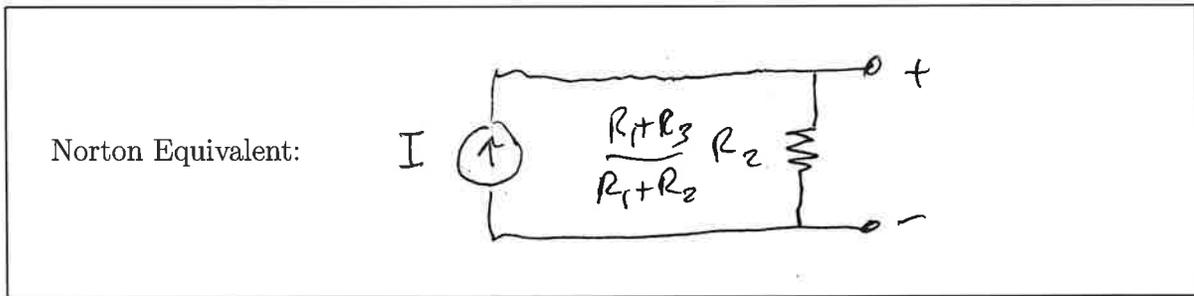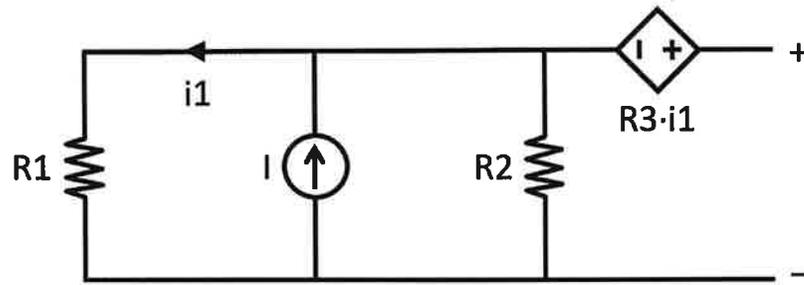(6D) Draw the Norton equivalent of the following circuit in the answer box provided below. Make sure to provide values for all components and label the terminal polarity.



$$V_{TH} = I \left( \frac{R_1 R_2}{R_1 + R_2} \right) + R_3 \left( \frac{R_2}{R_1 + R_2} \right) I = I \frac{R_1 + R_3}{R_1 + R_2} R_2$$

$i_1 \leftarrow$  For open terminals

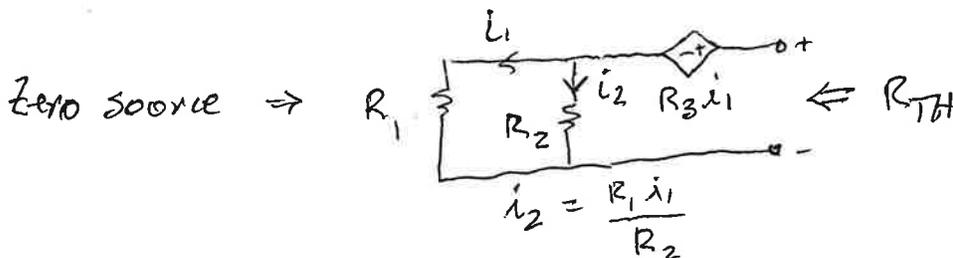

$$\text{Terminal current} = i_1 + i_2 = \left( 1 + \frac{R_1}{R_2} \right) i_1$$

$$\text{Terminal voltage} = i_1 R_1 + R_3 i_1$$

$$R_{TH} = \frac{\text{Terminal Voltage}}{\text{Terminal Current}} = \frac{R_1 + R_3}{\left( 1 + \frac{R_1}{R_2} \right)} = \frac{(R_1 + R_3) R_2}{R_2 + R_1}$$

$$I_N = \frac{V_{TH}}{R_{TH}} = I$$